
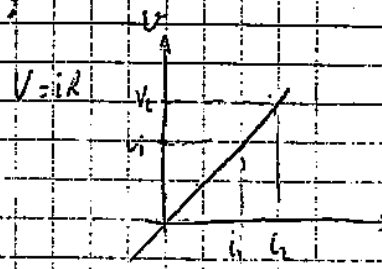


Resistors:

Note: First 8 hours are missing (G.C)


LTIC Resistors:

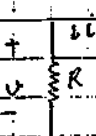


$v_1 = i_1 R$
 $v_2 = i_2 R$

If I have $i_1 + i_2$ as the current through the resistor. $\Rightarrow v_{i_1+i_2} = (i_1 + i_2)R = v_1 + v_2$

Linear system

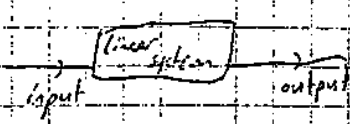


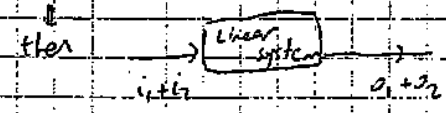i_1, i_2 as inputs
 o_1, o_2 as the corresponding outputs




Linear system is linear
 $y(t) = \alpha x(t)$
Linear systems

Time Variant

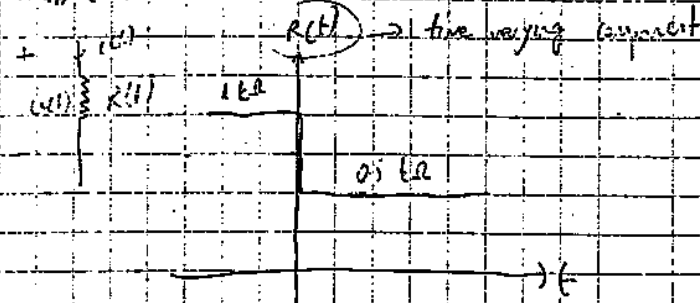


Non-linear resistors

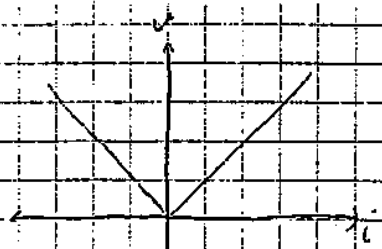

current controlled


$v = R_{CC} i$
 $v = f(i)$
 $v = |i|R$

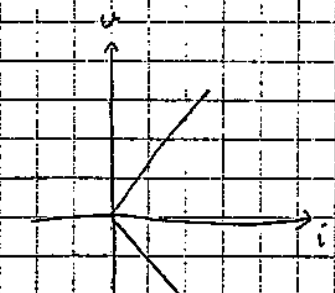

voltage controlled


$v = R_{VC} i$
 $i = f_{R_{VC}}(v)$
 $i = |v|/R$

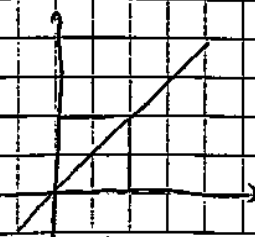A component is called current-controlled (voltage-controlled) if its branch voltage (current) is a function of its current (voltage)



Both current and voltage controlled

Diode

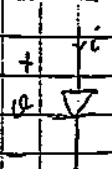

Neither voltage nor current controlled

Classification of Circuits

Memoryless Circuits
(Resistances and sources)

Dynamic Circuits
(Something evolving with time)
(R, L, C)



Passive, Active Components

$$\int_{-\infty}^t p(t) dt < 0 \quad \text{It} \rightarrow \text{component is active (generating energy)}$$


Circuits with active components \rightarrow active circuits

Any circuit with physically realizable components are passive (R, L, C)

Source Addition

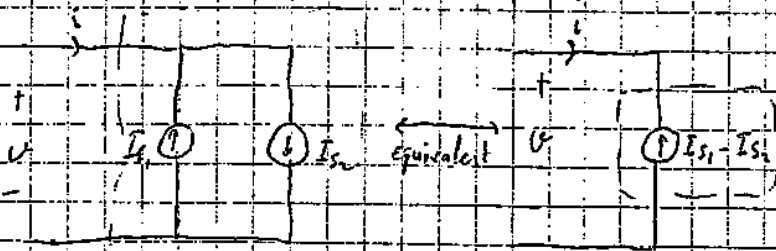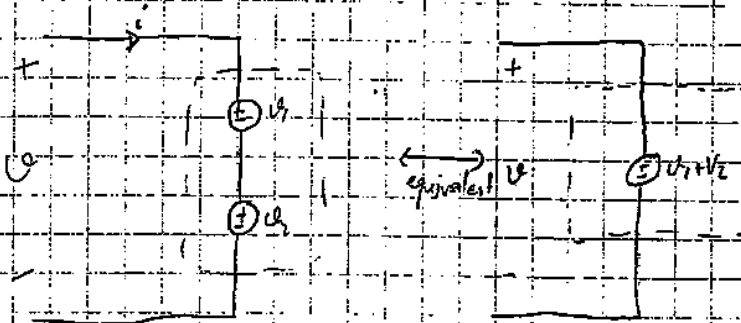


Source Transformation

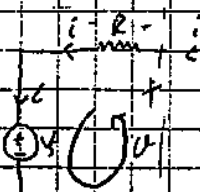

i-v characteristics



$$\begin{aligned} V_1 - V + R_1 i &= 0 \\ V &= V_1 + R_1 i \end{aligned}$$



equivalent

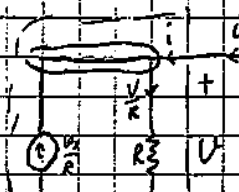


i-v characteristic
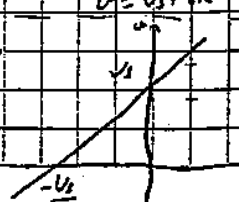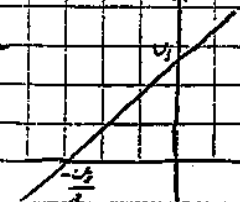
$$\begin{aligned} \frac{V_1}{R} + i - \frac{V}{R} &= 0 \\ V &= V_1 + IR \end{aligned}$$




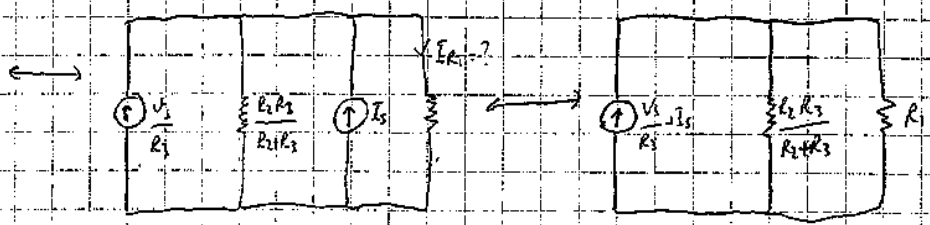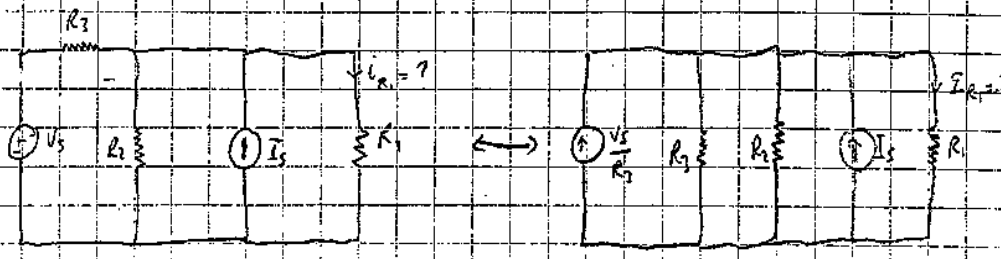

One Port Circuits

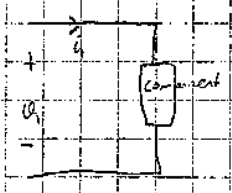


Two Port Circuits

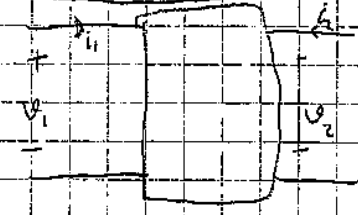

NODE-MESH ANALYSIS TECHNIQUES

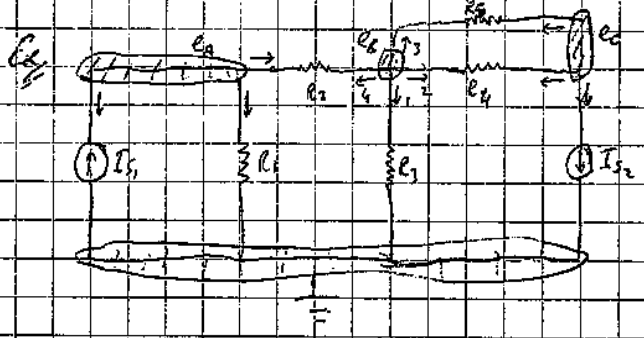- Node Method:
- 1) Introduce Datum Node
 - 2) Introduce Node Voltages (e_a, e_b, e_c, \dots)
 - 3) Write KCL at each node except datum node



KCL at e_a :

$$-I_{s1} + \frac{e_a - 0}{R_1} + \frac{e_a - e_b}{R_2} = 0$$

exiting current #1 e.c. #2 e.c. #3

KCL at e_b :


$$\frac{e_b - 0}{R_3} + \frac{e_b - e_c}{R_4} - \frac{e_b - e_a}{R_2} - \frac{e_b - e_a}{R_5} = 0$$

KCL at e_c :

$$I_{s2} + \frac{e_c - e_b}{R_4} + \frac{e_c - e_b}{R_5} = 0$$

$\frac{1}{R_1}$	$-\frac{1}{R_2}$	0	e_a	I_{s1}
$-\frac{1}{R_2}$	$\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}$	$-\frac{1}{R_4}$	e_b	0
0	$-\frac{1}{R_4}$	$\frac{1}{R_4} + \frac{1}{R_5}$	e_c	$-I_{s2}$


Node Analysis with Voltage Source

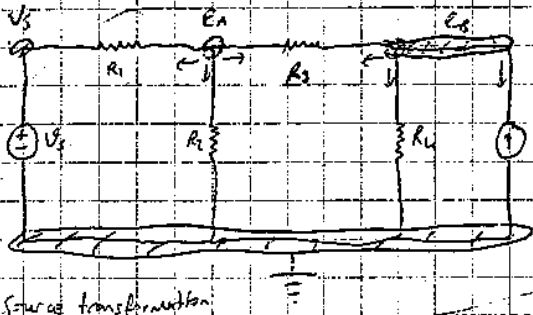

$$\text{KCL at } e_A = \frac{e_A - V_S}{R_1} + \frac{e_A - 0}{R_2} + \frac{e_A - e_B}{R_3} = 0$$

$$\text{KCL at } e_B = -i_S + \frac{e_B}{R_4} + \frac{e_B - e_A}{R_3} = 0$$


Source transformation

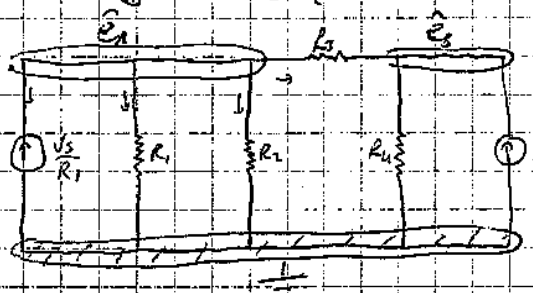

$$\text{KCL at } \hat{e}_A = \frac{\hat{e}_A}{R_1} + \frac{\hat{e}_A}{R_2} - \frac{V_S}{R_1} + \frac{\hat{e}_A - \hat{e}_B}{R_3} = 0$$

$$\text{KCL at } \hat{e}_B = \frac{\hat{e}_B}{R_4} + \frac{\hat{e}_B - \hat{e}_A}{R_3} - i_S = 0$$

Supernode:

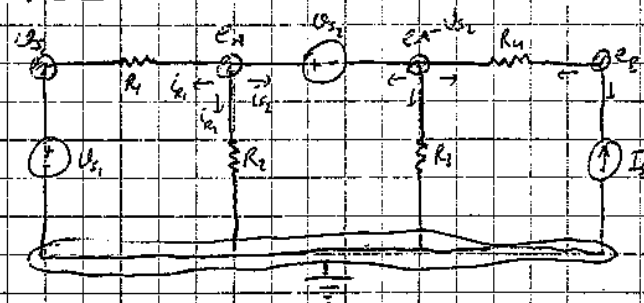


① KCL at e_A : $\frac{e_A - 0}{R_2} + \frac{e_A - V_{S1}}{R_1} + i_{S1} = 0$

② KCL at e_B : $\frac{e_B - (e_A - V_{S1})}{R_3} - I_S = 0$

③ KCL at " $e_A - V_{S1}$ " : $\frac{e_A - V_{S1}}{R_1} + \frac{e_A - V_{S1} - e_B}{R_3} - i_{S1} = 0$

Add ① + ③ = supernode eqn.

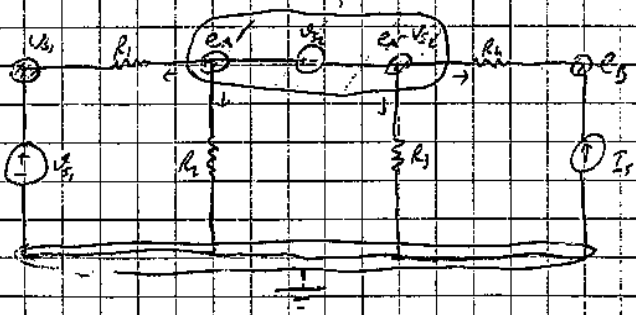


$$\text{KCL at } e_B = \frac{e_B - (e_A - V_{S1})}{R_3} - I_S = 0$$

$$\text{KCL at supernode: } \frac{e_A - V_{S1}}{R_1} + \frac{e_A}{R_2} + \frac{e_A - V_{S1}}{R_3} + \frac{e_A - V_{S1} - e_B}{R_3} = 0$$

2 eq., 2 unknowns

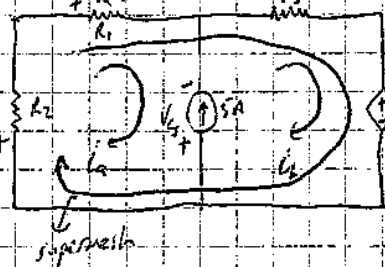Supernode Problem with current sources in the interior of the circuit!




$$i_b - i_a = i_s$$

$$\text{KVL around } i_a \text{ loop: } R_1 i_a + R_2 i_a - V_{cs} = 0$$

$$\text{KVL around } i_b: kV_s + V_{cs} + R_3 i_b = 0$$

$$\text{KVL around supernode: } R_1 i_a + R_2 i_a + R_3 i_b + kV_s = 0$$

Ex 11

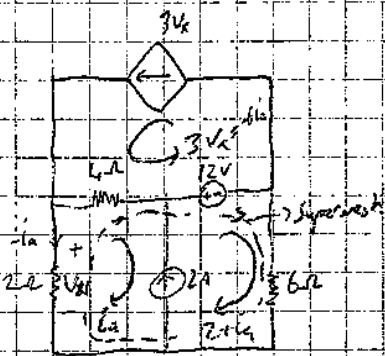

$$V_x = -2i_a$$

KVL around supernode

$$2i_a + 4(i_a - i_b) + 12 = 6(2 + i_a) = 0$$

$$-12i_a + 2i_b = 0$$

$$i_a = 2$$


Tree





Input Resistance Calculation

$$V = \underline{\underline{0}} \underline{\underline{e}}$$

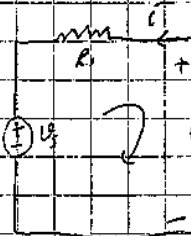
$$\underline{\underline{0}} \underline{\underline{e}} = \underline{\underline{0}} \rightarrow \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & 1 & 1 & 0 \\ 0 & 0 & 1 & 1 & 0 & 1 \\ 0 & 1 & 1 & -1 & 0 & 0 \\ 1 & 1 & 0 & 0 & -1 & 0 \\ 0 & 1 & 0 & 1 & 0 & 1 \end{bmatrix} \underline{\underline{e}} = \underline{\underline{0}}$$



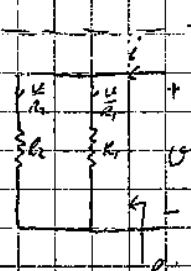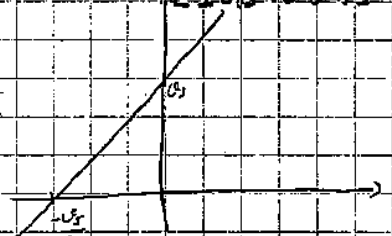
$$-V_s - R_1 i + V = 0 \Rightarrow V = V_s + R_1 i$$



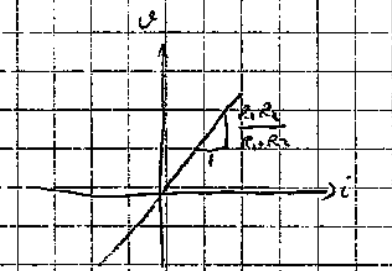
$$V = \frac{V}{R_1} + \frac{V}{R_2} \Rightarrow V = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V$$



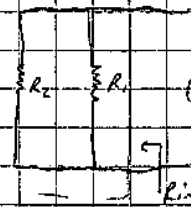Another method to find \$i_{in}\$ char (when you have only resistors)



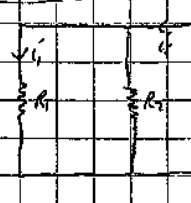
$$i = \frac{1}{R_1} + \frac{1}{R_2} \text{ when } V_s = 1V \Rightarrow \frac{1V}{R_{in}} = R_{in} \Rightarrow R_{in} = R_1 \parallel R_2$$




$$i_1 = \frac{R_2}{R_1 + R_2} \text{ for } i_1 = 1A \Rightarrow i_1 = \frac{R_2}{R_1 + R_2}$$
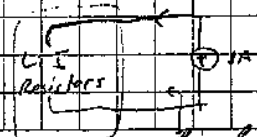
$$V = R_1 i_1 = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow V = \frac{R_1 R_2}{R_1 + R_2}$$



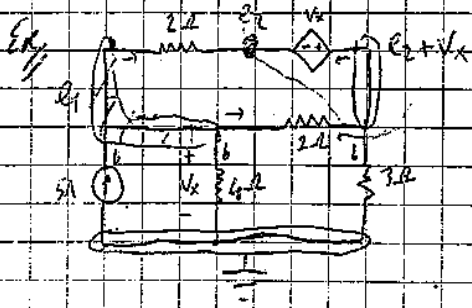
$$R_{in} = R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$




Find the power dissipated by 3Ω resistor

Nodal Analysis
 KCL at e_1 : $-5 + \frac{e_1 - 0}{2} - \frac{e_1 - e_2}{2} + \frac{e_1 - (e_2 + V_x)}{2} = 0$
 KCL at supernode: $\frac{e_2 - e_1}{2} + \frac{e_2 + V_x}{3} + \frac{e_2 + V_x - e_1}{2} = 0$


$\Rightarrow \begin{cases} 3e_1 - 4e_2 = 20 \\ -e_1 - 8e_2 = 0 \end{cases} \Rightarrow \begin{cases} e_1 = 5V \\ e_2 = 1V \end{cases}$

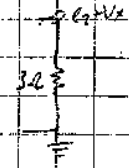\Rightarrow  $V_{3\Omega} = e_2 + e_1 = 9V$
 $P_{3\Omega} = \frac{V_{3\Omega}^2}{R} = \frac{81}{3} = 27W$

MESH ANALYSIS

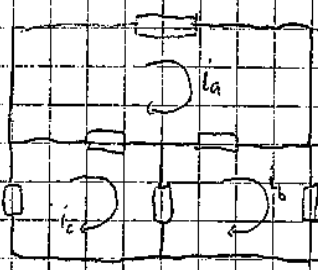


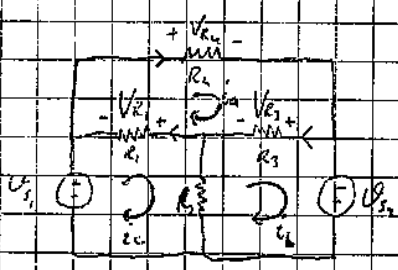Only applicable to planar circuits.
 KVL for i_1, i_2, \dots meshes



KVL for i_1 mesh
 $V_{R1} + V_{R2} + V_{R3} = 0$
 $i_1 R_1 + R_2(i_1 - i_2) + R_3 i_1 = 0$

KVL for mesh i_2

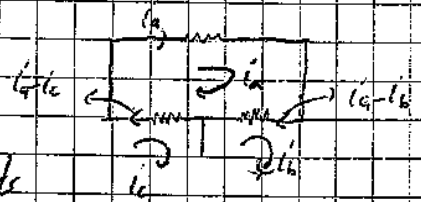

Express in terms mesh currents


$R_2 i_1 + R_2(i_1 - i_2) + R_4(i_2 - i_1) = 0$

For i_1

$-V_2 + R_2(i_1 - i_2) + R_3(i_1 - i_2) = 0$

For i_2

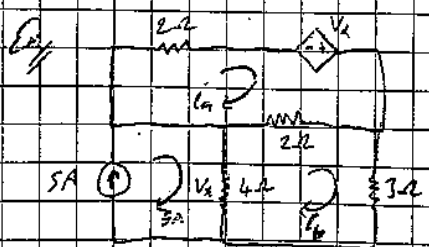
$-V_1 + R_4(i_2 - i_1) + R_2(i_2 - i_1) = 0$



KVL for i_1 $\rightarrow (2-16) \cdot 4$
 $i_1 = 2(i_1 - i_2) + 2i_1 - V_x = 0$
 $i_2 = 3i_2 + i_2(i_2 - 5) + 2(i_2 - i_1) = 0$

$\begin{bmatrix} 4 & 2 \\ -2 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 20 \end{bmatrix} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \frac{1}{40} \begin{bmatrix} 9 & -2 \\ 2 & 4 \end{bmatrix} \begin{bmatrix} 20 \\ 20 \end{bmatrix} = \begin{bmatrix} -\frac{2}{5} \\ 3 \end{bmatrix}$

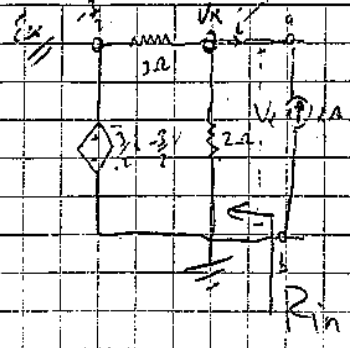$\Rightarrow i_1 = -\frac{2}{5}$
 $i_2 = 3$



Find $V_x \rightarrow \frac{V_x}{1} = R_{in}$

$\rightarrow R_{in} = \frac{V_x}{1} = 0.6 \Omega$

KCL at V_x : $\frac{V_x - 0}{2} + \frac{V_x - (-2A)}{2} = 0$
 $V_x = \frac{6-3}{5} = 0.6V$

$R_{in} = ?$

Linearity

Operator - A mapping between input and output



Linear Systems

$f_{out} = L\{f_{in}\}$
 ↳ A linear system

① $L\{af_{in}^1\} = aL\{f_{in}^1\}$ $L\{bf_{in}^2\} = bL\{f_{in}^2\}$

② $L\{af_{in}^1\} = aL\{f_{in}^1\}$





③ $L\{f_{in}^1 + f_{in}^2\} = L\{f_{in}^1\} + L\{f_{in}^2\}$

From (1)-(3)

$L\{0\} = 0$


$L\{f_{in}^1 - (-f_{in}^1)\} = L\{f_{in}^1\} - L\{-f_{in}^1\} \Rightarrow L\{0\} = 0$

$L\{-f_{in}^1\} = -L\{f_{in}^1\}$

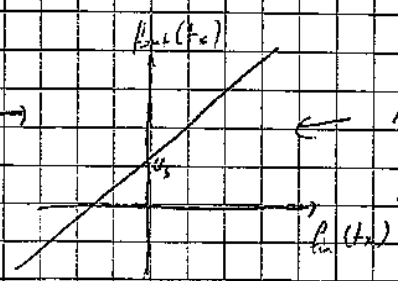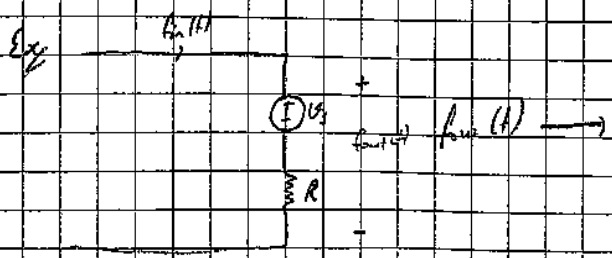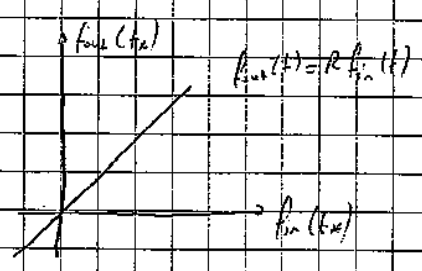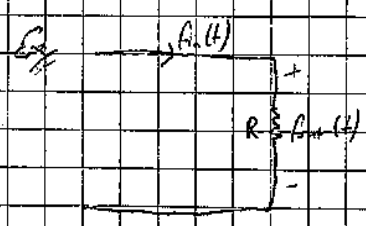

← Not a linear relation because of U_s source

Circuit with A Single Source

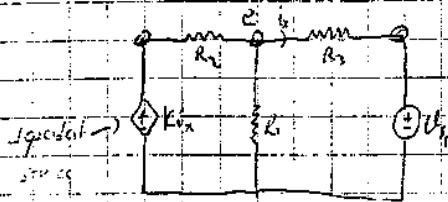


When V_{s1} is doubled \rightarrow all circuit variables are also doubled


$$\frac{e}{R_1} + e - k_{ix} \frac{e - V_{s1}}{R_1} + \frac{e - V_{s1}}{R_3} = 0$$

$$(\dots) e = \alpha V_{s1}$$

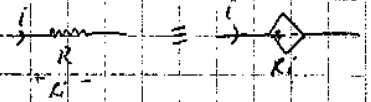!!! Never treat dependent sources as an independent source.




Multiple sources

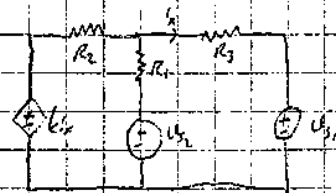

When V_{s1} and V_{s2} are doubled \rightarrow all circuit variables are also doubled.

Superposition Principle

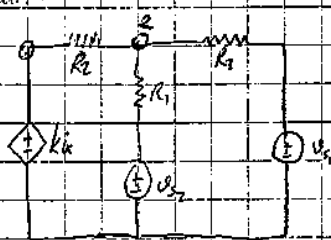A linear system with multiple inputs can be decomposed into several circuits with single input and addition of all output variables in the decomposition results in the solution of multiple input circuit.




$$(\text{a number}) e^{\text{total}} = (\dots) V_{s1} + (\dots) V_{s2}$$

$$\Rightarrow \begin{pmatrix} \downarrow \\ \downarrow \\ \downarrow \end{pmatrix} e^{\text{total}} = \begin{pmatrix} \downarrow \\ \downarrow \\ \downarrow \end{pmatrix} V_{s1}$$


$$\Rightarrow e^{\text{total}} = e^{\text{1}} + e^{\text{2}}$$

$$\begin{pmatrix} \downarrow \\ \downarrow \\ \downarrow \end{pmatrix} e^{\text{1}} = \begin{pmatrix} \downarrow \\ \downarrow \\ \downarrow \end{pmatrix} V_{s1}$$

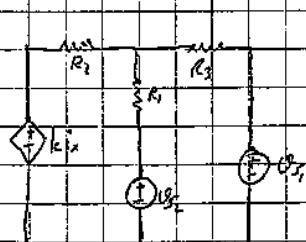
Turning OFF the sources (killing the sources)



($V_{s2} = 0$) kill V_{s2}

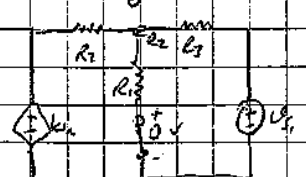

2nd sub circuit

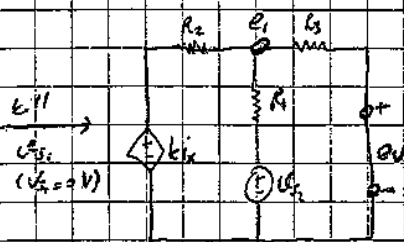


kill V_{s1} ($V_{s1} = 0$)

1st sub-circuit

① Solve both circuits for e^{1} and e^{2}

② $e^{\text{total}} = e^{\text{1}} + e^{\text{2}}$


Independent Current Sources

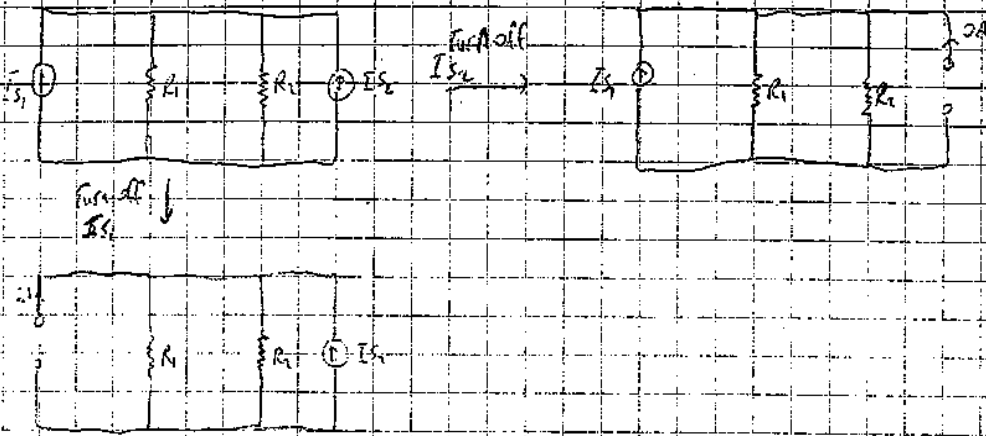


Superposition principle applies to all linear systems hence all linear circuits. To turn-off

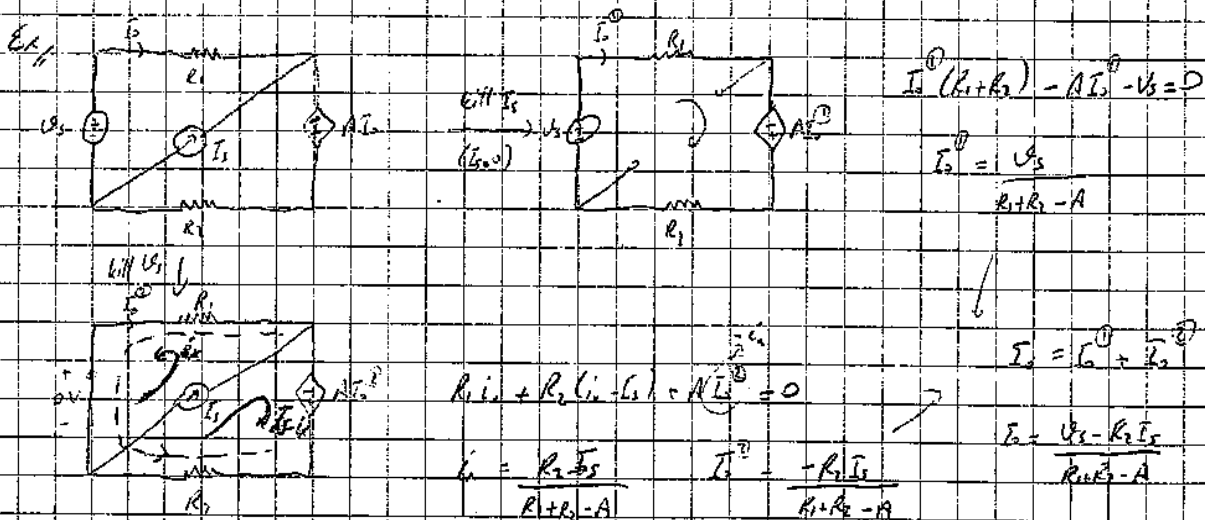- 1) Voltage source \rightarrow Replace with short circuit ($V_s = 0$)
- 2) Current source \rightarrow Replace with open circuit ($I_s = 0$)

Never treat dependent sources as independent sources. (Do not try to turn off dependent sources)



Thevenin-Norton Equivalent Circuits

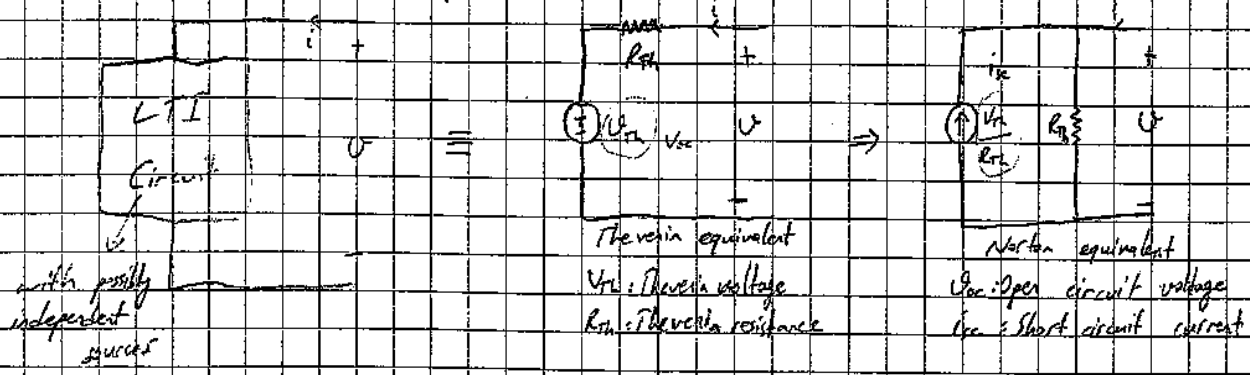

Procedure 3

1) Find V_{oc}

2) Find R_{th} → Kill all the independent sources and find R_{eq} seen from a-b terminals


→ Kill all the independent sources and apply 1V and find i_s of the 1V source → $R_{eq} = \frac{1V}{i_s}$

Procedure 2


1) Find V_{oc}

2) Find I_{sc}


3) $\frac{V_{oc}}{I_{sc}} = R_{th}$

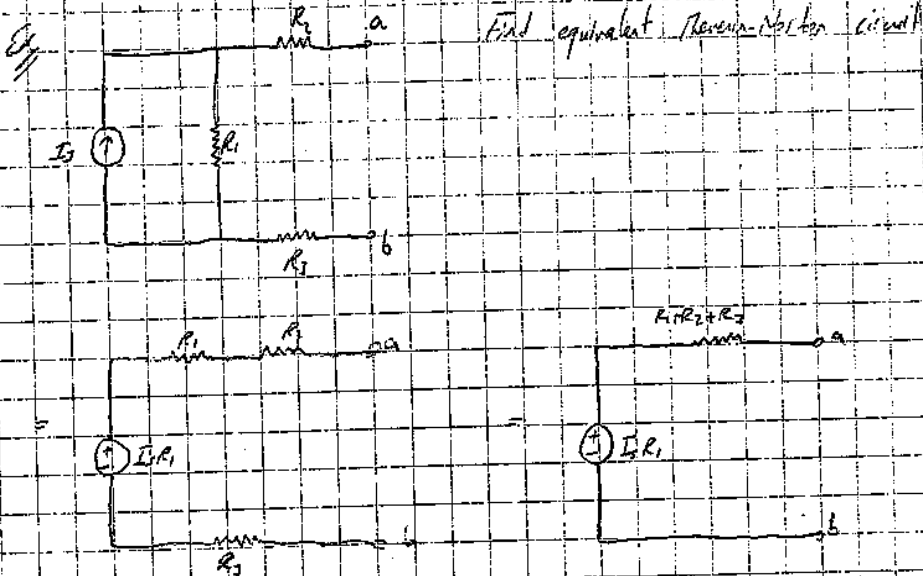

Procedure 1

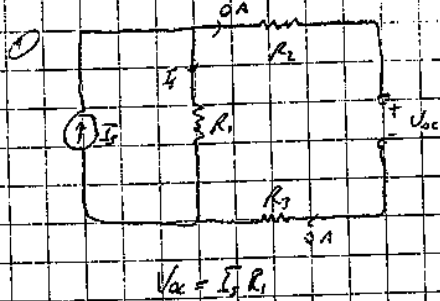


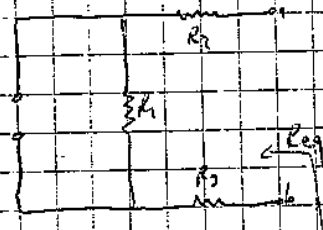2) Kill all independent sources ($V_s = 0V, I_s = 0A$)



$R_{eq} = R_1 + R_2 + R_3$

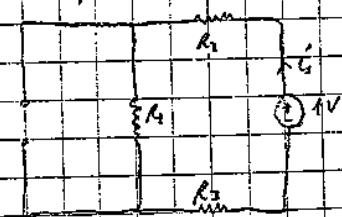
or
Kill all independent sources
apply 1V source



$i_s = \frac{1}{R_1 + R_2 + R_3}$

$R_{eq} = \frac{1}{i_s} = R_1 + R_2 + R_3$

Procedure (2)

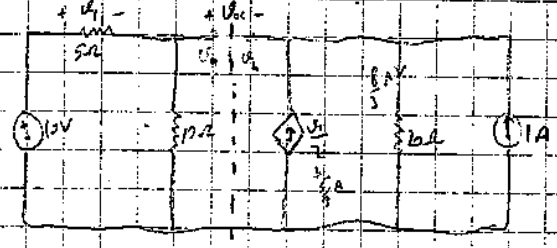


$$1) u_1 = 10 \frac{5}{5+10} = \frac{10}{3} V$$

$$u_{2a} = 20 \cdot \frac{8}{3} = \frac{160}{3} V$$

$$V_{oc} = u_a - u_b = \left(\frac{10 - \frac{10}{3}}{3} \right) - \left(\frac{160}{3} \right) = -\frac{140}{3} V$$

Remember
 $a + u_c = b$

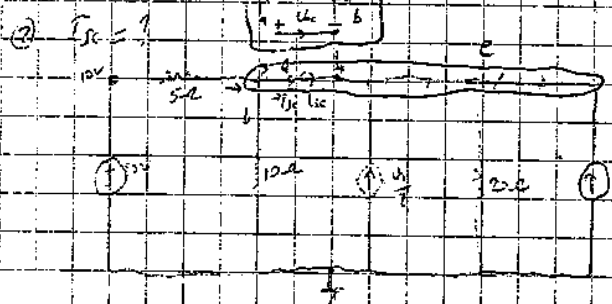


$$\frac{10}{5} - \frac{e}{10} - \frac{u_1}{2} - \frac{e}{20} = 0$$

$$(4 + 2 + 10 + 1)e = 60 + 100 \Rightarrow 20e = 160 \Rightarrow e = \frac{160}{20} = 8 A$$

$$i_{sc} = \frac{10 - e}{5} = \frac{10 - 8}{5} = \frac{2}{5} = 0.4 A$$
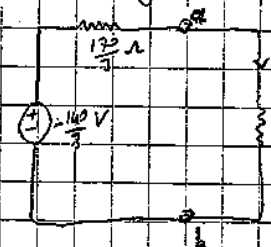
$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{-140/3}{-4/12} = \frac{170}{3} \Omega$$




- a) when $R = \infty$ $V_R = V_{oc} = -\frac{140}{3} V$
- b) when $R = 0$ $I_R = I_{sc}$


d) For any R

$$i_R = \frac{-140/3}{\frac{170}{3} + R}$$

Ex $R_{Th} = ?$ Using external source

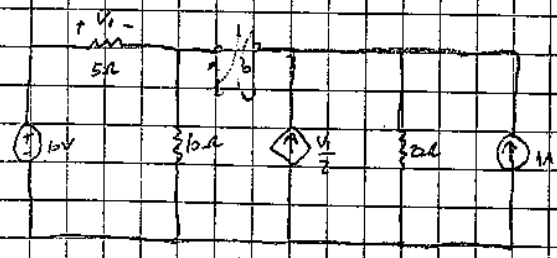

Kill int. sources.

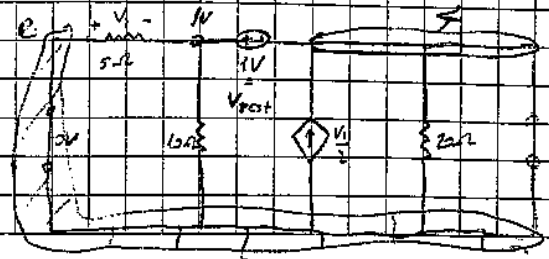

$$u_1 = e - 1$$


$$\frac{e-1}{5} + \frac{e-1}{10} + \frac{e-1}{2} + \frac{e}{20} = 0 \Rightarrow e = \frac{1}{17}$$

$$I_1 = \frac{1-e}{5} + \frac{1-e}{10} = 0.2 - 0.2e = 0.2 - 0.2 \cdot \frac{1}{17} = \frac{0.2}{17} = \frac{1}{85}$$


$$R_{Th} = \frac{V_{ext}}{I_1} = \frac{1}{1/85} = 85 \Omega$$

Maximum Power Transfer

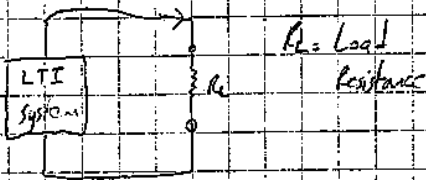In many situations, you would like to maximize energy/power delivered to a special component.




Power received by R_L

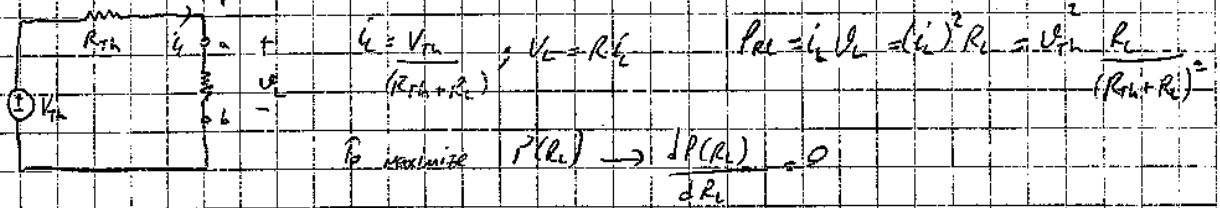

$$\frac{dP(R_L)}{dR_L} = \frac{V_m^2}{(R_m + R_L)^4} (R_m + R_L) - R_L \cdot 2(R_m + R_L) = 0 \Rightarrow (R_m + R_L)(R_m + R_L - 2R_L) = 0$$

$$R_L = \left\{ \begin{array}{l} R_m \\ R_m \end{array} \right\}$$

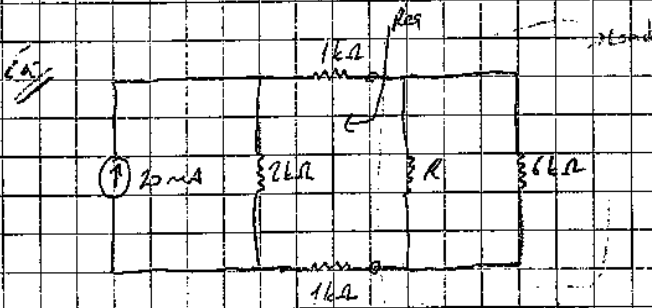
To maximize the power transferred, $R_L = R_m$



The resistance is adjusted to maximize power transfer to the load. Find the voltage and power delivered to load

$$R_{eq} = 1 + 2 + 1 = 4 \text{ k}\Omega$$

$$V_{oc} = 40 \text{ V}$$

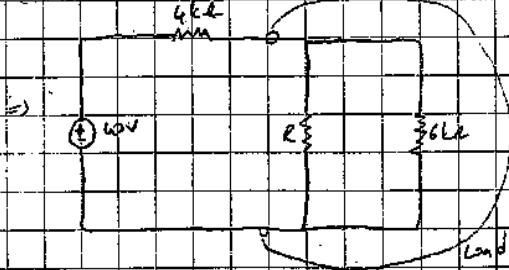


$$R \parallel 6 \text{ k}\Omega = 4 \text{ k}\Omega \Rightarrow R = 12 \text{ k}\Omega$$

$$V_{load} = 20 \text{ V}$$

$$P_{load} = \frac{20^2}{4 \text{ k}\Omega} = \frac{400}{4000} = 0.1 \text{ Watt}$$

One Port - Two Ports

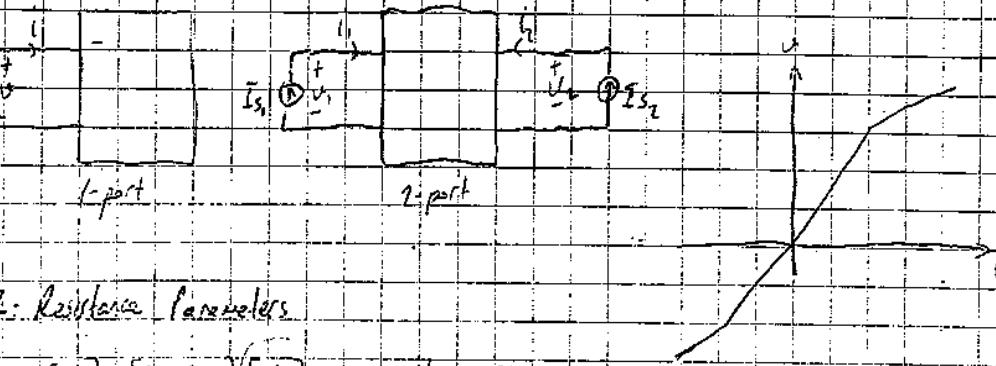

R: Resistance Parameters

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$ → current sources
 $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$ → input sources
 output circuit variables

G: Conductance Parameters

$(G^{-1} = R)$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

G

Hybrid Parameters (I)

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

H


Hybrid Parameters (II)

$$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = H^{-1} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

Transfer Parameters (ABCD) (Chain Parameters)

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -i_2 \end{bmatrix}$$

not in but in

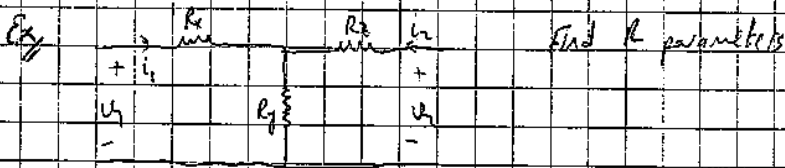

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



$$v_1 = I_{s1} R_1 + (I_{s1} + I_{s2}) R_4$$

$$v_1 = \begin{bmatrix} (R_1 + R_4) & R_4 \\ R_4 & R_2 \end{bmatrix} \begin{bmatrix} I_{s1} \\ I_{s2} \end{bmatrix}$$

$$v_2 = I_{s2} R_2 + (I_{s1} + I_{s2}) R_4$$


$$v_2 = \begin{bmatrix} R_4 & (R_4 + R_2) \\ R_4 & R_2 \end{bmatrix} \begin{bmatrix} I_{s1} \\ I_{s2} \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} (R_1 + R_4) & R_4 \\ R_4 & (R_4 + R_2) \end{bmatrix} \begin{bmatrix} I_{s1} \\ I_{s2} \end{bmatrix}$$

R

$$G = R^{-1} = \begin{bmatrix} R_4 + R_2 & -R_4 \\ -R_4 & (R_1 + R_4) \end{bmatrix} \cdot \frac{1}{(R_1 + R_4)(R_4 + R_2) - (R_4)^2}$$

G parameters using analysis

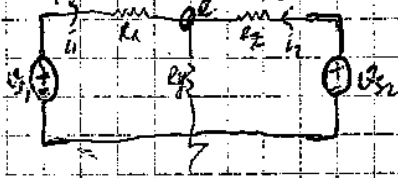

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} U_1 \\ U_2 \end{bmatrix} \rightarrow \text{Source}$$

unknowns

$$\frac{e - U_1}{R_1} + \frac{e}{R_3} + \frac{e - U_2}{R_2} = 0 \quad \text{Find } e?$$

$$i_1 = \frac{U_1 - e}{R_1}$$

$$i_2 = \frac{U_2 - e}{R_2}$$

$$\left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2} \right) e = \frac{U_1}{R_1} + \frac{U_2}{R_2}$$

$$i_1 = \frac{U_1}{R_1} - \frac{e}{R_1}$$

$$e = \frac{U_1/R_1 + U_2/R_2}{\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2}}$$


$$i_1 = \left(\frac{1}{R_1} - \frac{R_2 R_3}{R R_1} \right) U_1 - \left(\frac{R_2}{R} \right) U_2$$

\downarrow g_{11} \downarrow g_{12}


$$e = \frac{U_1 R_2 R_3 + U_2 R_1 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$i_1 = g_{11} U_1 + g_{12} U_2$$

T Network

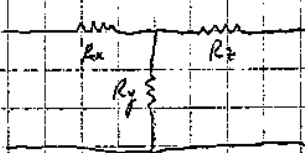

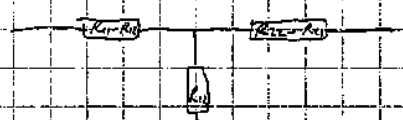
$$\begin{aligned} R_{11} &= R_1 + R_3 \\ R_{21} &= R_3 = R_3 \\ R_{22} &= R_2 + R_3 \end{aligned}$$



A given R parameters can be used to form a T-network


G parameters and π Network

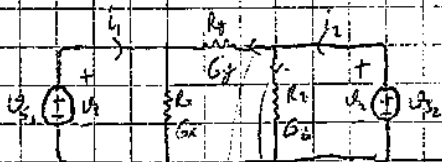

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} U_1 \\ U_2 \end{bmatrix}$$

$$i_1 = U_2 G_3 + (U_1 - U_2) G_1$$

$$= (-G_1) U_1 + (G_1 + G_3) U_2$$

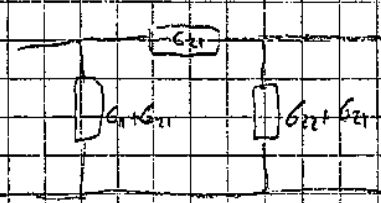

NOTE ON Two Ports

① Symmetry: R and G has to be symmetric?

\Rightarrow Symmetry occurs if we do not have dependent sources (only resistances \rightarrow symmetry)
(Inductors, capacitors \rightarrow symmetry)
(RLC)


$R = (R_{11}, R_{12}, R_{21}, R_{22}) ; R_{12} = R_{21}$

$$\begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

where ① $i_1 = 0 ; i_2 = I_s \rightarrow (u_1, u_2) = (R_{12} I_s, R_{22} I_s)$

② $i_1 = I_s ; i_2 = 0 \rightarrow (u_1, u_2) = (R_{11} I_s, R_{21} I_s)$

② Interconnection of Two Parts

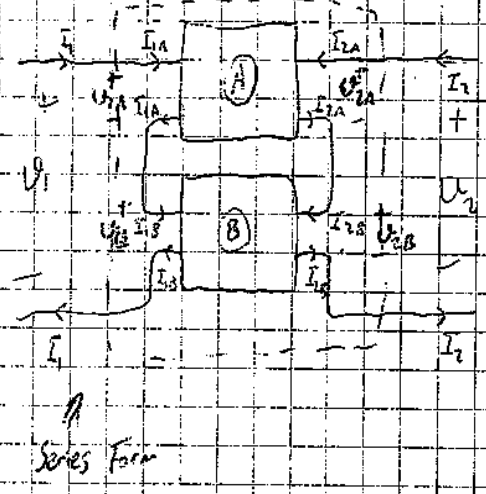


Parameters $\rightarrow R_A, R_B$

$R^{combined} = R_A + R_B$

$u_2 = u_{2A} + u_{2B}$
 $u_1 = u_{1A} + u_{1B}$


$I_{2A} = I_{2B} = I_2$
 $I_{1A} = I_{1B} = I_1$

Parallel Form

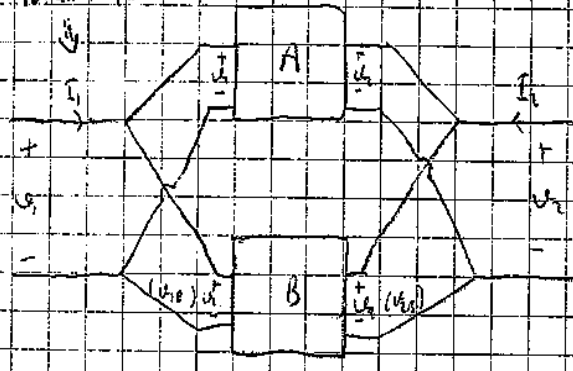

$G^{combined} = G_A + G_B$

③ Two Parts with Feedback Connection

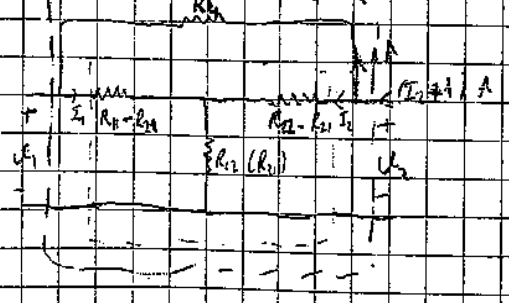

$$\begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

④ Transformers




$$\frac{U_1}{U_2} = N$$

$$\frac{i_1}{i_2} = \frac{1}{N}$$

because both i_1 and i_2 is entering

$N = 1$ (Turns ratio)

Ideal transformer

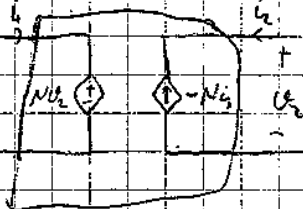

Note: Physically transformers can only operate with AC input BUT


In EEDP, we use transformers in DC circuit analysis to practice analysis with transformers

$$P_1 = U_1 i_1 \quad , \quad P_2 = U_2 i_2$$

$$P_1 + P_2 = 0 \Leftrightarrow \text{Ideal transformer}$$

On Parameter Calculation


R parameters

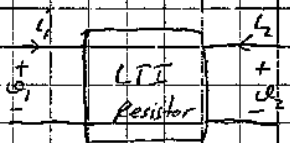

$$\begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$U_1 = r_{11} i_1 + r_{12} i_2$$

$$U_2 = r_{21} i_1 + r_{22} i_2$$

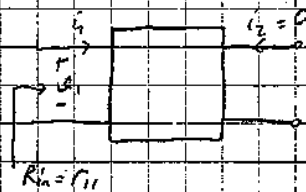


$$R_{in} = \frac{U_1}{i_1} \Big|_{i_2=0}$$

$$R_{in} = r_{11}$$




$$R_{out} = \frac{U_2}{i_2} \Big|_{i_1=0}$$


$$R_{out} = r_{22}$$

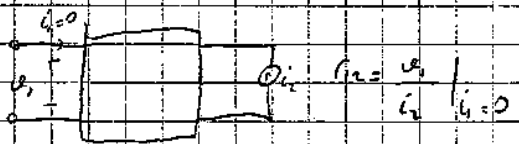

$$R_{21} = \frac{U_1}{i_2} \Big|_{i_1=0}$$

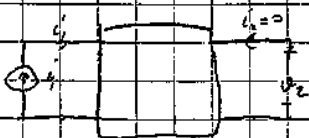

$$R_{12} = \frac{U_2}{i_1} \Big|_{i_2=0}$$

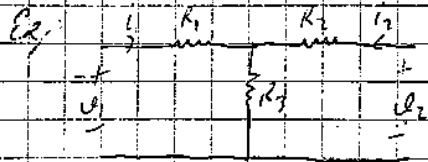

$$\begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$r_{11} = \frac{u_1}{i_1} \Big|_{i_2=0} = R_1 + R_2 \quad r_{12} = \frac{u_1}{i_2} \Big|_{i_1=0} = R_2$$

$$r_{22} = \frac{u_2}{i_2} \Big|_{i_1=0} = R_2 + R_1 \quad r_{21} = \frac{u_2}{i_1} \Big|_{i_2=0} = R_2$$

$$R = \begin{bmatrix} R_1 + R_2 & R_2 \\ R_2 & R_1 + R_2 \end{bmatrix}$$

Note R is symmetric ($r_{11} = r_{22}$) as expected since the network consists of only resistances.

Ex, Express H parameters in terms of R parameters

$$u_1 = r_{11} i_1 + r_{12} i_2 \quad (1) \quad u_1 = h_{11} i_1 + h_{12} u_2$$

$$u_2 = r_{21} i_1 + r_{22} i_2 \quad (2) \quad i_2 = h_{21} i_1 + h_{22} u_2$$

$$h_{11} = \frac{u_1}{i_1} \Big|_{u_2=0} \rightarrow (2) \rightarrow i_2 = -\frac{r_{21} i_1}{r_{22}} \text{ substitute } \rightarrow u_1 = r_{11} i_1 + \frac{r_{12} r_{21} i_1}{r_{22}}$$

$$h_{11} = \frac{u_1}{i_1} = \frac{r_{11} r_{22} + r_{12} r_{21}}{r_{22}} = \frac{|R|}{r_{22}}$$


$$h_{21} = \frac{i_2}{i_1} \Big|_{u_2=0} = -\frac{r_{21}}{r_{22}} \quad (3)$$

$$h_{22} = \frac{i_2}{u_2} \Big|_{i_1=0} = -\frac{1}{r_{22}}$$

$$h_{12} = \frac{u_1}{u_2} \Big|_{i_1=0} = \frac{r_{12}}{r_{22}}$$

If R matrix is symmetric ($r_{12} = r_{21}$) $\rightarrow H$ has the property that ($h_{12} = -h_{21}$)

Terminated Two Ports

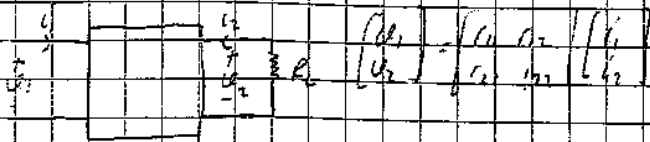

2 equations from two port equations
1 equation from load



$$u_2 = -R_L i_2$$

$$-R_1 i_1 = R_1 i_1 + R_2 i_2 \Rightarrow i_2 = \frac{-R_1}{R_1 + R_2} i_1$$

$$U_1 = R_1 i_1 + R_2 i_2$$

$$\frac{U_1}{i_1} = \frac{R_1 - R_1 R_2}{R_1 + R_2} \Rightarrow R_{in} = \frac{R_1 R_2 + R_1 R_2 - R_1 R_2}{R_1 + R_2}$$

2PS-II
(14=)

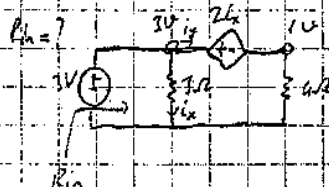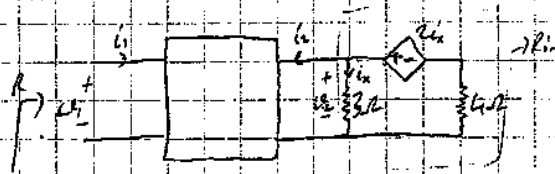

$$i_x = \frac{3}{3} = 1 \text{ A}$$


$$i_y = \frac{1}{4} \text{ A}$$

$$i_{sc} = 1 + \frac{1}{4} = 1.25 \text{ A}$$

$$R_{in} = \frac{3}{1.25} = \frac{12}{5} \Omega = 2.4 \Omega$$

if it is given
in question
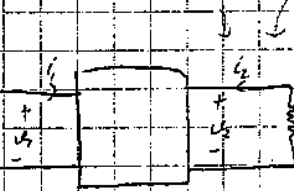
$$\begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} 3 & 2 \\ 2 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



$$U_2 = -2i_1$$

$$U_2 = 2i_1 - 4i_2$$

$$-1.4i_1 = 2i_1 + 4i_2$$


$$i_2 = -3.2i_1$$

$$U_1 = 3i_1 + 2i_2$$

$$U_1 = 3i_1 - 2 \cdot 3.2i_1$$

$$U_1 = \frac{3.8}{1.6} i_1$$
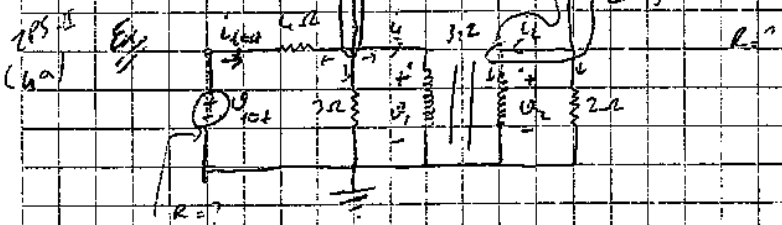
$$R = \frac{U_1}{i_1} = \frac{19}{8} \Omega = 2.375 \Omega$$



$$\text{KCL at } e_1: e_1 - \frac{e_1 - U_{test}}{2} - \frac{e_1 - \frac{3}{2}e_1}{3} + i_2 = 0 \xrightarrow{\times 2} (4+3+2)e_1 + 12i_2 = 3U_{test}$$



$$\text{KCL at } e_2: \frac{2e_1 - e_2}{3} - \frac{2e_1}{3} + i_2 = 0 \xrightarrow{\times 6} (4+4)e_1 - 9i_2 = 0$$

$$\begin{bmatrix} 9 & 12 \\ 4 & -9 \end{bmatrix} \begin{bmatrix} e_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 3U_{test} \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} e_1 \\ i_2 \end{bmatrix} = \frac{1}{-81-42} \begin{bmatrix} 9 & 12 \\ -4 & 9 \end{bmatrix} \begin{bmatrix} 3U_{test} \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{3}{11} U_{test} \\ \frac{1}{11} U_{test} \end{bmatrix}$$

$$i_{test} = \frac{U_{test} - e_1}{2}$$
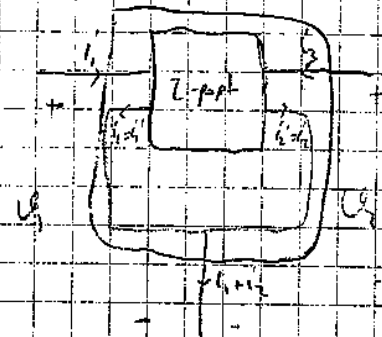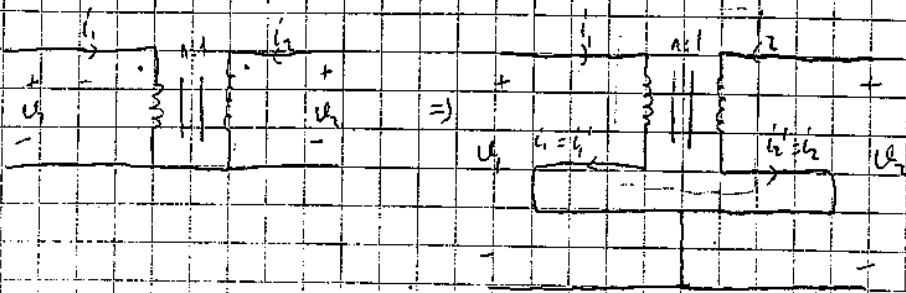
$$i_{test} = \frac{U_{test} - \frac{3}{11} U_{test}}{2} \Rightarrow i_{test} = \frac{4}{11} U_{test} \Rightarrow R = \frac{U_{test}}{i_{test}} = \frac{11}{4} \Omega$$



3 Terminal - 2 port



Ex
Then 3-terminal 2 port
 $i_1' = i_1, i_2' = i_2$

Reciprocity:


① R, G, H parameters have some special properties (symmetry or anti-symmetry (for H)) when 2 port is question does include only resistors, inductors, capacitors

Ex $r_{12} = r_{21}, g_{12} = g_{21}, h_{12} = -h_{21}$

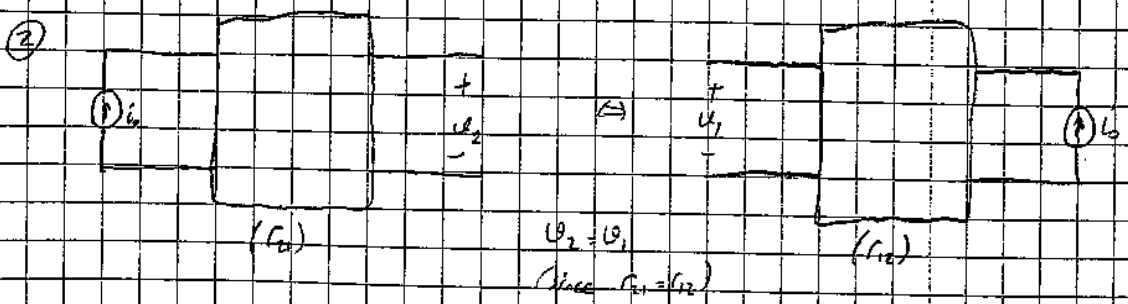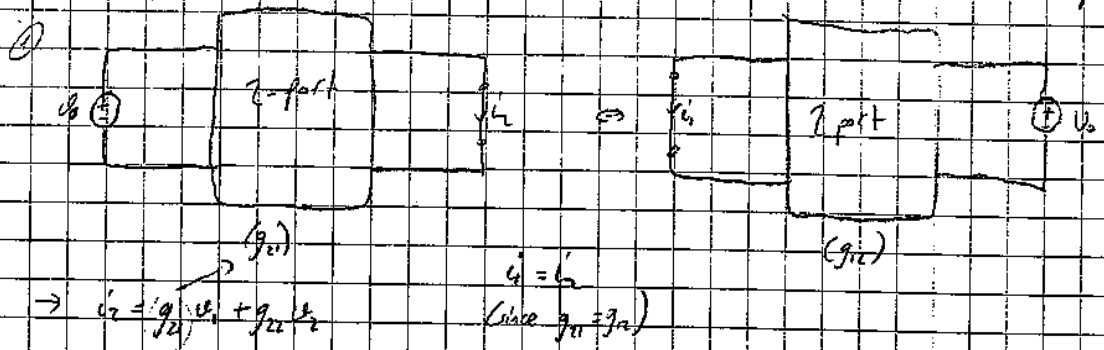② Reciprocity makes use of observation ① and is used also in measurements or experiments:



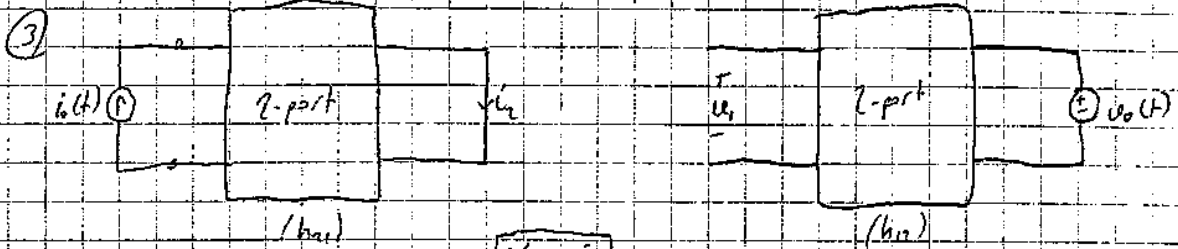
$\rightarrow V_1 = r_{11} i_1 + r_{12} i_2$
 $\rightarrow V_2 = r_{21} i_1 + r_{22} i_2$



Source: $i(t) - v(t)$

$$V_1 = I_2$$

Proofs of Reciprocity laws

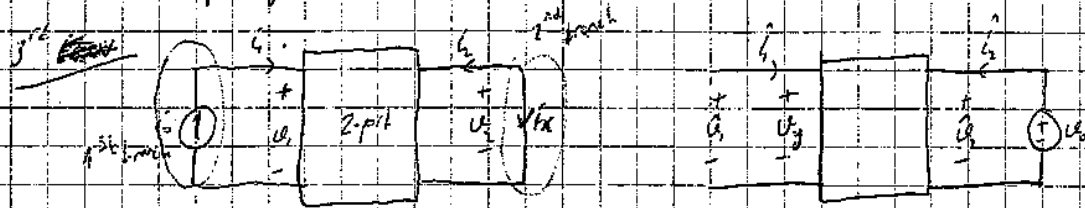

We would like to prove $i_1 = u_2$

$$\sum_{k=1}^{\# \text{ branches}} V_k \hat{i}_k = \sum_{k=1}^{\# \text{ of branches}} \hat{V}_k i_k = 0$$


$$V_1(-i_1) + V_2(-i_2) + \sum_{k=3}^{\# \text{ 2-port branches}} V_k \hat{i}_k = \hat{V}_1(-i_1) + \hat{V}_2(-i_2) + \sum_{k=3}^{\# \text{ 2-port branches}} \hat{V}_k i_k$$

$$0 = V_1(-i_1) + V_2(-i_2)$$

$$i_1(t) = v_2(t), \text{ i.e. } I_1 = V_2$$

$$\Rightarrow 0 = V_1 + I_2 \Rightarrow \hat{V}_1 = -I_2 \Rightarrow \boxed{I_1 = I_2}$$

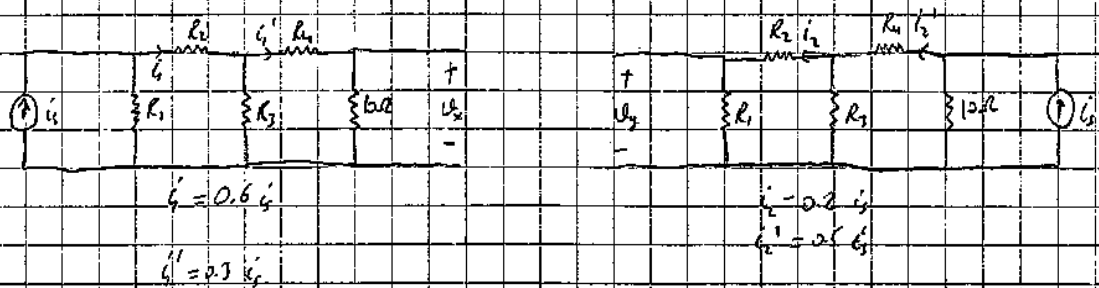Ex. Two sets of measurements are made. Calculate R_1 .



$$i_1 = 0.6 i_2$$

$$i_1' = 0.3 i_2'$$

$$i_2 = 0.2 i_1$$

$$i_2' = 0.1 i_1'$$

From reciprocity:


$$V_1 = V_2$$

$$i_1' 10 \Omega = I_1 R_1$$

$$(0.3 i_1) 10 \Omega = (0.2 i_1) R_1$$

$$R_1 = 15 \Omega$$



Symmetric Circuits

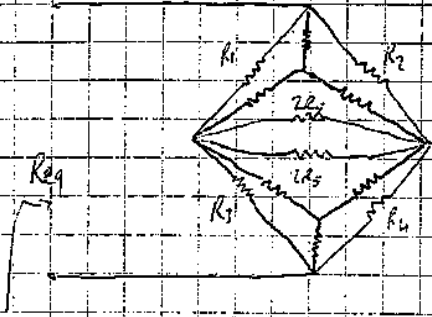

① $R_1 = R_2$ and $R_3 = R_4$ $R_{eq} = ?$



Write the node equations for V_a, V_b, V_c

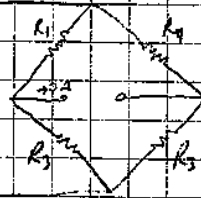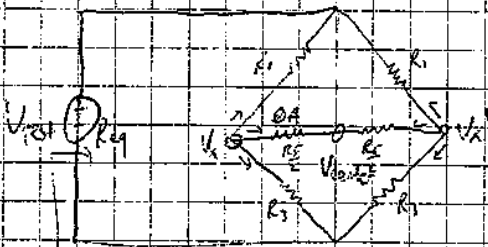If you exchange $V_a \leftrightarrow V_c$, you have the same equation




$R_{eq} = \frac{R_1 + R_2}{2}$

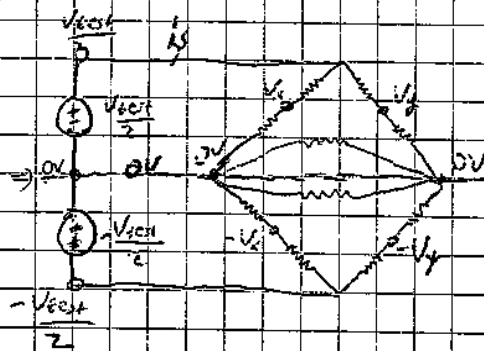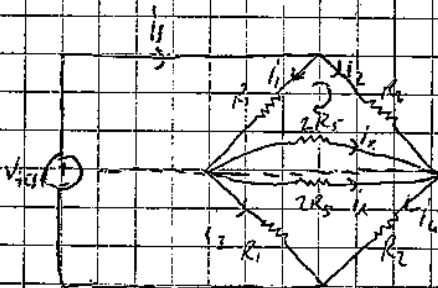
② $R_1 = R_2$ and $R_3 = R_4$ $R_{eq} = ?$



$i_1 = \frac{V_{test}}{2(R_1 || R_2)} \Rightarrow R_{eq} = \frac{V_{test}}{i_1} = 2(R_1 || R_2)$



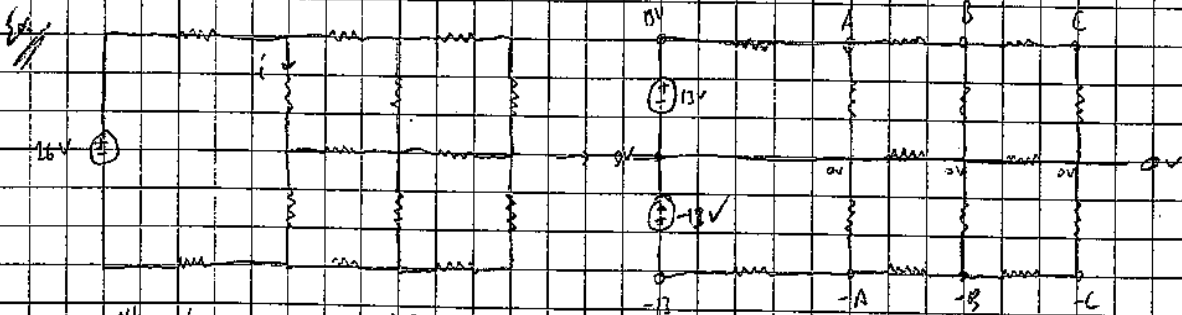


All resistors are 1Ω. $i = ?$


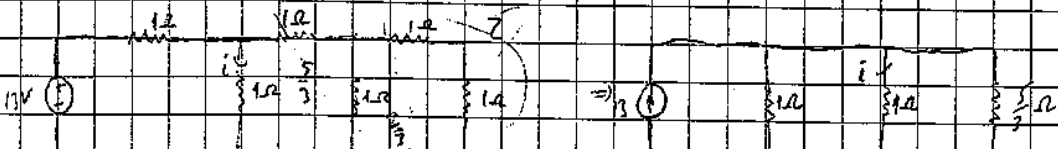


$i = \frac{13}{1+1+2} = 1.5A$

All resistances 1Ω , $\epsilon = 1$

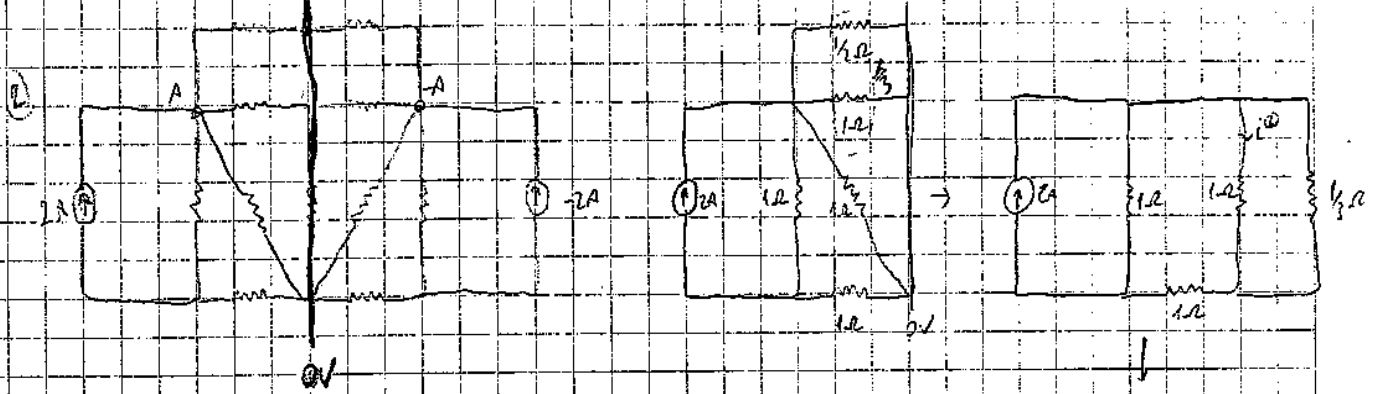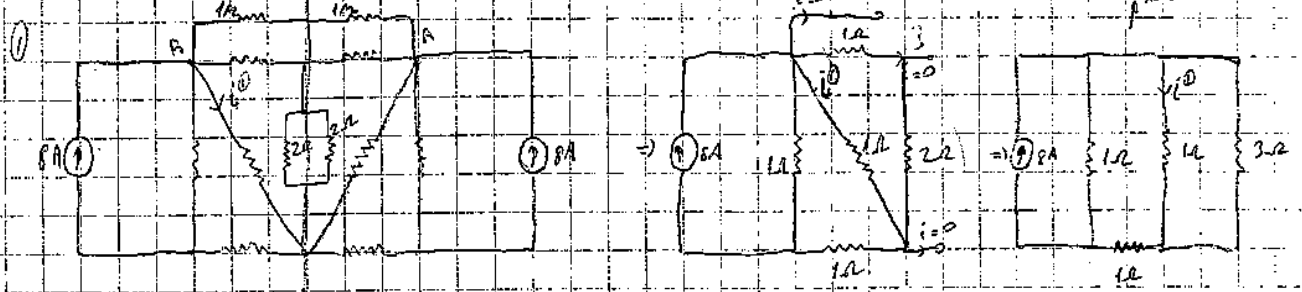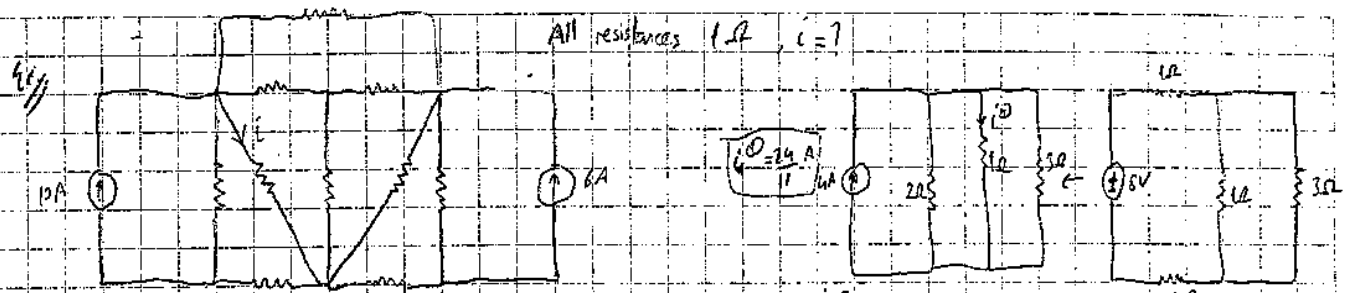


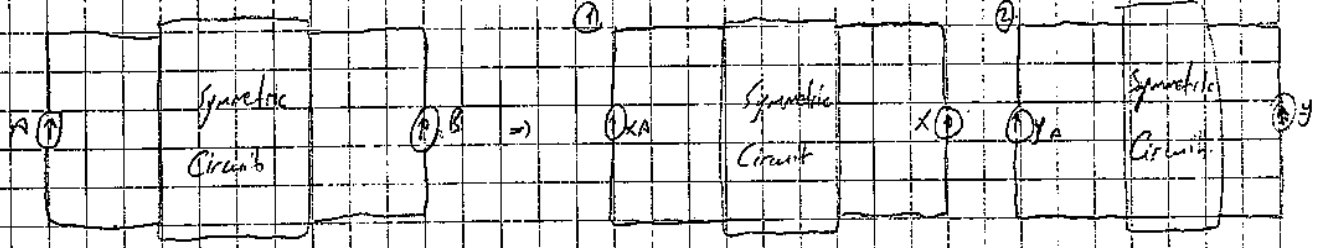
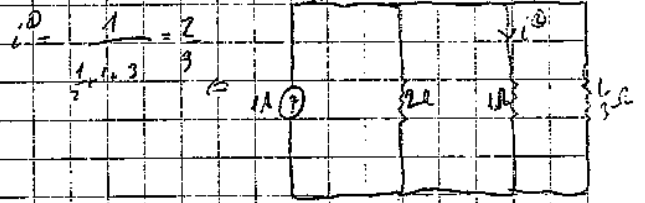
$$C = i^{\text{D}} + i^{\text{D}} = \frac{20}{11} + \frac{2}{9} = \frac{1738}{99}$$




$$\begin{cases} x + y = A \\ x - y = B \end{cases} \Rightarrow \begin{cases} x = \frac{A+B}{2} \\ y = \frac{A-B}{2} \end{cases}$$

Diodes (Non Linear Resistors)

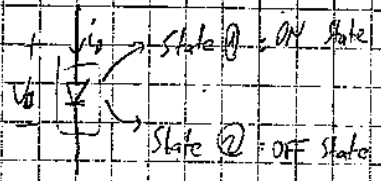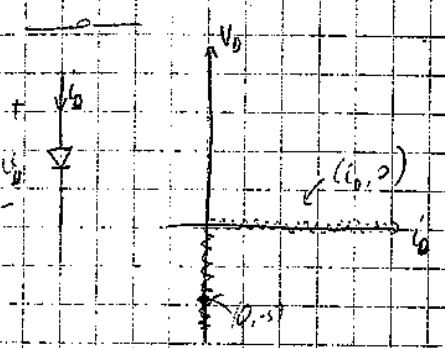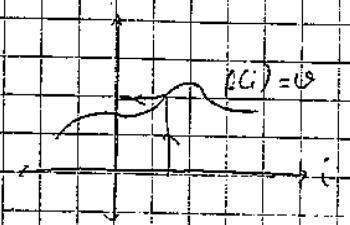
- * Current Controlled Component ($i_D = f(v_D)$)
- * Voltage Controlled Component ($i_D = g(v_D)$)



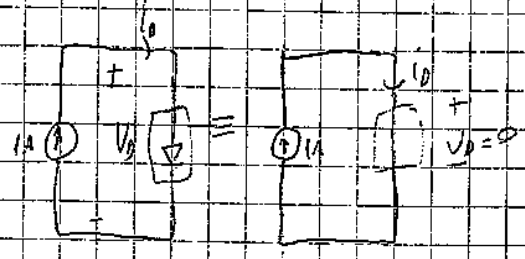
ON State (Conduction State): $i_D > 0$ (diode conducts)
 $v_D = 0$ (short circuit)



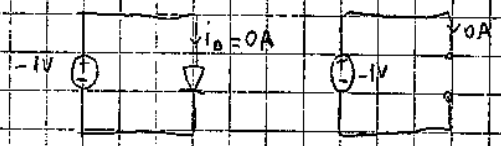OFF STATE (No Conduction): $v_D < 0 \rightarrow i_D = 0$



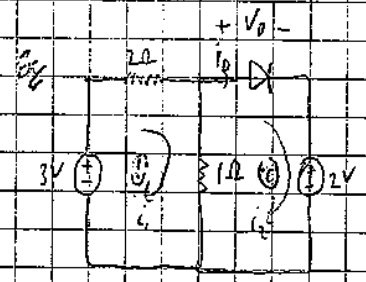OFF: Open-Circuit (No current conduction)




KVL around mesh ②:
 $2 + (i_D - i_1)1 + \int_{\text{diode}} v_D = 0$

KVL around mesh ①:
 $-3 + 2i_1 - (i_1 - i_D)1 = 0$

$v_{\text{diode}} = \int_{\text{diode}} v_D = (i_D)$



What we do is:

Assume diode is OFF (Assume $v_D < 0$)

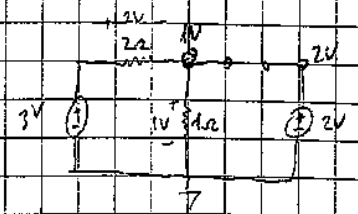


$v_D = (1-2)$
 $v_D = -1V$


Assumption holds ✓
 Analysis complete

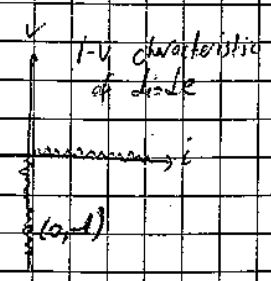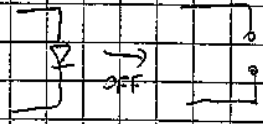


Bilateral Components

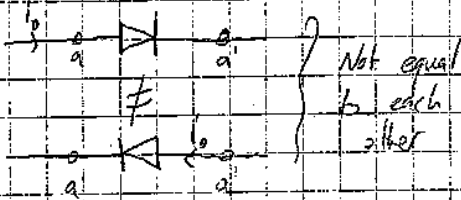

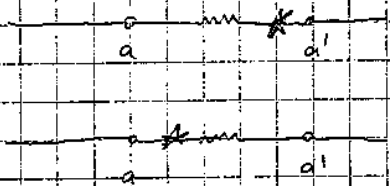
Simple LTI resistors (Ohm's law) are unilateral components.



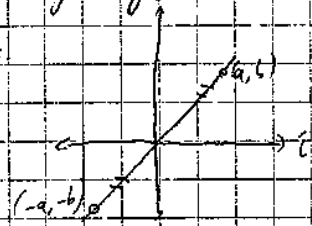Unilateral components have symmetry across the origin in their $i-v$ characteristics




Practical Diodes

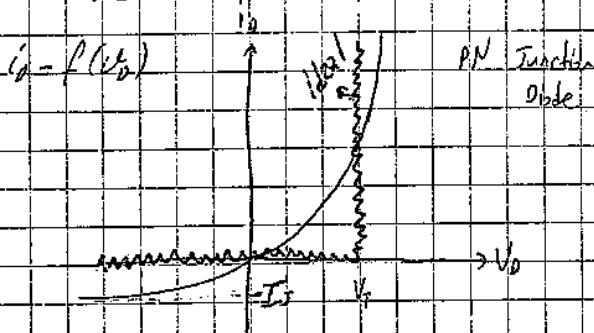







$$i_D = I_S (e^{V_D/V_T} - 1)$$

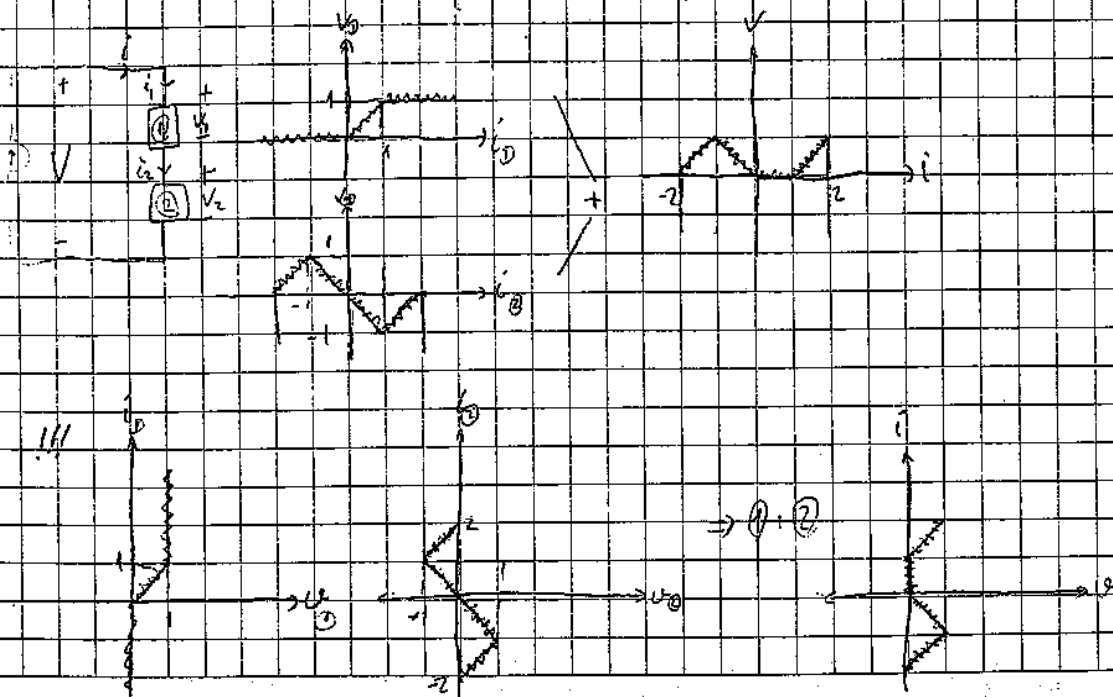Series and Parallel Combination of Ideal Diodes (Graphical Solutions)







Diodes (Series and Parallel Combination)

Analysis:

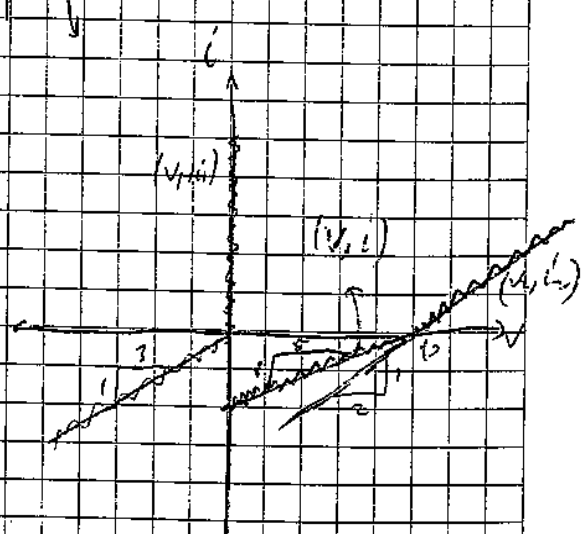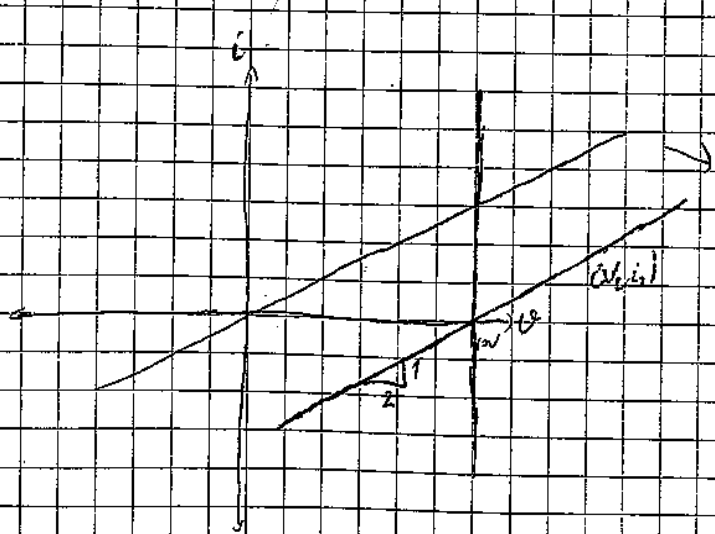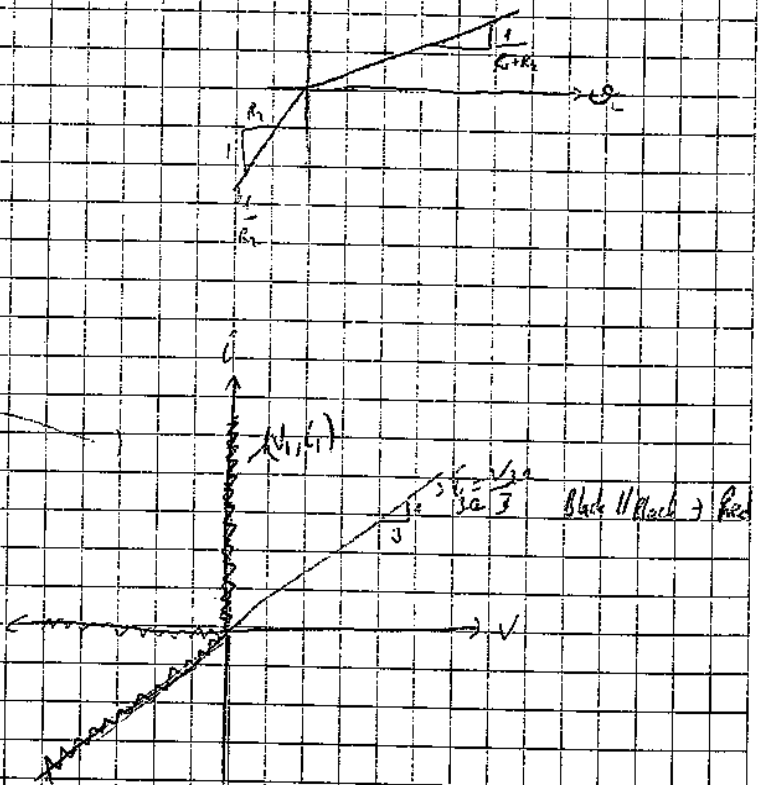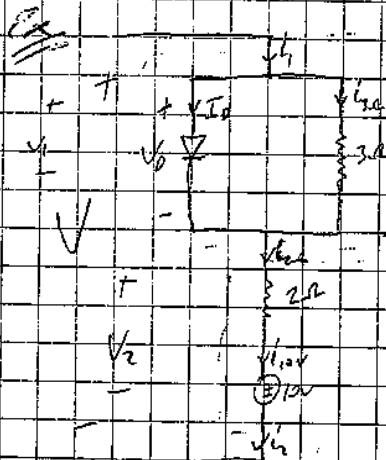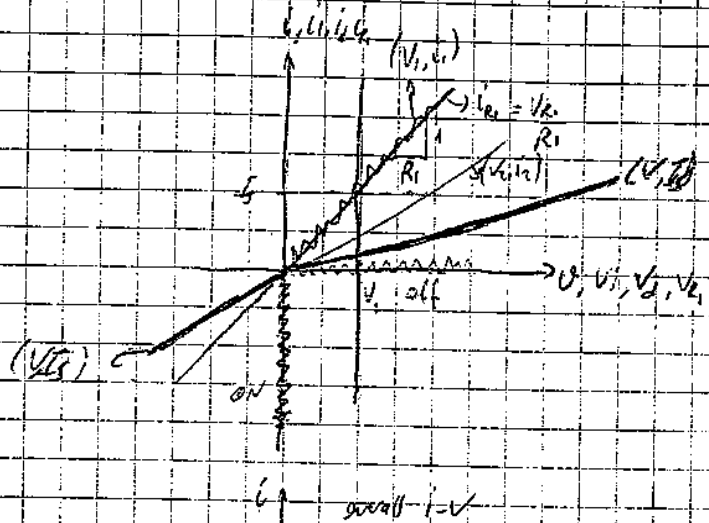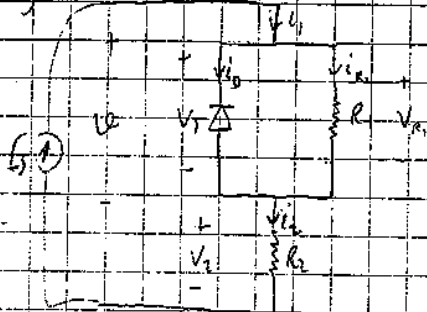


Synthesis (Design)

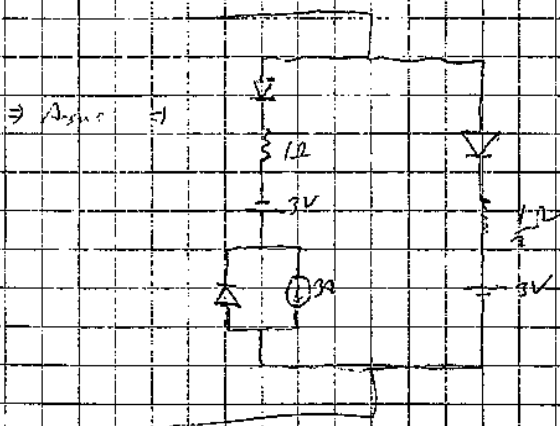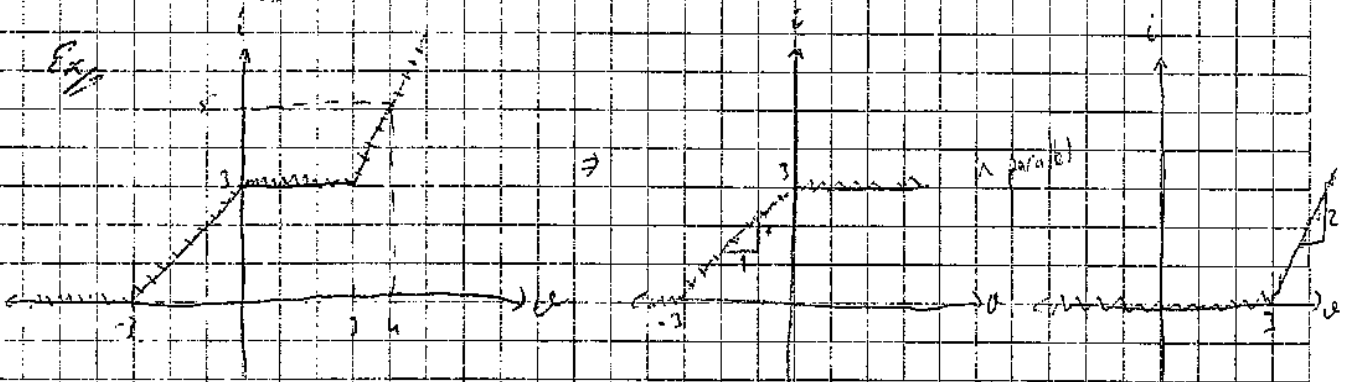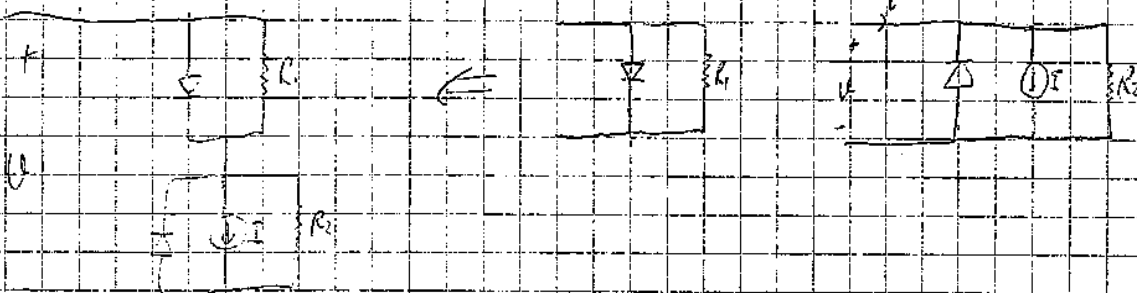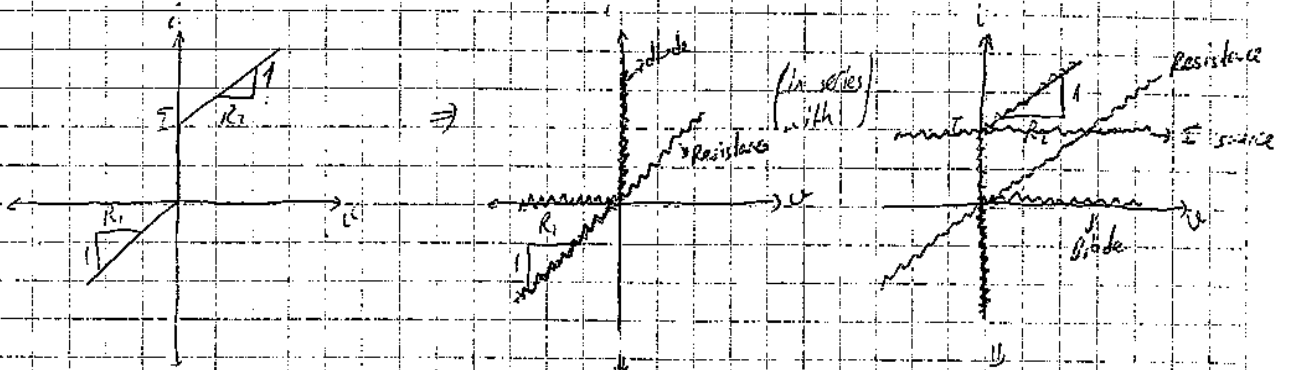
Design a circuit with R, Voltage source, current source and diodes such that



Diode Applications

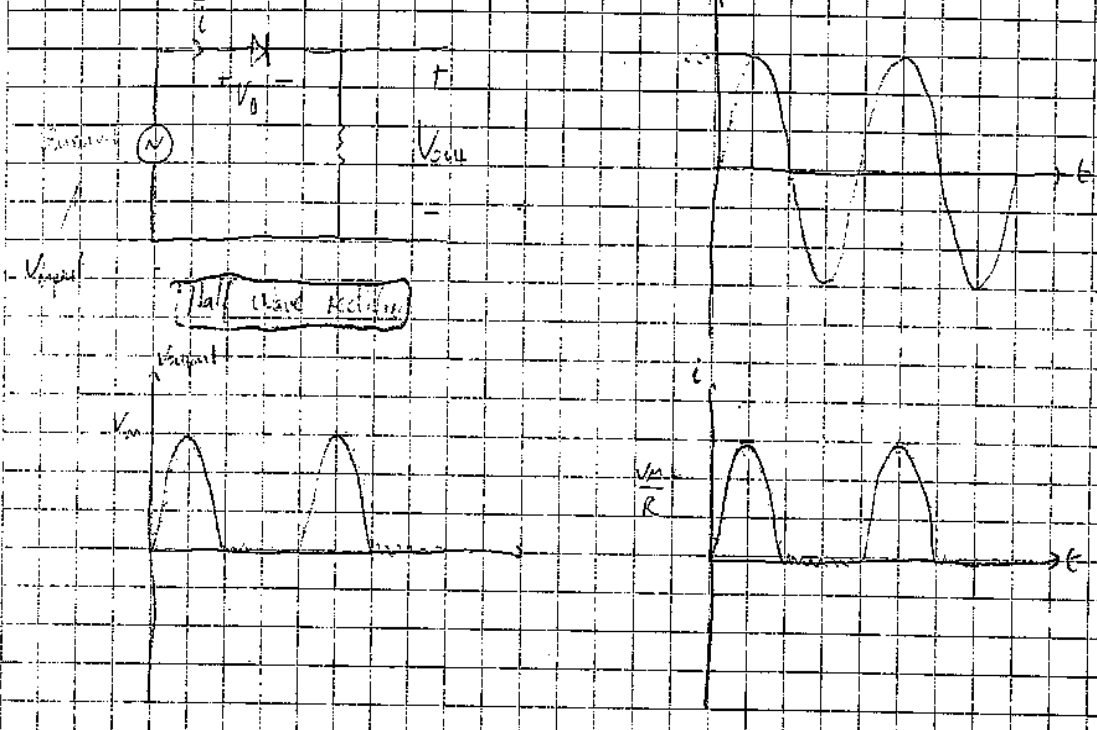



Full Wave Rectifier

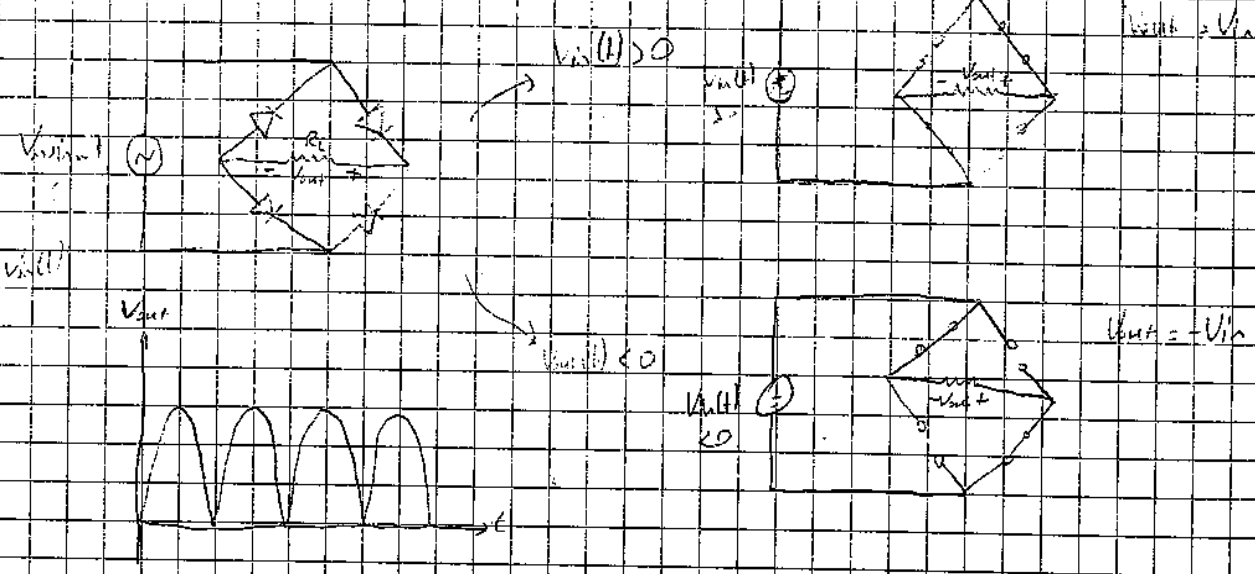

Circuits with a single non-linear element


Load Line:

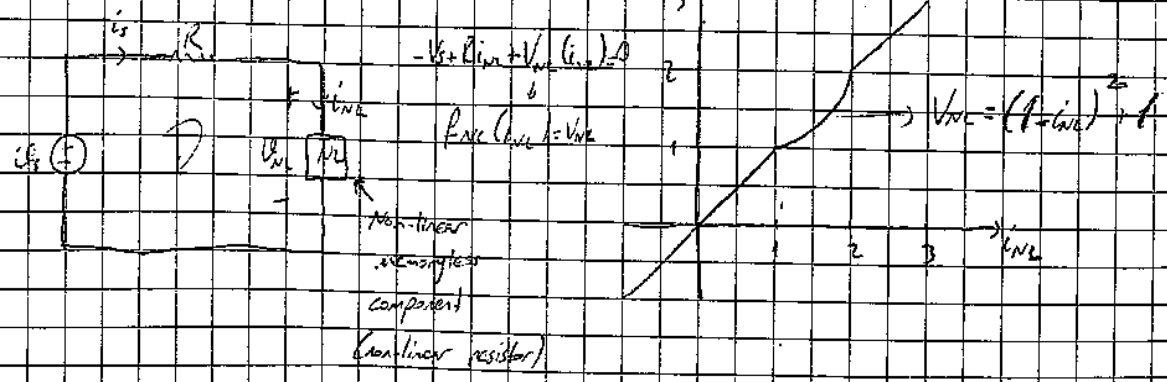

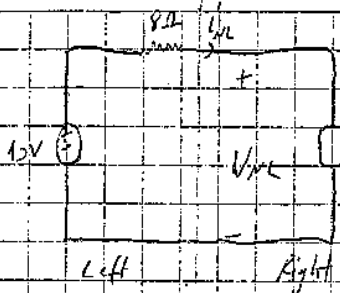


$$0 = -10 + R_{NL} + V_{NL}$$

P_{av}

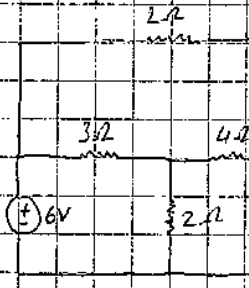


$$i_R = \begin{cases} 0.03 V_{NL}^2 & V_{NL} \geq 0 \\ 0 & V_{NL} < 0 \end{cases}$$

$$P_m = ((3/2) + 4)(12) = \frac{13}{9}$$

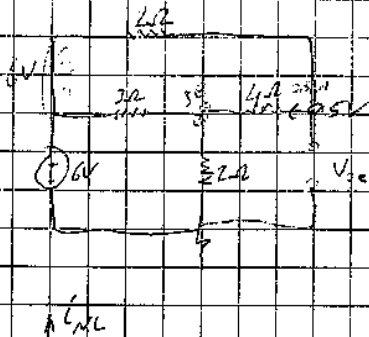


$$\frac{e-6}{3} + \frac{e}{2} = \frac{e-6}{2+h} = 0$$

$$|e = 3 \Rightarrow (V_{oc} = 5V)$$

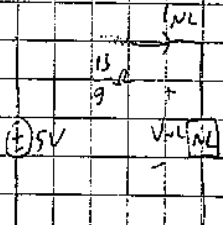

$$-5 + \frac{13}{9} V_{NL} + V_{NL} = 0$$
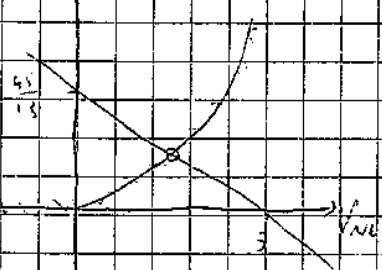
$$V_{NL} = \frac{45}{13} = \frac{3}{13} V_{oc}$$




$$\frac{45}{13} - \frac{9}{13} V_{NL} = (0.03)(V_{NL})^2$$

$$45 - 9 V_{NL} = 0.39 (V_{NL})^2 \quad V_{NL} \geq 0$$

$$V_{NL} = 4.72$$

Small Signal Analysis

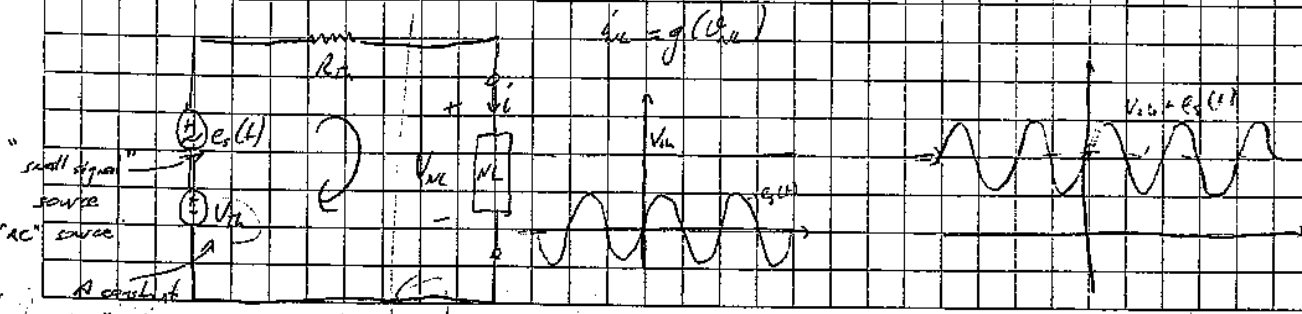Let's assume that we have a circuit with a single non-linear element. The Thévenin equivalent of this circuit is:




"small signal" source

Thévenin eq. seen

2) Find small signal conductance parameters

$$g_{m, \text{small}} = g'(\varphi_{m, \text{DC}}) \rightarrow \text{DC op. point}$$

3)

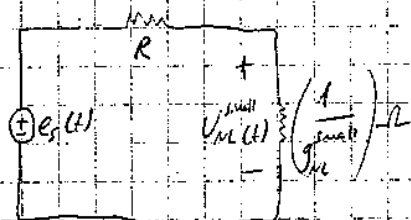


Find $\varphi_{m, \text{small}}(t)$

4)

Final solution

$$v_{m, \text{small}}(t) \approx v_{m, \text{DC}} + v_{m, \text{small}}(t)$$


EMH

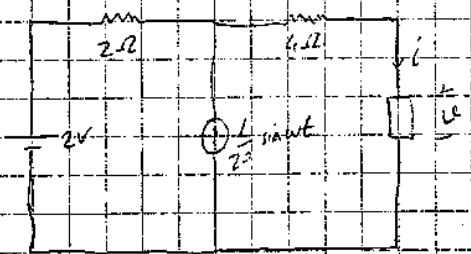

Thermin eq. Req = 6 ohm

$$v_{oc} = ? = 2 + \frac{1}{20} \sin \omega t \cdot 2 = (2 + 0.1 \sin \omega t)$$

1)

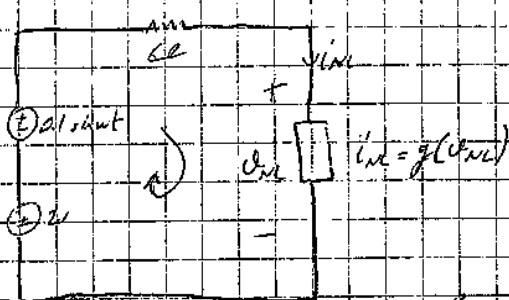

DC op. point = (Neglect AC source)

$$-2 + 6i_{m, \text{small}} + v_{m, \text{small}} = 0$$


$$-2 + 6v_{m, \text{small}}^2 + v_{m, \text{small}} = 0 \quad (\text{assuming } i_{m, \text{small}} = v_{m, \text{small}}^2 \text{ i.e. } v_{m, \text{small}} > 0)$$

$$v_{m, \text{small}}^2 + \frac{1}{6} v_{m, \text{small}} - \frac{1}{3} = 0 \rightarrow v_{m, \text{small}} = \left\{ \frac{1}{2}, \frac{-2}{3} \right\}$$

op. point.

DC op. point $\Rightarrow (v_{m, \text{DC}}, i_{m, \text{DC}}) = \left(\frac{1}{2}, \frac{1}{4} \right)$

then

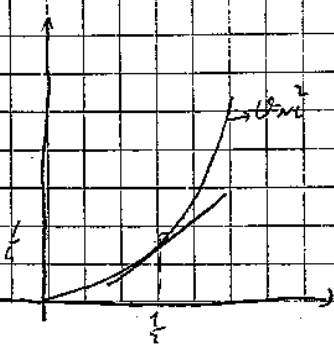


2) $i_{m, \text{small}} = v_{m, \text{small}}^2 = g'(v_{m, \text{small}}) v_{m, \text{small}}$

$$= \frac{1}{4} + \frac{(v_{m, \text{small}} - \frac{1}{2})}{1} g'(\frac{1}{2}) v_{m, \text{small}}$$

$$= \frac{1}{4} + (v_{m, \text{small}} - \frac{1}{2}) \cdot 1$$



3

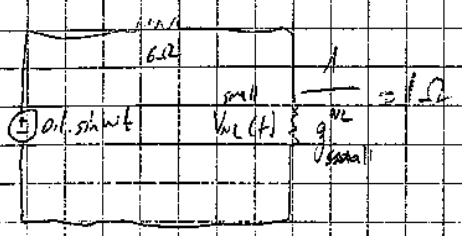



$$v_{L(t)} = 0.1 \sin \omega t$$

$$v_{L(t)} = \frac{1}{2} + \frac{\sin \omega t}{7}$$

AC AC

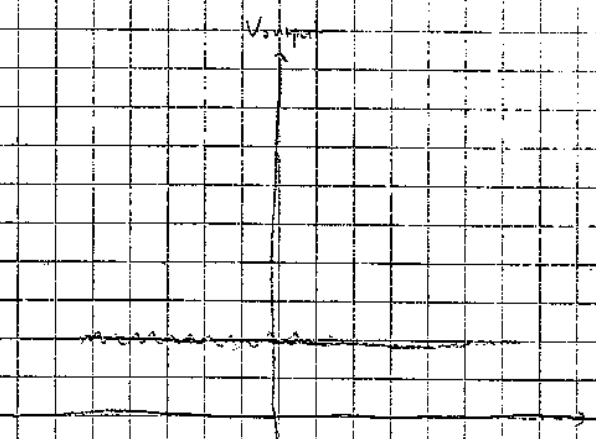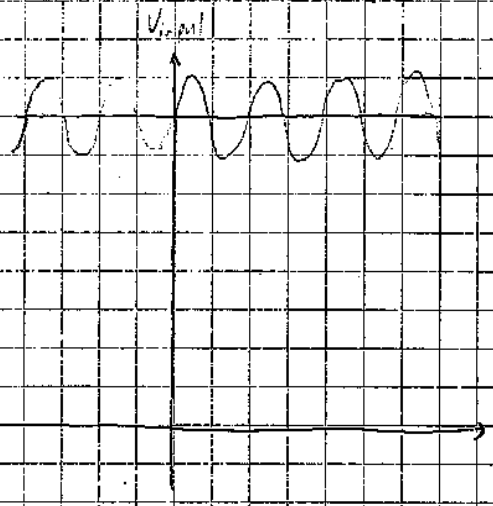


OPERATIONAL AMPLIFIERS

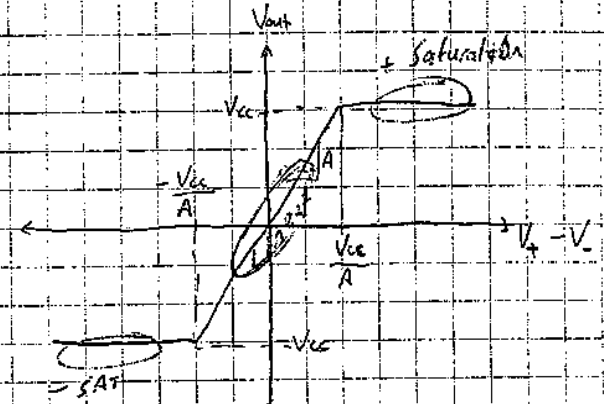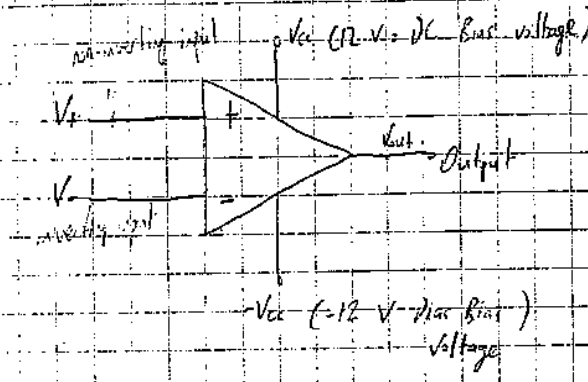

A: Open-loop gain (typically $10^5 - 10^8$)

A little more detailed model

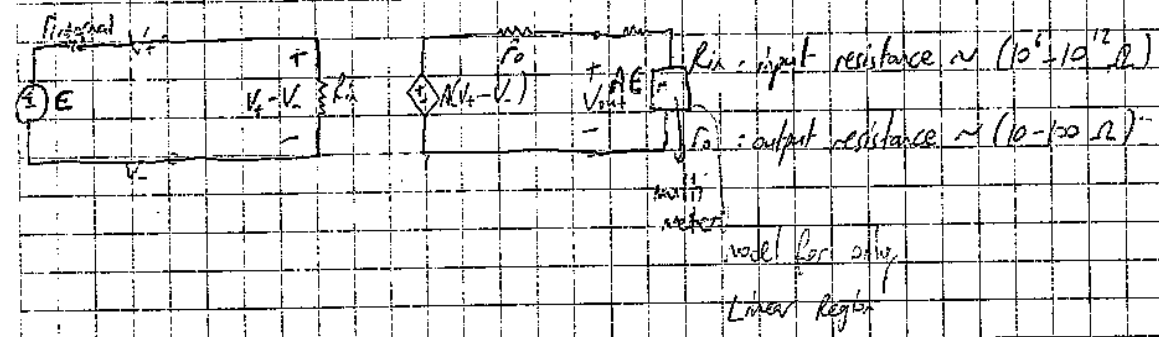

+SAT Region


$V_{out} = +E_{sat}$ and $(V_+ - V_-)$ should be positive and sufficiently large $(V_+ - V_-) \geq \frac{E_{sat}}{A}$

-SAT Region

$V_{out} = -E_{sat}$, $(V_+ - V_-) \leq -\frac{E_{sat}}{A}$


Ideal Op-Amp

For ideal Op-Amp

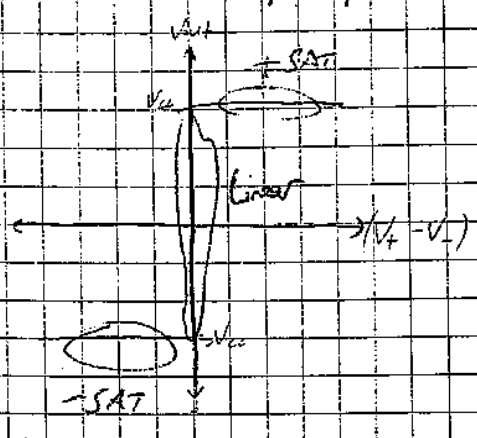

$R_{in} = \infty$, $R_{out} = 0$ (Linear region)

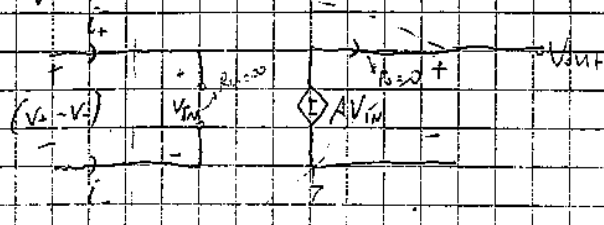
Using Ideal Op-Amp assumptions, we have in Linear Region;



(1) $V_+ = V_- = 0$ $A \leftarrow$ Linear region when $A = \infty$
 $(V_+ - V_-) = 0$

(2) $V_+ = V_-$ (for ideal opamp) in linear region



Inverting Amplifier (Ideal Op-Amp)

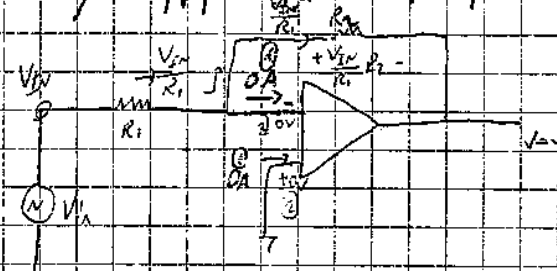

Assume linear region (assume V_{in} is adjusted so that Op-Amp is guaranteed to be in linear region)


$V_{out} = 0 - V_{R2}$

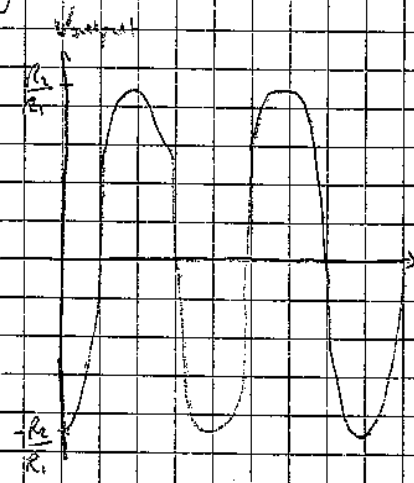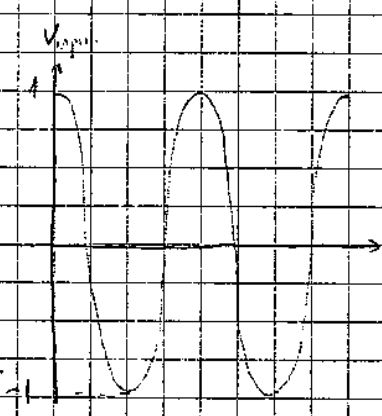$V_{out} = -V_{in} \frac{R_2}{R_1} \Rightarrow \boxed{\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}}$



Noninverting Op-Amp

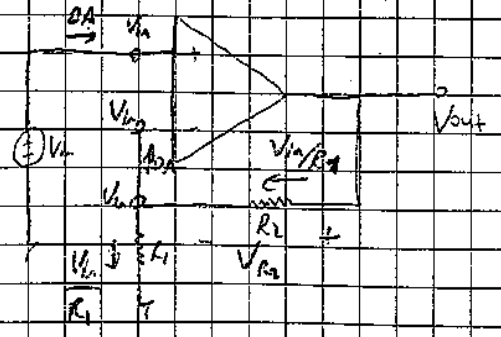Assume linear (V_{out} is sufficiently small)



Linear region ($A = \infty$)


$V_{R2} = \frac{V_{out}}{R_1} R_2$

$V_{out} = V_{in} + V_{R2}$

$V_{out} = V_{in} + \frac{V_{out} R_2}{R_1}$


$V_{out} = V_{in} \frac{R_1 + R_2}{R_1} \rightarrow$ a positive gain \rightarrow noninverting OPAMP

INVERTING AMPLIFIER

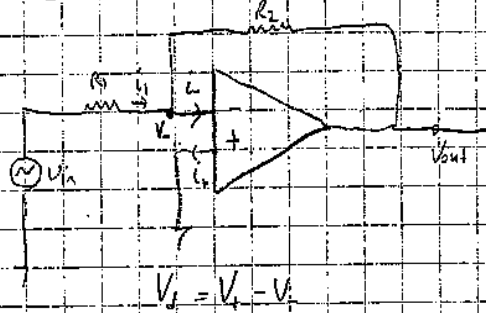

$$V_d = V_i - V_-$$

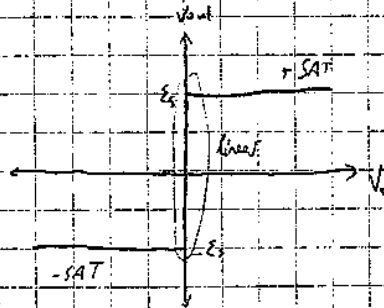Ideal Model ($A = \infty, R_{in} = \infty, r_o = 0$)



① Assume linear operation $\rightarrow (V_d = 0, i_- = i_+ = 0 A)$

$$V_d = 0 \rightarrow V_+ = V_- = 0$$

$$i_- = \frac{V_i}{R_i} \text{ and } V_{out} = 0 - V_{R2} = 0 - i_- R_2 = -\frac{R_2}{R_i} V_i$$


Check the validity of linear region assumption ($V_d = 0, -E_s < V_{out} < E_s$)

$$-E_s < -\frac{R_2}{R_i} V_i < E_s \Rightarrow \left(\frac{R_i}{R_2}\right) E_s > V_i > -\frac{R_i}{R_2} E_s \leftarrow \text{input in this results in}$$

opamp working in linear region

② Assume FSAT, ($V_i > 0, V_{out} = E_s$)
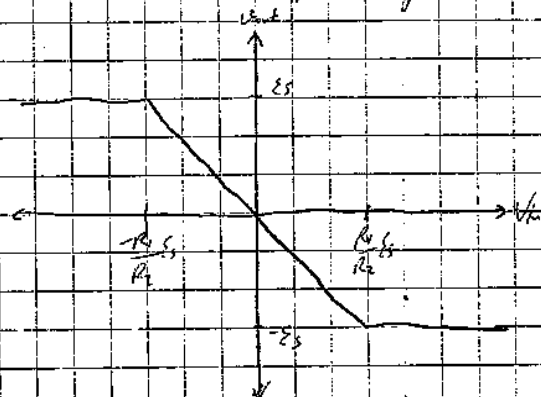
$$V_d = V_i - V_- > 0 \Rightarrow V_- < 0$$





Write equation at V_- :

$$\frac{(V_i - V_{out})}{R_i} + \frac{(V_- - V_{out})}{R_2} = 0$$

$$\left(\frac{1}{R_i} + \frac{1}{R_2}\right) V_- = \frac{V_i}{R_i} + \frac{-E_s}{R_2} \Rightarrow V_- = \frac{R_2}{R_i + R_2} V_i + \frac{R_i}{R_i R_2} \frac{-E_s}{E_s} < 0 \Rightarrow V_i < \frac{R_i}{R_2} E_s$$

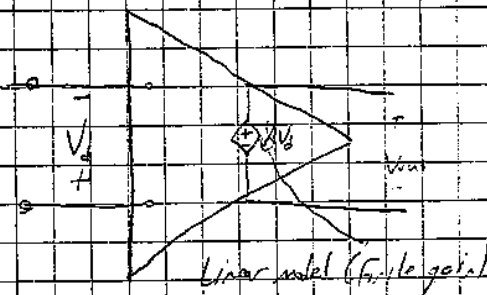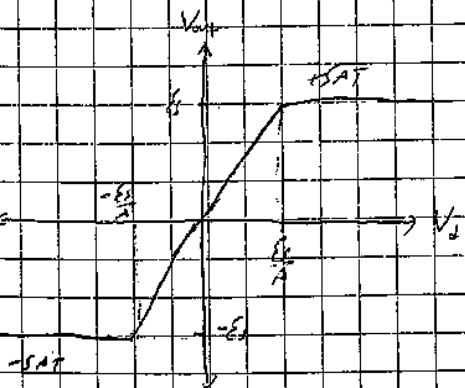Finite Gain ($A = \text{finite}, R_{in} = \infty, r_o = 0$)




Linear model (finite gain)

1) Assume linear:

$$|V_s| < E_s/A \rightarrow |V_-| < E_s/A$$

$$|V_{out}| < E_s \quad i_- = i_+ = 0 \quad (R_{in} = \infty)$$

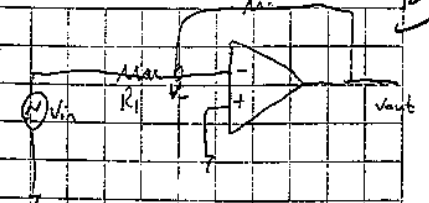

KCL at V_- :

$$-AV_- = -AV$$

$$\frac{(V_- - V_{in})}{R_1} + \frac{(V_- - V_{out})}{R_2} = 0$$


$$R_2(V_- - V_{out}) + R_1(V_- + AV_-) = 0 \Rightarrow V_- = \frac{R_2}{R_2 + (A+1)R_1} V_{in}$$

For the validity of linear region assumption

$$|V_-| < \frac{E_s}{A} \quad |V_{out}| < \frac{E_s(R_2 + (A+1)R_1)}{AR_2} \quad \text{if } A \rightarrow \infty \quad |V_{out}| < \frac{E_s R_1}{R_2}$$

$$V_{out} = AV_- = -AV$$
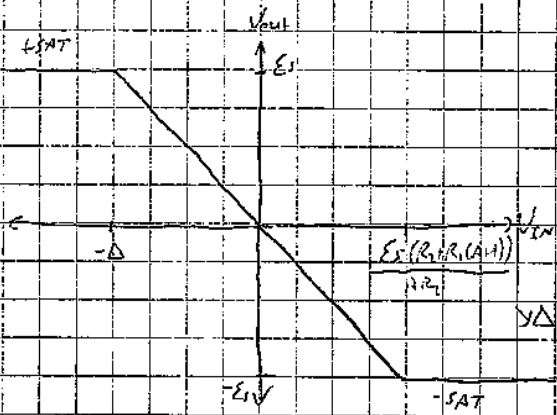
$$V_{out} = -A \frac{R_2}{R_2 + (A+1)R_1} V_{in} \quad A \rightarrow \infty \quad V_{out} = -\frac{R_2}{R_1} V_{in}$$



2) Assume -SAT

$$(V_- > \frac{E_s}{A}), R_{in} = \infty \quad (i_- = i_+ = 0)$$

Write node equation at V_-

$$\frac{(V_- - V_{in})}{R_1} + \frac{(V_- - V_{out})}{R_2} = 0$$


$$V_- = \frac{R_2 V_{in} + R_1 E_s}{R_1 + R_2}$$

$$V_{in} > \frac{E_s}{A} \rightarrow -V_{out} > \frac{E_s}{A}$$


$$V_{in} < -\frac{E_s}{A} \rightarrow V_{out} < -\frac{E_s}{A}$$

$$\frac{R_2 V_{in} + R_1 E_s}{R_1 + R_2} < -\frac{E_s}{A} \rightarrow V_{in} < -\left(\frac{E_s(R_1 + R_2)}{A R_2} + \frac{R_1 E_s}{R_2} \right)$$

Inverting Op-Amp

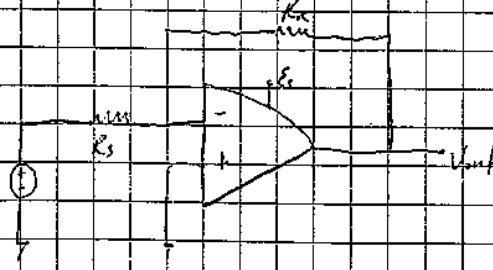

1) Assume linear region of operation

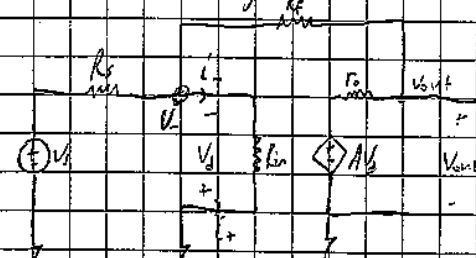

Node equation at V_- :

$$\frac{V_- - V_{in}}{R_s} + \frac{V_- - V_{out}}{R_f} = 0$$

$$\text{Node eqn at } V_+ : \frac{V_+ - V_-}{R_f} + \frac{V_+ - V_{out}}{R_s} = 0$$

$$V_{out} = -A + (V_+/R_s)$$

$$\frac{R_s(1+A+R_s/R_f)}{R_s} + \frac{R_s(1+A)}{R_s} + \frac{R_s}{R_f}$$

For the validity of the linear region mode


$$|V_{out}| < E_s \quad i_+ = 0 \quad i_- = 0$$

open	$(A = 10^6)$	$A = 10^5$
loop	$(R_f = 10-100 \text{ k}\Omega)$	$R_f = 100 \text{ k}\Omega$
gain	$R_s = \text{M}\Omega$'s	$R_s = 100 \text{ k}\Omega$


As expected as $\begin{cases} A \rightarrow \infty \\ R_o \rightarrow \infty \\ r_o \rightarrow 0 \end{cases} \Rightarrow V_{out} = -\frac{R_f}{R_s} V_s$

Important Note

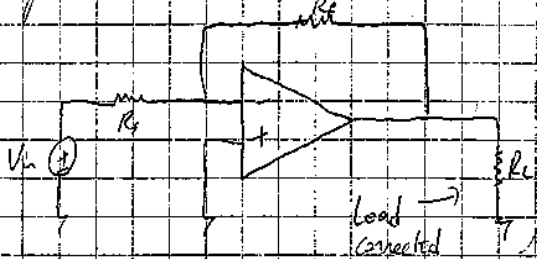① Using the model with finite A, R_o and $r_o \neq 0$, we can also analyze the following circuit



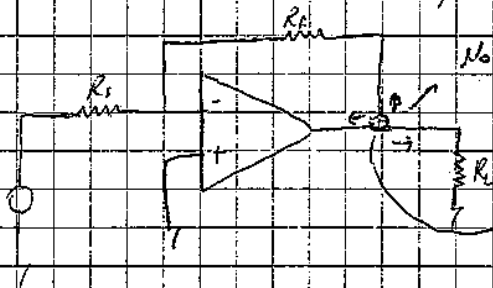② For the earlier less accurate models, it is not possible to include the effect of R_o , since




Not possible to write a KCL at output node

Since $r_o = 0$, the effect of R_o is not visible when models with $r_o = 0$ are used

Model Analysis For Op-Amp Circuits

If ideal model or finite gain model is used then writing node equations except at the output node can easily lead to the solution

Ex

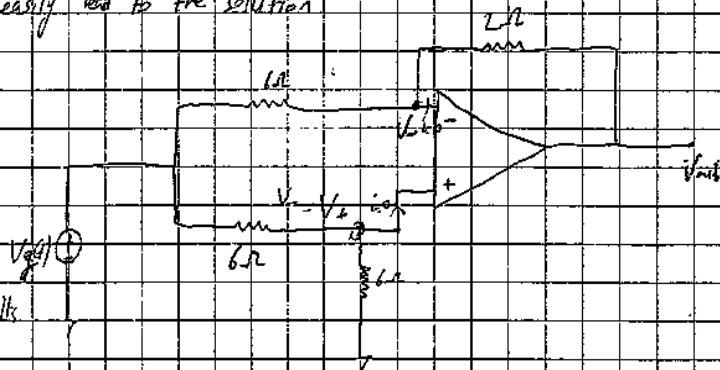

(Assume linear region operation and $A \rightarrow \infty$)


$V_{in} = V_s$ is not with

$$\text{KCL at } V_- = \frac{V_s - V_-}{6} + \frac{V_- - V_{out}}{4} = 0 \Rightarrow V_{out} = \frac{4}{3}V_s - \frac{V_-}{3} \Rightarrow V_{out} = \frac{4}{3}V_s$$

$$V_{out} = 2 \cos 2t$$

$$\text{KCL at } V_+ = \frac{V_-}{6} + \frac{V_- - V_-}{6} = 0 \Rightarrow V_- = \frac{V_s}{2}$$

Ex 11

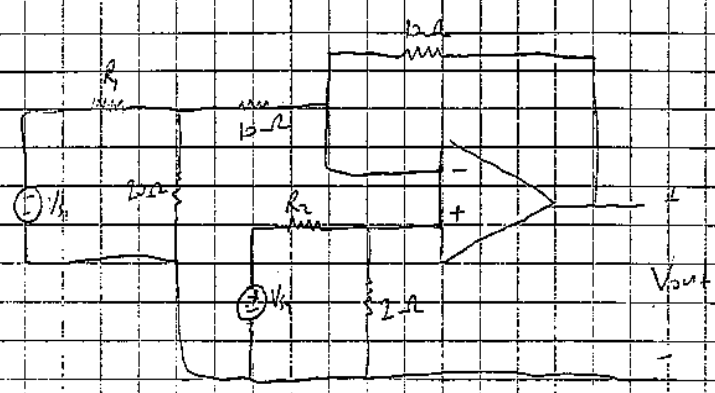


Assuming ideal op-amp and linear operation

Find R_1 and R_2 st

$$V_o = \frac{V_2}{4} - \frac{V_1}{4}$$

Ex 12

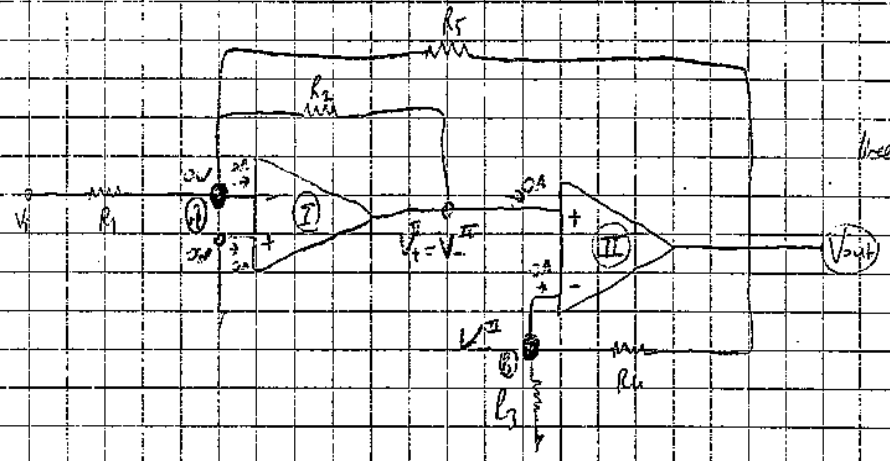

Assume both op-amp and linear region; find V_{out}

KCL at node A: $\frac{0 - V_i}{R_1} + \frac{0 - V_{out}}{R_3} + \frac{0 - V_x}{R_2} = 0$

KCL at node B: $\frac{V_x - V_{out}}{R_4} + \frac{V_x}{R_5} = 0$

Mathematical calculations

$$V_x = \frac{-R_3}{R_1} \frac{R_2 R_3}{R_2(R_3 + R_4) + R_1 R_3} \quad \text{and} \quad V_o = \frac{-R_5 R_2 (R_3 + R_4)}{R_2 (R_3 + R_4) + R_1 R_3} \frac{V_i}{R_1}$$

Let's check the conditions for V_{in} so that both op-amps are in linear region.

Op-Amp (I) $\Rightarrow V_{out}^I = V_x \quad |V_{out}^I| < E_s$

Op-Amp (II) $\Rightarrow V_{out}^{II} = V_{out} \quad |V_{out}^{II}| < E_s$


Both conditions should be satisfied at the same time for the validity of analysis.

$$V_{in} \in [A^I, B^I] \quad V_{in} \in [A^{II}, B^{II}]$$


Range for V_{in} for the opamp (I)

V_{in} should be the intersection of these two intervals


Transfer characteristics

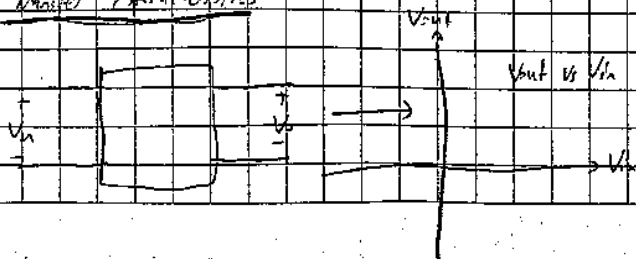

Input characteristics

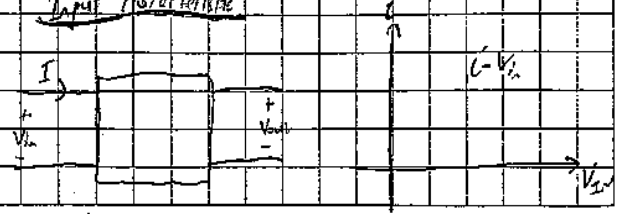

Sumner Amplifier

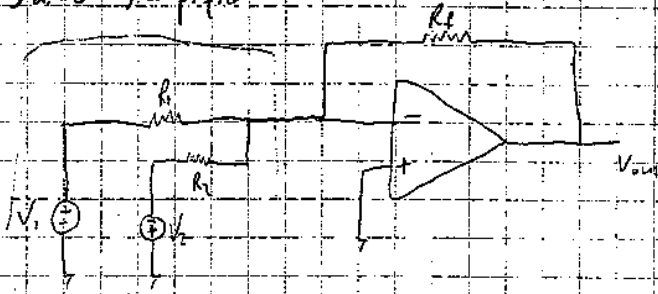

$V_{out} \Rightarrow$ by Thevenin eq. first.

$$R_1 || R_2 = R_{th}$$


$$V_{th} = \frac{V_1 R_2}{R_1 + R_2} + \frac{V_2 R_1}{R_1 + R_2} = V_{th}$$



$$V_{out} = \frac{R_f}{R_{th}} V_{th} = \frac{R_f (R_1 + R_2)}{R_1 R_2} \left(\frac{V_1 R_2 + V_2 R_1}{R_1 + R_2} \right)$$

$$V_{out} = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2$$


Difference Amplifier

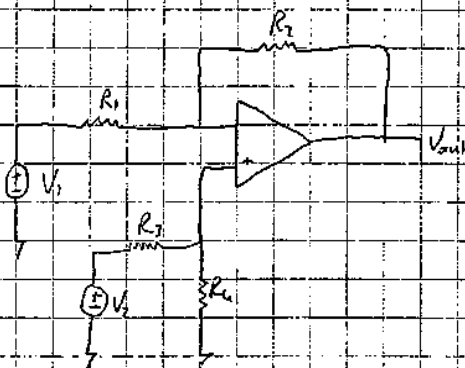

$$V_{out} = \left(\frac{R_2 + R_f}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) V_2 - \frac{R_f}{R_1} V_1$$

$$\text{if } \frac{R_3}{R_4} = \frac{R_2}{R_f} \Rightarrow V_{out} = \frac{R_f}{R_1} (V_2 - V_1)$$

Integrator

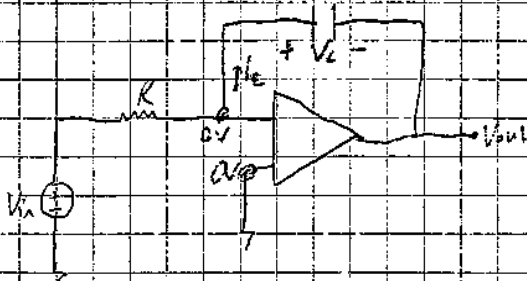

$$\frac{V_n}{R} = -i_c \quad \cdot \quad i_c = C \frac{dV_c(t)}{dt}$$

$$V_{out} = -V_c$$

$$\frac{V_n}{R} + i_c = 0$$


$$\frac{V_n(t)}{R} = -C \frac{dV_c(t)}{dt}$$

$$\Rightarrow \frac{dV_c(t)}{dt} = -\frac{1}{RC} V_n(t)$$

$$\int_0^t dV_c(t) = \int_0^t \frac{1}{RC} V_n(t) dt \Rightarrow V_c(t) - V_c(0) = \frac{1}{RC} \int_0^t V_n(t) dt$$

$t=0$ value is not given, assume $V_c(-\infty) = 0V = V_c(0) = \frac{1}{RC} \int_{-\infty}^t V_n(t) dt$

Differentiator

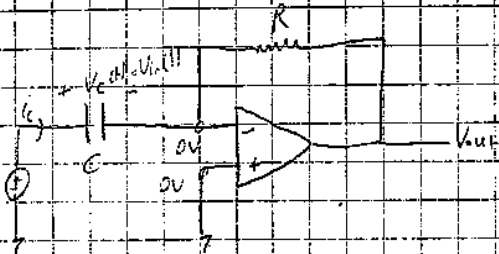


differentiable

$$i_c = C \frac{dV_c(t)}{dt} = C \frac{d(V_{in}(t))}{dt}$$

$$i_c = C \frac{dV_{in}(t)}{dt}$$

$$V_{out} = -R i_c = -RC \frac{dV_{in}(t)}{dt}$$

Opamps & Nonlinear Elements

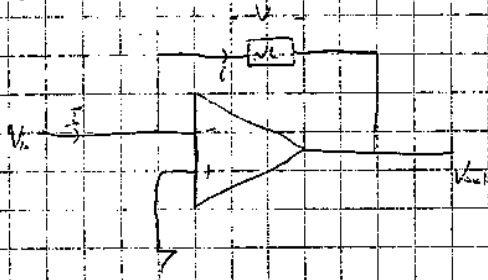

+SAT: $V_{out} = +E_s$ } $V_{in} < 0, V_{in} < 0$
 $V_{in} > V_s$ } $V_{out} = V_{in} - V_{out} = E_s$
negative
 $V_{out} < -E_s$

-SAT: $V_{out} = -E_s$ } $V_{in} > 0, V_{in} > 0$
 $V_{in} < V_s$ } $V_{out} = V_{in} - V_{out} = -E_s$
positive
 $V_{out} \geq E_s$

Linear: $V_{in} = V_{out} = 0$ } $V_{in} = 0, V_{in} = 0$
 $-E_s < V_{out} < E_s$ } $V_{out} = V_{in} = 0$
 $V_{out} = -V_{in}$
 $-E_s < V_{out} < E_s$






+SAT (Op-Amp) $\rightarrow V_{out} < -E_s \rightarrow$ Viado characteristic $i = 0$
 $V_{out} = E_s$
 $V_{in} < 0$

+SAT Op-Amp

-SAT (Op-Amp) $\rightarrow V_{out} > E_s \rightarrow$ not possible to have a current i so that $v > E_s$
 $V_{out} = -E_s$
 $V_{in} > 0$
 \rightarrow Op-Amp does not enter into -SAT region

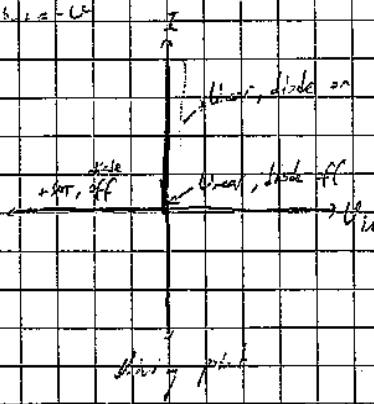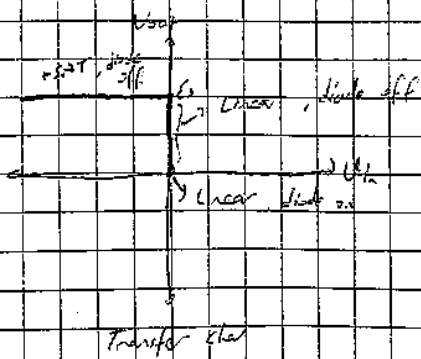Linear (Op-Amp) $\rightarrow -E_s < V_{out} < E_s \rightarrow$ only possible for
 $V_{in} = 0$
 $-E_s < V_{out} < E_s$
 $i_s = -i_o$





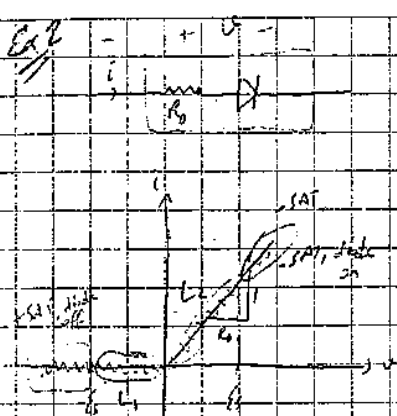


if SAT: $v_o < -E_s \rightarrow (1-0)$


Output as E_s

-SAT: $v_o > E_s \rightarrow i = \frac{v_i}{R_0} = \frac{v_i - (-E_s)}{R_0} \rightarrow v_i = (R_0 - E_s)$

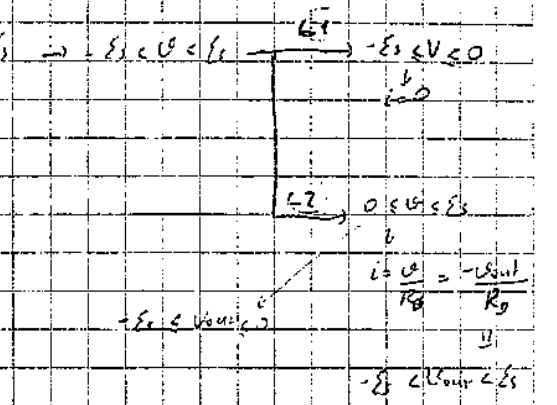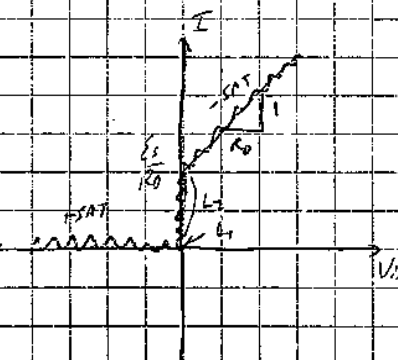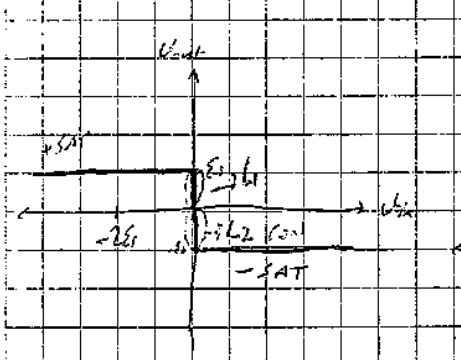Linear: $-E_s \leq v_{out} \leq E_s \Rightarrow -E_s \leq v_i \leq E_s$



The Common Mode Rejection Ratio (CMRR)

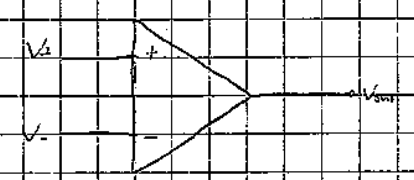

Ideal Op-Amp (Linear Region)

$$v_{out} = A(v_+ - v_-) = A v_+ - A v_-$$

Practical Op-Amp

$$v_{out} = A_+ v_+ - A_- v_- \text{ and } A_+ \neq A_-$$

if (Common) $\rightarrow v_c = \frac{v_+ + v_-}{2}$

if (Diff) $\rightarrow v_d = v_+ - v_-$

$$\left. \begin{aligned} v_+ &= v_c + v_d/2 \\ v_- &= v_c - v_d/2 \end{aligned} \right\}$$

Then practical op-amp:

$$v_{out} = A_+ v_+ - A_- v_- = A_+ \left(v_c + \frac{v_d}{2} \right) - A_- \left(v_c - \frac{v_d}{2} \right)$$


$$v_{out} = (A_+ - A_-) v_c + \frac{(A_+ + A_-)}{2} v_d$$

$$A_c \triangleq A_+ - A_- \text{ (Common Mode Gain)}$$

$$A_d \triangleq \frac{A_+ + A_-}{2} \text{ (Differential Mode Gain)}$$

Ideally: $A_c = 0$ $A_d = A$

$$CMRR \triangleq \left| \frac{A_d}{A_c} \right| \text{ (Ideally } \infty)$$

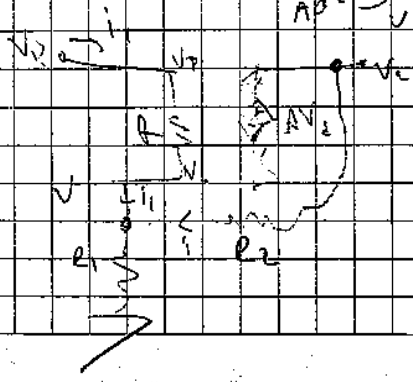


$$(CMRR)_{dB} = 20 \log_{10} \left| \frac{A_d}{A_c} \right|$$

$$\frac{v_1 - v_2}{R_1} = \frac{v_2 - v_o}{R_2} = \frac{v_o}{R_1}$$


$$\frac{v_1 - v_2}{R_1} + \frac{v_2 - v_o}{R_2} = A_d v_c$$

Positive-Negative Feedback

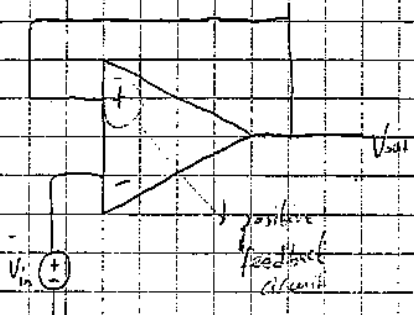

① +SAT: $V_{out} = E_s$ $V_i > 0 \Rightarrow V_{in} < E_s$
 $V_o = E_s - V_{in}$

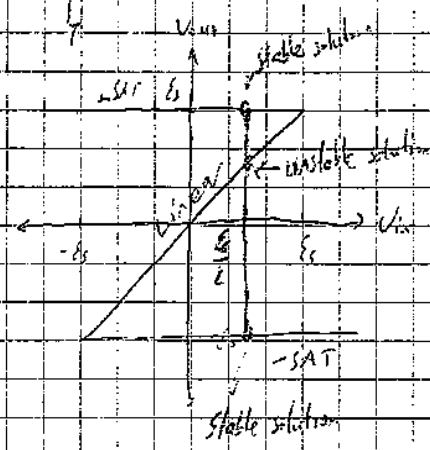
② -SAT: $V_{out} = -E_s$ $V_i < 0 \Rightarrow V_{in} > -E_s$
 $V_o = -E_s - V_{in}$



WAVEFORMS


* Unit step, ramp, impulses

1) Unit Step function

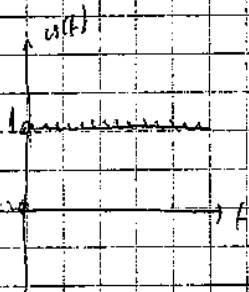

$$u(t) = \begin{cases} 1 & t > 0 \\ 0 & \text{other} \end{cases} \quad t > 0$$

2) Ramp function

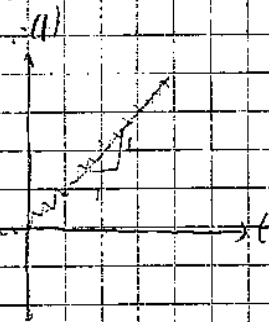


$$r(t) = t u(t)$$

Properties

$$\textcircled{1} \frac{d}{dt} u(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases} \quad (t \neq 0)$$


$$\textcircled{2} r(t) = \int_{-\infty}^t u(\tau) d\tau$$

Ex

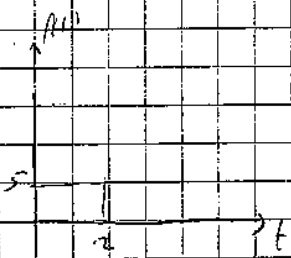


Express $f(t)$ as a linear combination of unit step functions

$$f(t) = 5u(t) - 5u(t-2)$$

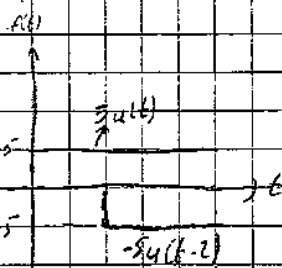



Ex

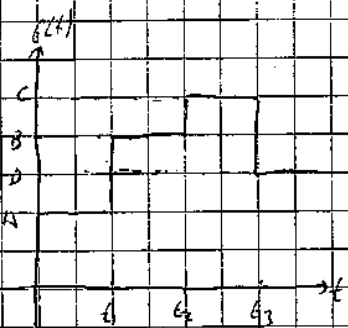


$$f(t) = Au(t) + (B-A)u(t-t_1) + (C-B)u(t-t_2) + (D-C)u(t-t_3)$$

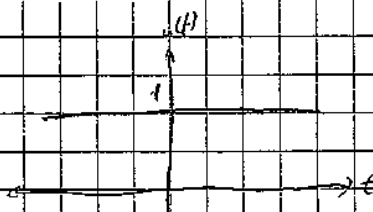Ex $u(t) \cdot 1$
 $\rightarrow + \in \text{Real number}$



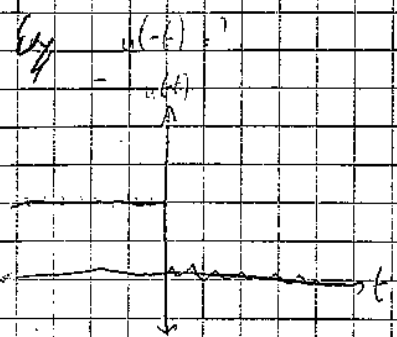

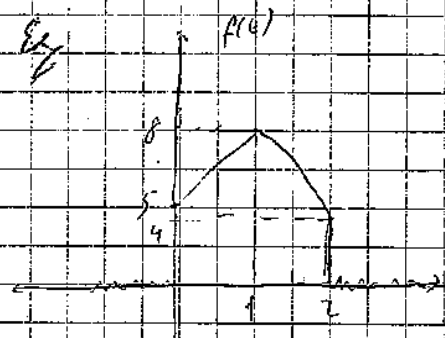
$u(-t)$ is the reflection of $u(t)$ wrt. y-axis.



$$5u(t) + 3r(t) - 7r(t-1) + 6r(t-2) - 4u(t-2)$$

Impulse function

$\delta(t)$: impulse function

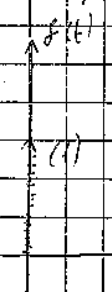

Properties





(1) sifting property: $\int_{-E}^E \delta(t) dt = 1 \quad \forall E > 0$

$\delta(t)$: Generalized function (function of "bits")




(2) $u(t) = \int_{-\infty}^t \delta(\tau) d\tau$

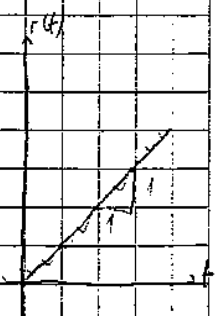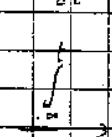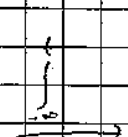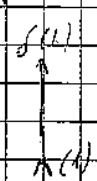(3) $\frac{d}{dt} u(t) = \delta(t)$ Using previously discussed Leibniz's rule $u(t) = \int_{-\infty}^t r(\tau) d\tau$



Sinusoidal Waveform

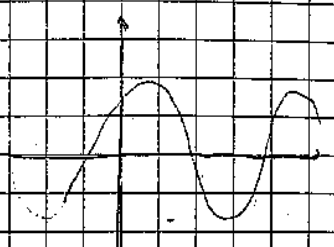


$s(t) = A \cos(\omega t + \phi)$

Amplitude A
Phase (radians) ϕ
Period T seconds

ω : rad/s angular freq (rad/sec)
 $T = \frac{1}{f} \Rightarrow T$: period (sec)

CAPACITORS

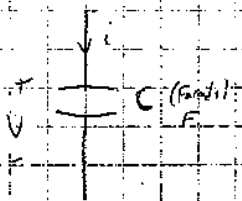

$$Q = CV$$

$$Q(t) = C \cdot V(t)$$

$$\frac{dQ(t)}{dt} = \frac{d(C \cdot V(t))}{dt} = C \frac{dV(t)}{dt} = i(t)$$

For LTI Capacitor $\Rightarrow C(t) = C$

$$i(t) = \frac{dQ(t)}{dt} = C \frac{dV(t)}{dt}$$

$$p(t) = V(t) \cdot i(t) \quad (\text{Instantaneous power})$$

$$\text{Energy} \Rightarrow \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t V(\tau) C \frac{dV(\tau)}{d\tau} d\tau$$

$$= C \int_{V_0}^{V(t)} u du = C \left[\frac{u^2}{2} \right]_{V_0}^{V(t)}$$

$$= \frac{C}{2} (V^2(t) - V_0^2)$$

$$E_C(t) = \frac{C}{2} V^2(t)$$


$$i(t) = f(t) = f_1(t) f_2(t)$$

$$\frac{d f(t)}{dt} = f_1'(t) f_2(t) + f_1(t) f_2'(t)$$

$$\frac{d f_1(t)}{dt}$$

$$E_{ex} \quad p(t) = \cos(t) \sin(t)$$

$$E_{ex} = \cos(t) \sin(t)$$

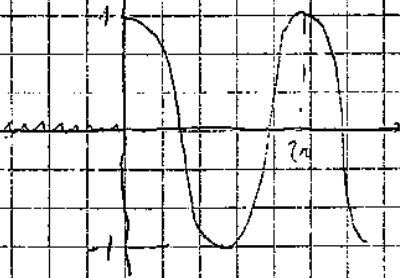



$$p(t) = \cos(t) \sin(t)$$

$$i(t) = -\sin(t) u(t) = \cos(t) \frac{d u(t)}{dt}$$

$$f(t) = -\sin(t) u(t) + \cos(t) \delta(t)$$

$$p(t) = -\sin(t) u(t) + \cos(t) \delta(t)$$


$$i(t) = -\sin(t) u(t) = \delta(t)$$

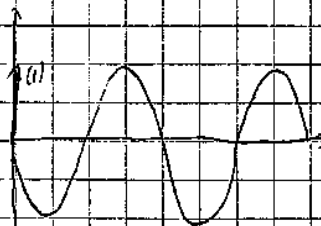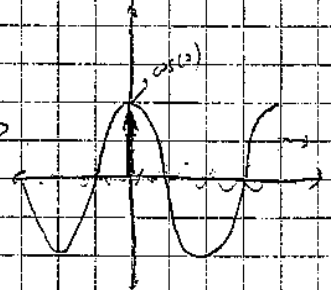

LTI Capacitors

$Q = CV$ is not a function of time

$$\frac{dQ}{dt} = C \frac{dV(t)}{dt}$$

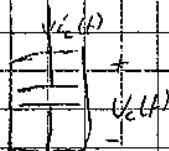

Most Important Fact

Capacitor voltage is a continuous function if input (current through the capacitor) is bounded (not infinity)

True since:

$$i_c(t) = C \frac{dV_c(t)}{dt}$$


$$V_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(\tau) d\tau = \frac{1}{C} \int_{-\infty}^b i_c(\tau) d\tau + \frac{1}{C} \int_b^t i_c(\tau) d\tau \quad t < t$$

$$V_c(t) = V_c(t_0) + \frac{1}{C} \int_{t_0}^t i_c(\tau) d\tau$$

$$V_c(t_0^+) = V_c(t_0) + \frac{1}{C} \int_{t_0}^{t_0 + \epsilon} i_c(\tau) d\tau \quad \text{finite } i_c(\tau) \leq M^+ \quad \epsilon \rightarrow 0 \text{ (arbitrarily small)}$$

$$V_c(t_0^+) \leq V_c(t_0) + \frac{1}{C} M \epsilon \rightarrow V_c(t_0^+) = V_c(t_0) \text{ as } \epsilon \rightarrow 0$$

Initial Condition Models for Capacitors

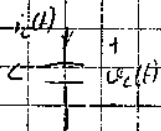

$$V_c(t_0) = V_0$$


$$E_{cap}(t_0) = \frac{1}{2} C V_0^2 \text{ Joules}$$

$$V_c(t) = V_c(t_0) + \frac{1}{C} \int_{t_0}^t i_c(\tau) d\tau \quad t > t_0$$

$\rightarrow V_c^{empty}(t) + V_0 u(t-t_0) \Rightarrow V_c(t) \stackrel{!}{=} V_c(t)$
 $V_c(t_0) = \frac{1}{C} \int_{-\infty}^{t_0} i_c(\tau) d\tau + V_0 u(t-t_0) \stackrel{!}{=} V_c(t)$
 $V_0 + \frac{1}{C} \int_{t_0}^t i_c(\tau) d\tau \quad (t > t_0)$

$V_c(t_0) = V_0$
 $V_c^{empty}(t_0) = 0V$

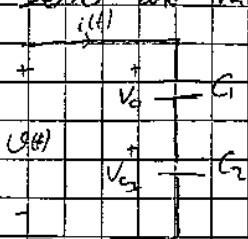Series and Parallel Combination of Capacitors




$$\rightarrow V_c(t) = V_{c1}(t) = V_{c2}(t)$$

$$= \frac{1}{C_1} \int_{-\infty}^t i_c(\tau) d\tau = \frac{1}{C_2} \int_{-\infty}^t i_c(\tau) d\tau = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \int_{-\infty}^t i_c(\tau) d\tau = \frac{1}{C_{eq}} \int_{-\infty}^t i_c(\tau) d\tau$$

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$



Voltage Divider

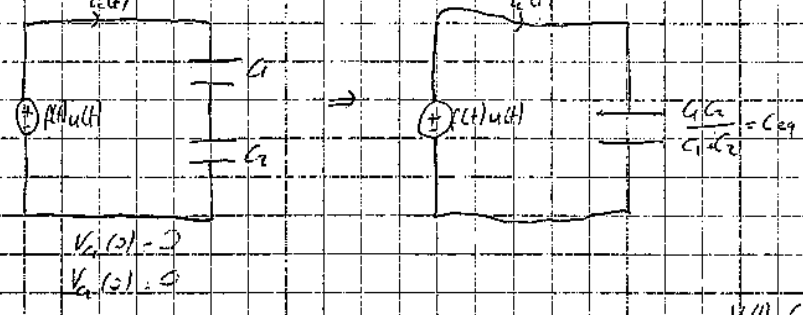


$$i_c(t) = C_{eq} \frac{dV_c(t)}{dt} = C_{eq} \left[p'(t)u(t) + f(t)u(t) \right]$$

$$V_c(t) = \frac{1}{C_1} \int_0^t i_c(\tau) d\tau = \frac{C_{eq}}{C_1} \int_0^t \left[p'(\tau)u(\tau) + f(\tau)u(\tau) \right] d\tau$$



$$V_c(t) = \frac{C_{eq}}{C_1} \left[\int_0^t p'(\tau)u(\tau) d\tau + f(t)u(t) \right] \quad t > 0$$

$$V_c(t) = \frac{C_2}{C_1 C_2} p(t)u(t) \quad \leftarrow \quad V_c(t) = \frac{C_{eq}}{C_1} \left[p(t)u(t) + f(t)u(t) \right]$$

Ex 1

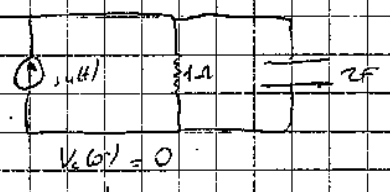


Final $t \rightarrow \infty$ solution

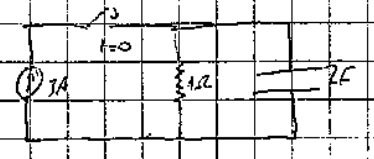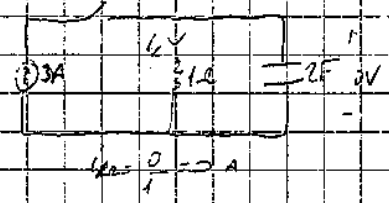

$V_c(0^+) - V_c(0^-) = 0V$ Continuity of cap. voltage


$i_1(0^+) = 0A$ $i_c(0^+) = 3 - i_1 = 3A$

Ex 2

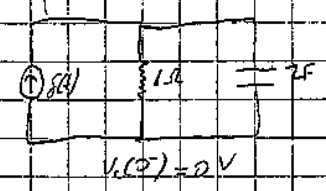



$$\left. \begin{aligned} i_c(t) &= f(t) \\ i_1(t) &= 0A \end{aligned} \right\} 0^- < t < 0^+$$
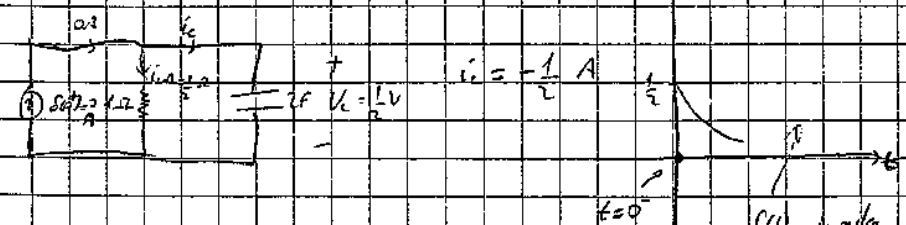
$$V_c(0^+) = \frac{1}{C} \int_0^{0^+} i_c(\tau) d\tau = \frac{1}{C} \int_0^{0^+} f(\tau) d\tau = \frac{1}{C} \Rightarrow V_c(0^+) = \frac{1}{2} V$$




$f(t)$ = impulse input
 $V_c(t)$ is not continuous at $t=0$

Revision

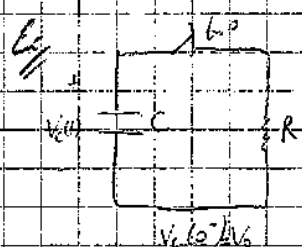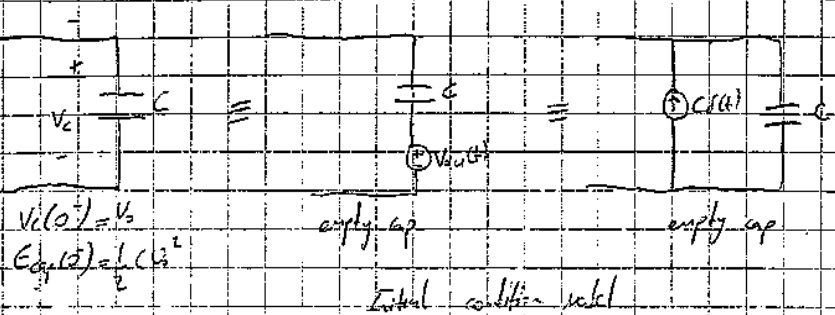

Analyze the circuit for $t \geq 0$

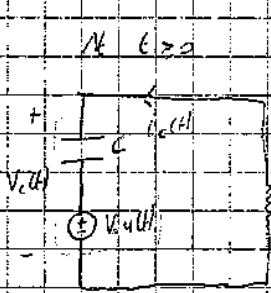

$$V_c(t) + V_R(t) + (i_c(t))R = 0$$

$$V_c(t) + V_0 u(t) + RC \frac{dV_c(t)}{dt} = 0$$

$$\left(\frac{d}{dt} + \frac{1}{RC}\right) V_c(t) = -\frac{V_0}{RC} \quad t \geq 0$$


$$\Rightarrow \left(\frac{d}{dt} + \frac{1}{RC}\right) V_c(t) = -\frac{V_0}{RC}$$

$$V_c(0^-) = 0V$$

$$V_c(t) = \alpha e^{-t/RC} + A \quad t \geq 0$$

$$V_c(t) = \alpha e^{-t/RC} - V_0 \quad t \geq 0$$
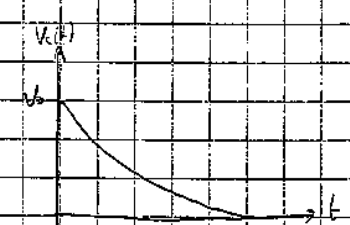
$$V_c(0^+) = V_c(0^-) = V_c(0) = 0 \Rightarrow \alpha = V_0$$




$$\Rightarrow V_c(t) = V_0 \left(e^{-t/RC} - 1 \right) u(t) \quad t \geq 0$$

$\Rightarrow V_c(t) = V_0 u(t) + V_x$ \rightarrow u(t) probability $A \geq 0$ alignment
 \rightarrow u(t) say t_0 between

$$V_c(t) = V_0 e^{-t/RC} u(t)$$


$$V_c(0^+) = V_c(0^-) = V_c(0) = V_0$$

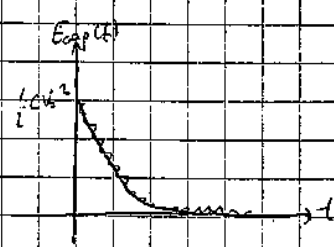

What has happened to the energy initially stored $\left(\frac{1}{2} C V_0^2\right)$?


$$W_{resistor}(t) = \int_0^t i_R(t') v_R(t') dt' = \int_0^t \frac{V_c'(t')}{R} dt' = \frac{V_0^2}{R} \int_0^t e^{-2t'/RC} dt' = \frac{V_0^2}{R} \left(\frac{e^{-2t'/RC}}{-2/R} \Big|_0^t \right)$$
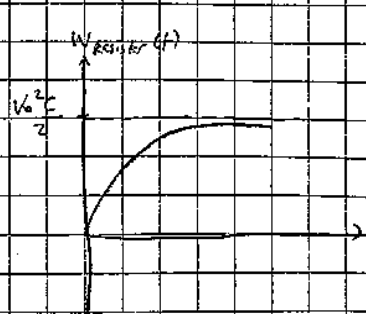
$$W_{resistor}(t) = \frac{C V_0^2}{2} \left[1 - e^{-2t/RC} \right] \text{ Joules}$$



Total energy in Cap at $t = t_0$
 $+$
 Total energy consumed by R in $[0, t_0]$
 $=$ Initial energy.

INDUCTORS

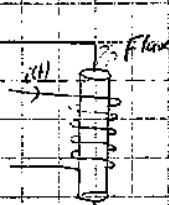


webers

$$\Phi(t) = L(t) i(t)$$

$$v_L(t) = \frac{d\Phi(t)}{dt} = i(t) \frac{dL(t)}{dt} + L(t) \frac{di(t)}{dt}$$

E.T.E. Inductors = $v_L(t) = L \frac{di_L(t)}{dt}$

$$E_{ind}(t) = \frac{1}{2} L i^2(t)$$


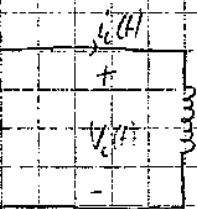


$$i_L(0^-) = i_0 A$$


$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$i_L(t) = i_0 + \frac{1}{L} \int_0^t v_L(\tau) d\tau \quad t \geq 0$$

Initial condition switch

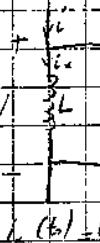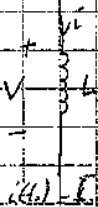

$$i_L(0^-) = 0$$


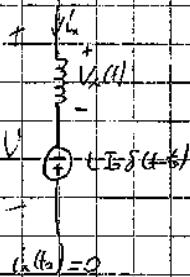


$$i_L(0^-) = 0$$

$$v_L(t) = L \frac{di_L(t)}{dt} = L \frac{d}{dt} \left(i_0 u(t-\delta) + \frac{1}{L} \int_0^t v_L(\tau) d\tau \right)$$

$$v_L(t) = (L I_0 \delta(t-\delta)) + v_L(t)$$

Inductor in Series

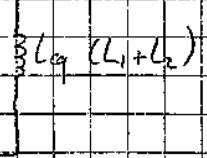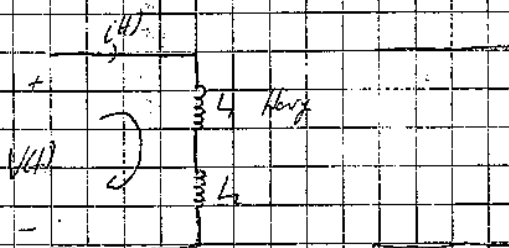

$$i_L(0^-) = i_{L_2}(0^-) = 0$$

$$v(t) = v_{L_1}(t) + v_{L_2}(t)$$

$$= L_1 \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt}$$

$$v(t) = (L_1 + L_2) \frac{di(t)}{dt}$$


Inductors in Parallel



$$i(t) = i_{L_1}(t) + i_{L_2}(t)$$

$$= \frac{1}{L_1} \int v(t) dt + \frac{1}{L_2} \int v(t) dt$$

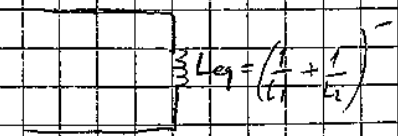
$$= \left(\frac{1}{L_1} + \frac{1}{L_2} \right) \int v(t) dt$$




$$i_{L_1}(0^-) = i_{L_2}(0^-) = 0$$

Inductor has $i_L(t)$ as a continuous function of time (unless there is an impulse source in the system)
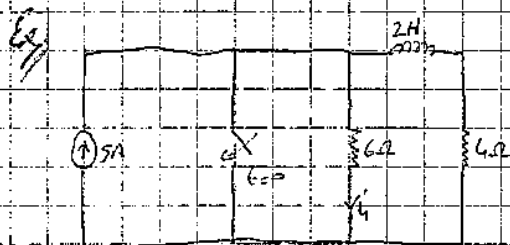
$$i_L(t) = i_L(t_0) + \frac{1}{L} \int_{t_0}^t v_L(z) dz \Rightarrow i_L(t_0^+) = i_L(t_0) \text{ unless } v_L(t) = \delta(t-t_0) \Rightarrow \text{impulse at } t=t_0$$




$i_L(0^-) = 2A$ Find $i_L(0^+)$, $i_L'(0^+)$, $\frac{d i_L(t)}{dt} \Big|_{t=0^+}$

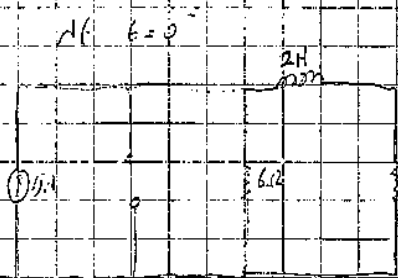

$i_L(0^-) = 3A$


$V_{4\Omega}(0^-) = 12V$

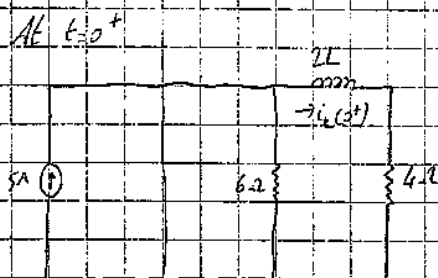


$i_L(0^+) = 3A$ $i_L'(0^+) = 0A$

$L \frac{d i_L(0^+)}{dt} + 4 i_L(0^+) = 0$

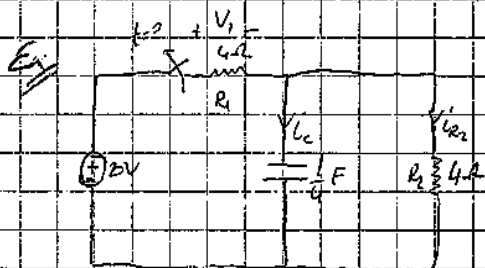$\frac{d i_L(0^+)}{dt} = \frac{-4 i_L(0^+)}{L} = \frac{-4 \cdot 3}{2} = -6$



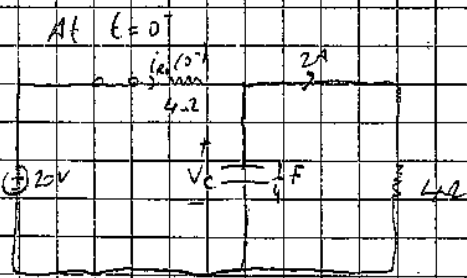
$i_{R2}(0^-) = 2A$ Find $q(0^-)$, $q(0^+)$, $i_{R1}(0^-)$, $i_{R2}(0^-)$, $i_C(0^-)$, $i_C(0^+)$



$V_C(0^-) = 8V$; $q(0^-) = C V_C = 2 \text{ Coulombs}$

$i_{R1}(0^-) = \frac{20-8}{4} = 3A$

$i_C(0^-) = 1A$

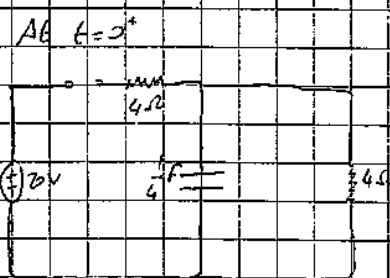


$V_C(0^+) = 8V$; $q(0^+) = 2 \text{ Coulombs}$

$i_{R2}(0^+) = 2A$ $i_{R1}(0^+) = 0A$

$i_C(0^+) = -2A$ $C \frac{d V_C(0^+)}{dt} = -2 \Rightarrow \frac{d V_C(0^+)}{dt} = -8$

Some Pathological Cases

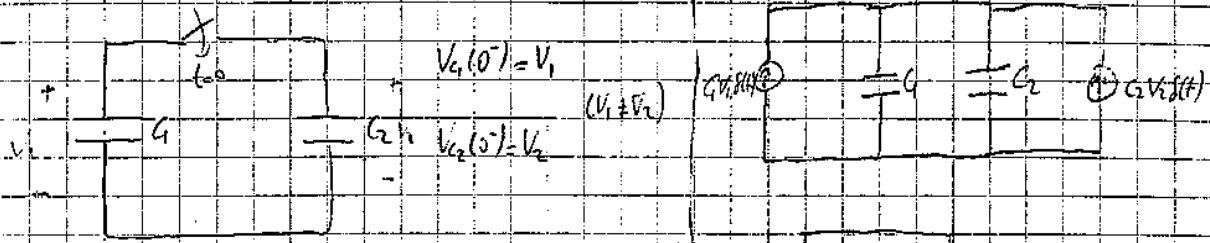


Explanation at $t=0^+$

$$Q_{tot}(0^+) = Q_{eq}(0^+)$$

$$C_1 V_1 + C_2 V_2 = (C_1 + C_2) V_{common}(0^+)$$
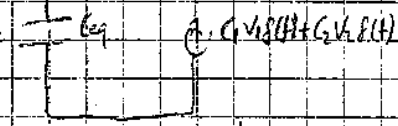
$$V_{common}(0^+) = \frac{C_1}{C_1 + C_2} V_1 + \frac{C_2}{C_1 + C_2} V_2$$



$$V_{eq}(0^+) = V_{eq}(0^-) + \int_{0^-}^{0^+} (C_1 V_1 \delta(t) + C_2 V_2 \delta(t)) dt$$


Total energy at $t=0^-$

$$\frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2$$

Total energy at $t=0^+$

$$\frac{1}{2} (C_1 + C_2) \left(\frac{C_1}{C_1 + C_2} V_1 + \frac{C_2}{C_1 + C_2} V_2 \right)^2$$

Mutual Inductor (Coupled Inductors)

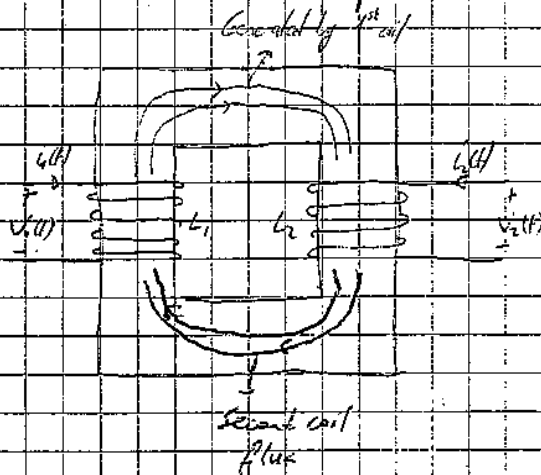

$$\begin{cases} v_1(t) = L_1 i_1(t) + M i_2(t) \\ v_2(t) = M i_1(t) + L_2 i_2(t) \end{cases} \Rightarrow \begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$

$$\frac{d \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}}{dt} = \begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} \Rightarrow \begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{di_1(t)}{dt} \\ \frac{di_2(t)}{dt} \end{bmatrix}$$


① Special case $M=0 \Rightarrow$ self induction

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & 0 \\ 0 & L_2 \end{bmatrix} \frac{d \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}}{dt}$$

② $M = \sqrt{L_1 L_2}$ then $k = \frac{M}{\sqrt{L_1 L_2}} = 1$ coupling coefficient


Then we say that coils are perfectly coupled \rightarrow No loss in power as ideal transformer.

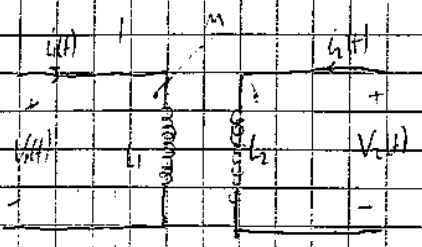(More on perfect coupling coupling coefficient at a later time)




$$\begin{bmatrix} V_1(t) \\ V_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$

Use the dot convention!

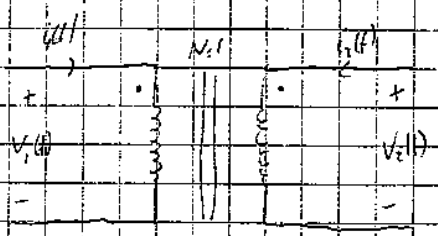

$$\frac{V_1(t)}{i_1(t)} = \frac{L_1}{i_1(t)} + \frac{M}{i_2(t)}$$

Same dot convention

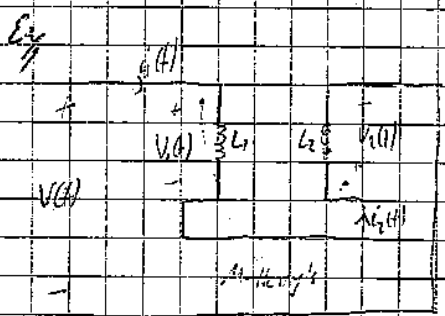

Express $V_2(t)$ in terms of $i_1(t)$

$$i_2(t) = i_1(t)$$

$$\begin{bmatrix} V_1(t) \\ V_2(t) \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i_1(t) \\ i_1(t) \end{bmatrix}$$

Since I have exactly obeyed dot convention.

$$V_2(t) = V_1(t) + V_2(t)$$

$$= \left(L_1 \frac{d}{dt} i_1(t) + M \frac{d}{dt} i_1(t) \right) + \left(M \frac{d}{dt} i_1(t) + L_2 \frac{d}{dt} i_1(t) \right)$$

$$V_2(t) = (L_1 + L_2 + 2M) \frac{d}{dt} i_1(t)$$

FIRST ORDER CIRCUITS


$(D + \delta)x(t) = f(t)$

δ : constant real number
 $f(t)$: forcing term
 $x(t)$: unknown function
 $x(0) = x_0$ is the solution at $t=0$
 Find $x(t)$ for $t > 0$

Solution terminology

- 1) Homogeneous, particular solutions
- 2) Zero-input, zero-state solutions
- 3) Transient, Steady-state solutions
- 4) Complete solution

RC Series

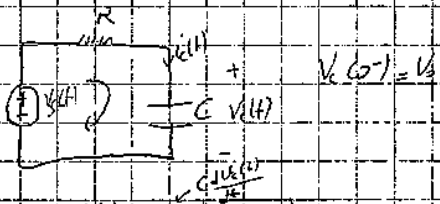


KVL: $-v_s(t) + R i(t) + v_C(t) = 0 \quad t > 0$

$(RC \frac{d}{dt} + 1) v_C(t) = v_s(t) \quad t > 0$

$(D + \frac{1}{RC}) v_C(t) = \frac{v_s(t)}{RC} \quad t > 0$

Dual

RL Parallel

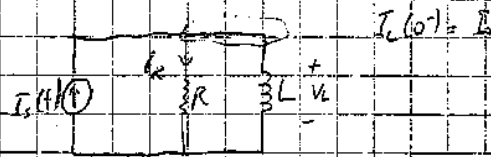

KCL: $-i_s(t) + \frac{v_L(t)}{R} + i_L(t) = 0$

$(\frac{L}{R} \frac{d}{dt} + 1) i_L(t) = i_s(t) \quad t > 0$

$(D + \frac{R}{L}) i_L(t) = \frac{R}{L} i_s(t) \quad t > 0$

(i) Homogeneous, particular: (RC Series)


$(D + \frac{1}{RC}) v_C(t) = \frac{v_s(t)}{RC} \quad t > 0$

Homogeneous $\Rightarrow (D + \frac{1}{RC}) v_C(t) = 0 \Rightarrow v_C(t) = \alpha e^{-\frac{t}{RC}} \quad t > 0$
 $\forall \alpha \in \mathbb{R}$


Particular $\Rightarrow (D + \frac{1}{RC}) v_C(t) = \frac{v_s(t)}{RC}$

$v_C(t) = \beta u(t)$

Let's say that $v_C(t) = \beta u(t)$

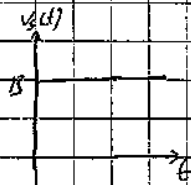

$V_c(t) = \beta u(t)$

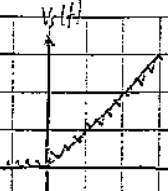

$(D + \frac{1}{RC}) V_c(t) = \frac{\beta}{RC} \quad t > 0$

after substitution

$V_c(t) = A + Bt$

$(\frac{B+A}{RC}) + \frac{B}{RC} = \frac{\beta t}{RC} \quad \forall t$

$B = \beta \Rightarrow A = -\beta RC$

$V_c(t) = -\beta RC + \beta t \quad t > 0$

Complete solution


$V_c(t) = V_c^{(h)}(t) + V_c^{(p)}(t)$

Remember "x" is yet to be determined. "x" is set such that

$V_c(0) = V_c(0) = 0$

7) Zero Input/Zero State Solutions

Zero State:

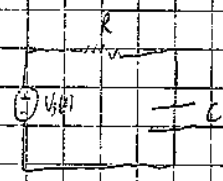

State: (State vector, state variables)

State variables allow us to exactly characterize the circuit.

$V_c(t), I_c(t)$

Zero state \Rightarrow All state variables ($V_c(t)$) are equal to zero at $t=0$

$V_c(0) = 0V \Rightarrow$ No initial energy in the circuit.

Zero state solution \Rightarrow

$(D + \frac{1}{RC}) V_c(t) = \frac{\beta}{RC} \quad V_c(0) = 0V \quad t > 0$

1) $u(t) = \beta u(t) \Rightarrow V_c^{(h)}(t) = (\beta - \beta e^{-\frac{t}{RC}}) u(t) \quad t > 0$

$V_c(0) = 0$ and $V_c^{(h)}(t)$ satisfies $(D + \frac{1}{RC}) V_c(t) = \frac{\beta}{RC} \quad t > 0$

\therefore it's the complete solution for zero initial condition.


2) $u(t) = \beta t u(t)$

$V_c^{(h)}(t) = \beta RC e^{-\frac{t}{RC}} + \beta(t - RC) \Rightarrow V_c(0) = 0 \Rightarrow V_c^{(h)}(t)$ satisfies

$(D + \frac{1}{RC}) V_c(t) = \frac{\beta t}{RC} \quad t > 0$

Zero-Input solution

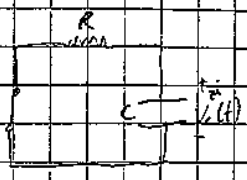The solution when $V_c(t) = 0V$ (all independent sources are killed, there is no forcing term in the differential equation)



$V_c(0) = V_0$

$(D + \frac{1}{RC}) V_c(t) = 0 \leftarrow (\frac{V_c(t)}{RC}) \leftarrow V_c(t) = 0$

$V_c(0) = V_0 \Rightarrow V_c(t) = V_0 e^{-\frac{t}{RC}}$

Complete solution: $V_c(t) = V_c^{(h)}(t) + V_c^{(p)}(t)$

$$\begin{bmatrix} \frac{1}{RC} & \omega \\ -\omega & \frac{1}{RC} \end{bmatrix} \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \begin{bmatrix} \frac{A}{RC} \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} \alpha \\ \beta \end{bmatrix} = \frac{1}{\frac{1}{(RC)^2} + \omega^2} \begin{bmatrix} \frac{1}{RC} & -\omega \\ \omega & \frac{1}{RC} \end{bmatrix} \begin{bmatrix} \frac{A}{RC} \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{A}{(RC)^2} \\ \frac{A\omega}{RC} \end{bmatrix} \frac{1}{\left(\frac{1}{RC}\right)^2 + \omega^2}$$


$$U^{sp}(t) = \alpha \cos(\omega t) + \beta \sin(\omega t) - \omega e^{-\frac{t}{RC}} \quad t > 0$$

Since $U^{sp}(0) = 0$

Complete solution

$$U^{sp}(t) = U^{pr}(t) + U^{si}(t)$$



DC Excitation

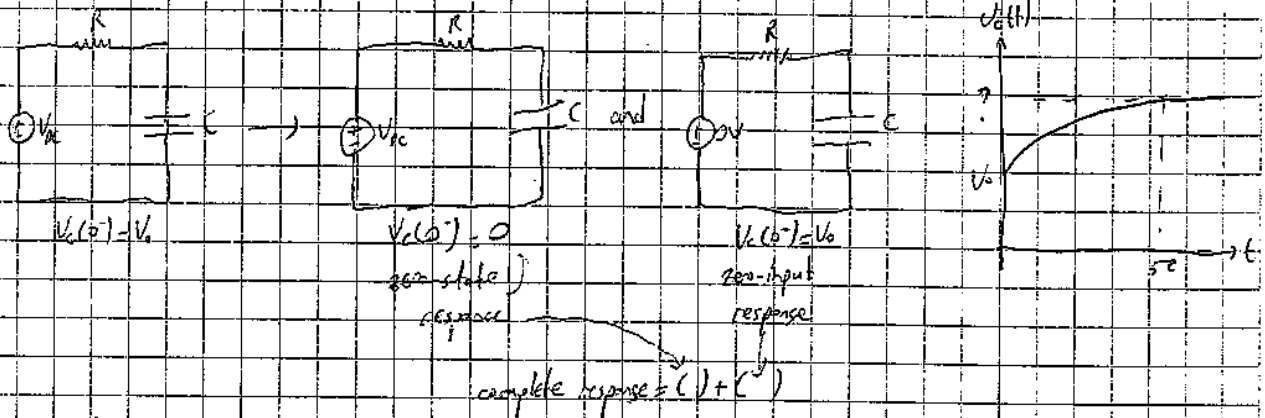

$$U_c^{complete}(t) = (A + B e^{-\frac{t}{RC}}) u(t) \quad \text{for a DC input}$$

$$A, B = ? \quad U_c(0^+) = U_0 \quad U_c(\infty) = U_{DC}$$
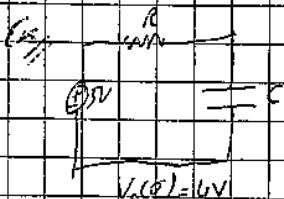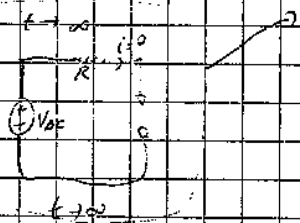
$$U_c(t) = \left[U_c(\infty) + (U_c(0^+) - U_c(\infty)) e^{-\frac{t}{RC}} \right] u(t) \quad \text{General solution for DC input}$$





$$U_c(t) = ?$$

$$U_c(\infty) = 5V \Rightarrow U_c(t) = \left[5 + (U_c(0^+) - 5) e^{-\frac{t}{RC}} \right] u(t)$$

$$U_c(t) = \left[5 - 1 e^{-\frac{t}{RC}} \right] u(t)$$

RL Circuit

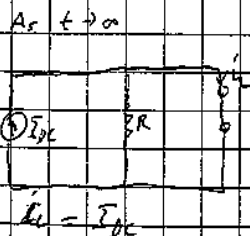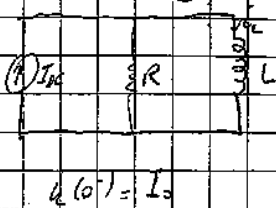


$$i_L^{complete} = \left[I_L(\infty) + (I_L(0^+) - I_L(\infty)) e^{-\frac{t}{RC}} \right] u(t)$$

For DC inputs

Capacitor $\xrightarrow{t \rightarrow \infty}$ open circuit


Inductor $\xrightarrow{t \rightarrow \infty}$ short circuit

Ex

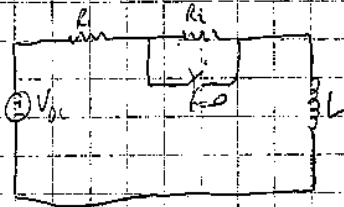


Assume switch is open for a long time, then closes at $t=0$
Find $i_L(t)$, $t > 0$


At $t=0^-$

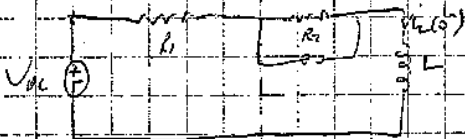

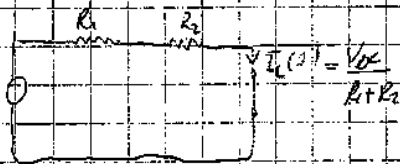Since circuit is in this config for a long time, we expect $i_L(0^-)$ to reach the steady state value.



At $t > 0$

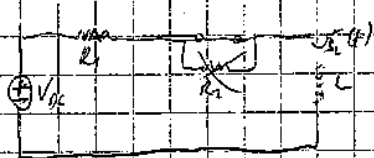


$$i_L(t) = i_L(\infty) + (i_L(0^-) - i_L(\infty)) e^{-\frac{t}{\tau}} u(t) \quad \tau = \frac{L}{R_1}$$

$$i_L(0^-) = i_L(0^+) = i_L(0) = \frac{V_{dc}}{R_1 + R_2}$$

$$i_L(\infty) = \frac{V_{dc}}{R_1}$$

Ex

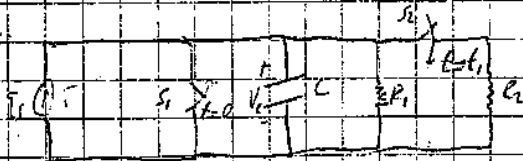


Switch S_1 is opened at $t=0$ $V_C(0) = 0V$
Switch S_2 is closed at $t=t_1 > 0$ $V_C(t) = ?$ $t > 0$

$0 < t < t_1$




$$V_C(t) = \frac{I_s R_1}{R_1} + \left[\frac{V_C(0)}{0} - \frac{V_C(\infty)}{R_1} \right] e^{-\frac{t}{RC}} u(t)$$

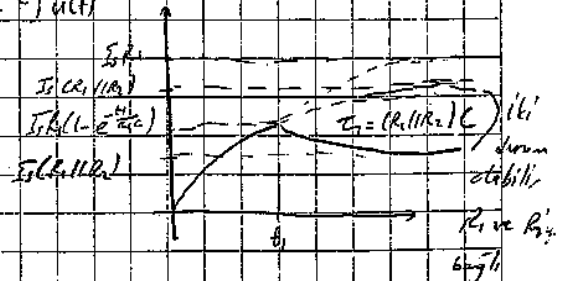$\tau = (\text{equivalent resistance seen by capacitor}) \times \text{Capacitor} = RC$



$t_1 < t < \infty$


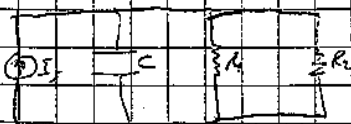


$$V_C(t_1^-) = V_C(t_1^+) = V_C(t_1)$$

$$V_C(t_1) = I_s R_1 \left(1 - e^{-\frac{t_1}{RC}} \right)$$

$$V_C(\infty) = I_s \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

Linearity of Zero-State Response.

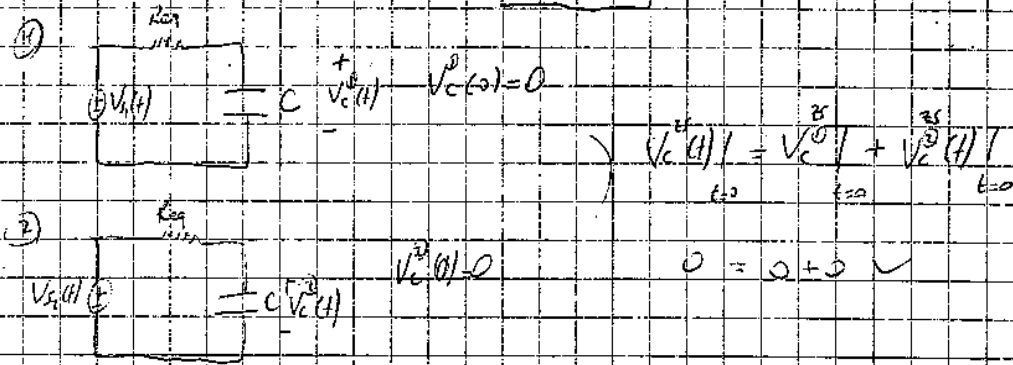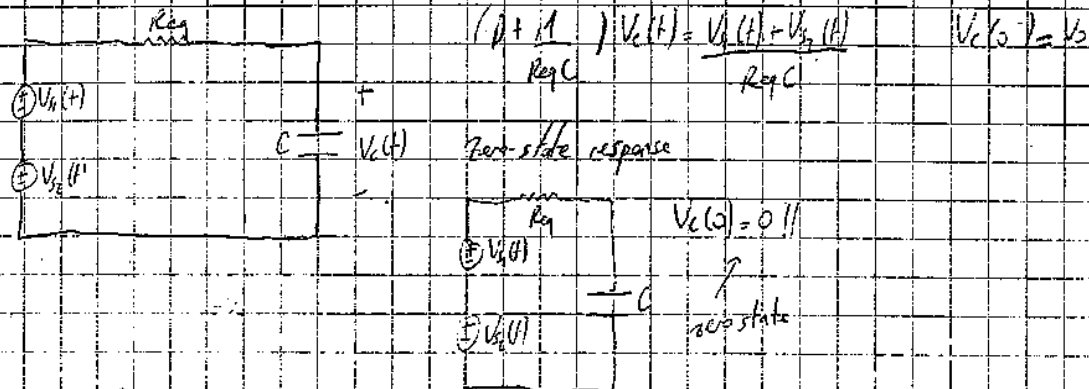

Whether:

$V_c^0(t) = V_c^1(t) + V_c^2(t)$ satisfies the diff eqn or not

Then from ① circuit diff eqn is $(D+1) \frac{V_c^0(t)}{R_{eq}} = \frac{V_1(t)}{R_{eq}}$ Then from ② circuit $(D+1) \frac{V_c^2(t)}{R_{eq}} = \frac{V_2(t)}{R_{eq}}$

Adding two diff eqn's


$$(D+1) \frac{V_c^0(t) + V_c^2(t)}{R_{eq}} = \frac{V_1(t) + V_2(t)}{R_{eq}}$$

The original diff eqn.

$$(D+1) \frac{V_c(t)}{R_{eq}} = \frac{V_1(t) + V_2(t)}{R_{eq}}$$


Finally the superposition solution (i.e. zero-state) satisfies the original diff eqn and the initial condition (i.e. zero-state solution) \rightarrow So superposition solution is the solution of the circuit.

Time Invariance

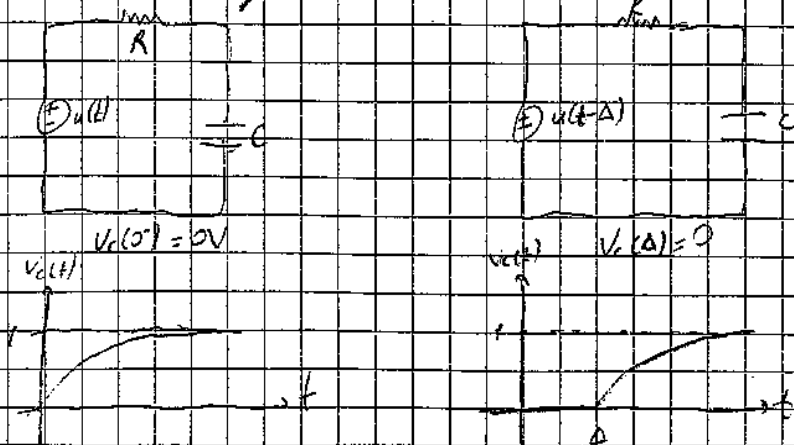


$$\left(0 + \frac{1}{RC}\right) v_c(t) = p(t) \leftarrow \text{forcing term } v_c(t) \text{ is solution for } f(t)$$
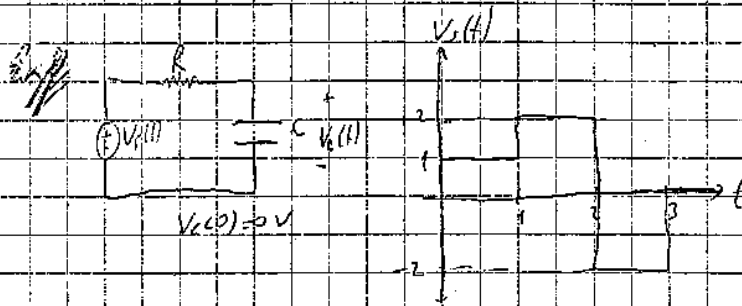
$$\left(0 + \frac{1}{RC}\right) x(t) = x(t-\Delta) \rightarrow x(t) \stackrel{?}{=} v_c(t-\Delta) \text{ Put it in diff. eqn. See if it is equal! } \checkmark$$



Find $v_c(t)$
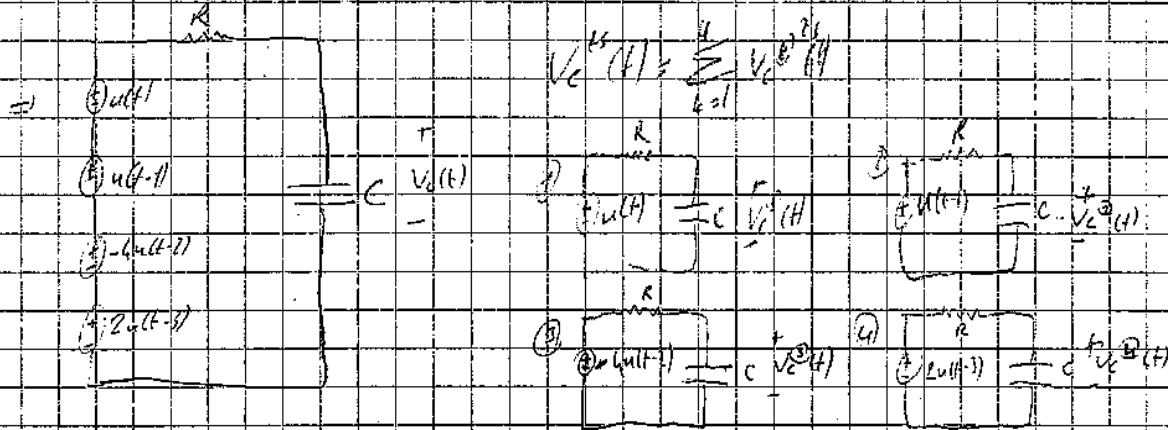
$$v_c(t) = u(t) + u(t-1) - 4u(t-2) + 2u(t-3)$$



$$v_c^1(t) = \left(1 - e^{-\frac{t}{RC}}\right) u(t)$$

$$v_c^2(t) \stackrel{\text{invariance}}{=} v_c^1(t-1) = \left(1 - e^{-\frac{t-1}{RC}}\right) u(t-1)$$

$$v_c^3(t) = -4 v_c^1(t-2)$$

$$v_c^4(t) = 2 v_c^1(t-3)$$

$$v_c(t) = \left(1 - e^{-\frac{t}{RC}}\right) u(t) + \left(1 - e^{-\frac{t-1}{RC}}\right) u(t-1)$$


$$-4 \left(1 - e^{-\frac{t-2}{RC}}\right) u(t-2) + 2 \left(1 - e^{-\frac{t-3}{RC}}\right) u(t-3)$$

Impulse Response (Always analyzed under zero-state conditions)

* When we consider impulse / step / ramp response, we always talk about zero-state solution. (That is the initial conditions are all zero)


$$v_c(0^-) = 0V \quad \left(0 + \frac{1}{RC}\right) v_c(t) = \frac{\delta(t)}{RC} \quad \text{Since } v_c(t) = \delta(t); v_c(0^-) \neq v_c(0^+)$$

$$0^- < t < 0^+$$

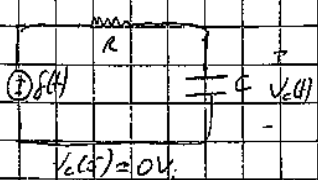


$$v_c(t) = \frac{\delta(t)}{R}$$
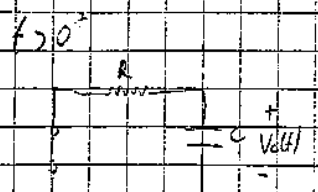
$$v_c(0^+) = v_c(0^-) + \frac{1}{C} \int_0^+ v_c(\tau) d\tau = \frac{1}{RC} \int_0^+ \frac{\delta(\tau)}{R} d\tau = \frac{1}{RC}$$




$V_C(s) = \frac{1}{RC}$ $V_C(t) = \frac{1}{RC} e^{-t/\tau}$ $t > 0$ $\tau = RC$

$h(t)$: impulse response

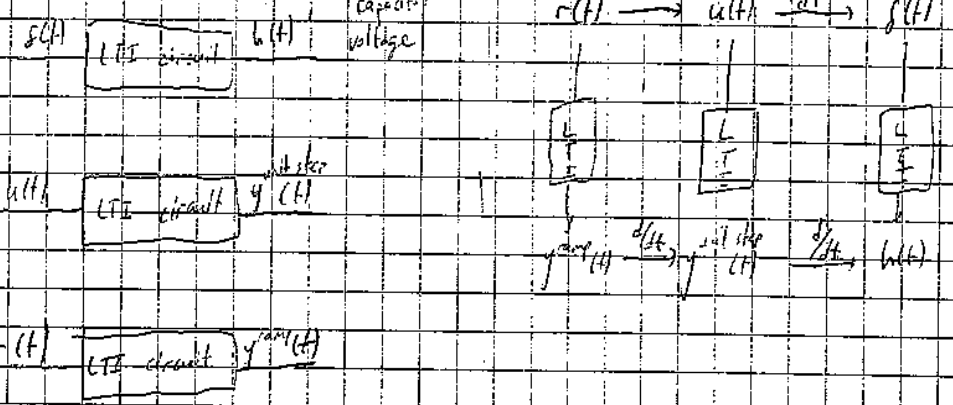


Ex: RC circuit impulse response $h(t) = \frac{1}{RC} e^{-t/RC} u(t)$ Unit step response?

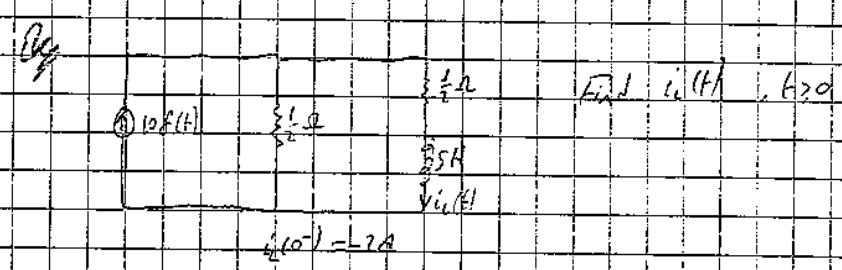unit-step $y(t) = \int_{-\infty}^t h(\tau) u(\tau) d\tau = \int_{-\infty}^t \frac{1}{RC} e^{-\tau/RC} u(\tau) d\tau = \int_0^t \frac{1}{RC} e^{-\tau/RC} d\tau = \left[-e^{-\tau/RC} \right]_0^t = 1 - e^{-t/RC}$




Zero state

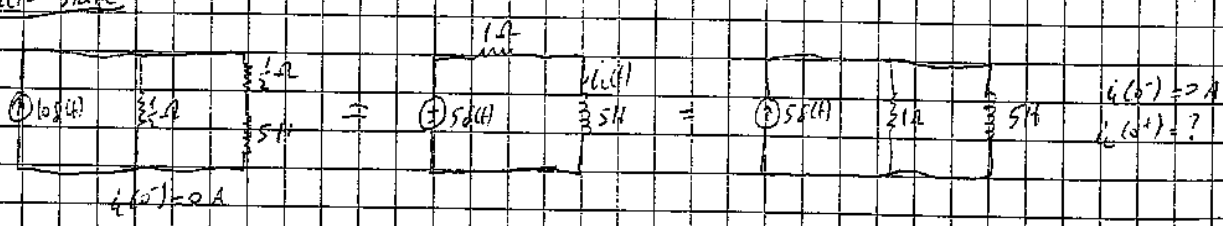


$t < 0$

$i_{zs}(t) = 5e^{-t/5} u(t) \rightarrow v_L(t) = 5e^{-t/5} u(t); i_L(0^+) = i_L(0^-) = \int_{-\infty}^0 v_L(\tau) / L = 1A$

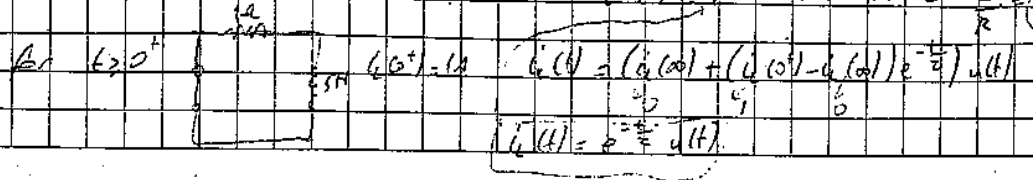For $t > 0$ $i^{zs}(t) = 1e^{-t/5} u(t) \Leftrightarrow \tau = \frac{L}{R} = 5 \text{ sec}$




200 Input

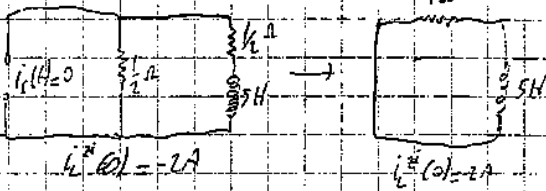

$$i_L(t) = -2e^{-t/5} u(t) \quad \tau = \frac{L}{R} = 5$$

$$i_L^{complete}(t) = i_L^{zs}(t) + i_L^{nh}(t) = e^{-t/5} u(t) - 2e^{-t/5} u(t) = -e^{-t/5} u(t)$$

200 Output

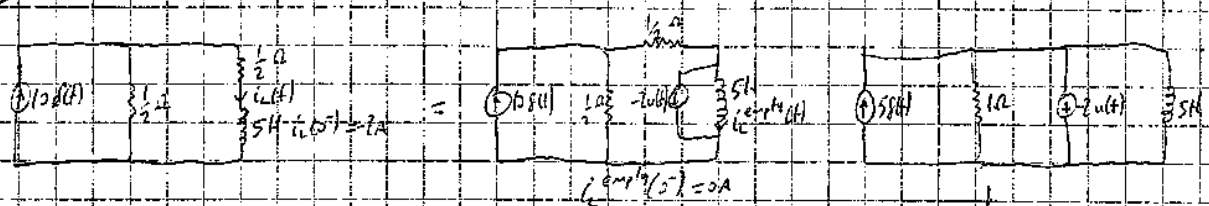


$$i_L(t) = 2e^{-t/5} u(t) + 5 \frac{di_L(t)}{dt}$$

$$i_L(t) = 2(1 - e^{-t/5}) + 5 \left(-\frac{1}{5} e^{-t/5}\right) = 2 - e^{-t/5}$$


$$i_L(t) = i_L^{zs}(t) - 2u(t) = -e^{-t/5} u(t)$$

$$i_L(t) = (1 - e^{-t/5}) u(t) \quad (\tau = 5)$$

Ex

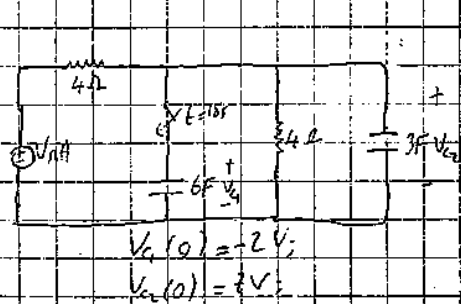


$$V_C(0) = +2V; \quad V_C(0) = -2V$$

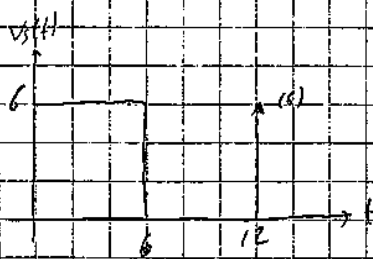


$$V_C(t) = ?$$

F- ACIS (Before switch closes)

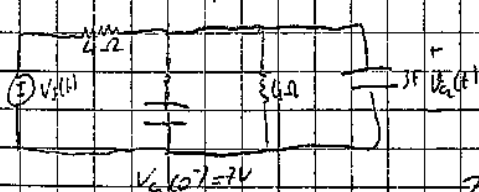

$$V_C(0) = 7V$$

25

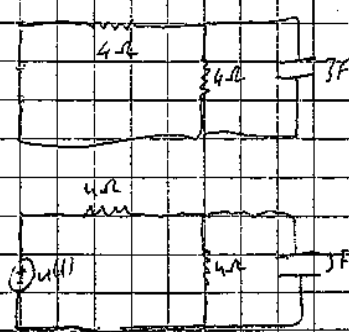

$$V_C(t) = 7e^{-t/6} u(t) \quad \tau = (4)(3) = 6 \text{ sec}$$

$$V_C^{complete}(t) = \frac{1}{2} + \frac{1}{2} e^{-t/6} u(t) \quad \tau = 6 \text{ sec}$$

a) $i_c(t) = \left(e^{-\frac{t}{\tau}} u(t) \right)$; $\tau = RC = 1 \text{ sec.}$

b) $V_c(t) + R(t) i_c(t) = 0$

$V_c(t) + R(t) C \frac{dV_c(t)}{dt} = 0$ $V_c(0) = 1V$

$\frac{dV_c(t)}{dt} = -\frac{V_c(t)}{RC} \rightarrow \dot{V}_c(t) = -(1+0.5 \cos t) V_c(t) \Rightarrow \frac{dV_c(t)}{V_c(t)} = -(1+0.5 \cos t) dt$

$\ln V_c(t) = -(t + 0.5 \sin t) + K$


$V_c(t) = A e^{-(t + 0.5 \sin t)}$ $V_c(0) = 1V \Rightarrow 1 = A \Rightarrow V_c(t) = e^{-(t + 0.5 \sin t)} u(t)$

c) $C \frac{dV_c(t)}{dt} = -i_R(t) = -(V_c(t))^2$

$\frac{dV_c(t)}{(V_c(t))^2} = -dt \rightarrow -\frac{1}{V_c(t)} = -t + K \Rightarrow V_c(t) = \frac{1}{t + K}$

$V_c(0) = \frac{1}{K} = 1 \Rightarrow K = 1$


$V_c(t) = \frac{1}{t+1} u(t)$

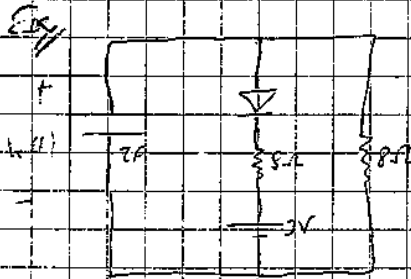


$V_c(0) = 10V$ $i_c(t) = ?$

Method 1: Block 3V when $V_c(t) \geq 3V$


For $V_c(t) \geq 3V$

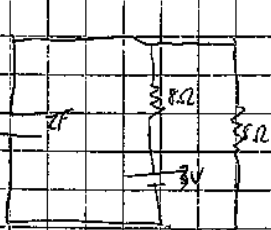

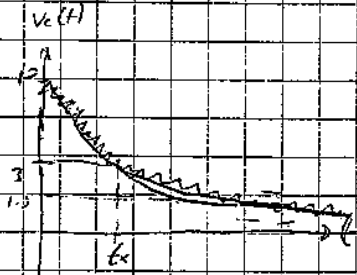$V_c(0) = \frac{3}{2} V$
 $V_c(t) = \left(\frac{3}{2} + \left(10 - \frac{3}{2} \right) e^{-\frac{t}{2}} \right)$
 $V_c(t) = \frac{3}{2} + \frac{17}{2} e^{-\frac{t}{2}}$





For $V_c(t) < 3V$

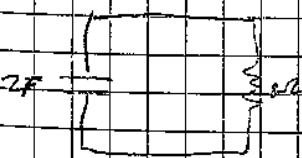

$V_c(t) = 3 e^{-\frac{(t-t_0)}{2}} u(t-t_0)$

Ex 4

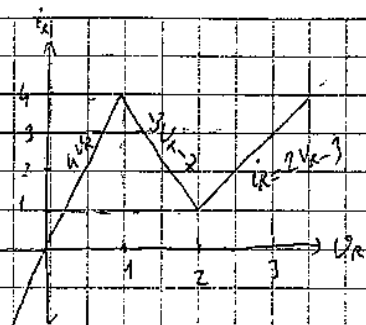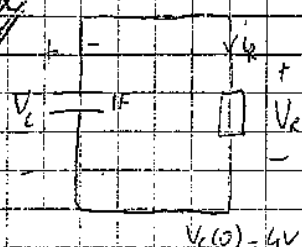

Find $V_c(t)$

$V_c(0^+) = V_c(0^-) = 4V$

when $V_c(t) > 0$, then $V_c(t)$ is decreasing.

$C \frac{dV_c}{dt} = -i_c$
 $i_c > 0$ when $V_c > 0$
 $i_c < 0$ when $V_c < 0$

a) $2 < V_c(t) < 4 \rightarrow i_c = 2V_c - 3$

$\frac{dV_c(t)}{dt} = -2(V_c - \frac{3}{2}) \rightarrow DV_c = -2(V_c - \frac{3}{2})$
 $(0+2)V_c = 3$

$\frac{dV_c}{dt} < 0$ when $V_c(t) > 0$

$V_c(t) = 2 + 2 = 5e^{-\frac{t}{2}} + 3$

$V_c = \alpha e^{-\frac{t}{2}} + \frac{3}{2}$

$t_c = \frac{\ln 5}{2} \approx 0.8 \text{ sec}$

$V_c(0^+) = 4 \rightarrow \alpha = \frac{5}{2}$


b) $1 < V_c(t) < 2; \frac{dV_c}{dt} = -(2(V_c - \frac{2}{3}))$

$V_c(t_c) = 2V$

$V_c(t) = \frac{5e^{-\frac{t}{2}} + 3}{2} u(t)$

$V_c = \frac{2}{3} - \frac{1}{3} e^{-\frac{t}{2}}$

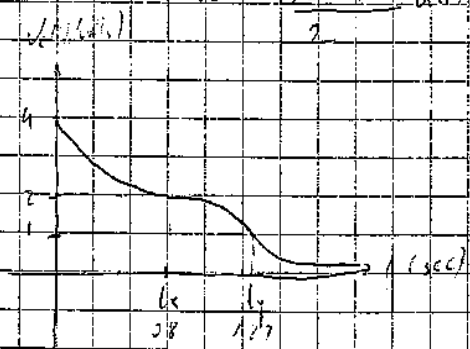$V_c(t_y) = 1V \Rightarrow t_y = 1.27 \text{ sec}$





c) $2 < V_c < 4$

$\frac{dV_c}{dt} = -\frac{1}{C} V_c$, $V_c(t_y) = 1$

$V_c(t) = e^{-\frac{t}{C}}$, $t > t_y$

Ex 5

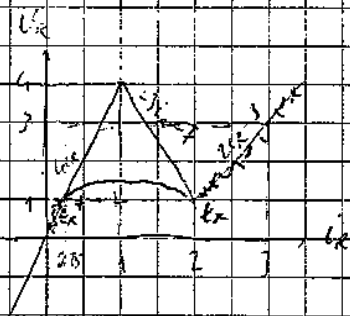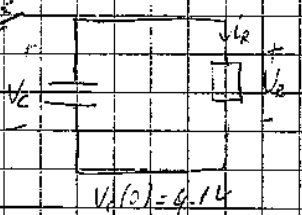

Find $V_c(t)$


$C \frac{dV_c(t)}{dt} = -i_c \rightarrow i_c > 0 \rightarrow V_c(t)$ decreases

a) $i_c \geq 2 \rightarrow \frac{dV_c(t)}{dt} = -(V_c) = -(\frac{V_c + 3}{2})$, $V_c(0) = 4.1V \Rightarrow V_c(t) = \alpha e^{-\frac{t}{2}} - 3$
 $i_c = \frac{V_c + 3}{2}$, $V_c(t) = 7.1e^{-\frac{t}{2}} - 3$

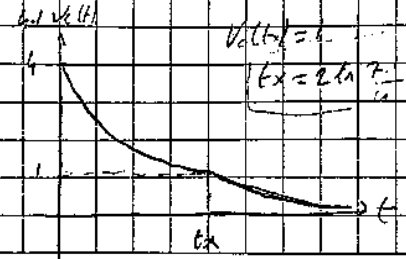b) $V_c(t) = 1V$

$i_c < 0.25 \rightarrow$ on the segment $\frac{dV_c(t)}{dt} = -\frac{1}{C} V_c(t)$
 $V_c = \alpha e^{-\frac{t}{C}}$

$\Rightarrow V_c(t) = 1e^{-\frac{(t-t_y)}{C}}$, $t > t_y$



SECOND ORDER CIRCUITS

Parallel RLC (Series RLC)



$$i_s(0) = I_s$$

$$v_c(0) = V_0$$

$$i_s(t) = i_R(t) + i_C(t) + i_L(t)$$

$$i_s(t) = i_R(t) + i_C(t) + \frac{C dv_c(t)}{dt} \quad v_c(t) = v_R(t) = v_L(t)$$

$$i_s(t) = \frac{v_c(t)}{R} + \frac{v_c(t)}{L} + C \frac{dv_c(t)}{dt}$$

$$L \frac{d^2 v_c(t)}{dt^2} + \frac{L}{R} \frac{dv_c(t)}{dt} + v_c(t) = \int i_s(t) dt$$

$$\frac{d}{dt} \left(\frac{L}{R} \frac{dv_c(t)}{dt} + v_c(t) \right) = \frac{L}{R} \frac{d^2 v_c(t)}{dt^2} + \frac{dv_c(t)}{dt}$$

$$\frac{d^2 v_c(t)}{dt^2} + \frac{1}{RC} \frac{dv_c(t)}{dt} + \frac{v_c(t)}{LC} = \frac{1}{C} \frac{di_s(t)}{dt}$$

$$\left(CD^2 + \frac{1}{R} D + \frac{1}{L} \right) v_c(t) = \frac{1}{C} \frac{di_s(t)}{dt} \quad \text{forcing term}$$

$$v_c(0) = V_0$$

$\frac{d}{dt} v_c(0) = ?$ ← need to find this from given initial conditions

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) v_c(t) = \frac{1}{C} \frac{di_s(t)}{dt} \quad \leftarrow \text{parallel RLC}$$

Write a 1st order matrix dif eqn. for RLC circuit

State variables: $(v_c(t), i_L(t))$

$\frac{d}{dt} \begin{bmatrix} v_c(t) \\ i_L(t) \end{bmatrix} = \begin{bmatrix} \alpha v_c(t) + \beta i_L(t) + \gamma i_s(t) \end{bmatrix}$ ← in terms of a linear combination of state variables and input.

$$C \frac{dv_c(t)}{dt} = i_C(t) = i_s(t) - i_R(t) - i_L(t)$$

$$(1) \frac{dv_c(t)}{dt} = -\frac{1}{RC} v_c(t) - \frac{1}{C} i_L(t) + \frac{1}{C} i_s(t)$$

$$L \frac{di_L(t)}{dt} = v_L(t) = v_c(t)$$

$$(2) \frac{di_L(t)}{dt} = \frac{v_c(t)}{L}$$

$$\begin{bmatrix} \frac{d}{dt} v_c(t) \\ \frac{d}{dt} i_L(t) \end{bmatrix} = \begin{bmatrix} -\frac{1}{RC} & -\frac{1}{C} \\ \frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} v_c(t) \\ i_L(t) \end{bmatrix} + \begin{bmatrix} \frac{1}{C} \\ 0 \end{bmatrix} i_s(t)$$

$$v_c(0) = V_0$$

$$i_L(0) = I_s$$

$$\frac{d^2 V_c(t)}{dt^2} = -\frac{1}{RC} \frac{dV_c(t)}{dt} - \frac{1}{C} \frac{dI_c(t)}{dt} + \frac{1}{C} dI_c(t)$$

→ (1) state equation = $\frac{dV_c(t)}{dt}$

$$D^2 V_c(t) - \frac{1}{RC} D V_c(t) - \frac{1}{C} V_c(t) + \frac{1}{C} dI_c(t)$$

← equivalent to the earlier form

Type of zeros - Input Solutions (parallel RLC)

$$(D^2 + 2\alpha D + \omega_0^2) V_c(t) = 0 \quad \leftarrow \text{zero input (no forcing term)}$$

Parallel RLC $2\alpha = \frac{1}{RC} \quad \omega_0^2 = \frac{1}{LC}$

Characteristic polynomial = $s^2 + 2\alpha s + \omega_0^2 = 0$


$$s_{1,2} = \frac{-2\alpha \pm \sqrt{(2\alpha)^2 - 4\omega_0^2}}{2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$V_c(t) = C_1 e^{s_1 t} + C_2 e^{s_2 t}$$


3 cases of s_1 and s_2

- ① Real and distinct ($\Delta > 0$) \Rightarrow Over-damped $V_c(t) = C_1 e^{s_1 t} + C_2 e^{s_2 t}$ $s_1 = -2, s_2 = -3$
- ② Real and same ($\Delta = 0$) \Rightarrow Critically damped $V_c(t) = C_1 e^{s_1 t} + C_2 t e^{s_1 t}$ $s_1 = -1, s_2 = -1$
- ③ Imaginary roots ($\Delta < 0$) \Rightarrow Underdamped $V_c(t) = 2 e^{-\alpha t} (C_1 \cos \omega_d t + C_2 \sin \omega_d t)$ $s_1 = -1 + j, s_2 = -1 - j$


① Over-damped \rightarrow

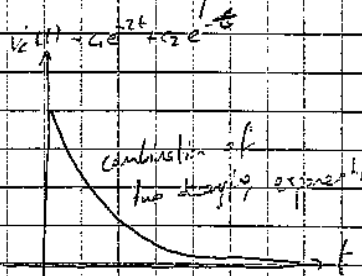


② Critically damped \rightarrow

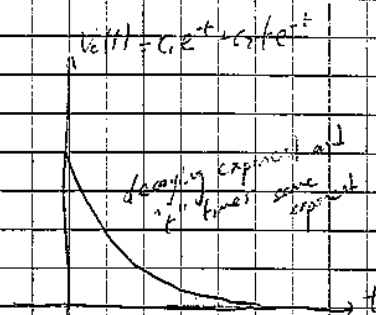

③ Under-damped \rightarrow

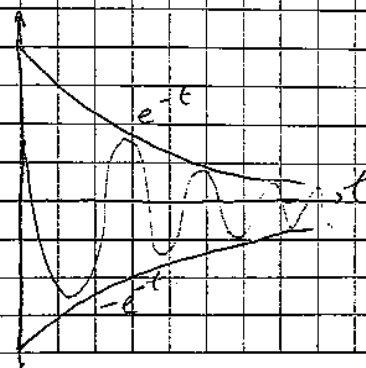

Ex 1

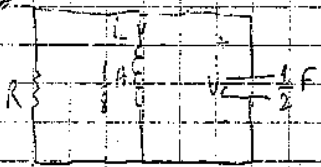

$i(0^+) = -4A$
 $v_c(0^+) = 5V$

a) $R = \frac{1}{3} \Omega$

$(D^2 + 10D + 16) v_c(t) = 0$

$(D^2 + 2\alpha D + \omega_0^2) \rightarrow A^2 + (2\alpha)A + \omega_0^2 = 0 \Rightarrow \lambda_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

α : Damping rate
 ω_0 : Natural frequency

$(D^2 + \frac{1}{3}D + \frac{1}{4C}) v_c(t) = 0 \Rightarrow \dots$


$v_c(0^+) = 5$
 $\frac{d v_c(0^+)}{dt} = \dots$

$\alpha = 5$
 $\omega_0 = 4$
 $\alpha > \omega_0 \rightarrow$ overdamped response

$v_c(t) = (Ae^{-2t} + Be^{-8t}) u(t) \quad t \geq 0$

$v_c(0^+) = 5V \Rightarrow A+B=5$

$\lambda_{1,2} = \{-2, -8\}$

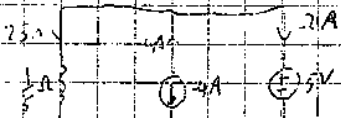

$\frac{d v_c(0^+)}{dt} = -21A \Rightarrow \frac{d v_c(0^+)}{dt} = -42 = -2A - 8B$

$v_c(t) = \frac{16}{3} e^{-2t} - \frac{16}{3} e^{-8t}$

$A+B=5$

$A-6B=91$

$A = \frac{16}{3}, B = -\frac{1}{3}$

b) $R = 1 \Rightarrow \alpha = 4, \omega_0 = 4$

$\alpha = \omega_0 \Rightarrow$ critically damped response

$(D^2 + 2\alpha D + \omega_0^2) = (D + \omega_0)^2$

$\Rightarrow v_c(t) = (5 - 12A) e^{-4t} u(t)$

c) $R = \frac{1}{5} \Rightarrow \alpha < \omega_0$ ($\lambda_{1,2}$ = complex roots for characteristic equation) (under damped)

$\lambda_{1,2} = \{-3 \pm j\sqrt{7}\}$

$v_c(t) = ce^{2t} + c^* e^{2t}$
 $= ce^{2t} + c^* e^{2t}$
 $= \|c\| e^{j\omega t} e^{\alpha t} + \|c^*\| e^{-j\omega t} e^{\alpha t}$

$= \|c\| [e^{2t + j\sqrt{7}t} + e^{2t - j\sqrt{7}t}]$
 $= \|c\| [e^{2t + j\sqrt{7}t} + e^{2t - j\sqrt{7}t}]$
 $= \|c\| e^{2t} [e^{j\sqrt{7}t} + e^{-j\sqrt{7}t}]$

$\Rightarrow v_c(t) = \|c\| e^{-3t} 2 \cos(\sqrt{7}t + \phi)$ - real number in radians


$v_c(0^+) = 5$

$\frac{d v_c(0^+)}{dt} = -72 \Rightarrow v_c(t) = e^{-3t} 4\sqrt{7} \cos(\sqrt{7}t + \tan^{-1} \frac{\sqrt{7}}{5})$

Burada ne yaptik?

Bu notasyonu kullanmaya gerek var mi?
 Ince sorularda kullanmamizdir

d) $R \rightarrow \infty$

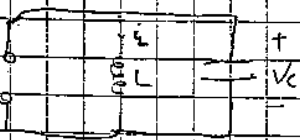

(Lossless System)

$(D^2 + \frac{1}{LC}) v_c(t) = 0$

$\alpha \rightarrow 0$ as $R \rightarrow \infty$

$(D^2 + \frac{1}{LC}) v_c(t) = 0$

$(D^2 + 16) v_c(t) = 0$

$v_c(t) = ce^{-j4t} + de^{j4t}$

$v_c(t) = A \cos(4t) + B \sin(4t)$

$v_c(t) = C \cos(4t + \phi)$


$v_c(0) = 5$

$\frac{d v_c(0)}{dt} = 0$

$v_c(t) = 5 \cos(4t) + 2 \sin(4t)$

Ramp / Unit Step / Impulse Response (Elementary Zero-State Response)

Ex)

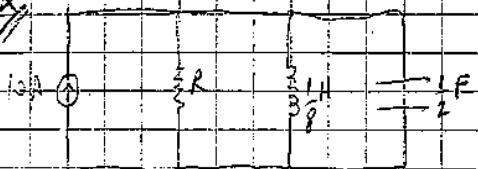

$a) R = \frac{1}{3} \Omega \rightarrow V_c^{zi} = -\frac{1}{3} e^{-2t} + \frac{16}{3} e^{-3t}$
 $(j^2 + 10j + 16) V_c(t) = \frac{1}{C} \frac{d i_c(t)}{dt} = 0$

$V_c(t) = a + \alpha e^{-2t} + \beta e^{-3t} \rightarrow V_c(\infty) = 0 \rightarrow a = 0$
 $\Rightarrow V_c(t) = 3e^{-2t} + 2e^{-3t}$
 $i_c(t) = 10 \int_{-\infty}^t e^{-2t} - 2e^{-3t}$
 (1) analysis at $t = 0^+$

Ramp response

$i_c(t) = r(t) \quad v(t)$

$(j^2 + 2\alpha j + \omega_0^2) V_c(t) = \frac{1}{C} \frac{d i_c(t)}{dt}$
 $V_c(0^-) = 0$
 $\frac{d V_c(0^-)}{dt} = 0$ } Zero-State!!

$V_c(0^+) = ?$
 $\frac{d V_c(0^+)}{dt} = ?$
 $(j^2 + 2\alpha j + \omega_0^2) V_c(t) = \frac{1}{C} \frac{d i_c(t)}{dt}$
 $t > 0$
 $V_c(t) = A + B e^{-2t} + C e^{-3t}$


Ramp we will response in multibeen zero state in output (impulse gain)

$V_c(0^+) = V_c(0^-)$
 $\frac{d V_c(0^+)}{dt} = \frac{d V_c(0^-)}{dt}$
 same flow in = impulse



Unit Step Response

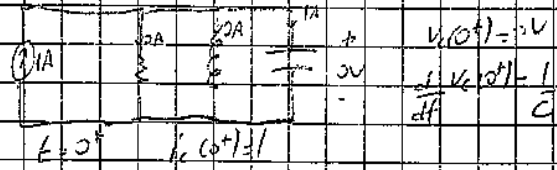$(j^2 + 2\alpha j + \omega_0^2) V_c(t) = \frac{1}{C} \frac{d i_c(t)}{dt}$



Then for $t > 0$


$(j^2 + 2\alpha j + \omega_0^2) V_c(t) = 0 \quad V_c(0^+) = 0 \quad \frac{d V_c(0^+)}{dt} = \frac{1}{C}$

$(j^2 + 2\alpha j + \omega_0^2) V_c(t) = \frac{\delta(t)}{C} \rightarrow \ddot{V}_c(t) = \frac{1}{C} \delta(t)$
 $\Rightarrow V_c(0^+) = \frac{1}{C}$
 $V_c(0^-) = 0$

$\int_0^{0^+} \delta(t) dt + \int_0^{0^+} \ddot{V}_c(t) dt + \omega_0^2 \int_0^{0^+} V_c(t) dt = \frac{1}{C} \int_0^{0^+} \delta(t) dt$

$[V_c(0^+) - V_c(0^-)] + 2\alpha [V_c(0^+) - V_c(0^-)] + \omega_0^2 \int_0^{0^+} V_c(t) dt = \frac{1}{C}$
 $V_c(0^+) + 2\alpha(0-0) + \omega_0^2(0) = \frac{1}{C}$

Impulse Response (Zero-State Analysis)

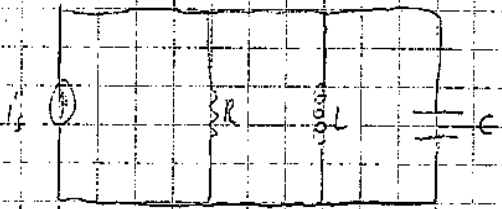


$$(D^2 + 2\alpha D + \omega_0^2) v_c(t) = \frac{1}{C} \delta(t)$$

$$\left. \begin{aligned} v_c(0^-) &= 0 \\ \dot{v}_c(0^-) &= 0 \end{aligned} \right\} \begin{aligned} v_c(0^+) &= 0 \\ i_c(0^+) &= 0 \end{aligned}$$

$i_s(t) \rightarrow \delta(t) \Rightarrow (D^2 + 2\alpha D + \omega_0^2) v_c(t) = \frac{1}{C} \delta(t)$

method / Verzucht

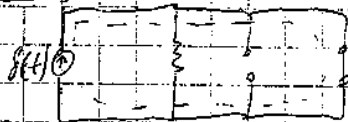

$$0 < t < 0^+$$

$$i_s(t) = \delta(t) \rightarrow v_c(0^+) = \frac{1}{C} \int_0^{0^+} \delta(t) dt = \frac{1}{C}$$

$$v_c(t) = 0V \rightarrow i_c(0^+) = \frac{1}{L} \int_0^{0^+} 0 dt = 0$$

at $t=0^+$



$$i_R(0^+) = \frac{1}{CR}$$

$$i_c(0^+) = -\frac{1}{CR}$$

$$C \dot{v}_c(0^+) = -\frac{1}{CR} \Rightarrow \dot{v}_c(0^+) = -\frac{1}{CR^2}$$

for $t > 0^+$

$$(D^2 + 2\alpha D + \omega_0^2) v_c(t) = 0$$

$$v_c(0^+) = \frac{1}{C}$$

$$\dot{v}_c(0^+) = -\frac{1}{CR^2}$$

$$v_c(t) = h(t) = A e^{\alpha t} + B e^{\beta t}$$

Method $(D^2 + 2\alpha D + \omega_0^2) v_c(t) = \frac{1}{C} \delta(t)$ (I)

$$v_c(t) \times \int_0^t \delta(t) dt \rightarrow v_c(t) \times \delta(t) \rightarrow v_c(t) \times u(t) \text{ But integral never exists!}$$

Integrate (I) in between $\int_{0^-}^{0^+}$

$$\int_{0^-}^{0^+} \ddot{v}_c(t) dt + 2\alpha \int_{0^-}^{0^+} \dot{v}_c(t) dt + \omega_0^2 \int_{0^-}^{0^+} v_c(t) dt = \frac{1}{C} \int_{0^-}^{0^+} \delta(t) dt$$

Impulse oblige ist $v_c(0^-) \neq v_c(0^+)$
 But the integral exists
 sufficient for both
 purposes no?

$$[v_c(0^+) - v_c(0^-)] + 2\alpha [v_c(0^+) - v_c(0^-)] + \omega_0^2 [0] = \frac{1}{C}$$

$$v_c(0^+) + \frac{1}{RC} v_c(0^+) = 0 \quad (1)$$

$$(D^2 + 2\alpha D + \omega_0^2) v_c(t) = \frac{1}{C} \delta(t) \Rightarrow \text{Apply } D^{-1} \quad (D^{-2} = \int \int dt)$$

$$D^{-1} (D^2 + 2\alpha D + \omega_0^2) v_c(t) = \frac{1}{C} D^{-1} \delta(t)$$

$$(D + 2\alpha + \omega_0^2 D^{-1}) v_c(t) = \frac{1}{C} \delta(t) \quad (\text{New diff eqn.})$$

Integrate the new DE between $t=0^-$ and $t=0^+$



$$\int_0^+ V_C(t) dt + 2 \int_0^+ V_C(t) dt + \omega_0^2 \int_0^+ (V_C(t) dt) = \frac{1}{C}$$

$V_C(t) = u(t)$

$$V_C(0^+) - V_C(0^-) = \frac{1}{C}$$

$$V_C(0^+) = \frac{1}{C}$$
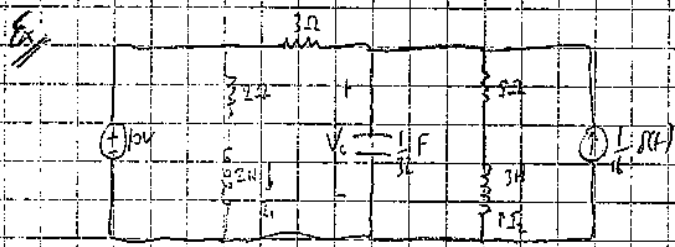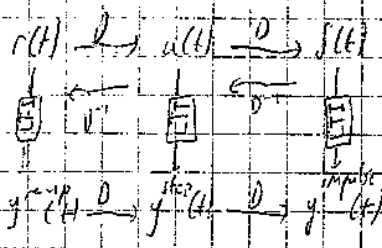
$$V_C(0^+) = -\frac{1}{RC^2} \text{ (from (1))}$$




$$V_C(0^-) = 1V$$

$$I_1(0^-) = 0A$$

$$I_2(0^-) = 5A$$

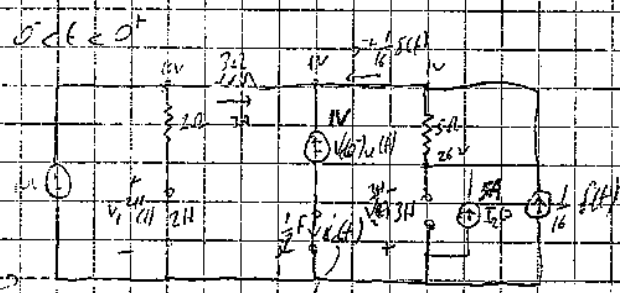Find all currents at $t=0^+$ and $t \rightarrow \infty$



$$V_{L1}(t) = 10V$$

$$V_{L2}(t) = 26V$$

$$V_C(0^+) = \frac{1}{C} \int_0^+ i_C(\tau) d\tau = 2V$$

$$I_{2H}(0^+) = \frac{1}{L_1} \int_0^+ 10 d\tau = 0A$$


$$I_{3H}(0^+) = \frac{1}{L_2} \int_0^+ 26 d\tau = 0A$$

By using components above have no energy


$$V_C(0^+) = V_C(0^+) + V_C(0^-) = 3V$$

$$I_1(0^+) = 2A \quad I_2(0^+) = 5A$$

$t \rightarrow \infty$

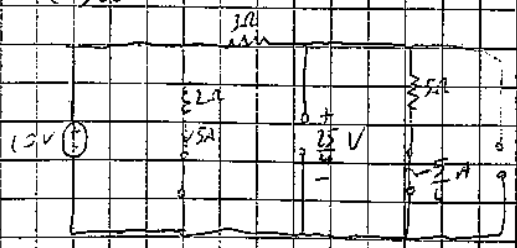

Series RLC

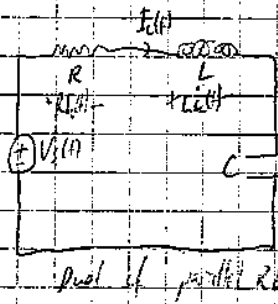


Parallel RLC $(D^2 + \frac{D}{RC} + \frac{1}{LC}) \cdot V_c(t) = \frac{1}{C} I(t)$

$(D^2 + \frac{D}{LC} + \frac{1}{LC}) I_c(t) = \frac{1}{L} D V_s(t)$

$V_R + V_L + V_C = V_s(t)$

$DV_R(t) + DV_L(t) + DV_C(t) = DV_s(t)$

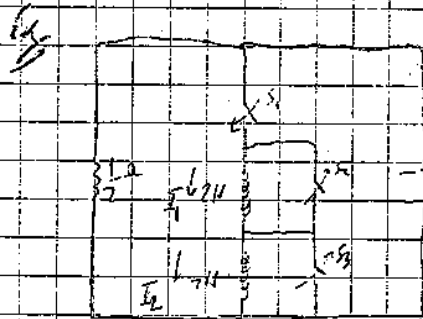$R I_c(t) + L \frac{dI_c(t)}{dt} + \frac{1}{C} I_c(t) = V_s(t)$




$I_1(0) = 1A \quad I_2(0) = -2A \quad V_c(0) = 5V \quad V_c(t) = ?$

S_1 closes at $t = 4$ sec

S_2 opens at $t = 8$ sec

S_3 opens at $t = 12$ sec


1) $0 < t < 4$

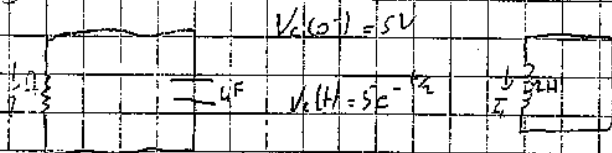

$V_c(0^+) = 5V$
 $V_c(t) = 5e^{-t/4}$

$I_1(t) = 1A$
 $I_2(t) = -2A$

2) $4 < t < 8$

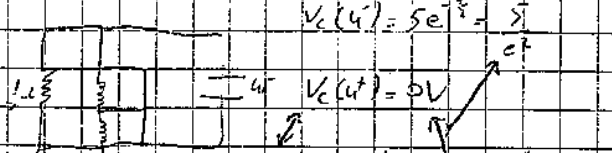


$V_c(4^+) = 5e^{-1} = \frac{5}{e}$

$I_1(4^+) = I_2(4^+) = 1A$

$I_2(4^+) = I_1(4^+) = -2A$

3) $8 < t < 12$

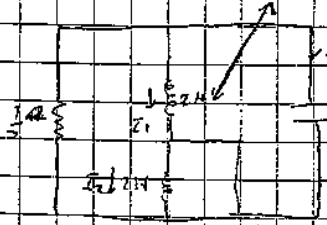

S_1 in rangkaian pertama generator

S_2 in rangkaian kedua generator?

$V_c(8^+) = 0V$
 $I_1(8^+) = 1A$
 $I_2(8^+) = -2A$

$(D^2 + 2\alpha D + \omega_0^2) V_c(t) = 0$

$V_c(t) = A e^{\lambda_1 t} + B e^{\lambda_2 t} \quad \lambda_{1,2} = \frac{-1 \pm j\sqrt{3}}{4}$

$V_c(t) = e^{-\frac{t}{4}} \left(A \cos\left(\frac{\sqrt{3}t}{4}\right) + B \sin\left(\frac{\sqrt{3}t}{4}\right) \right)$

$V_c(t) = e^{-\frac{t}{4}} \left(A \cos\left(\frac{\sqrt{3}(t-8)}{4}\right) + B \sin\left(\frac{\sqrt{3}(t-8)}{4}\right) \right) u(t-8)$

$\alpha = \frac{1}{RC} = \frac{1}{2} \rightarrow \alpha = \frac{1}{4}$

$\omega_0^2 = \frac{1}{LC} = \frac{1}{8} \rightarrow \omega_0 = \frac{1}{2\sqrt{2}}$

$|\alpha| < \omega_0 \rightarrow$ underdamped response

Need $V_c(8^+) = ? + 0V$

$V_c(8^+) = ?$

$V_c(8^+) = -I_1(8^+) = -1$

$V_c(8^+) = -\frac{1}{4}$

computation $\Rightarrow A = 0$


$B = -1 \Rightarrow V_c(t) = e^{-\frac{t}{4}} \left(-\sin\left(\frac{\sqrt{3}t}{4}\right) \right)$

$$V_c(t) = -e^{-t} \left(\sin\left(\frac{t-\pi}{4}\right) \right) = -0.31$$

$$I_1(t) = -\frac{V_c(t) - V_c(t-1)}{R}$$

$$I_1(t) = -\frac{V_c(t) - V_c(t-1)}{R} = \boxed{-\frac{1}{e}}$$

$t > 12$

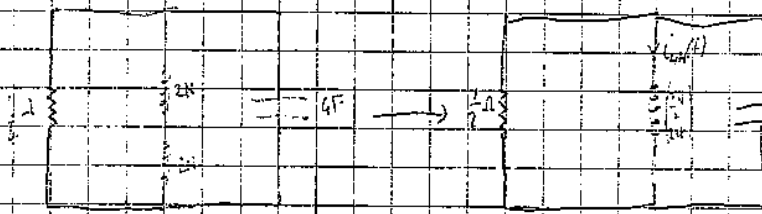

$$L \frac{d^2 V_c(t)}{dt^2} + R \frac{dV_c(t)}{dt} + \frac{1}{C} V_c(t) = 0$$

$$\frac{d^2 V_c(t)}{dt^2} + 2 \frac{dV_c(t)}{dt} + \frac{1}{4} V_c(t) = 0$$

$$V_c(12^+) = -0.31 \text{ V}$$

$$V_c(12^+) = -0.31 \text{ V}$$

$$I_1(t) = \frac{1}{e}$$

$$I_2(t) = -2 \text{ A}$$

$$(D^2 + 2 \times D + \omega_0^2) V_c(t) = 0$$

$$\frac{1}{R} = \frac{1}{2} \quad \frac{1}{LC} = \frac{1}{16}$$

$\omega = \frac{1}{4} \quad \omega_0 = \frac{1}{4} \quad \text{critically damped}$

$$V_c(t) = A e^{-\frac{t}{4}} + B t e^{-\frac{t}{4}}$$

$$V_c(12^+) = 0.45 \quad V_c(12^+) = -0.31 \text{ V}$$

$$V_c(t) = \left[A e^{-\frac{t}{4}} + B(t-12) e^{-\frac{t-12}{4}} \right] u(t-12) \leftarrow A = -0.31 \quad B = 0.37$$

