
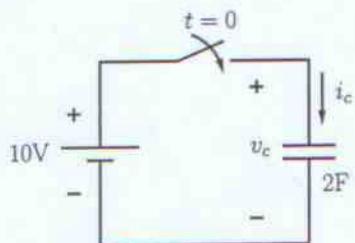


Question 3 (20 pts)

(a)

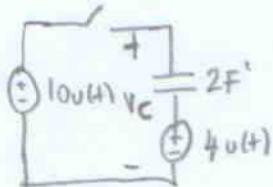


Given $v_c(0^-) = 4 \text{ V}$. Find $i_c(t)$.



$$i_c(t) = C \frac{dv_c}{dt} \xrightarrow{\text{empty}} i_c(t) = 12\delta(t)$$

(b)

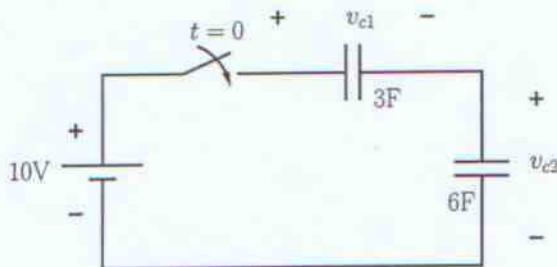


Given $v_{c1}(0^-) = 3 \text{ V}$, $v_{c2}(0^-) = 1 \text{ V}$. Find $v_{c2}(t)$ for $t > 0$.

$$\vartheta_{c2}(t) = \vartheta_{c2}(0^-) + \frac{1}{C_2} \int_0^t i_c(z) dz$$

$$= 1 + 2, \quad t > 0 \\ = 3, \quad t > 0.$$

(c)

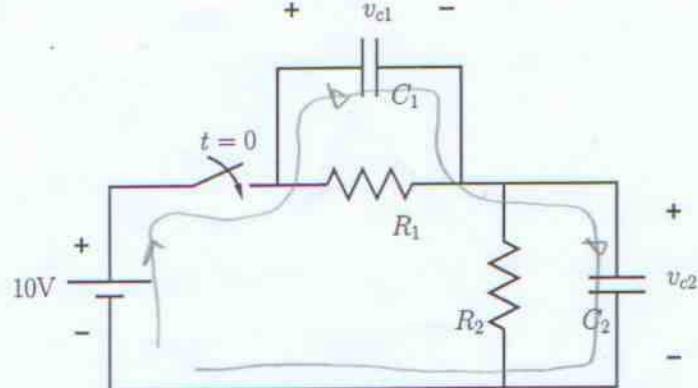

Given $v_{c1}(0^-) = 0$, $v_{c2}(0^-) = 0$.

(i) Express $v_{c2}(0^+)$ and $v_{c2}(+\infty)$ in terms of the source voltage and R_1, R_2, C_1, C_2 .

(ii) Given $v_{c2}(t) = 6 - 2e^{-t/6} \text{ V}$ for $t > 0$, find suitable R_1, R_2, C_1, C_2 values.

$$i) \vartheta_{c2}(0^+) = \frac{v_{c2}}{v_{c1} + v_{c2}} \cdot 10 = \frac{C_1}{C_1 + C_2} \cdot 10, \quad \vartheta_{c2}(+\infty) = 10 \cdot \frac{R_2}{R_1 + R_2}$$

$$ii) \frac{R_2}{R_1 + R_2} = \frac{3}{5}, \quad \frac{C_1}{C_1 + C_2} = \frac{2}{5}, \quad \tau = (C_1 + C_2) \cdot R_1 // R_2 = 6$$

$$\downarrow \quad \quad \quad \downarrow \quad \quad \quad \tau = (\frac{5}{2} C_1) \cdot R_1 \cdot \frac{3}{5} = \frac{C_1 R_1}{2} \cdot 3 = 6$$

(d) Let R_1, R_2, C_2 be as in part (c-ii) and $v_{c2}(t) = 6 \text{ V}$ for $t > 0$. Find C_1 .

$$\left| \begin{array}{l} R_1 = 1 \Omega \\ R_2 = \frac{3}{2} \Omega \uparrow \\ C_1 = 4 \text{ F} \uparrow \\ C_2 = 6 \text{ F} \uparrow \end{array} \right.$$

$$6 = \vartheta_{c2}(0^+) = \vartheta_{c2}(+\infty) \rightarrow \frac{C_1}{C_1 + C_2} \cdot 10 = 10 \cdot \frac{R_2}{R_1 + R_2} = 6 \rightarrow \frac{C_1}{C_1 + C_2} = \frac{3}{5} \rightarrow C_1 = \frac{3}{2} C_2$$

$$C_1 = 9 \text{ F}$$