
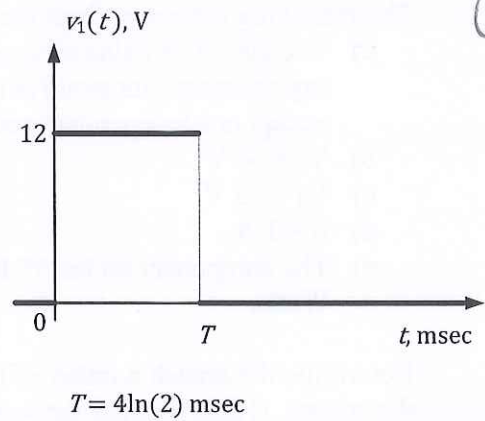


Question 5 (20 pts)

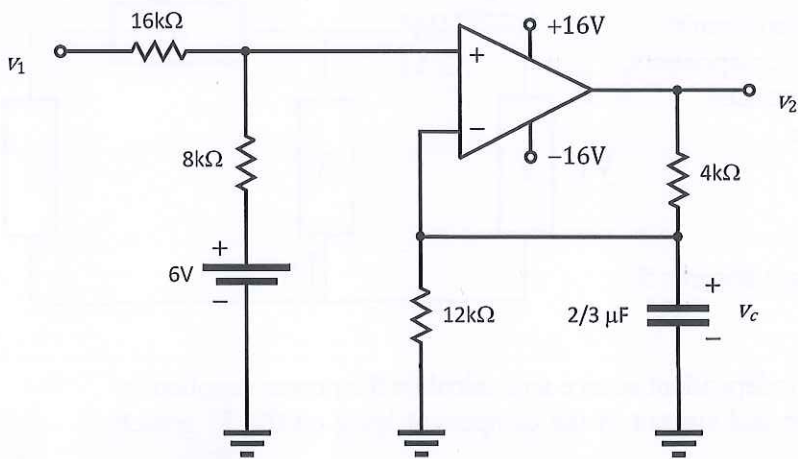


$v_c(0^-) = 4V$.

Find and sketch $v_c(t)$ for $t \geq 0$.

Solu.

We need to find the state of op-amp (its operating region) at $t=0^+$ to start the solution. We know that $v_c(0^+) = v_c(0^-) = 4V$.

Assume +SAT at $t=0^+$:

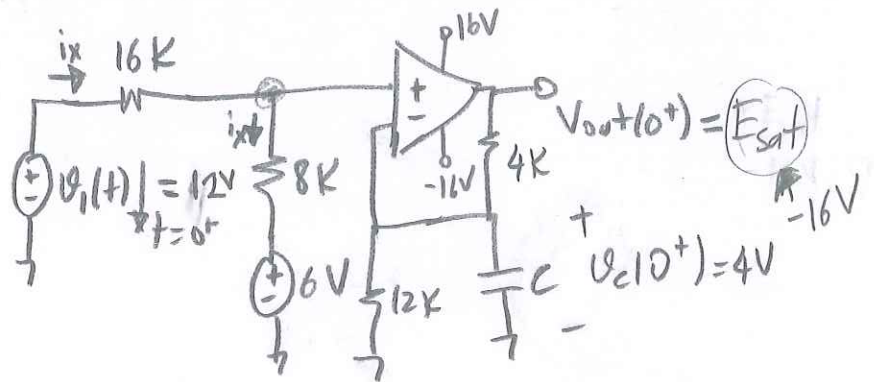

$V_+ = ? \quad i_x = \frac{12-6}{24} \text{ mA} = \frac{1}{4} \text{ mA}$

$V_+ = 12 - (16k) i_x = 8 \text{ Volts}$

$V_d = V_+ - V_- = 8 - 4 = 4 > 0$

but for the assumption to be valid $V_d < 0!$; so assumption is not correct.

Assume linear region for op-amp at $t=0^+$ $\rightarrow |V_{out}| < 16V$
 $\rightarrow V_d = 0$

but $V_+ = 8V$ and $V_- = 4V \rightarrow$ So, can not be linear region either.

Assume +SAT: (This should be the answer! (Why?))

$$\left. \begin{array}{l} V_{out} = 16V = +E_{sat} \\ V_d > 0 \end{array} \right\}$$

$$V_d = V_+ - V_- = 4V > 0$$


8V 4V

Indeed, this is the correct region.

Note: Op-amp operates under negative feedback, hence at a given capacitor voltage, there is one and only one operation region for op-amp. If op-amp has a positive feedback connection also and positive feedback dominates negative feedback, then there can be a case (cap. voltage) that op-amp can be in all 3 regions. For such a problem, additional information should be provided to determine the $t=0^+$ operational region.

In this case, we are sure that op-amp is in +SAT region at $t=0^+$.

$0 < t < T_x$?

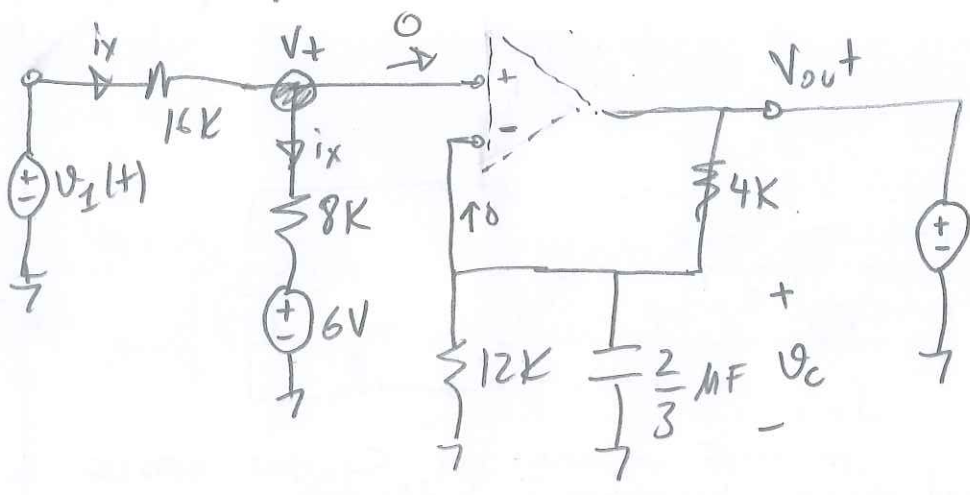


$V_c(0^+) = 4V$

Op-amp output at +SAT

$V_+ = 6 + \frac{V_1 - 6}{24} \cdot 8 = \frac{V_1}{3} + 4$ Volts,

$V_- = V_c = ?$


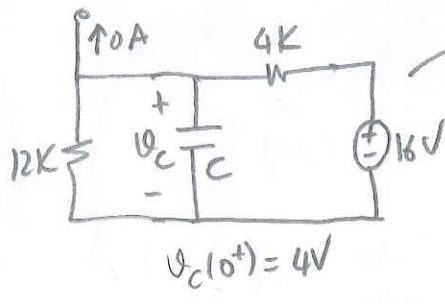


First order circuit

$V_c(t) = 12 - 8e^{-t/\tau}$ Volts

$\tau = (12/4) \cdot \frac{2}{3} \text{ msec} = 2 \text{ msec}$

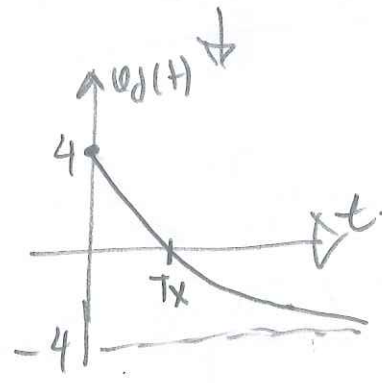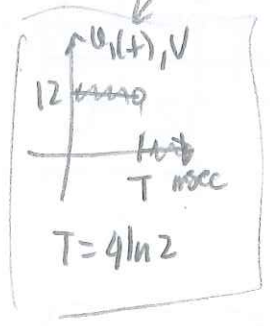$V_d = V_+ - V_- = \frac{V_1}{3} - 8 + 8e^{-t/\tau} \Rightarrow V_d(t) = -4 + 8e^{-t/\tau}$




Note that when $t > T_x$

Op-amp leaves +SAT since $V_d > 0$ not valid.

$V_d(T_x) = 0 = -4 + 8e^{-T_x/\tau} \Rightarrow T_x = \tau \ln 2 = 2 \ln 2 \text{ msec}$

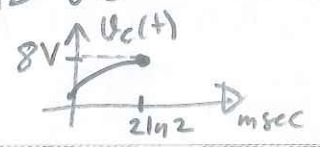Then, $V_c(t) = 12 - 8e^{-t/\tau}$ is valid for $0 < t < T_x = 2 \ln 2 \text{ msec}$.




What is the state of op-amp at $t = T_x^+ = 2 \ln 2^+ \text{ msec.}$? (4)

$V_+(T_x^+) = 8 \text{ Volts.}$
 $V_-(T_x^+) = 8 \text{ Volts.}$

$\rightarrow V_d(T_x^+) = 0 \text{ V} \rightarrow$ Seems to be at linear region.

Let's assume linear region and check:

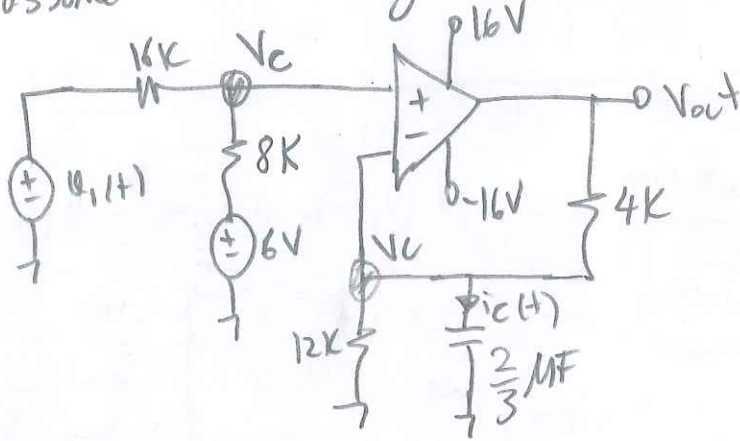


$$T_x^+ < t < T$$

$V_c(T_x^+) = 8 \text{ Volts.}$

$V_+ = V_c(t) = 8 \text{ Volts}$ (constant!)
 $T_x^+ < t < T \rightarrow i_c(t) = 0 \rightarrow V_{out} = \frac{8}{12} \cdot 16 = \frac{32}{3} \text{ Volts}$

\downarrow
 $|V_{out}| < E_{sat} = 16 \text{ V}$

Op-amp is indeed in linear region

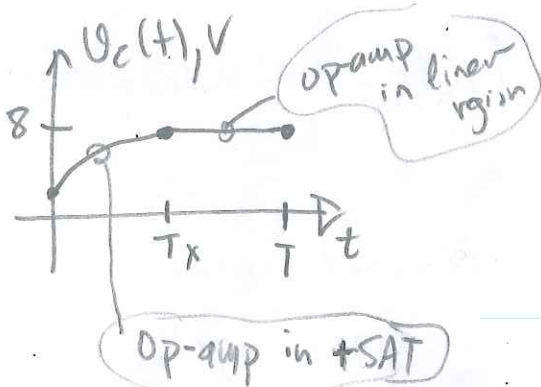

What is the state of op-amp at $t = T^+$?

$V_+(T^+) = \frac{V_1(T^+)}{3} + 4 = 4 \text{ V}$ (page 3)
 $V_-(T^+) = V_c(T^+) = 8 \text{ V}$

$V_d = 4 - 8 = -4 < 0$

\downarrow
 Op-amp seems to enter -SAT

Let's assume -SAT then for $t > T$. 5


As in page 3, with some minor changes

$$V_c(t) = -12 + 20 e^{-(t-T)/\tau} \text{ Volts}, \quad t > T$$

$\tau = 2 \text{ msec}$


$$V_d(t) = V_+(t) - V_c(t)$$

$$= 16 - 20 e^{-(t-T)/\tau}$$

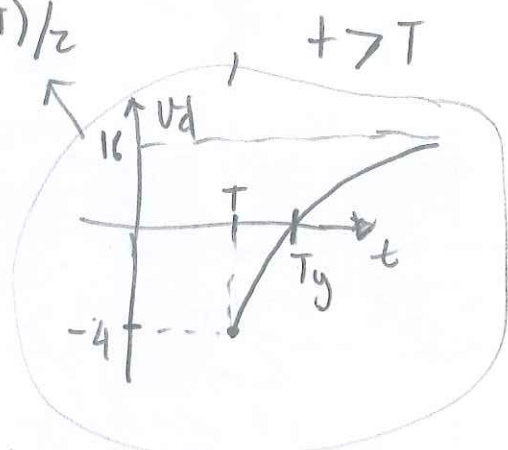

-SAT assumption is valid between $T < t < T_y$ since $V_d < 0$ is not satisfied $t > T_y$! $V_d(T_y) = 0 \rightarrow T_y = T + \tau \ln \frac{5}{4}$

$T_y = 2 \ln 5 \text{ msec}$

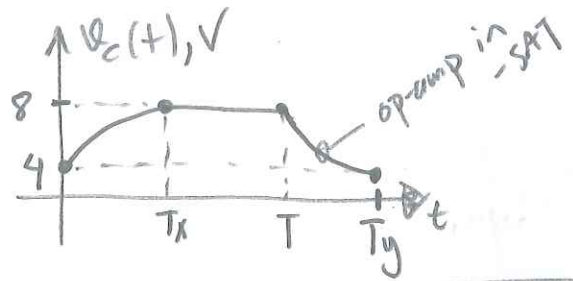


What is op-amp state at $t = T_y^+$?

Assume linear,
check results given page 4
and

$$V_c(t) = 4 \text{ V}, \quad t > T_y \rightarrow i_c(t) = 0, \quad t > T_y \rightarrow V_{out} = \frac{4}{12} \cdot 16 < 16$$

Final Answer

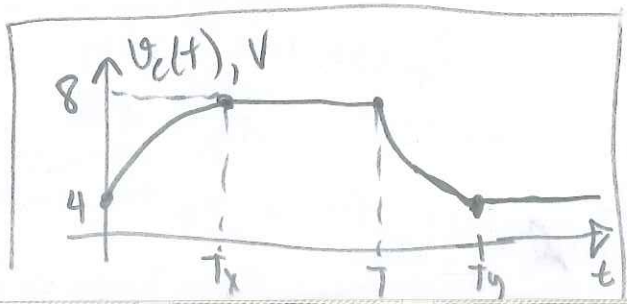

Op-amp is indeed in linear