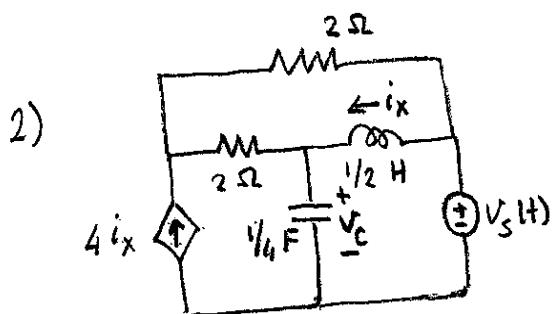


$$i(t) = I_m \cos(\omega t + \Theta) \text{ A}$$

The one-port is in the SSS.

- (a) Determine the frequencies at which the one-port is (i) resistive, (ii) inductive, (iii) capacitive.


(b) For $i(t) = 3 \cos(6t + 35^\circ)$ A find $v(t)$.



$$v_s(t) = 10 \sin(4t + 35^\circ) \text{ V}$$

The circuit is in the SSS.


Find $v_c(t)$ and $i_x(t)$.

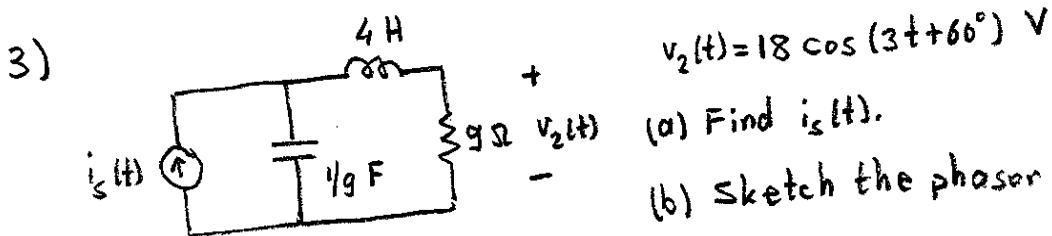

$$v_2(t) = 18 \cos(3t + 60^\circ) \text{ V}$$

(a) Find $i_s(t)$.

(b) Sketch the phasor diagram.

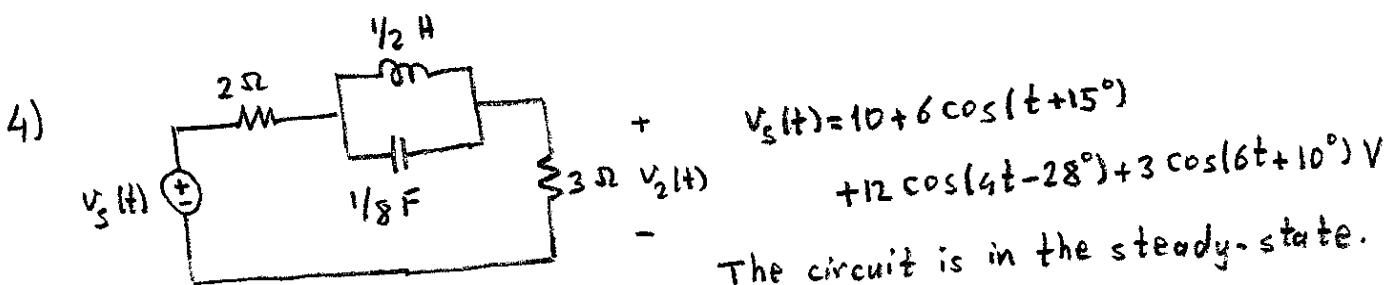


$$v_s(t) = 10 + 6 \cos(t + 15^\circ)$$

$$+ 12 \cos(4t - 28^\circ) + 3 \cos(6t + 10^\circ) \text{ V}$$

The circuit is in the steady-state.


(a) Find $v_2(t)$.

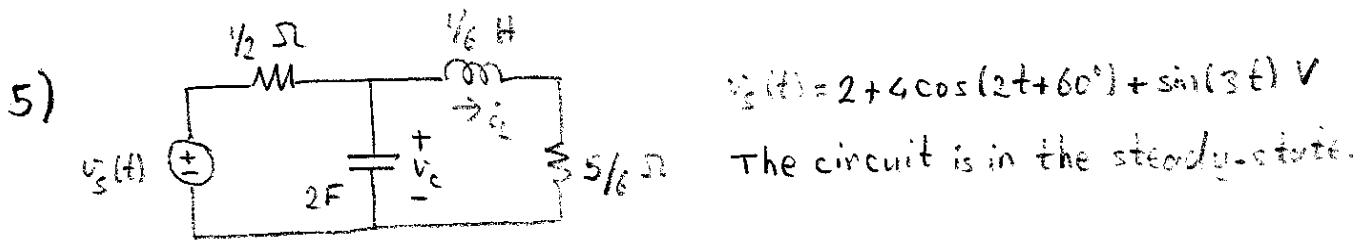(b) Find the average power delivered to the 3 ohm resistor.




(a) Find $v_c(t)$ and $i_c(t)$.

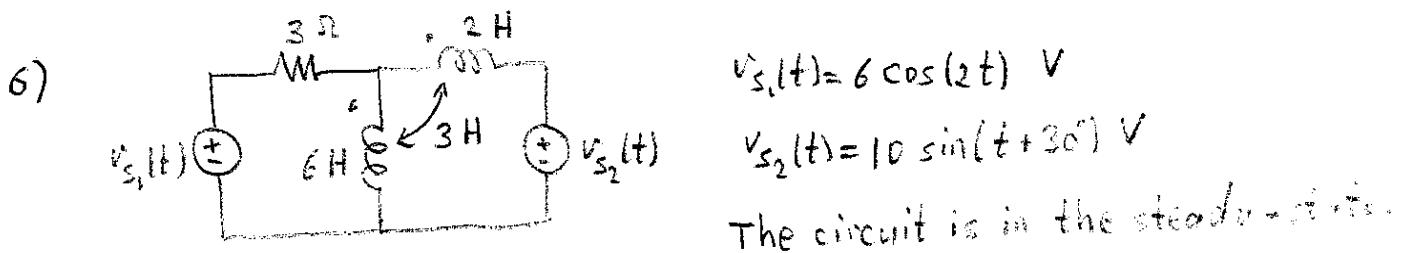(b) Compute the average powers delivered to the resistors, the average power supplied by the source, the average stored energies in the capacitor and in the inductor.



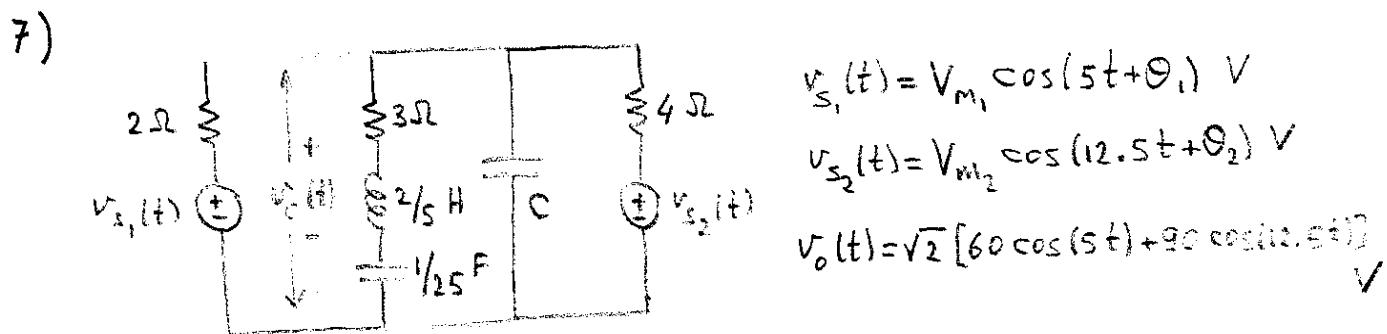
Compute the average power delivered to the resistor, the average powers supplied by the sources, the average stored energy in the coupled inductor.



(a) Compute $P_{3\Omega_{avg}}$.

(b) The average power supplied by the left source is 2 kW.


Compute $P_{2\Omega_{avg}}$.

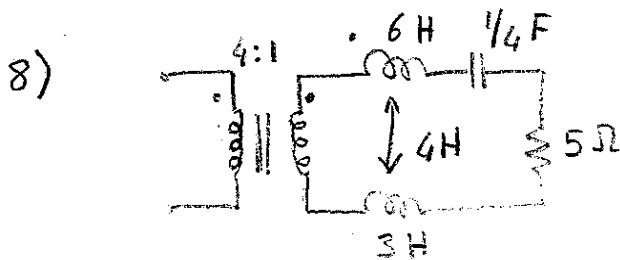

The one-port is in the SSS at the frequency ω rad/sec.

(a) Find the input impedance $Z(i\omega)$.

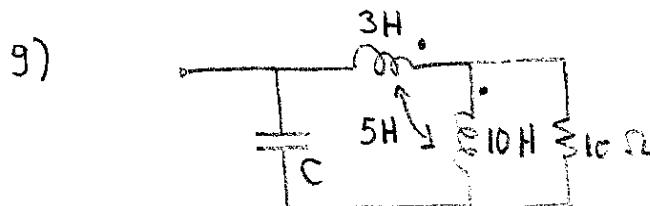(b) For which values of ω is the one-port resistive?
capacitive? inductive?




The one-port is in the SSS at the frequency 2 rad/sec.

(a) Express the input admittance $Y = G + jB$ in terms of C .

(b) Define $\gamma \triangleq G/|Y|$. Determine the value of C such that

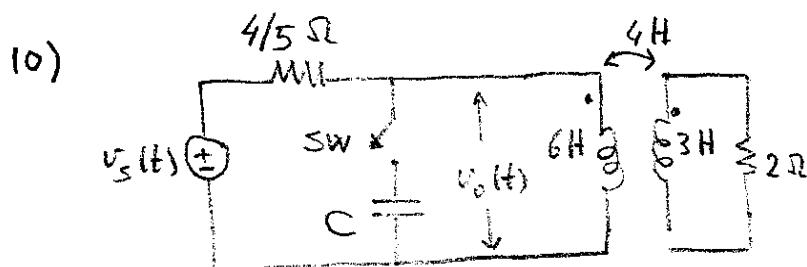(i) $\gamma = 1$, (ii) $\gamma = 0.8$, $B > 0$, (iii) $\gamma = 0.8$, $B < 0$.



$$v_s(t) = V_m \cos(2t + \theta_s) \text{ V}$$


The circuit is in the SSS.

(a) The switch is open, $V_{o,\text{eff}} = 10 \text{ V}$.

Compute $P_{2\Omega,\text{avg}}$ and the average stored energy in the coupled inductor.

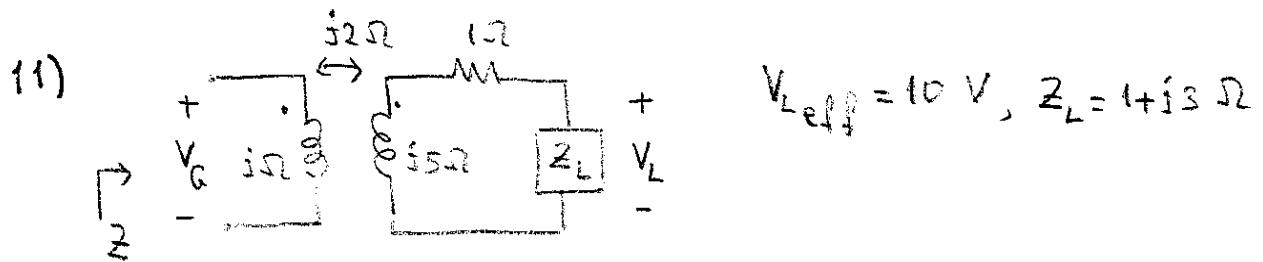(b) The switch is closed, $V_{o,\text{eff}} = 10 \text{ V}$.


Determine the value of C so that the average power supplied by the source is 1 W less than that of Part (a).



$$V_{L\text{eff}} = 10 \text{ V}, Z_L = 1 + j3 \Omega$$

(a) Find Z and $V_{L\text{eff}}$.

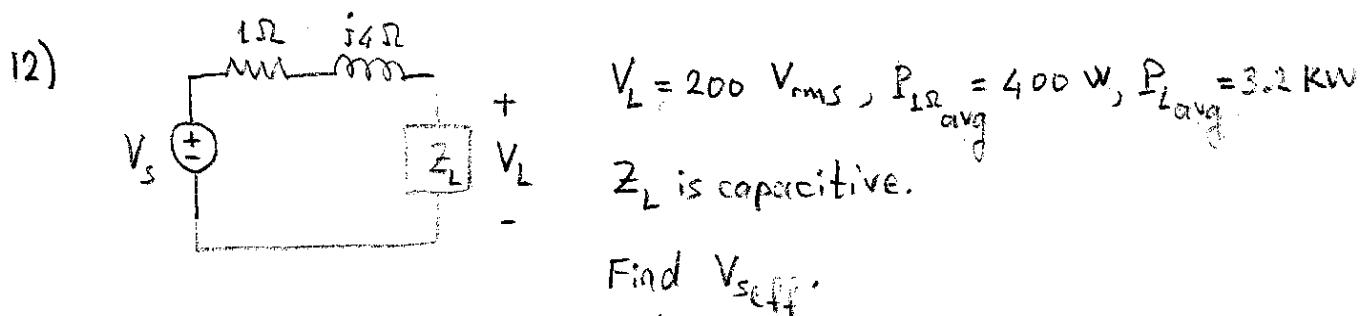
(b) Compute the average power delivered to the resistor and the ratio of the average stored energies in Z_L and in the coupled inductor.



$$V_L = 200 \text{ V}_{\text{rms}}, P_{1\Omega \text{ avg}} = 400 \text{ W}, P_{L \text{ avg}} = 3.2 \text{ kW}$$

Z_L is capacitive.

Find $V_{L\text{eff}}$.

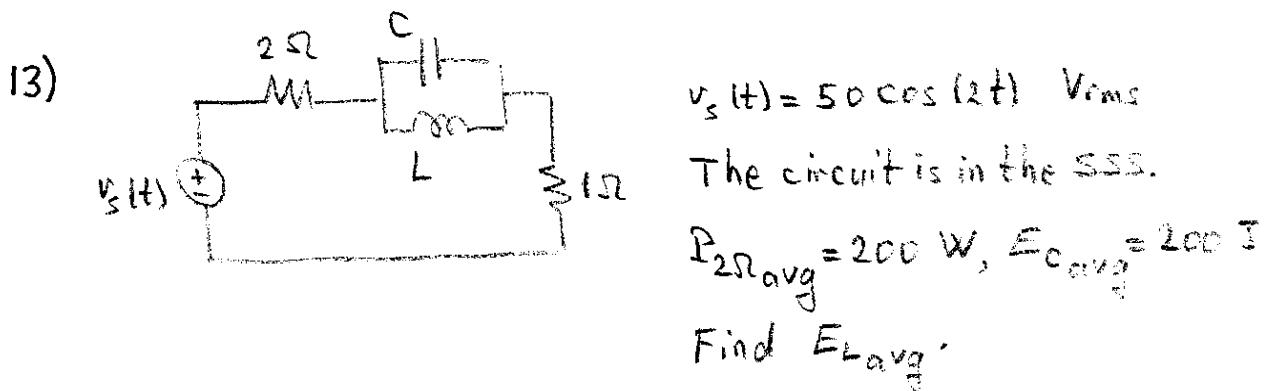


$$v_s(t) = 50 \cos(2t) \text{ V}_{\text{rms}}$$

The circuit is in the SSS.

$$P_{2\Omega \text{ avg}} = 200 \text{ W}, E_{C \text{ avg}} = 200 \text{ J}$$

Find $E_{L \text{ avg}}$.

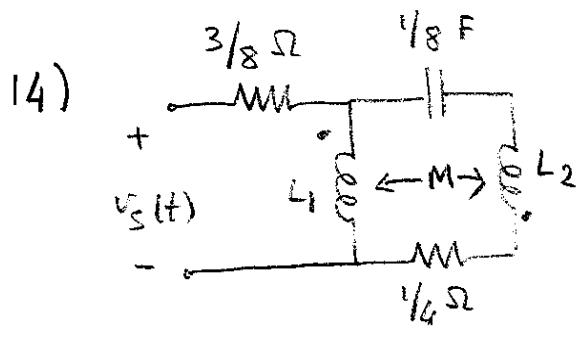

$$v_s(t) = V_m \cos(\omega t + \theta_s) \text{ V}$$

The coupled inductor is passive.

The one-port is in the SSS.

$$P_{\frac{3}{8}\Omega \text{ avg}} = 6 \text{ W}, E_{C \text{ avg}} = 4 \text{ J}$$

The input impedance of the one-port is $Z = Z_m(0.6 - j0.8) \Omega$.

Find V_m and Z_m .