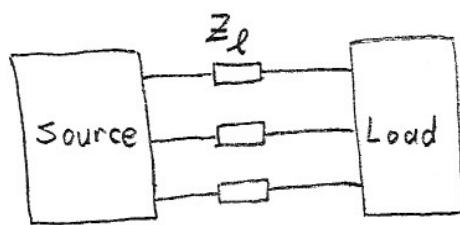


1)



A balanced 3-phase circuit.


Load: 12 kVA,  $P_{L}^f = 0.8$  lagging

$$P_{\text{source}} = 12 \text{ kW}$$

$$Z_L = \frac{1}{2} + j \frac{3}{4} \Omega$$

Find the effective line voltages at the load and source ends.

2)

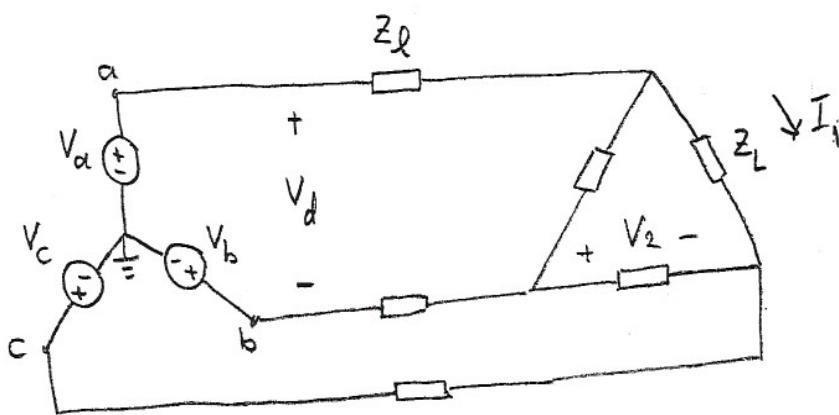

$$S_L = \sqrt{3} \cdot P_L$$

$$f = 50 \text{ Hz}$$

$Z_L$  is inductive.

A balanced 3-phase circuit. The phase sequence is a-b-c.

(a)  $S_L = 48 + j24 \text{ kVA}$ ,  $|S_S| = 75 \text{ kVA}$ ,  $V_d = 500 \angle 60^\circ \text{ V}_{\text{rms}}$

Percent efficiency: 80 %,

Find  $I_1$ ,  $Z_L$ ,  $Z_L$ ,  $V_2$ .

(b) A capacitor bank is connected in parallel with the load.


$S_L$  is as above.

The real power delivered to the lines is reduced by 19 %.

Find the capacitance of each capacitor.

What is the (new) effective value of  $V_d$ .

3)

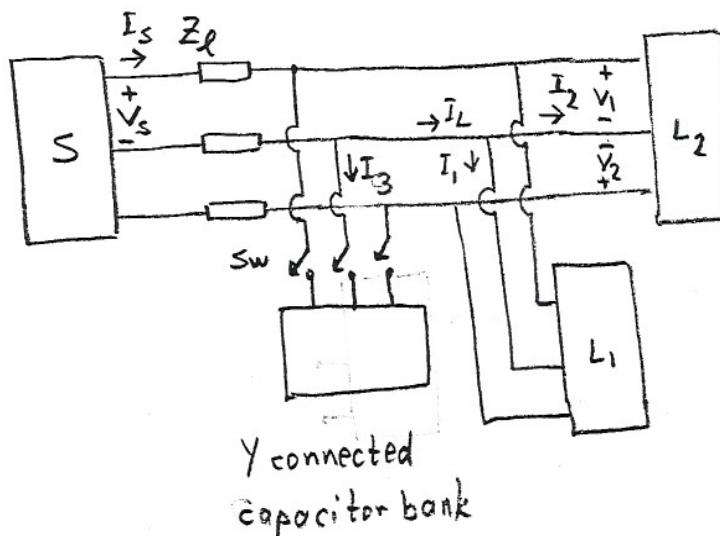

$$V_1 = V_m \angle 30^\circ$$

$$V_2 = V_m \angle -30^\circ$$

$$f = 50 \text{ Hz}$$

$$Z_L = 0.1 + j0.8 \Omega$$

A balanced 3-phase circuit.

L<sub>1</sub>:  $S_{L_1m} = 45 \text{ kVA}$ ,  $P_f = 0.8$  lagging

L<sub>2</sub>:  $S_{L_2m} = 9\sqrt{17} \text{ kVA}$ , inductive


(a) SW is open.  $P_s = 75 \text{ kW}$ ,  $P_d = 3 \text{ kW}$ .

Find  $V_m$ ,  $I_1$ ,  $I_2$ ,  $I_L$ ,  $V_s$ , the percent efficiency.

(b) SW is closed. The power factor of  $L_1 - L_2 - \text{Capacitor Bank}$  combination is 0.96 lagging. ( $V_m$ ,  $S_{L_1}$ ,  $S_{L_2}$  are as above.)

Find the capacitance of each capacitor,  $I_3$ ,  $I_s$ ,  $V_s$ ,  $S_s$  and the percent efficiency.

4)

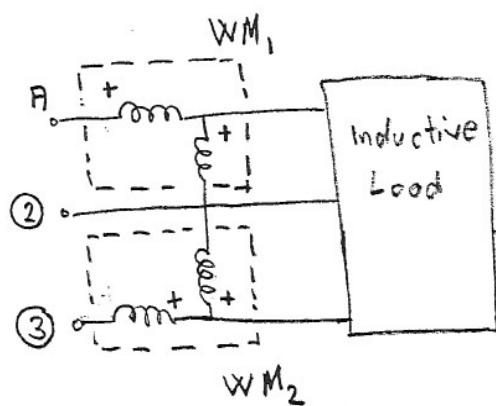

A balanced 3-phase load.

The phase sequence is positive.

The wattmeter readings:

$$WM_1: 800 \text{ W}, WM_2: 200 \text{ W}$$

(a) Determine the real and reactive powers delivered to the load.

(b) Should we label the terminal ② as B or C?