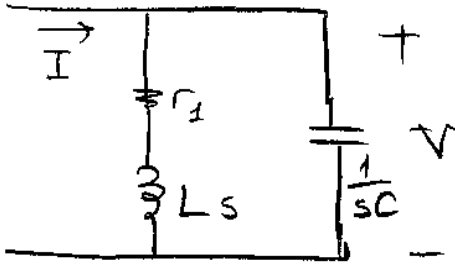


# Effect of Internal Resistance of an Inductor

Parallel LC:



$$H(s) = \frac{V(s)}{I(s)} = Z(s)$$

$$Z(s) = \frac{(r_1 + sL) \cdot \frac{1}{sC}}{r_1 + sL + \frac{1}{sC}} = \frac{r_1 + sL}{s^2 LC + s r_1 C + 1}$$

$$H(s) = Z(s) = \frac{s \cdot \frac{1}{C} + \frac{r_1}{LC}}{s^2 + s \frac{r_1}{L} + \frac{1}{LC}}$$

Define:  $\omega_a \triangleq \frac{1}{\sqrt{LC}}$  : Not the resonance frequency!

$$Q \triangleq \frac{\omega_a}{r_1/L} = \frac{1}{\sqrt{LC}} \cdot L = \sqrt{\frac{L}{C}} \cdot \frac{1}{r_1} \cdot \frac{\sqrt{C}}{\sqrt{C}}$$

Also NOTE:  $\Rightarrow Q = \frac{\sqrt{LC}}{C r_1} = \frac{1}{\omega_a C r_1}$

Resonance Frequency:

At the resonance frequency;  $Z(j\omega)$  and  $Y(j\omega)$  are purely real.

Use  $Z(j\omega)$ :

$$Z(j\omega) = \frac{j\omega \frac{r_1}{L} + \frac{1}{LC}}{-\omega^2 + \frac{1}{LC} + j\omega \frac{r_1}{L}}$$

$$= \frac{(j\omega \frac{r_1}{L} + \frac{1}{LC}) (-\omega^2 + \frac{1}{LC} - j\omega \frac{r_1}{L})}{\underbrace{\left(-\omega^2 + \frac{1}{LC}\right)^2 + \left(\omega \frac{r_1}{L}\right)^2}_{D(\omega): \text{Real}}}$$

Note that, at  $\omega = \omega_0$ ;  $\text{Im}\{Z(j\omega_0)\} = 0$

$$\text{Im}\{Z(j\omega)\} = \left[ \frac{\omega}{c} \left( \frac{1}{LC} - \omega^2 \right) - \frac{\omega r_1}{L} \cdot \frac{r_1}{LC} \right] \cdot \frac{1}{D(\omega)}$$

$$\frac{\omega_0}{c} (\omega_a^2 - \omega_0^2) - \omega_0 \frac{r_1^2}{L} \cdot \omega_a^2 = 0$$

$$\omega_a^2 - \omega_0^2 = \frac{c}{L} r_1^2 \omega_a^2$$

$$\omega_a^2 \left( 1 - \frac{c}{L} r_1^2 \right) = \omega_0^2$$

Recall:  $Q = \sqrt{\frac{L}{C}} \cdot \frac{1}{r_1} \Rightarrow r_1^2 \cdot \frac{C}{L} = \frac{1}{Q^2}$

(3)

$$\Rightarrow \omega_0^2 = \omega_a^2 \left(1 - \frac{1}{Q^2}\right)$$

$$\boxed{\omega_0 = \omega_a \sqrt{1 - \frac{1}{Q^2}}}$$

Resonance  
frequencyUse  $Y(j\omega)$ :

$$Y(j\omega) = j\omega C + \frac{1}{r_1 + j\omega L} = \frac{j\omega C r_1 - \omega^2 L C + 1}{r_1 + j\omega L (r_1 - j\omega L)}$$

$$= \frac{(1 - \omega^2 L C + j\omega r_1 C) (r_1 - j\omega L)}{\underbrace{r_1^2 + (\omega L)^2}_{D(\omega)}}$$

$$\text{Im}\{Y(j\omega)\} = \frac{1}{D(\omega)} \cdot (-\omega L (1 - \omega^2 L C) + \omega r_1 C r_1)$$

$$= \frac{1}{D(\omega)} \cdot (-\omega L + \omega^3 L^2 C + \omega C r_1^2)$$

$$\text{Im}\{Y(j\omega_0)\} = 0$$

$$\Rightarrow \omega_0 (\omega_0^2 L^2 C + C r_1^2 - L) = 0$$

$$\omega_0^2 = \frac{L - C r_1^2}{L^2 C} = \underbrace{\frac{1}{LC}}_{\omega_a^2} - \underbrace{\frac{r_1^2}{L^2}}_{\omega_a^2 / Q^2}$$

$$\Rightarrow \boxed{\omega_0^2 = \omega_a^2 \left(1 - \frac{1}{Q^2}\right)}$$

$$Z(j\omega_0) = \frac{1}{D(\omega)} \cdot \underbrace{\left[ r_1 \omega_a^2 (\omega_a^2 - \omega_0^2) + \omega_0^2 \omega_a^2 \right]}_{r_1 \cdot \omega_a^4}$$

Let us focus on  $D(\omega)$ :


$$\begin{aligned} D(\omega_0) &= (\omega_a^2 - \omega_0^2)^2 + \omega_0^2 \left( \frac{r_1^2}{L^2} \right) \cdot \frac{\omega_a^2}{Q^2} \\ &= \omega_a^4 - 2\omega_a^2\omega_0^2 + \omega_0^4 + \omega_0^2\omega_a^2 \cdot \frac{1}{Q^2} \\ &= \omega_a^4 \left[ 1 - 2\frac{\omega_0^2}{\omega_a^2} + \frac{\omega_0^4}{\omega_a^4} + \frac{\omega_0^2}{\omega_a^2} \cdot \frac{1}{Q^2} \right] \end{aligned}$$

$$\Rightarrow Z(j\omega_0) = \frac{r_1}{1 - 2\left(\frac{\omega_0}{\omega_a}\right)^2 + \left(\frac{\omega_0}{\omega_a}\right)^4 + \frac{1}{Q^2}\left(\frac{\omega_0}{\omega_a}\right)^2}$$

If  $\omega_0 \approx \omega_a$  (High Q,  $Q \geq 10$ )

$$\Rightarrow \boxed{Z(j\omega_0) \approx Q^2 r_1}$$

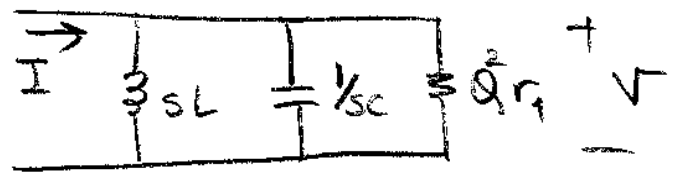$\Rightarrow$  High Q equivalent circuit:



Let us rewrite  $Z(s)$  in terms of  $Q$  and  $\omega_a$ :

$$Z(s) = \frac{\frac{r_1}{LC} + \frac{s}{C}}{s^2 + s \frac{r_1}{L} + \frac{1}{LC}} = \frac{\frac{s}{C} + r_1 \omega_a^2}{s^2 + s \frac{\omega_a}{Q} + \omega_a^2}$$

$$= \frac{\cancel{\omega_a^2} r_1 \left( s \cdot \frac{1}{\omega_a^2 r_1 C} + 1 \right)}{\cancel{\omega_a^2} \left( \frac{s^2}{\omega_a^2} + s \frac{1}{Q \omega_a} + 1 \right)}$$


Recall:  
 $\frac{1}{\omega_a r_1 C} = Q$

$$= \frac{r_1 \left( \frac{s}{\omega_a} \cdot Q + 1 \right)}{\left( \frac{s}{\omega_a} \right)^2 + \left( \frac{s}{\omega_a} \right) \cdot \frac{1}{Q} + 1}$$

$$= Q^2 r_1 \cdot \frac{\frac{1}{Q} \left( \frac{s}{\omega_a} + \frac{1}{Q} \right)}{\left( \frac{s}{\omega_a} \right)^2 + \left( \frac{s}{\omega_a} \right) \cdot \frac{1}{Q} + 1}$$

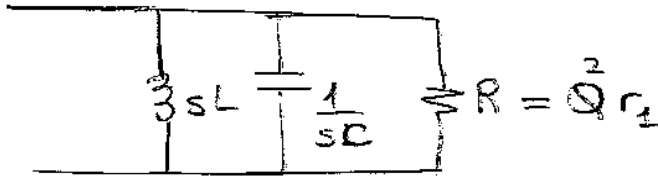(6)

Now, find  $Z_{RLC}(s)$  for the approximate RCL:



$$Z_{RLC}(s) = \frac{1}{\frac{1}{sL} + sC + \frac{1}{R}} = \frac{sLR}{R + s^2RLC + sL}$$

$$Z_{RLC}(s) = \frac{\frac{1}{C} \cdot s}{s^2 + s \left( \frac{1}{RC} \right) + \left( \frac{1}{LC} \right)} \rightarrow \omega_0^2$$

$$2\sigma\omega_0 = \text{BW}$$

$$Q^{\text{new}} = \frac{\omega_0}{\text{BW}} = \omega_0 RC$$

If  $\omega_a \approx \omega_0$ ;  $R \approx Q^2 r_1$  where  $Q = \frac{\omega_a}{r_1/L} = \frac{1}{\omega_a r_1 C}$

$$Q^{\text{new}} = \omega_0 Q^2 r_1 C = \omega_0 \cdot \frac{1}{\omega_a^2 r_1^2 C^2} \cdot r_1 C$$

$$\approx \frac{1}{\omega_a r_1 C} \Rightarrow \boxed{Q^{\text{new}} \approx Q}$$

Also note;

$$Z_{RLC}(s) = \frac{\frac{1}{C} s}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$$

use  $\omega_0 \approx \omega_a$

$$Q = \frac{1}{\omega_a r_1 C} \approx \frac{1}{\omega_0 r_1 C}$$

$$R \approx Q^2 r_1$$

$$= \frac{\frac{1}{C} s}{s^2 + s \frac{1}{Q^2 r_1 C} + \omega_0^2}$$

$$\frac{1}{Q^2 r_1 C} = \frac{\omega_0}{Q}$$

$$= \frac{\frac{1}{C} \cdot s}{\omega_0^2 \left( \frac{s^2}{\omega_0^2} + \frac{s}{\omega_0} \cdot \frac{1}{Q} + 1 \right)}$$

$$\rightarrow \omega_0^2 = \frac{1}{Q^2 r_1^2 C^2}$$

$$= \frac{Q^2 r_1 r_1 C^2 \cdot \frac{1}{C} \cdot s}{\frac{s^2}{\omega_0^2} + \frac{s}{\omega_0} \cdot \frac{1}{Q} + 1}$$

$$r_1 C = \frac{1}{\omega_0 Q}$$

$$Z_{RLC}(s) = \frac{Q^2 r_1 \cdot \frac{1}{Q} \frac{s}{\omega_0}}{\left(\frac{s}{\omega_0}\right)^2 + \frac{1}{Q} \left(\frac{s}{\omega_0}\right) + 1}$$

of the RLC

Compare with the true  $Z(s)$ :

can be neglected for large Q.

$$Z(s) = \frac{Q^2 r_1 \cdot \frac{1}{Q} \left( \frac{s}{\omega_a} + \frac{1}{Q} \right)}{\left(\frac{s}{\omega_a}\right)^2 + \frac{1}{Q} \left(\frac{s}{\omega_a}\right) + 1}$$

If Q is large;  $\omega_0 \approx \omega_a$ ;  $Z_{RLC}(s) \approx Z(s)$

- \* The two circuits have approximately  
 the same  $Q$ ,  
 the same input impedance  
 the same resonance frequencies.

Circuit Interpretation; sketch of  $|Z(j\omega)|$ :

At  $\omega = 0$ ;  $L$  is short;  $C$  is open;


$$|Z(j\omega)| = r_1$$

At  $\omega \rightarrow \infty$ ,  $L$  is open,  $C$  is short;

$$|Z(j\omega)| = 0$$


At  $\omega = \omega_0$  ( $\approx \omega_a$  for large  $Q$ )

$$|Z(j\omega)| \approx Q^2 r_1 \quad \text{where } Q \approx \frac{\omega_0}{r_1/L} = \frac{1}{\omega_0 r_1 C}$$

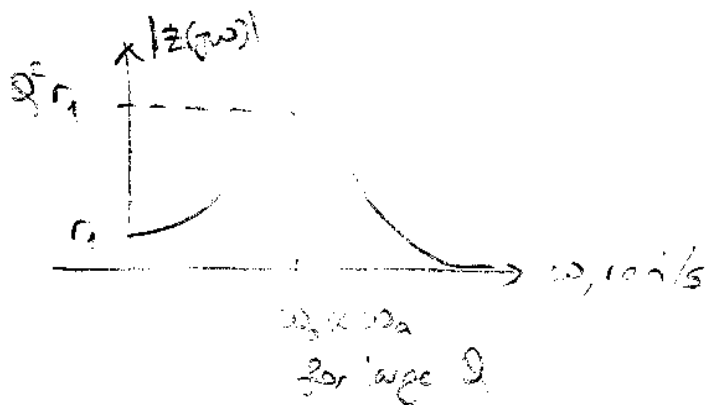



Similarly;

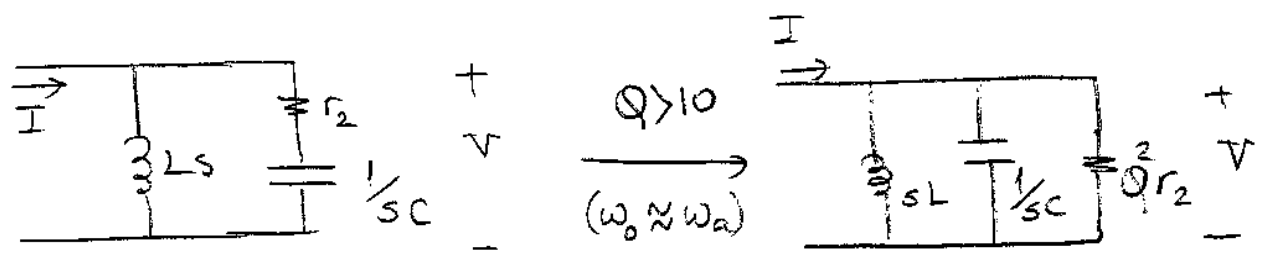

$$Q \triangleq \frac{1}{\omega_a r_2 C} = \frac{\omega_a}{r_2/L} ;$$

$$\omega_a \triangleq \frac{1}{\sqrt{LC}}$$

Show that the resonance frequency is:

$$\omega_0 = \frac{\omega_a}{\sqrt{1 - 1/Q^2}}$$