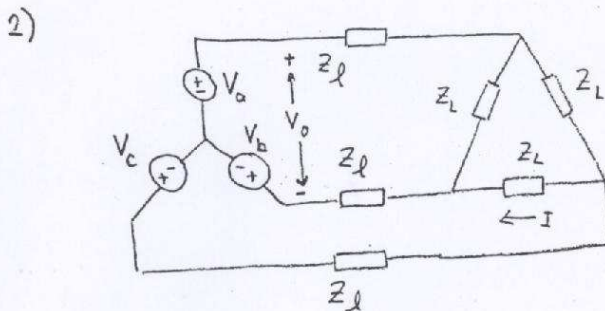


$$V_2 = V_1 \angle -120^\circ, V_3 = V_1 \angle +120^\circ$$

Express  $V_4, V_5, V_6$  in terms of  $V_1$  and  $Z_1, Z_2, Z_3$  in terms of  $Z$ .




$$V_b = V_a \angle -120^\circ, V_c = V_a \angle +120^\circ$$

$$Z_l = 1 + j5 \Omega$$

$$Z_L = 15 + j9 \Omega$$

$$I = 10 \angle 15^\circ \text{ Arms}$$

Find  $V_o$ .

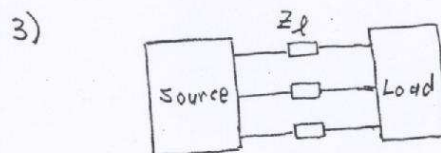

A balanced 3-phase circuit.

$$Z_l = 0.5 + j\frac{2}{3} \Omega$$


$$P_s = 12 \text{ kW}$$

$$\text{Load: } 12 \text{ KVA, } \text{pf}_L = 0.8 \text{ lagging}$$

Find the line voltages at the load and source ends and the complex power supplied by the source.

- 4) In a balanced 3-phase circuit the line impedance is  $1.5 + j2.5 \Omega$ , the total real power lost on the lines is  $1.8 \text{ kW}$ , the total real power delivered to the inductive load is  $10.2 \text{ kW}$ , the line voltage at the source end is  $250\sqrt{3} \text{ Vrms}$ . Find the load power factor and the line voltage at the load end.

5)

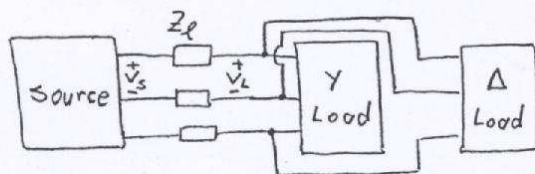

A balanced 3-phase circuit.

$$Z_l = \frac{1+j}{30} \Omega$$


Y load: 15 kVA,  $\text{pf} = 0.8$  lagging

$\Delta$  load:  $Z_L = 1.6 + j1.2 \Omega$

$$V_{\text{Leff}} = 100 \text{ Vrms}$$

Find  $V_{\text{seff}}$  and the complex power supplied by the source.

6)

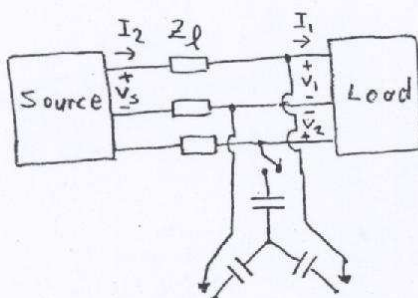

A balanced 3-phase circuit.

Load: 400 kW,  $\text{pf} = \frac{1}{\sqrt{2}}$  lagging


$$V_1 = 400 \angle 30^\circ \text{ Vrms}, V_2 = 400 \angle -30^\circ \text{ Vrms}$$

$$Z_l = 0.07 + j0.16 \Omega$$

(a) The switches are open: Find  $I_1$ ,  $V_{\text{seff}}$ , the complex power supplied by the source and the efficiency.

(b) The switches are closed: The power factor of the load-capacitor bank combination is 0.8 lagging. Find the susceptance of a capacitor,  $I_1$ ,  $I_2$ ,  $V_{\text{seff}}$ , the complex power supplied by the source and the efficiency.

7)

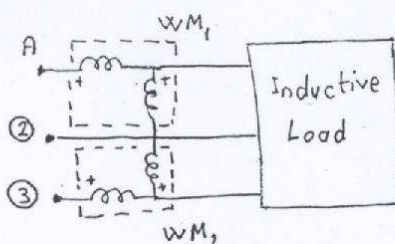

A balanced 3-phase circuit.

The readings of the wattmeters:

$$WM_1: 600 \text{ W}, WM_2: 400 \text{ W}$$

The load power factor:  $\text{pf} > \frac{1}{2}$

Find the real and reactive powers delivered to the load.

Assuming that the phase sequence is A-B-C, should we label the terminal ② as B or C?