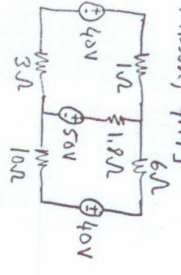



Node - Mesh - Superposition - Source Transformation:

[Nissov, 4.17]



Find the power delivered by the 50V source.

Solution by Node Analysis:

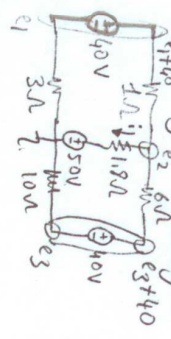

$$\frac{e_1 + 40 - e_2}{3} + \frac{e_1}{1.8} = 0$$

$$\frac{e_2 - e_1 + 10}{1.8} + \frac{e_2 - (e_3 + 10)}{6} = 0$$

$$\frac{e_3 + 40 - e_2}{6} + \frac{e_3}{10} = 0$$


$$\begin{bmatrix} 4 & -3 & 0 \\ -18 & 31 & -3 \\ 0 & -5 & 8 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} 1340 \\ -120 \\ -200 \end{bmatrix}$$

3 eqns, 3 unknowns

$$e_1 = 4.8V ; e_2 = 46.4V ; e_3 = 4V$$

$$i = \frac{(46.4 - 50)}{1.8} = -2A ; P_{50V} = 50(-2) = -100 \text{ Watts}$$

Solution by Mesh Analysis:

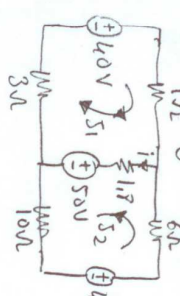

$$-40 + (3 + 1 + 1.8)I_1 + 1.8I_2 + 50 = 0 \quad (1)$$

$$-40 + 1.8I_1 + (6 + 10 + 1.8)I_2 + 50 = 0 \quad (2)$$


$$(1) - (2) : 4I_1 = 16I_2 \rightarrow I_1 = 4I_2$$

$$\text{From (1)} : (5.8)(4I_2) + 1.8I_2 = -10 \rightarrow I_2 = -0.44A$$

$$I_1 = 5I_2 = -2.2A \rightarrow P_{50V} = -100 \text{ Watts}$$

2 eqns 2 unknowns

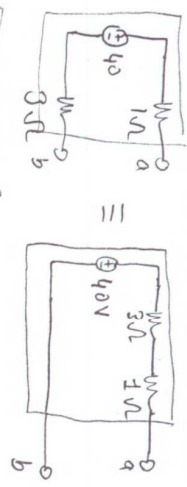Solution by circuit simplification: (Equivalent circuits)






Both circuits have the same (i.e) characteristics. (Thermin Equivalent or exchanging series branches)

Since we are only interested in "i", we can substitute the rest of branches and their nodes with simpler but equivalent circuits.


Node Equation: $\frac{e - 50}{1.8} + \frac{e - 40}{4} + \frac{e - 40}{16} = 0 \rightarrow \frac{8(e - 50)}{9} + \frac{8(e - 40)}{16} = 0$

1 equation, 1 unknown $\rightarrow i = \frac{46.4 - 50}{1.8} = -2A ; P_{50V} = -100 \text{ Watts}$

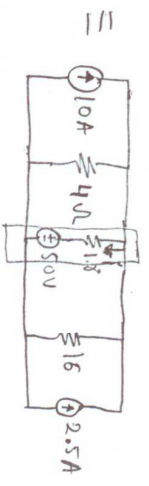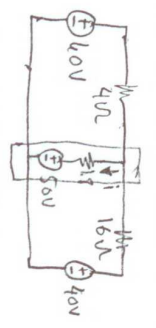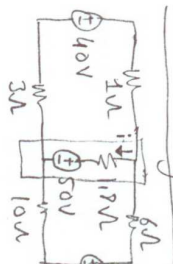Solution by Source Transformation and Superposition:



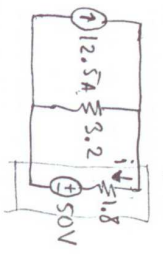Direct solution
No unknowns,
No equations



By superposition $i = (12.5) \frac{3.2}{5} - \frac{50}{5} = 8 - 10 = -2A ; P_{50V} = -100 \text{ Watts}$

current division $\frac{50}{R}$