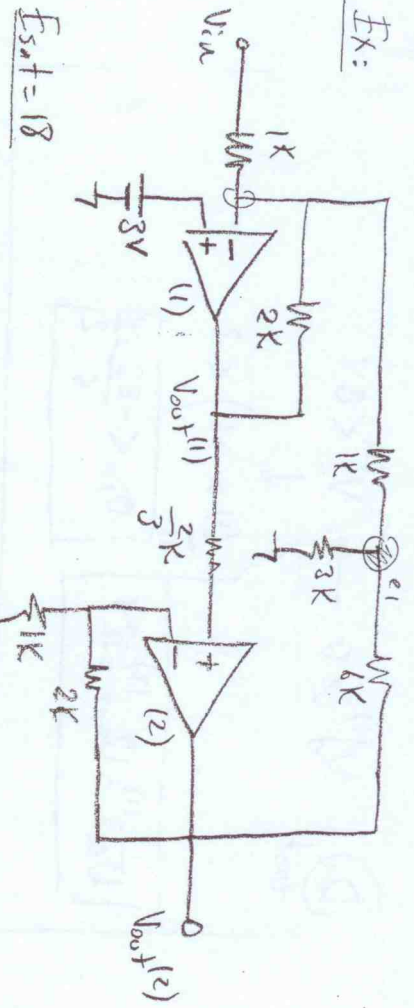


Op-Amp Example:

Ex:



Equations valid for all op-amp regions:

$$V_{-}^{(1)} - V_{in} + \frac{V_{-}^{(1)} - V_{out}^{(1)}}{2} + \frac{V_{-}^{(1)} - e_1}{1} = 0 \rightarrow 5V_{-}^{(1)} = 2V_{in} + V_{out}^{(1)} + 2e_1 \quad (1)$$

$$\frac{e_1 - V_{-}^{(1)}}{1} + \frac{e_1 + e_1 - V_{out}^{(2)}}{6} = 0 \rightarrow 9e_1 = 6V_{-}^{(1)} + V_{out}^{(2)} \quad (2)$$

Replace e_1 in (1):

$$\left[5 - \frac{4}{3} \right] V_{-}^{(1)} = 2V_{in} + V_{out}^{(1)} + \frac{2V_{out}^{(2)}}{9} \quad (I)$$

$$V_{+}^{(2)} = V_{out}^{(1)} \quad (II)$$

$$V_{-}^{(2)} = \frac{V_{out}^{(2)}}{3} \quad (III)$$

Op-Amp (I) & (II) } $V_{-}^{(1)} = V_{+}^{(1)} = 3V$
 Op-Amp (I) & (III) } $V_{-}^{(2)} = V_{+}^{(2)} \Rightarrow \frac{V_{out}^{(2)}}{3} = V_{out}^{(1)}$

Insert in (I):

$$11 = 2V_{in} + V_{out}^{(1)} + \frac{2}{9} \frac{V_{out}^{(2)}}{3V_{out}^{(1)}}$$

$$V_{out}^{(1)} = \frac{3}{5} (11 - 2V_{in})$$

$$V_{out}^{(2)} = \frac{9}{5} (11 - 2V_{in})$$

$|V_{out}^{(1)}| < 18 \rightarrow |2V_{in} - 11| < 30 \rightarrow -\frac{19}{2} < V_{in} < \frac{41}{2}$

$|V_{out}^{(2)}| < 18 \rightarrow |2V_{in} - 11| < 10 \rightarrow \frac{1}{2} < V_{in} < \frac{21}{2}$

$|V_{out}^{(1)}| < 18$ and $|V_{out}^{(2)}| < 18 \rightarrow \frac{1}{2} < V_{in} < \frac{21}{2}$

Op-Amp (I) & (II) } $V_{-}^{(1)} = V_{+}^{(1)} = 3V$; $V_{out}^{(2)} = 18V$
 Op-Amp (I) & (III) } $V_{out}^{(1)} > \frac{V_{out}^{(2)}}{3} = 6$

From (I): $11 = 2V_{in} + V_{out}^{(1)} + 4$

$$V_{out}^{(1)} = 7 - 2V_{in}$$

$|V_{out}^{(1)}| < 18 \rightarrow -11 < V_{in} < \frac{25}{2}$
 $V_{out}^{(1)} > 0 \rightarrow V_{out}^{(1)} > 6 \rightarrow V_{in} < \frac{1}{2}$
 $V_{out}^{(2)} > 0 \rightarrow \frac{1}{2} < V_{in} < \frac{1}{2}$

C) Op-Amp (I) (II)
 $\frac{d_{in} + S_{at}}{-S_{at}}$

$V_{out}^{(1)} = V_{in}^{(1)} = 3V$, $V_{out}^{(2)} = -18V$
 $V_{out} = \frac{V_{out}^{(2)}}{3} = -6$

From (I): $11 = 2V_{in} + V_{out}^{(1)} - 4$


$V_{out}^{(1)} = 15 - 2V_{in}$

$V_{out}^{(1)} < 18 \rightarrow -3 < V_{in} < \frac{33}{2}$

$V_{out}^{(2)} < 0 \rightarrow V_{out}^{(1)} < -6 \rightarrow V_{in} > \frac{21}{2}$

Both satisfied when

$\frac{21}{2} < V_{in} < \frac{33}{2}$

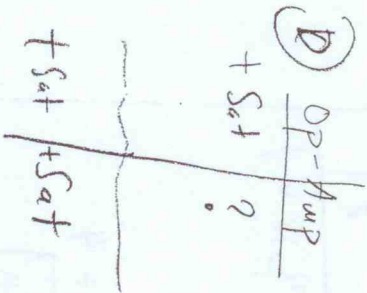

$V_{out}^{(1)} = 18V$

$V_{out}^{(2)} = \frac{V_{out}^{(1)}}{3}$ has the maximum value of 6V

$V_{out}^{(2)} = 18 - V_{out}^{(1)} > 6 \rightarrow V_{out}^{(1)} > 12$
 (Op-Amp always in $+S_{at}$)

From (I): $\frac{11}{3} V_{out}^{(1)} = 2V_{in} + 18 + 4 \rightarrow V_{in}^{(1)} = \frac{6}{11} V_{in} + 6$

D) $\frac{+S_{at}}{+S_{at}}$
 $V_{out}^{(1)} > 0 \rightarrow V_{in}^{(1)} < 3V$

$V_{out}^{(1)} = V_{out}^{(2)} = 18V$

$\frac{6V_{in} + 6}{11} < 3$
 $V_{in} < \frac{-33}{6} = -\frac{11}{2}$

E) Op-Amp
 $\frac{(1) - S_{at}}{(2) - S_{at}}$

$V_{out}^{(1)} = V_{out}^{(2)} = -18V$
 $V_{in}^{(1)} > 3V$

$V_{in}^{(1)} = \frac{6}{11} V_{in} - 6$

$V_{in}^{(1)} > 3 \rightarrow \frac{6}{11} V_{in} - 6 > 3$

$V_{out}^{(1)} = V_{out}^{(2)} = -18V$

$V_{in} > \frac{33}{2}$

