
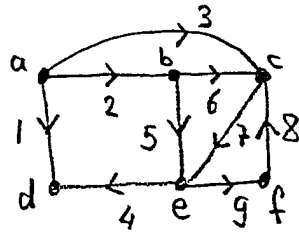


1)

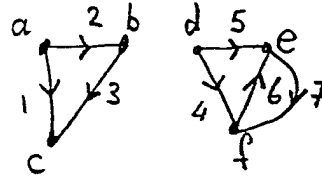

(a)



(b)


Given the circuit graph:

- (i) Write all the current and voltage equations.
  - (ii) Write the incidence and mesh matrices.
  - (iii) Pick a reference node (reference nodes) and write the reduced incidence matrix.
  - (iv) Pick a tree and write the fundamental loop and fundamental cutset matrices.
  - (v) Using the reduced incidence (fundamental cutset) matrix obtain a set of independent current equations.
  - (vi) Using the mesh (fundamental loop) matrix obtain a set of independent voltage equations.
  - (vii) Express the branch voltages in terms of the node (cutset) voltages.
  - (viii) Express the branch currents in terms of the mesh (loop) currents.
  - (ix) Assign arbitrary currents (voltages) to the branches so as to satisfy the KCL (KVL).
- Verify the Tellegen's theorem.

2) Obtain the dual of the graph of Problem 1-a.

Repeat Problem 1 for this circuit graph.

3) Given the circuit graph:

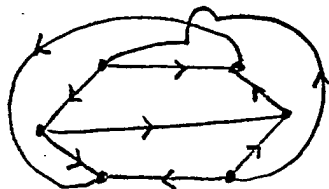

Assign arbitrary currents (voltages) to the branches so as to satisfy the KCL (KVL).

Verify the Tellegen's theorem.

4) Given the circuit matrix. Draw the circuit graph.

(a)

$$A = \begin{bmatrix} 1 & 1 & 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 & -1 & 0 \\ -1 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

(b)

$$M = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & -1 & -1 \end{bmatrix}$$

(c)

$$B = \begin{bmatrix} 0 & -1 & 0 & -1 & 1 & 0 & 0 & 0 \\ 1 & -1 & 0 & -1 & 0 & 1 & 0 & 0 \\ 0 & -1 & -1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

(d)

$$Q = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$$

5) Classify the following resistors as linear or nonlinear; time-invariant or time-varying; bilateral or nonbilateral; passive or active; voltage-controlled, or current-controlled, or both voltage and current controlled or neither voltage nor current controlled.

(a)  $2v - 3i = 0$

(b)  $2v - 3i = 4$

(c)  $2v + 3i = 0$

(d)  $i = (3 \cdot \cos t)v$

(e)  $v = [3 + 2 \cos(4t + 30^\circ)]i$

(f)  $v = [2 + \cos(3t)]i + 4$


(g)  $i = 4e^{-v/6}$

(h)  $i = 4[e^{v/6} - 1]$







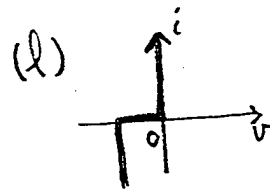
(i)  $i = 3v^4$

(j)  $v = i^5$

(k)  $i = \begin{cases} v^2, & v \geq 0 \\ 0, & v < 0 \end{cases}$






6) Obtain the port characteristics.

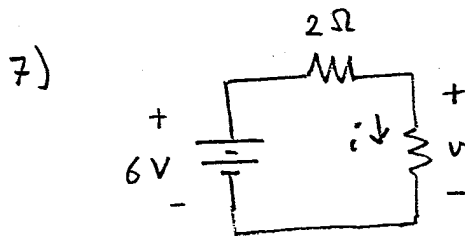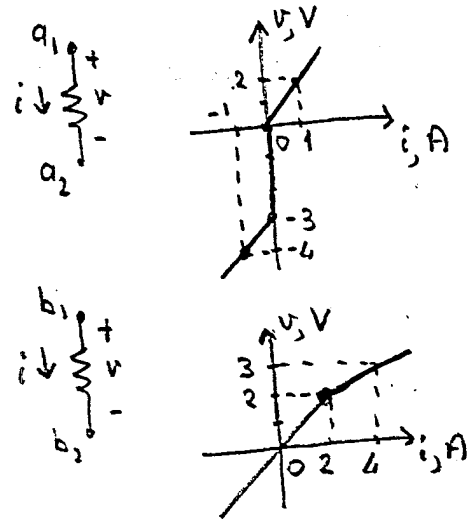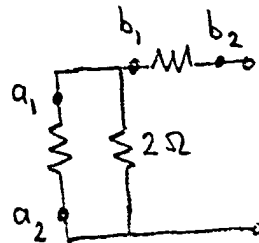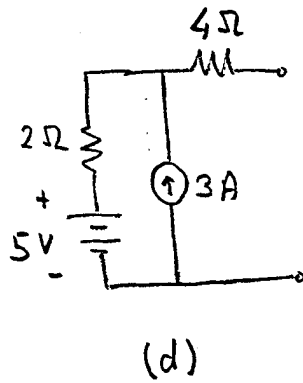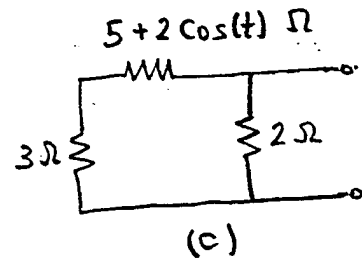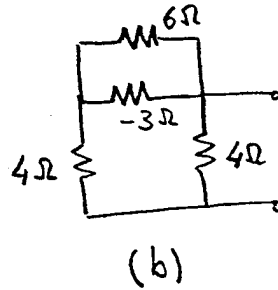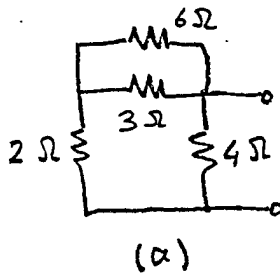






Classify the circuit and find  $v$  and  $i$ .

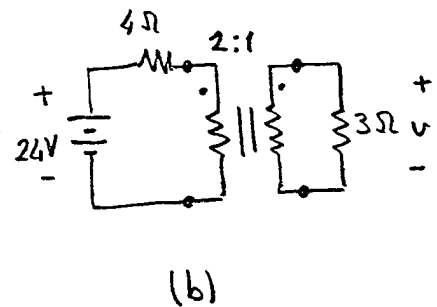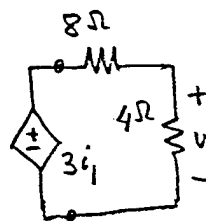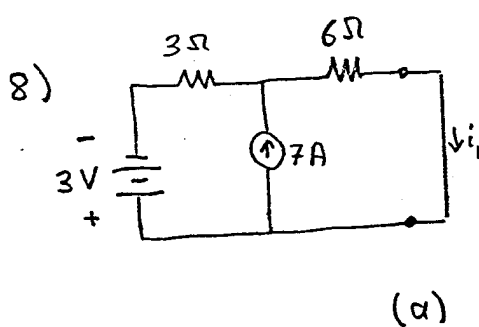(a)  $v = 4i$ , (b)  $v = -4i$ , (c)  $v = [2 + \cos(3t)]i$ , (d)  $i = \begin{cases} \frac{1}{2}v^2, & v \geq 0 \\ 0, & v < 0 \end{cases}$






Find  $v$ . Compute the instantaneous powers delivered to (supplied by) the elements.

9)

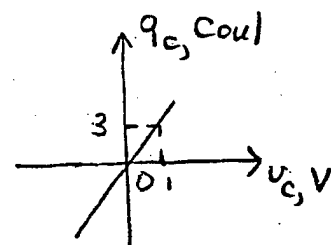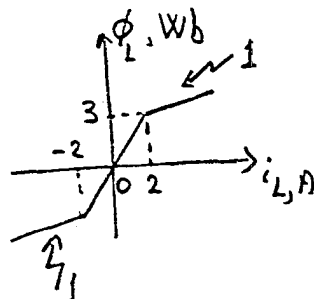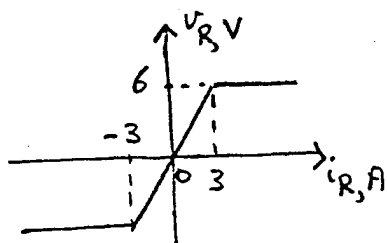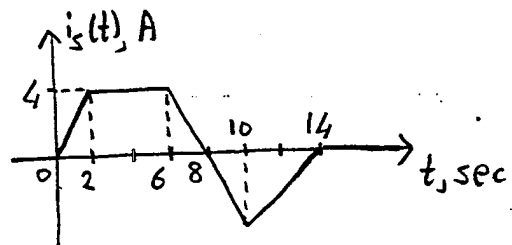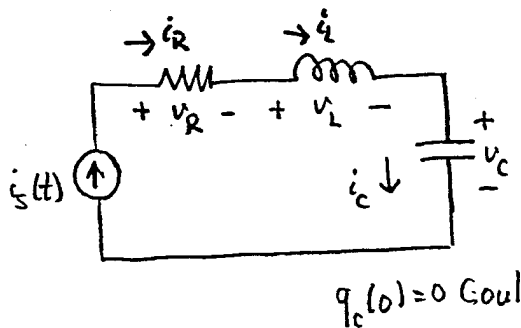

Sketch  $v_R(t)$ ,  $v_L(t)$  and  $v_C(t)$ .


10)

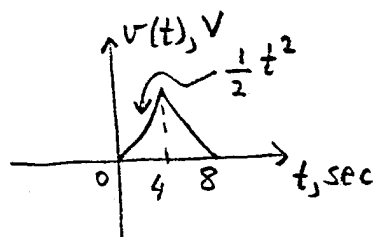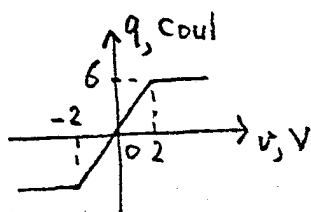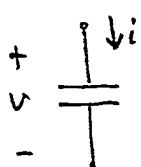

(a) Sketch the current waveform,  $i(t)$ .

(b) Compute the stored energies at  $t = 6 \text{ sec}$  and  $t = 7.5 \text{ sec}$ .

11)

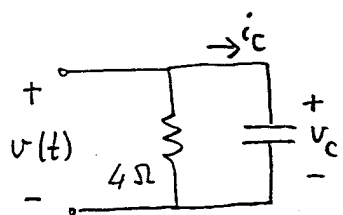


$$v_C = 2q_C^{1/3}$$


$$v(t) = 2t + 4 \text{ V}$$

Compute the energy delivered to the one-port on the interval  $[2 \text{ sec}, 3 \text{ sec}]$ .


12)

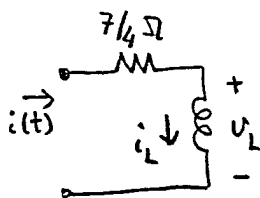


$$\phi_L = (2i_L)^{1/3}$$

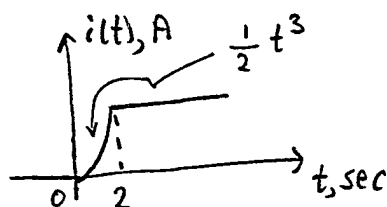


Compute the energy delivered to the one-port on the interval  $(-\infty, 3 \text{ sec}]$ .

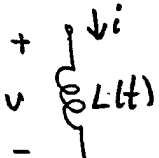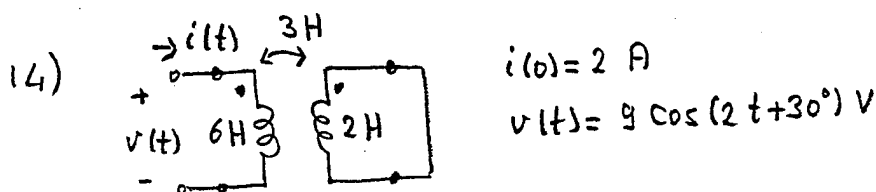13)   $L(t) = 2 + \cos(3t) \text{ H}$   
 $i(t) = 3e^{2t} \text{ A}$

Find  $v(t)$ . Compute the (electrical) energy delivered to the inductor on the interval  $[2 \text{ sec}, 3 \text{ sec}]$ .



Find  $i(t)$  for  $t \geq 0$ .

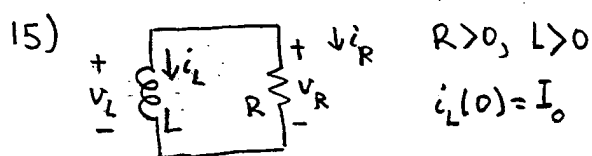

(a) Obtain the differential equation satisfied by  $i_L(t)$ .

(b) Solve this equation and find  $i_L(t)$  for  $t \geq 0$ .


(c) Find  $v_R(t), i_R(t), v_L(t)$  for  $t \geq 0$ .

(d) Compute the energy delivered to the resistor on the interval  $[0, T]$ .


Compute the energies stored in the inductor at  $t=0$  and  $t=T$ .

Comment.

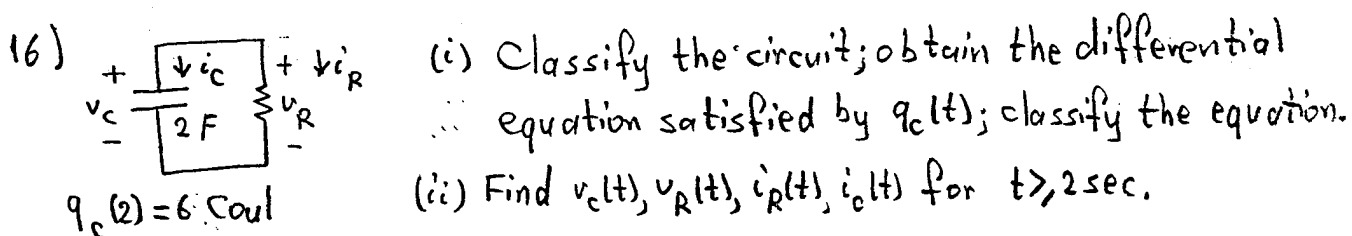Hint: The solution to the equation  $\frac{dx(t)}{dt} + ax(t) = 0$  subject to the initial constraint  $x(t_0) = X_0$  is  $x(t) = X_0 e^{-a(t-t_0)}$ .



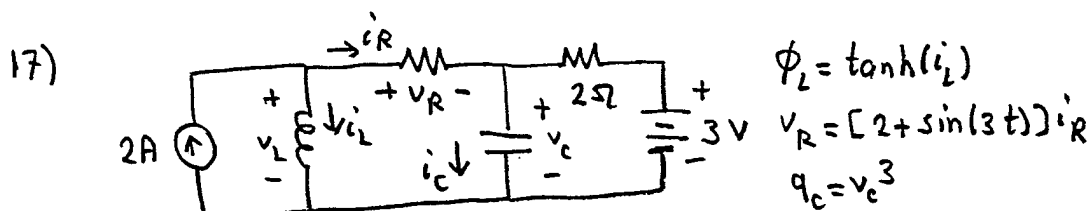(a)  $v_R = 3 i_R$ , (b)  $v_R = -3 i_R$ , (c)  $v_R = i_R^{1/3}$ , (d)  $i_R = [2 + \cos(t)] v_R$



Obtain the dual circuit.