
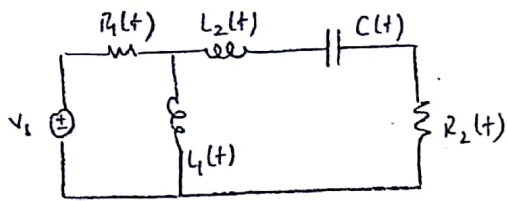


MODELING CIRCUITS WITH LTV / NONLINEAR ELEMENTS

Example (time-varying elements)

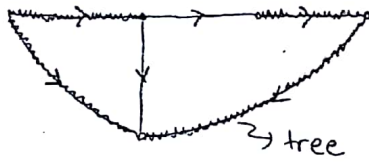

⇓



$$\Rightarrow \text{KCL: } C \dot{v}_C + \dot{C} v_C = i_{L_2}$$

$$\text{KVL: } L_1 \dot{i}_{L_1} + \dot{L}_1 i_{L_1} - v_s + R_1 (i_{L_1} + i_{L_2}) = 0$$

$$\text{KVL: } L_2 \dot{i}_{L_2} + \dot{L}_2 i_{L_2} + v_C + R_2 i_{L_2} - v_s + R_1 (i_{L_1} + i_{L_2}) = 0$$

$$\Rightarrow \dot{v}_C = - \frac{\dot{C}(t)}{C(t)} v_C + \frac{1}{C(t)} i_{L_2}$$

$$\dot{i}_{L_1} = - \frac{R_1(t) + \dot{L}_1(t)}{L_1(t)} i_{L_1} - \frac{R_1(t)}{L_1(t)} i_{L_2} + \frac{1}{L_1(t)} v_s$$

$$\dot{i}_{L_2} = - \frac{1}{L_2(t)} v_C - \frac{R_1(t)}{L_2(t)} i_{L_1} - \frac{R_1(t) + R_2(t) + \dot{L}_2(t)}{L_2(t)} i_{L_2} + \frac{1}{L_2(t)} v_s$$


Hence,

$$\begin{bmatrix} \dot{v}_C \\ \dot{i}_{L_1} \\ \dot{i}_{L_2} \end{bmatrix} = \begin{bmatrix} -\frac{\dot{C}(t)}{C(t)} & 0 & \frac{1}{C(t)} \\ 0 & -\frac{R_1(t) + \dot{L}_1(t)}{L_1(t)} & -\frac{R_1(t)}{L_1(t)} \\ -\frac{1}{L_2(t)} & -\frac{R_1(t)}{L_2(t)} & -\frac{R_1(t) + R_2(t) + \dot{L}_2(t)}{L_2(t)} \end{bmatrix} \begin{bmatrix} v_C \\ i_{L_1} \\ i_{L_2} \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L_1(t)} \\ \frac{1}{L_2(t)} \end{bmatrix} v_s$$

In general, LTV state equation reads

$$\boxed{\dot{x}(t) = A(t)x(t) + \delta(t)w(t)}$$

example (nonlinear elements)

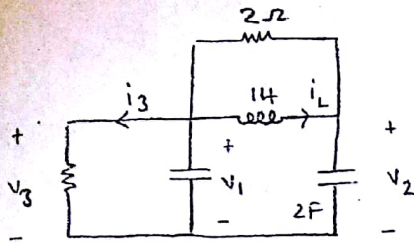

$i_3 = \tanh(v_3)$, nonlinear resistor

$v_1 = 2(q_1 - \frac{1}{10} q_1^3)$, nonlinear capacitor

For a nonlinear capacitor (inductor) choose charge (flux) as the state variable. Let our state be $x = [q_1, v_2, i_L]^T$

$$\begin{aligned} \dot{q}_1 &= -i_3 - i_L - \frac{v_1 - v_2}{2} = -\tanh(v_3) - i_L - \frac{1}{2} v_1 - \frac{1}{2} v_2 \\ &= -\tanh\left\{2q_1 - \frac{1}{5} q_1^3\right\} - i_L - q_1 + \frac{1}{10} q_1^3 - \frac{1}{2} v_2 \quad (1) \end{aligned}$$

$$\dot{v}_2 = \frac{1}{2} \left\{ i_L + \frac{v_1 - v_2}{2} \right\} = \frac{1}{2} i_L + \frac{1}{4} v_1 - \frac{1}{4} v_2 = \frac{1}{2} i_L + \frac{1}{2} \left(q_1 - \frac{1}{10} q_1^3 \right) - \frac{1}{4} v_2 \quad (2)$$

$$\dot{i}_L = v_1 - v_2 = 2q_1 - \frac{1}{5} q_1^3 - v_2 \quad (3)$$

$$(1), (2), (3) \Rightarrow \begin{bmatrix} \dot{q}_1 \\ \dot{v}_2 \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} -\tanh\left(2q_1 - \frac{1}{5} q_1^3\right) - q_1 + \frac{1}{10} q_1^3 - \frac{1}{2} v_2 - i_L \\ \frac{1}{2} q_1 - \frac{1}{20} q_1^3 - \frac{1}{4} v_2 + \frac{1}{2} i_L \\ 2q_1 - \frac{1}{5} q_1^3 - v_2 \end{bmatrix}$$

In general, nonlinear state equation reads $\dot{x} = f(x, u)$

(In our case, we didn't have any input and had $\dot{x} = f(x)$ with $f: \mathbb{R}^3 \rightarrow \mathbb{R}^3$)