
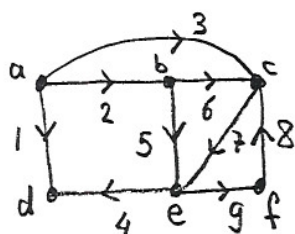


1)

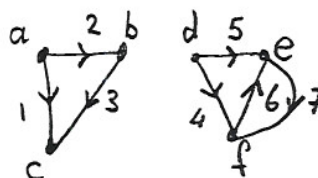

(a)



(b)


Given the circuit graph:

- (i) Write all the current and voltage equations.
 - (ii) Write the incidence and mesh matrices.
 - (iii) Pick a reference node (reference nodes) and write the reduced incidence matrix.
 - (iv) Pick a tree and write the fundamental loop and fundamental cutset matrices.
 - (v) Using the reduced incidence (fundamental cutset) matrix obtain a set of independent current equations.
 - (vi) Using the mesh (fundamental loop) matrix obtain a set of independent voltage equations.
 - (vii) Express the branch voltages in terms of the node (cutset) voltages.
 - (viii) Express the branch currents in terms of the mesh (loop) currents.
 - (ix) Assign arbitrary currents (voltages) to the branches so as to satisfy the KCL (KVL).
- Verify the Tellegen's theorem.

2) Obtain the dual of the graph of Problem 1-a.

Repeat Problem 1 for this circuit graph.

3) Given the circuit graph:

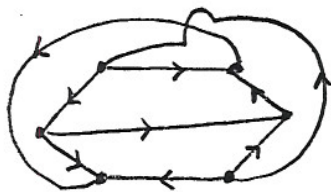

Assign arbitrary currents (voltages) to the branches so as to satisfy the KCL (KVL).

Verify the Tellegen's theorem.

4) Given the circuit matrix. Draw the circuit graph.

(a)
$$A = \begin{bmatrix} 1 & 1 & 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 & -1 & 0 \\ -1 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

(b)
$$M = \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & -1 & -1 \end{bmatrix}$$

(c)
$$B = \begin{bmatrix} 0 & -1 & 0 & -1 & 1 & 0 & 0 & 0 \\ 1 & -1 & 0 & -1 & 0 & 1 & 0 & 0 \\ 0 & -1 & -1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

(d)
$$Q = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$$

5) Classify the following resistors as linear or nonlinear; time-invariant or time-varying; bilateral or nonbilateral; passive or active; voltage-controlled, or current-controlled, or both voltage and current controlled or neither voltage nor current controlled.

(a) $2v - 3i = 0$

(b) $2v - 3i = 4$

(c) $2v + 3i = 0$

(d) $i = (3 \cdot \cos t)v$

(e) $v = [3 + 2 \cos(4t + 30^\circ)]i$

(f) $v = [2 + \cos(3t)]i + 4$


(g) $i = 4e^{-v/6}$

(h) $i = 4[e^{v/6} - 1]$







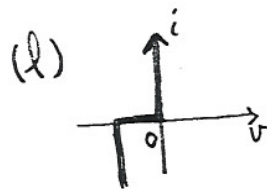
(i) $i = 3v^4$

(j) $v = i^5$

(k) $i = \begin{cases} v^2, & v \geq 0 \\ 0, & v < 0 \end{cases}$






6) Obtain the port characteristics.

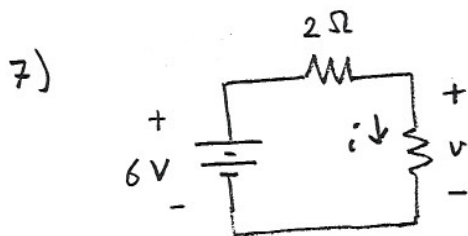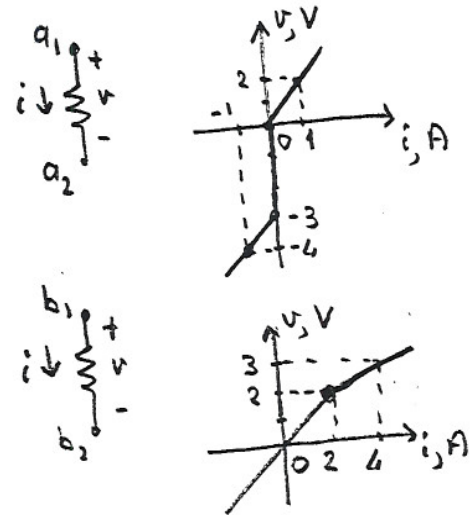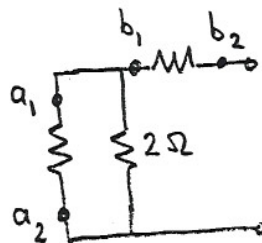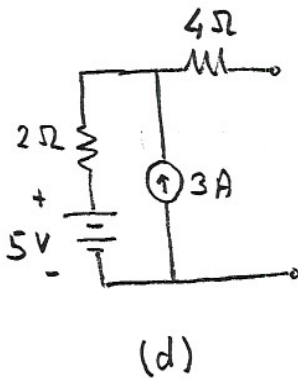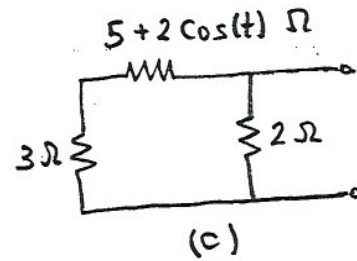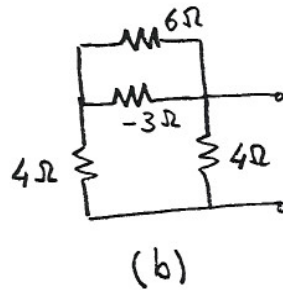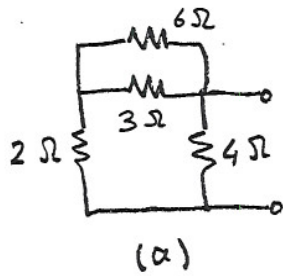


Classify the circuit and find v and i .

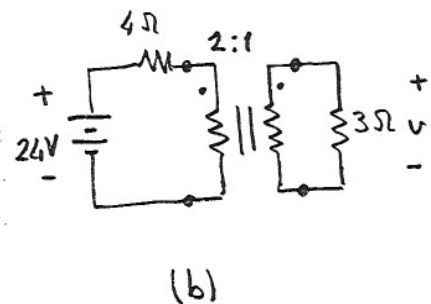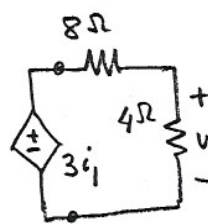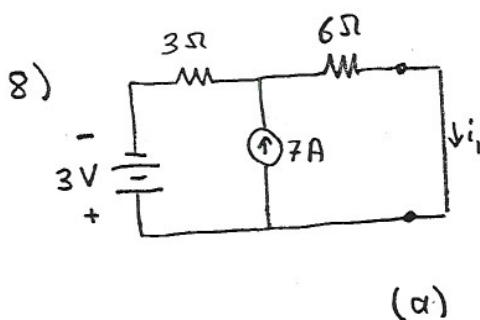
(a) $v = 4i$, (b) $v = -4i$, (c) $v = [2 + \cos(3t)]i$, (d) $i = \begin{cases} \frac{1}{2}v^2, & v \geq 0 \\ 0, & v < 0 \end{cases}$



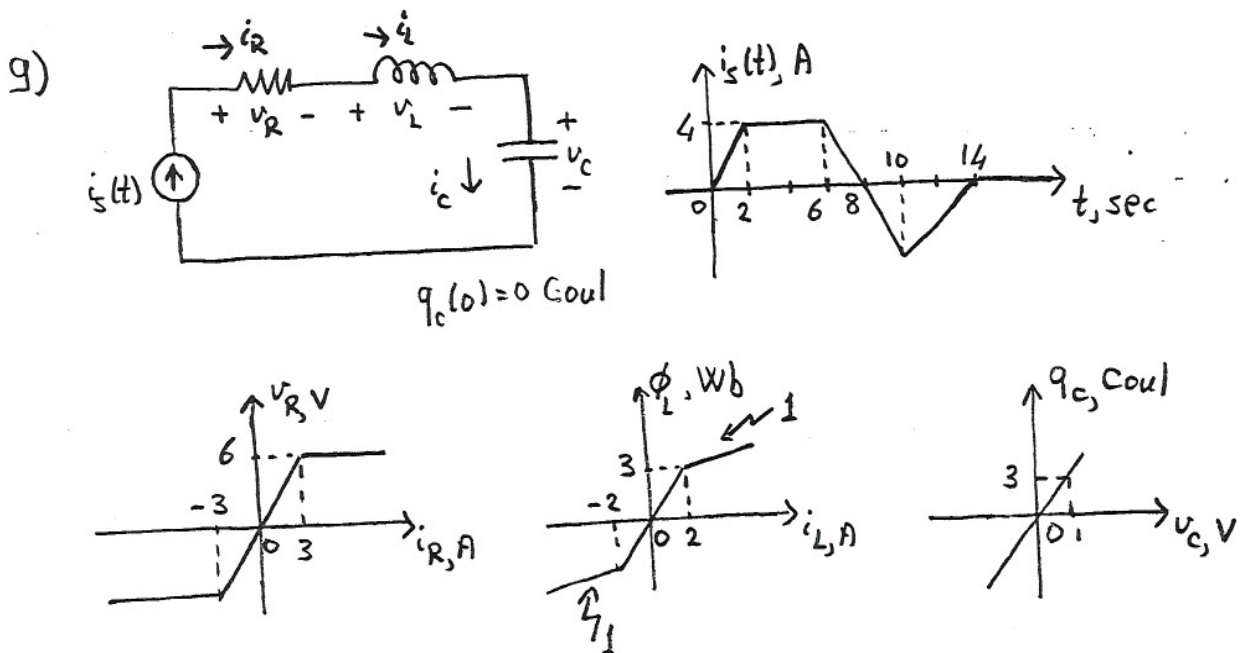Find v . Compute the instantaneous powers delivered to (supplied by) the elements.




Sketch $v_R(t)$, $v_L(t)$ and $v_C(t)$.

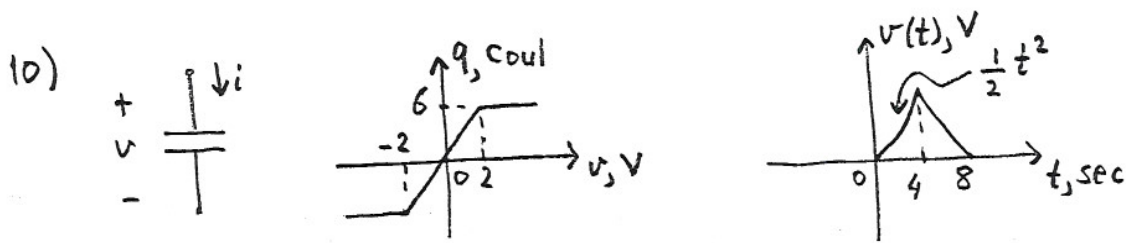


(a) Sketch the current waveform, $i(t)$.

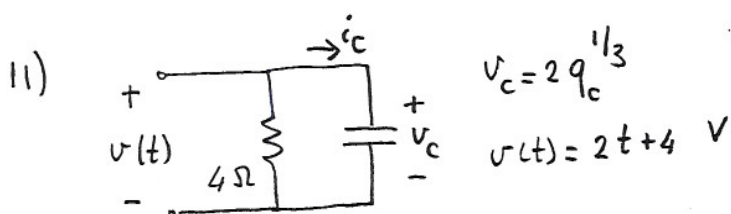
(b) Compute the stored energies at $t = 6$ sec and $t = 7.5$ sec.



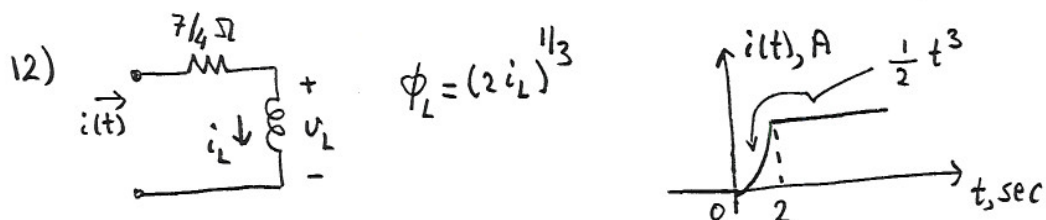
Compute the energy delivered to the one-port on the interval $[2 \text{ sec}, 3 \text{ sec}]$.




Compute the energy delivered to the one-port on the interval $(-\infty, 3 \text{ sec}]$.

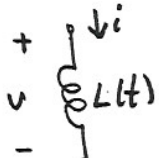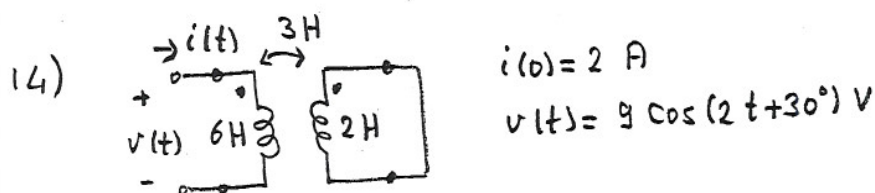13)  $L(t) = 2 + \cos(3t) \text{ H}$
 $i(t) = 3e^{2t} \text{ A}$

Find $v(t)$. Compute the (electrical) energy delivered to the inductor on the interval $[2 \text{ sec}, 3 \text{ sec}]$.



Find $i(t)$ for $t \geq 0$.

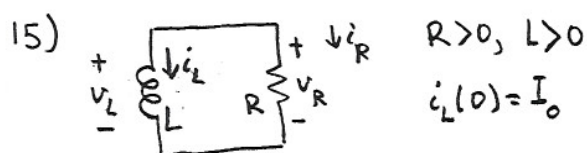

(a) Obtain the differential equation satisfied by $i_L(t)$.

(b) Solve this equation and find $i_L(t)$ for $t \geq 0$.


(c) Find $v_R(t), i_R(t), v_L(t)$ for $t \geq 0$.

(d) Compute the energy delivered to the resistor on the interval $[0, T]$.


Compute the energies stored in the inductor at $t=0$ and $t=T$.

Comment.

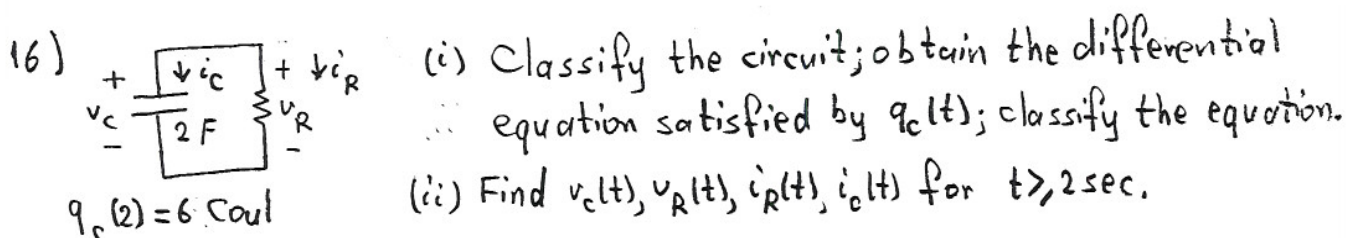Hint: The solution to the equation $\frac{dx(t)}{dt} + ax(t) = 0$ subject to the initial constraint $x(t_0) = X_0$ is $x(t) = X_0 e^{-a(t-t_0)}$.



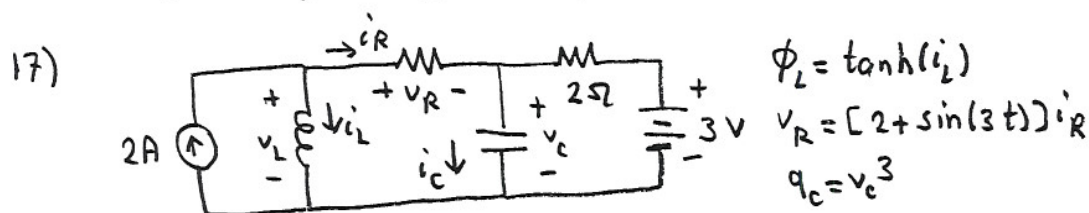(a) $v_R = 3 i_R$, (b) $v_R = -3 i_R$, (c) $v_R = i_R^{1/3}$, (d) $i_R = [2 + \cos(t)] v_R$



Obtain the dual circuit.