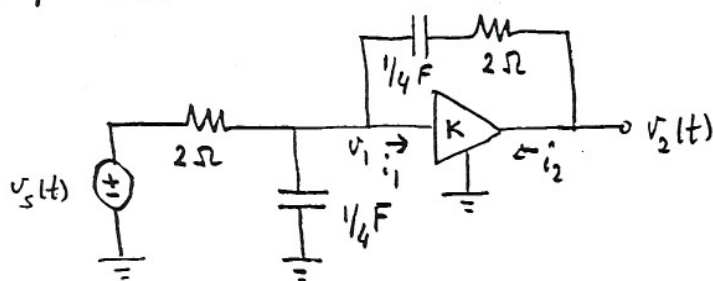


1)




$$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ K & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

$$K > 1$$

$$v_s(t) = V_m \cos(\omega t + \theta_s)$$

- Find the particular solution when $\omega = 3$ rad/sec.
- Find the homogeneous solution for (i) $K=2$, (ii) $K=3$, (iii) $K=4$, (iv) $K=5$, (v) $K=6$.
- For each K value above discuss whether the steady-state is well defined or not. In case the steady-state well defined, find the steady-state solution.
- Find the particular solution when $\omega = 2$ rad/sec and $K=2$. Discuss the existence of the steady-state solution.

2)

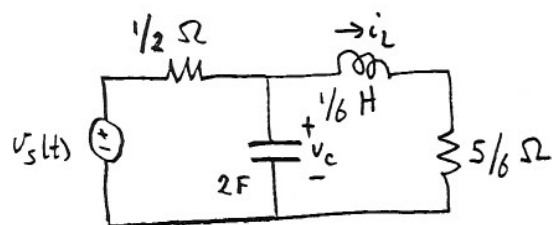


$$v_s(t) = 2 + 4 \cos(2t + 60^\circ) + \sin(3t) \text{ V}$$

The circuit is in the steady-state.

(a) Find $v_c(t)$ and $i_L(t)$.

(b) Compute the average powers delivered to the resistors, the average power supplied by the source, the average stored energies in the capacitor and in the inductor.


3)

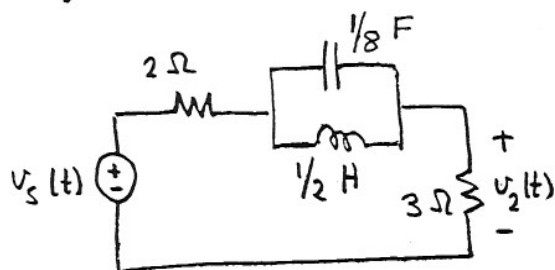

$$v_s(t) = 10 + 6 \cos(t + 15^\circ) + 12 \cos(4t - 28^\circ) + 3 \cos(6t + 10^\circ) \text{ V}$$


The circuit is in the steady-state

Find $v_2(t)$.

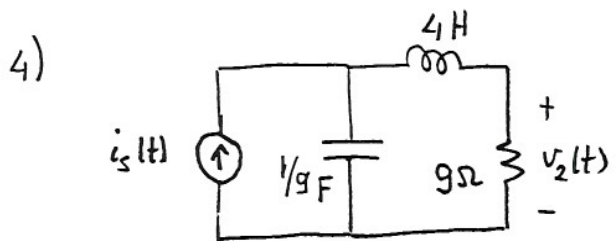

$$v_2(t) = 18 \cos(3t + 60^\circ) \text{ V}$$

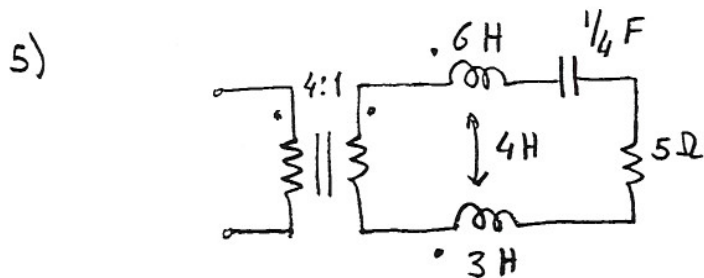
- (a) Find $i_s(t)$.
 (b) Sketch the phasor diagram.



The one-port is in the SSS at the frequency ω rad/sec.


Find the input impedance $Z(j\omega)$.

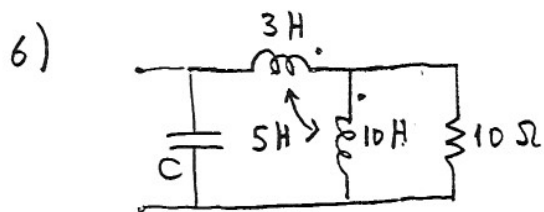For which values of ω is this one-port resistive? capacitive? inductive?



The one-port is in the SSS at the frequency 2 rad/sec.

- (a) Find the input admittance $Y = G + jB$ in terms of C .
 (b) Define $\gamma \triangleq G/|Y|$. Determine the value of C such that
 (i) $\gamma = 1$, (ii) $\gamma = 0.8, B > 0$, (iii) $\gamma = 0.8, B < 0$.

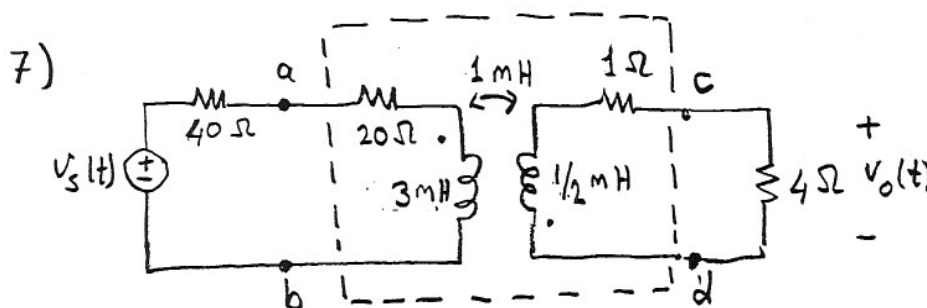


$$v_s(t) = 20 \cos(4 \times 10^3 t) \text{ V}$$


The circuit is in the SSS.

- (a) Transform the circuit to the phasor domain.
 (b) Obtain the chain parameters of the indicated two-port.
 (c) Using the chain parameters find the Thevenin equivalent as seen to the left of the terminal pair c-d.
 (d) Find $v_o(t)$.

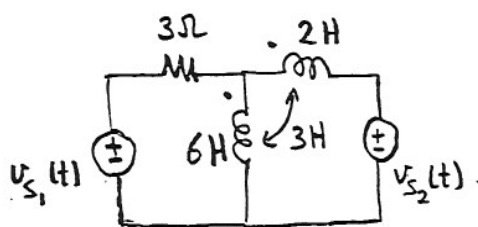
- 8) The circuit is in the steady-state. Compute the average power delivered to the resistor and the average stored energy in the coupled inductor.


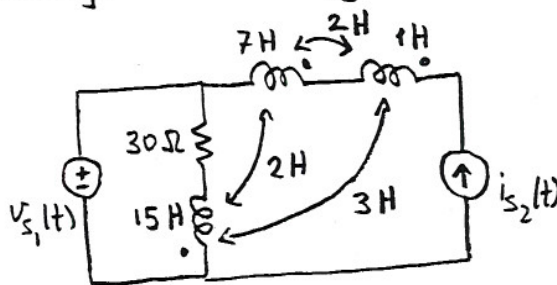
$$\begin{aligned} v_{s1}(t) &= 6 \cos(2t) \text{ V} \\ v_{s2}(t) &= 10 \sin(t + 30^\circ) \text{ V} \end{aligned} \quad (a)$$



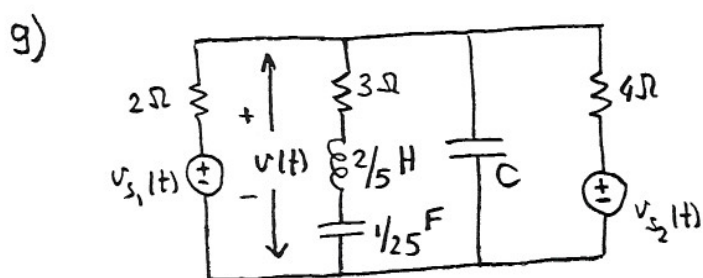
$$\begin{aligned} v_{s1}(t) &= 30 \sin(2t) \text{ V} \\ i_{s2}(t) &= \frac{\sqrt{13}}{6} \cos(3t - 15^\circ) \text{ A} \end{aligned} \quad (b)$$



$$\begin{aligned} v_{s1}(t) &= V_{m1} \cos(5t + \theta_1) \text{ V} \\ v_{s2}(t) &= V_{m2} \cos(12.5t + \theta_2) \text{ V} \\ v(t) &= \sqrt{2} [60 \cos(5t) + 90 \cos(12.5t)] \text{ V} \end{aligned}$$

(a) Compute $P_{3\Omega \text{ avg}}$.

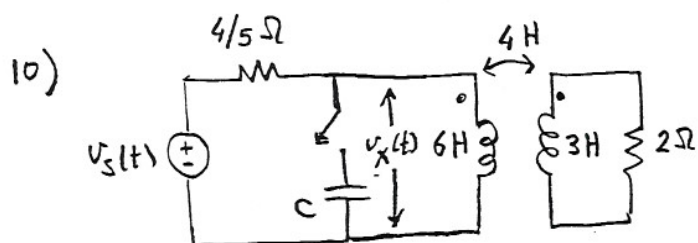
(b) The average power supplied by the left source is 2 kW. Compute $P_{2\Omega \text{ avg}}$.



$$\begin{aligned} v_{s1}(t) &= V_m \cos(2t + \theta_s) \text{ V} \\ \text{The circuit is in the SSS.} \end{aligned}$$

(a) The switch is open, $V_{x \text{ eff}} = 10 \text{ V}$. Compute $P_{2\Omega \text{ avg}}$ and the average stored energy in the coupled inductor.

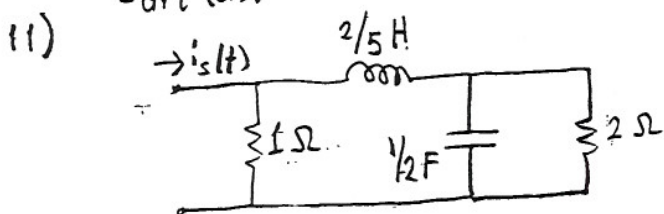(b) The switch is closed, $V_{x \text{ eff}} = 10 \text{ V}$. Determine the value of C so that the average power supplied by the source is 1 W less than that of Part (a).




$$\begin{aligned} i_s(t) &= \sqrt{2} \cos(3t) \text{ A} \\ \text{The circuit is in the SSS.} \end{aligned}$$

(a) Find the input impedance Z of the one-port.

(b) Show that $Z I_{s \text{ eff}}^2 = [P_{1\Omega \text{ avg}} + P_{2\Omega \text{ avg}}] + j2 \times 3 \times [E_{L \text{ avg}} - E_{C \text{ avg}}]$.


12)

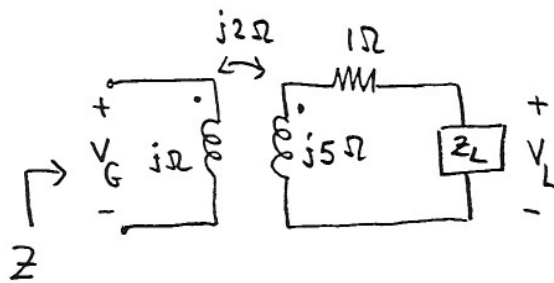

$$|V_L| = \sqrt{2} 10 \text{ V}, \quad Z_L = 1 + j3 \Omega$$

(a) Find $|V_G|$ and Z .(b) Compute the average power delivered to the resistor and the ratio of the average stored energies in the coupled inductor and in Z_L .

13)

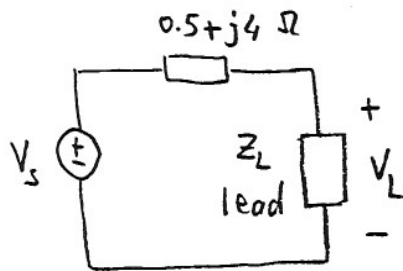


$$V_L = 200 \text{ Vrms}$$

$$P_{s,avg} = 3.4 \text{ kW}, \quad P_{L,avg} = 3.2 \text{ kW}$$

Find V_{seff} .

14)

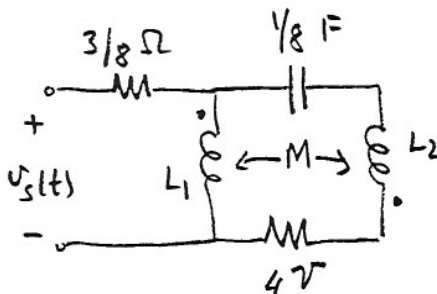

$$v_s(t) = V_m \cos(\omega t + \theta_s) \text{ V}$$

The coupled inductor is passive.


The one-port is in the SSS.

The average power delivered to the $3/8 \Omega$ resistor is 6 W.

The average stored energy in the coupled inductor is 4 J.

The input impedance of the one-port is $Z = Z_m (0.6 - j0.8) \Omega$.Find V_m and Z_m .

15)

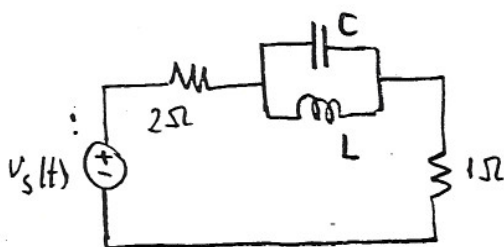

$$v_s(t) = \sqrt{2} 50 \cos(2t) \text{ V}$$

The circuit is in the SSS.

$$P_{2\Omega,avg} = 200 \text{ W}, \quad E_{C,avg} = 200 \text{ J}$$

Find $E_{L,avg}$.