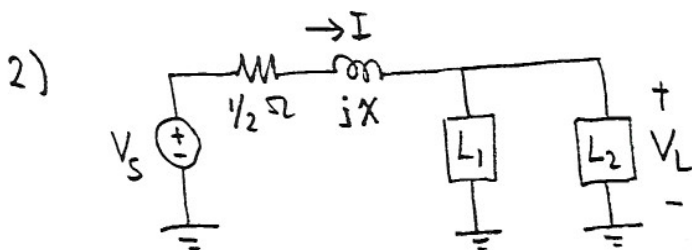


$$v_s(t) = 30 \cos(4t + 24^\circ) \text{ V}$$

The circuit is in the SSS.

- Compute the complex power supplied by the source.
- Compute the real powers delivered to the resistive elements and the reactive powers delivered to the dynamic elements.
- Verify that the real and reactive powers are conserved.
- Compute the average stored energies in the dynamic elements.




$$L_1: 4 \text{ W, resistive}$$

$$L_2: 5 \text{ VA, } pf_2 = 0.6 \text{ leading}$$

$$S_s = 9 + j7 \text{ VA}$$

Find I_{eff} , X , V_{Leff} , V_{seff} .

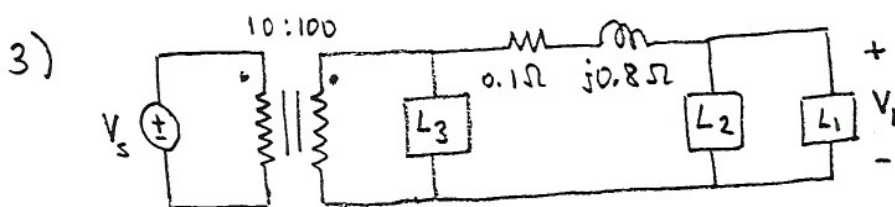


$$L_1: 0.5 + j0.5 \text{ KVA}$$

$$L_2: 2 \text{ KVA, } pf_2 = 0.8 \text{ leading}$$

$$L_3: 3 \text{ KVA, } pf_3 = 0.8 \text{ lagging}$$

$$V_{Leff} = 140 \text{ Vrms}$$

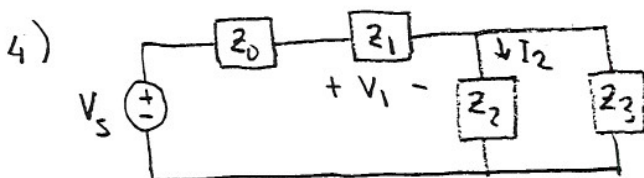Compute the complex power supplied by the source. Find V_{seff} .




$$V_1 = 0.2 + j0.6 \text{ Vrms, } I_2 = 0.6 + j0.8 \text{ Arms}$$

$$|V_s| = 1.5 \text{ V, } pf_{\text{source}} = 0.8 \text{ leading}$$

$$S_1 = 0.8 + j0.4 \text{ VA, } S_2 = -j \text{ VA}$$

Find Z_0, Z_1, Z_2, Z_3, V_s .

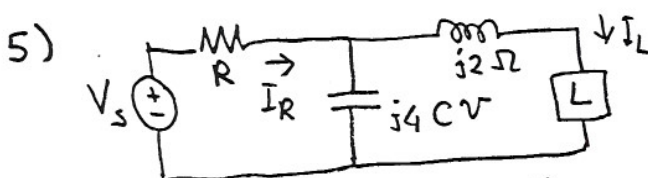


$$S_s = 6.6 + j1.5 \text{ VA}$$

$$L: -4 \text{ VAR, } pf = 0.6$$

$$I_{Leff} = 2 \text{ Arms}$$

Find R, C, I_{Reff} and V_{seff} .

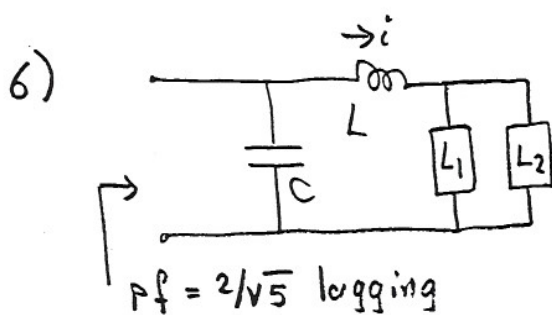


The circuit is in the SSS at $f = 50$ Hz.

$$i_{eff} = 10\sqrt{5} \text{ Arms}, L = \frac{2}{25\pi} \text{ H}$$

$L_1: \sqrt{29} \text{ KVA}, 5 \text{ KW}, \text{capacitive}$

$L_2: 3 \text{ KVAR}, P_{f2} = 1/\sqrt{2}$ lagging.

Find C.

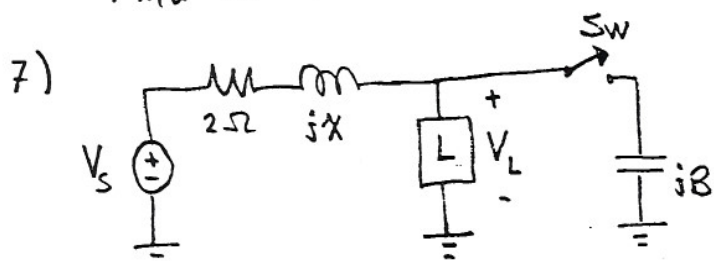


$$V_{Leff} = 10 \text{ Vrms}$$

$L: 5 \text{ VA}, \text{inductive}$

$$P_s = 4.5 \text{ W}$$


(a) Sw is open; Find X , P_{load} and S_s given $V_{seff} = 15 \text{ Vrms}$.

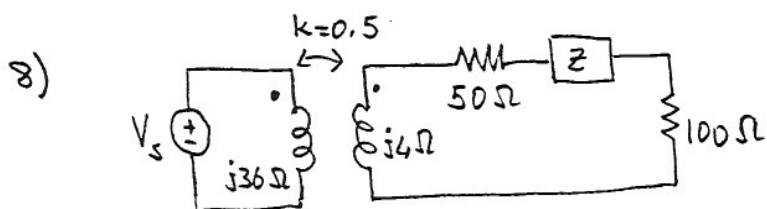(b) Sw is closed ($V_{Leff} = 10 \text{ Vrms}$); Determine B so that P_{load} (including the capacitor) is 0.96 lagging. Also find S_s and V_{seff} .



$$V_s = 60 \angle 17^\circ \text{ V}$$

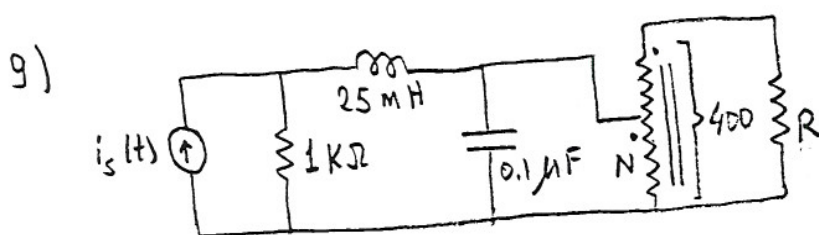Determine Z so that the average power delivered to 100Ω resistor is maximum. Also compute this power.




$$i_s(t) = 10 \cos(4 \times 10^4 t) \text{ mA}$$

The circuit is in the SSS.

$$R = 800\sqrt{2} \Omega$$

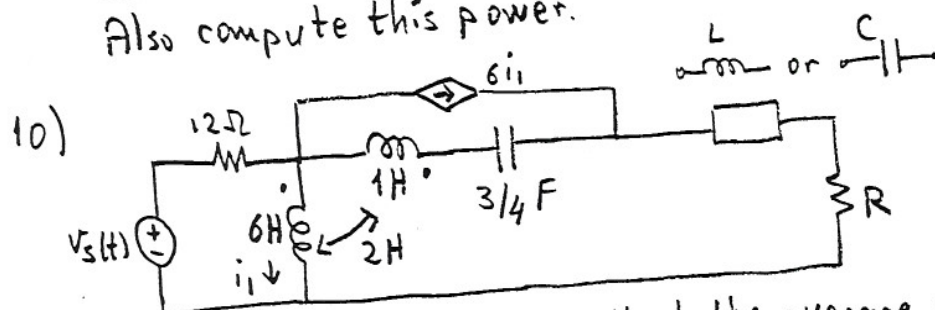Determine N so that the average power delivered to R is maximum. Also compute this power.



$$V_s(t) = 20 \cos(2t + 30^\circ) \text{ V}$$

The circuit is in the SSS.

Determine R and L or C so that the average power delivered to R is maximum. For these values of R and L or C compute the complex powers supplied by the sources and the average powers delivered to the resistors.