
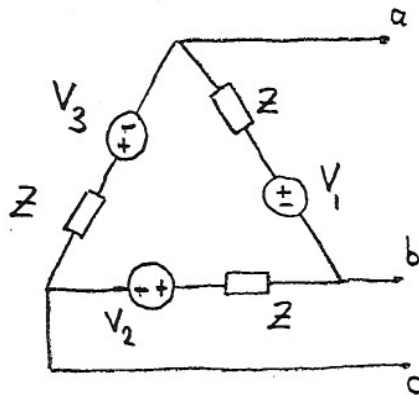


1)

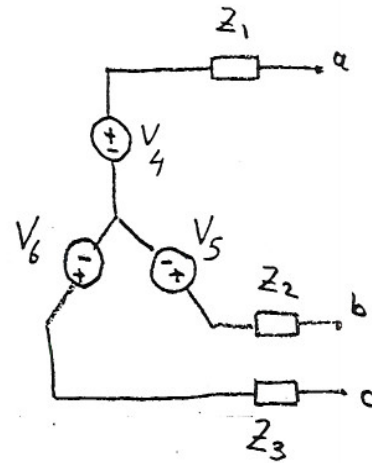


$\equiv$



$$V_2 = V_1 \angle -120^\circ, V_3 = V_1 \angle +120^\circ$$

Express V_4, V_5, V_6 in terms of V_1 and Z_1, Z_2, Z_3 in terms of Z .

2)

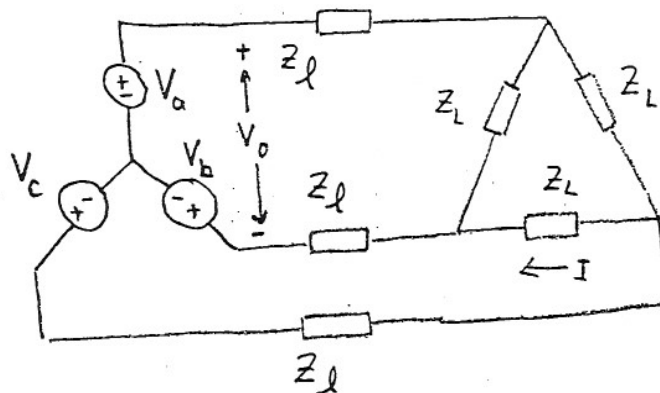

$$V_b = V_a \angle -120^\circ, V_c = V_a \angle +120^\circ$$


$$Z_l = 1 + j5 \Omega$$

$$Z_L = 15 + j9 \Omega$$

$$I = 10 \angle 15^\circ \text{ Arms}$$

Find V_0 .

3)

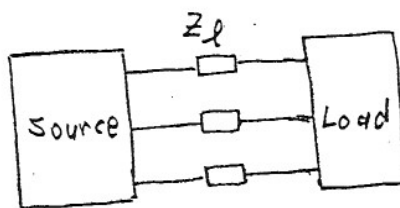

A balanced 3-phase circuit.

$$Z_l = 0.5 + j\frac{2}{3} \Omega$$


$$P_s = 12 \text{ KW}$$

$$\text{Load: } 12 \text{ KVA, } \text{pf}_L = 0.8 \text{ lagging}$$

Find the line voltages at the load and source ends and the complex power supplied by the source.

4) In a balanced 3-phase circuit the line impedance is $1.5 + j2.5 \Omega$, the total real power lost on the lines is 1.8 KW , the total real power delivered to the inductive load is 10.2 KW , the line voltage at the source end is $250\sqrt{3} \text{ Vrms}$. Find the load power factor and the line voltage at the load end.

5)

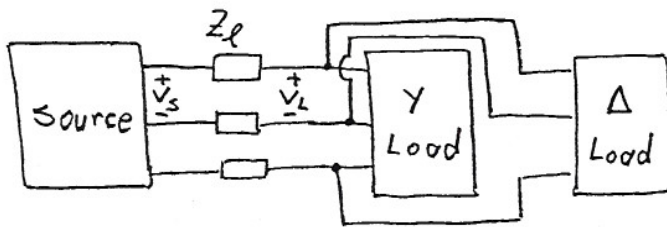

A balanced 3-phase circuit.


$$Z_l = \frac{1+j}{30} \Omega$$

Y load: 15 kVA, $P_f = 0.8$ lagging Δ load: $Z_L = 1.6 + j1.2 \Omega$

$$V_{Leff} = 100 \text{ Vrms}$$

Find V_{seff} and the complex power supplied by the source.

6)

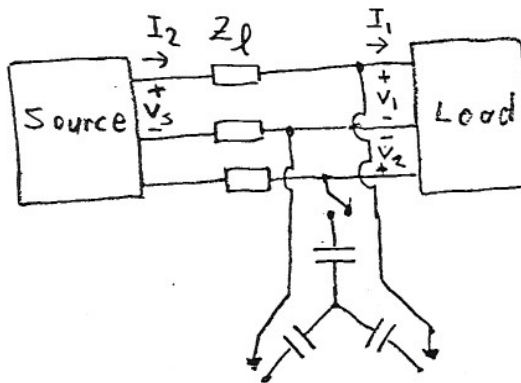

A balanced 3-phase circuit.


Load: 400 kW, $P_f = \frac{1}{\sqrt{2}}$ lagging

$$V_1 = 400 \angle 30^\circ \text{ Vrms}, V_2 = 400 \angle -30^\circ \text{ Vrms}$$

$$Z_l = 0.07 + j0.16 \Omega$$

- (a) The switches are open: Find I_1 , V_{seff} , the complex power supplied by the source and the efficiency.
- (b) The switches are closed: The power factor of the load-capacitor bank combination is 0.8 lagging. Find the susceptance of a capacitor, I_1 , I_2 , V_{seff} , the complex power supplied by the source and the efficiency.

7)

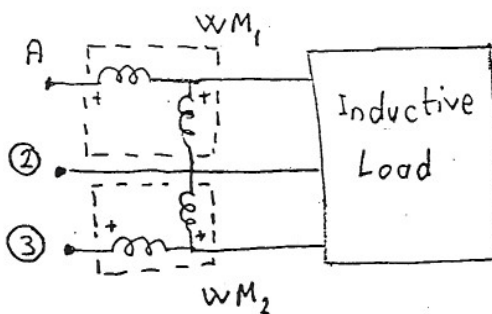

A balanced 3-phase circuit.

The readings of the wattmeters:

$$WM_1: 600 \text{ W}, WM_2: 400 \text{ W}$$

The load power factor: $P_f > \frac{1}{2}$

$$P_f = 0.945$$

Find the real and reactive powers delivered to the load.

Assuming that the phase sequence is A-B-C, should we label the terminal ② as B or C?