

First name: _____

Last name: Sollu _____

Student ID: _____


Signature: _____

Read before you start:


- There are four questions.
- The examination is closed-book.
- No computer/calculator is allowed.
- The duration of the examination is 120 minutes.
- Besides correctness, the CLARITY of your presentation will also be graded.

Q1	Q2	Q3	Q4	Total


Q1.

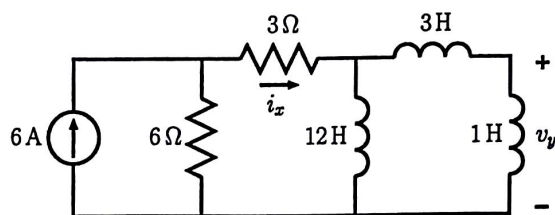

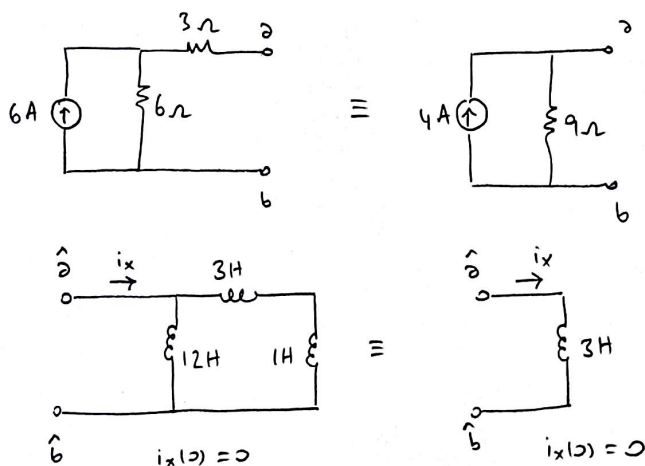The initial inductor currents are zero in the above circuit. Find $i_x(t)$ and $v_y(t)$ for $t \geq 0$.



Therefore we can work with

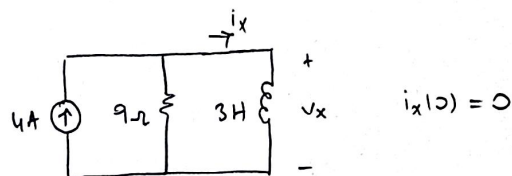

$$\tau = \frac{L}{R} = \frac{3}{9} = \frac{1}{3} \text{ sec}$$

$$i_x(\infty) = 4A$$


$$\Rightarrow i_x(t) = i_x(\infty) + (i_x(0) - i_x(\infty)) e^{-t/\tau}$$

$$= \boxed{4 - 4e^{-3t} A}$$

$$\text{Then } v_x(t) = L \frac{di_x(t)}{dt}$$

$$= 3 \frac{d}{dt} \{4 - 4e^{-3t}\} = 36e^{-3t} \text{ V}$$

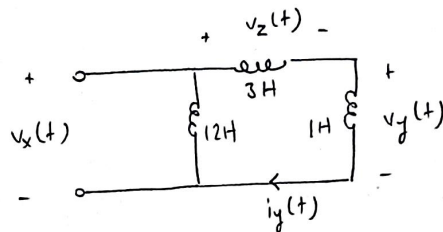Now, we return to the original configuration




$$\left. \begin{aligned} v_y(t) &= 1 \frac{di_y(t)}{dt} \\ v_z(t) &= 3 \frac{di_y(t)}{dt} \end{aligned} \right\} v_z(t) = 3v_y(t)$$

$$v_x(t) = v_z(t) + v_y(t) = 4v_y(t)$$

$$\Rightarrow v_y(t) = \frac{1}{4} v_x(t) = \boxed{9e^{-3t} \text{ V}}$$


Q2.

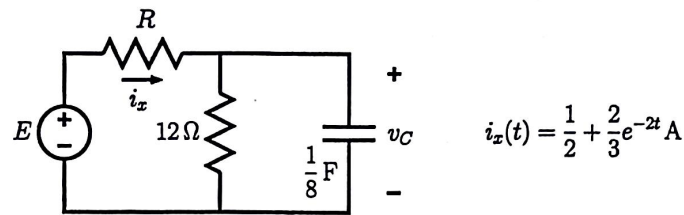

In the above circuit E is constant. Find R , E , and $v_C(0)$.

The time constant of the circuit is $\tau = \frac{1}{2} \text{ sec.}$

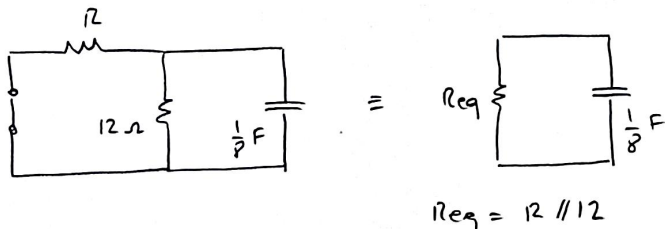
Now, τ is independent of the input. So, kill the voltage source.



$$\tau = R_{eq} \cdot C \Rightarrow \frac{1}{2} = R_{eq} \cdot \frac{1}{8} \Rightarrow R_{eq} = 4 \Omega$$


$$\Rightarrow 12 \parallel 12 = 4 \Rightarrow \boxed{12 = 6 \Omega}$$

$t = \infty$

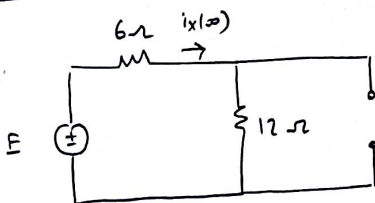


$$i_x(\infty) = \frac{1}{2} = \frac{E}{6 + 12} \Rightarrow \boxed{E = 9 \text{ V}}$$

$t = 0$

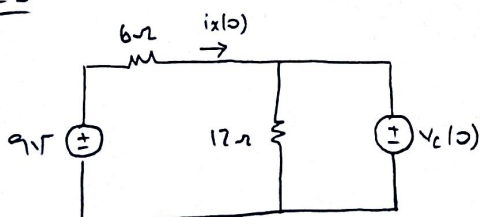

$$i_x(0) = \frac{1}{2} + \frac{2}{3} = \frac{7}{6} = \frac{9 - v_C(0)}{6} \Rightarrow \boxed{v_C(0) = 2 \text{ V}}$$

Q3.

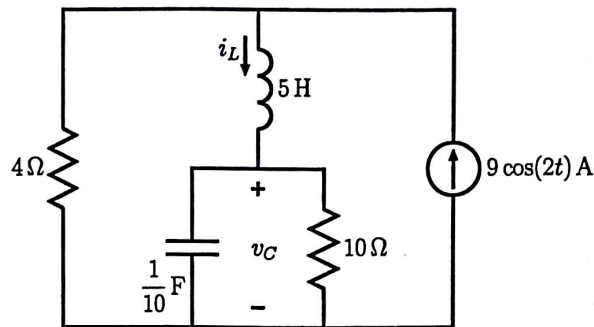

The circuit above is in sinusoidal steady state. Find $i_L(t)$ and $v_C(t)$.

obtain the phasor-domain circuit $[\omega = 2 \text{ rad/sec}]$

By current division

$$I_L = \frac{4}{4 + Z_2} \cdot 9 = \frac{4}{6 + j6} \cdot 9 = 3 - j3 \text{ A} \quad (1)$$

Then

$$V_C = Z_1 \cdot I_L = (2 - j4)(3 - j3) = -6 - j18 \text{ V} \quad (2)$$



Now,

$$(1) \Rightarrow I_L = 3\sqrt{2} \angle -\frac{\pi}{4} \text{ A}$$


$$\Rightarrow i_L(t) = 3\sqrt{2} \cos(2t - \frac{\pi}{4}) \text{ A}$$

$$(2) \Rightarrow V_C = 6\sqrt{10} \angle \pi + \tan^{-1} 3 \text{ V}$$
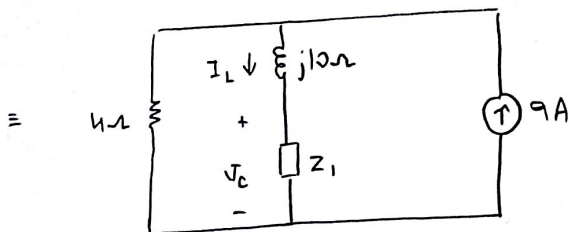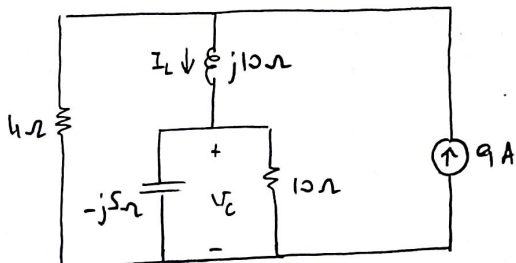
$$\Rightarrow v_C(t) = 6\sqrt{10} \cos(2t + \pi + \tan^{-1} 3) \text{ V}$$



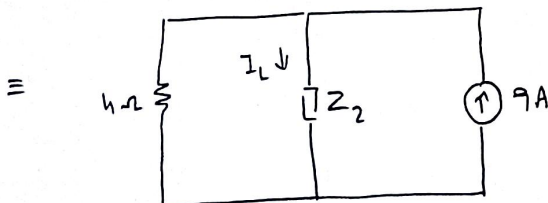
$$Z_1 = -j5 \parallel 10 = \frac{10(-j5)}{10 - j5} = 2 - j4 \Omega$$





$$Z_2 = Z_1 + j10 = 2 + j6 \Omega$$

Q4.

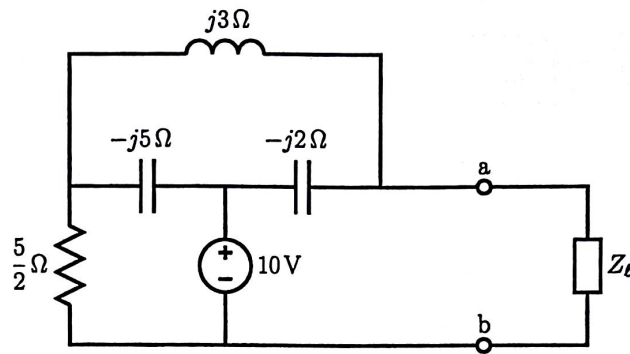


In the (phasor-domain) circuit above find the Thevenin equivalent circuit seen by the load impedance Z_L .

Z_{th} (Kill the voltage source)

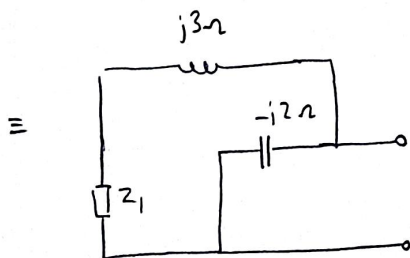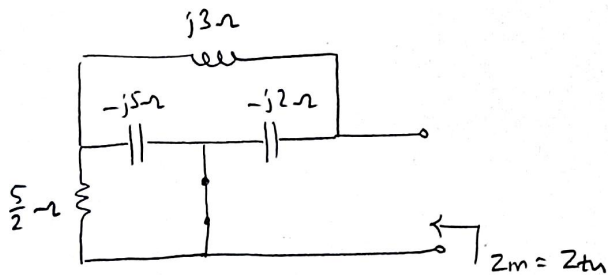

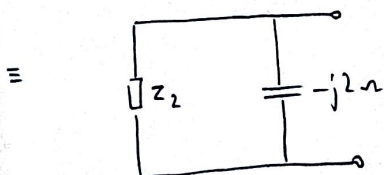
$$Z_1 = -j5 \parallel \frac{5}{2} = \frac{-j5 \cdot \frac{5}{2}}{\frac{5}{2} - j5} = 2 - j \Omega$$



$$Z_2 = Z_1 + j3 = 2 + j2 \Omega$$

$$\Rightarrow Z_{th} = (2 + j2) \parallel -j2 = \frac{-j2(2 + j2)}{2} = \underline{2 - j2 \Omega}$$

Compute I_{sc}

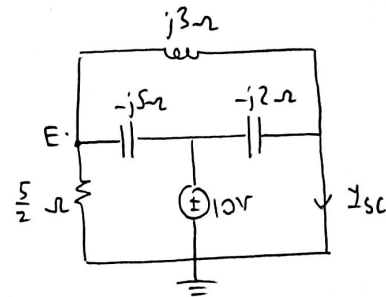

$$\frac{E}{5/2} + \frac{E - 10}{-j5} + \frac{E}{j3} = 0 \Rightarrow E = -\frac{3}{2} + j\frac{9}{2} V$$

$$\Rightarrow I_{sc} = \frac{E}{j3} + \frac{10}{-j2} = \frac{3}{2} + j\frac{11}{2} A$$

$$\Rightarrow V_{th} = Z_{th} I_{sc} = (2 - j2) \left(\frac{3}{2} + j\frac{11}{2} \right) = \underline{14 + j8 V}$$

Hence, we have

