

First name: \_\_\_\_\_

Last name: Sol'n

Student ID: \_\_\_\_\_


Signature: \_\_\_\_\_

**Read before you start:**

- There are four questions.
- The examination is closed-book.
- No computer/calculator is allowed.
- The duration of the examination is 100 minutes.
- Besides correctness, the CLARITY of your presentation will also be graded.

| Q1 | Q2 | Q3 | Q4 | Total |
|----|----|----|----|-------|
|    |    |    |    |       |

Q1.

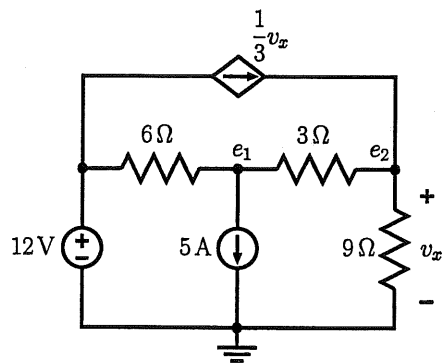

Find the node voltages  $e_1$  and  $e_2$ .

$$\text{Node ①: } \frac{e_1 - 12}{6} + 5 + \frac{e_1 - e_2}{3} = 0$$

$$\Rightarrow \frac{1}{2}e_1 - \frac{1}{3}e_2 = -3 \quad (1)$$


$$\text{Node ②: } \left. \begin{aligned} \frac{e_2 - e_1}{3} + \frac{e_2}{9} - \frac{1}{3}v_x &= 0 \\ v_x &= e_2 \end{aligned} \right\}$$

$$\Rightarrow \frac{e_2 - e_1}{3} + \frac{e_2}{9} - \frac{e_2}{3} = 0$$

$$\Rightarrow -\frac{1}{3}e_1 + \frac{1}{9}e_2 = 0 \quad (2)$$

$$(1) \text{ and } (2) \Rightarrow \boxed{e_1 = 6V} \quad \& \quad \boxed{e_2 = 18V}$$

Q2.

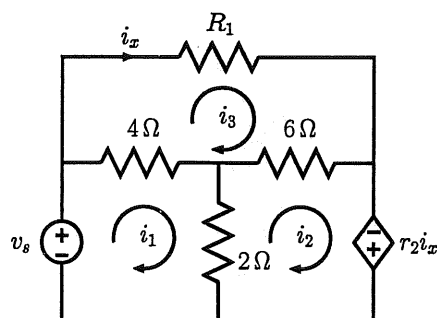

(a) Write the mesh equations in matrix form.

(b) Suppose the mesh currents are measured as  $i_1 = 4\text{ A}$ ,  $i_2 = 3\text{ A}$ , and  $i_3 = 2\text{ A}$ .

(i) Find  $R_1$ ,  $r_2$ , and  $v_s$ .

(ii) Find the power supplied/absorbed by the dependent source.

a)

$$\text{Mesh ①: } -v_s + 4(i_1 - i_3) + 2(i_1 - i_2) = 0$$

$$\Rightarrow 6i_1 - 2i_2 - 4i_3 = v_s \quad (1)$$

$$\text{Mesh ②: } 2(i_2 - i_1) + 6(i_2 - i_3) - r_2 i_x = 0$$

$$i_x = i_3$$

$$\Rightarrow 2(i_2 - i_1) + 6(i_2 - i_3) - r_2 i_3 = 0$$

$$\Rightarrow -2i_1 + 8i_2 - (r_2 + 6)i_3 = 0 \quad (2)$$

$$\text{Mesh ③: } 4(i_3 - i_1) + R_1 i_3 + 6(i_3 - i_2) = 0$$

$$\Rightarrow -4i_1 - 6i_2 + (R_1 + 10)i_3 = 0 \quad (3)$$

(1), (2), (3) imply

$$\begin{bmatrix} 6 & -2 & -4 \\ -2 & 8 & -(r_2 + 6) \\ -4 & -6 & R_1 + 10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} v_s \\ 0 \\ 0 \end{bmatrix}$$

b) i)

$$(1) \Rightarrow 6 \cdot 4 - 2 \cdot 3 - 4 \cdot 2 = v_s$$

$$\Rightarrow \boxed{v_s = 10\text{ V}}$$

$$(2) \Rightarrow -2 \cdot 4 + 8 \cdot 3 - (r_2 + 6) \cdot 2 = 0$$

$$\Rightarrow \boxed{r_2 = 2\ \Omega}$$

$$(3) \Rightarrow -4 \cdot 4 - 6 \cdot 3 + (R_1 + 10) \cdot 2 = 0$$

$$\Rightarrow \boxed{R_1 = 7\ \Omega}$$

ii) Let  $P$  be the power of dep. source


$$P = (r_2 i_x) \cdot (-i_2) = -r_2 i_3 i_2$$

$$= -2 \cdot 2 \cdot 3$$

$$= -12\text{ W}$$

Hence the dep. source supplies 12 W power.

Q3.

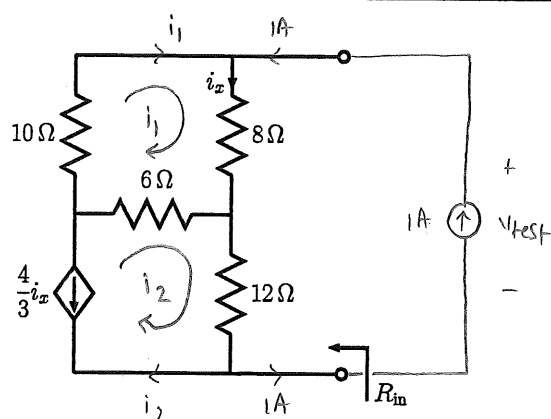

Compute the input resistance  $R_{in}$ .

$$\text{Mesh ①: } 10i_1 + 8(i_1 + 1) + 6(i_1 - i_2) = 0$$

$$\Rightarrow 24i_1 - 6i_2 = -8 \quad (1)$$

$$\text{constraint: } \left. \begin{array}{l} \frac{4}{3}i_x = -i_2 \\ i_x = i_1 + 1 \end{array} \right\} \frac{4}{3}(i_1 + 1) = -i_2$$


$$\Rightarrow \frac{4}{3}i_1 + i_2 = -\frac{4}{3} \quad (2)$$

$$(1) \text{ and } (2) \Rightarrow i_1 = -\frac{1}{2} \text{ A} \quad \& \quad i_2 = -\frac{2}{3} \text{ A}$$

$$\begin{aligned} v_{test} &= v_{8\Omega} + v_{12\Omega} = 8(i_1 + 1) + 12(i_2 + 1) \\ &= 8\left(\frac{1}{2}\right) + 12\left(\frac{1}{3}\right) \\ &= 4 + 4 = 8 \text{ V} \end{aligned}$$

$$R_{in} = \frac{v_{test}}{1 \text{ A}} = \frac{8 \text{ V}}{1 \text{ A}} \Rightarrow \boxed{R_{in} = 8 \Omega}$$

Q4.

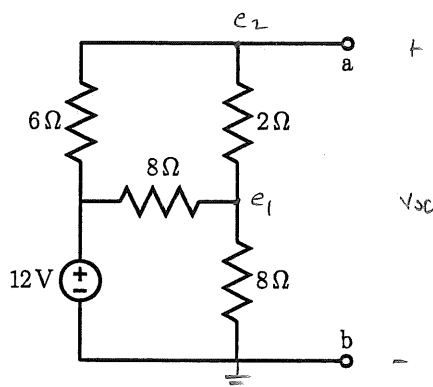

Find and draw the Thevenin equivalent of the above one-port circuit.

Find the open-circuit voltage  $V_{oc}$ .

$$\text{Node ①: } \frac{e_1 - 12}{8} + \frac{e_1}{8} + \frac{e_1 - e_2}{2} = 0$$

$$\Rightarrow \frac{3}{4}e_1 - \frac{1}{2}e_2 = \frac{3}{2} \quad (1)$$


$$\text{Node ②: } \frac{e_2 - 12}{6} + \frac{e_2 - e_1}{2} = 0$$

$$\Rightarrow -\frac{1}{2}e_1 + \frac{2}{3}e_2 = 2 \quad (2)$$

$$(1) \& (2) \Rightarrow e_1 = 8V, \quad e_2 = 9V$$

$$V_{oc} = e_2 \Rightarrow \boxed{V_{th} = 9V}$$

Find the input resistance  $R_{in}$ .

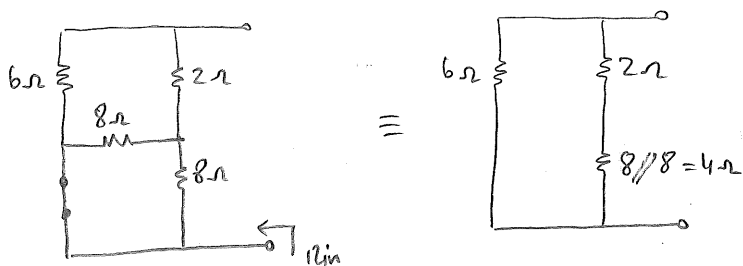

$\equiv$

$\equiv$



$$\Rightarrow \boxed{R_{th} = 3\Omega}$$

Hence the Thevenin equiv. is

