

First name: _____

Last name: Sol'n _____

Student ID: _____


Signature: _____

Read before you start:

- There are four questions.
- The examination is closed-book.
- No computer/calculator is allowed.
- The duration of the examination is 100 minutes.
- Besides correctness, the CLARITY of your presentation will also be graded.

Q1	Q2	Q3	Q4	Total

Q1.

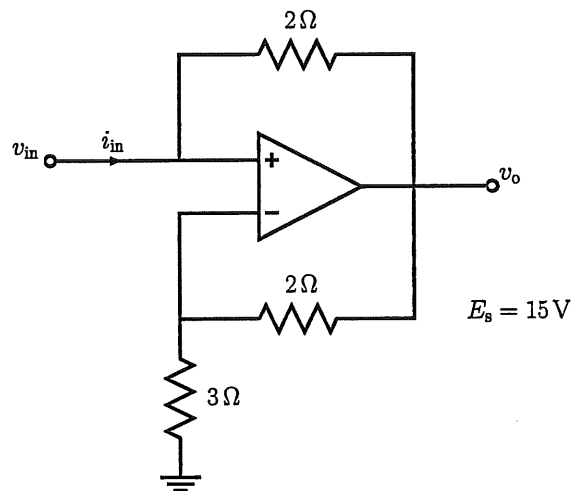

Find and sketch the transfer ($v_{in} - v_o$) and input ($v_{in} - i_{in}$) characteristics.

$$v_+ = v_{in} \quad (1)$$

$$\frac{v_-}{3} + \frac{v_- - v_o}{2} = 0 \Rightarrow v_- = \frac{3}{5} v_o \quad (2)$$

$$i_{in} = \frac{v_{in} - v_o}{2} \quad (3)$$

linear $v_+ = v_-$ and $-15 \leq v_o \leq 15$

$$(1) \& (2) \Rightarrow v_{in} = \frac{3}{5} v_o \Rightarrow v_o = \frac{5}{3} v_{in}$$

$$\Rightarrow -15 \leq \frac{5}{3} v_{in} \leq 15 \Rightarrow -9 \leq v_{in} \leq 9$$

$$(3) \Rightarrow i_{in} = \frac{1}{2} v_{in} - \frac{1}{2} v_o = \frac{1}{2} v_{in} - \frac{1}{2} \left(\frac{5}{3} v_{in} \right)$$

$$\Rightarrow i_{in} = -\frac{1}{3} v_{in}$$

sat $v_+ > v_-$ and $v_o = 15V$



$$(1) \& (2) \Rightarrow v_{in} > \frac{3}{5} (15) \Rightarrow v_{in} > 9$$

$$(3) \Rightarrow i_{in} = \frac{1}{2} (v_{in} - 15)$$


sat $v_+ < v_-$ and $v_o = -15V$

$$(1) \& (2) \Rightarrow v_{in} < \frac{3}{5} (-15) \Rightarrow v_{in} < -9$$
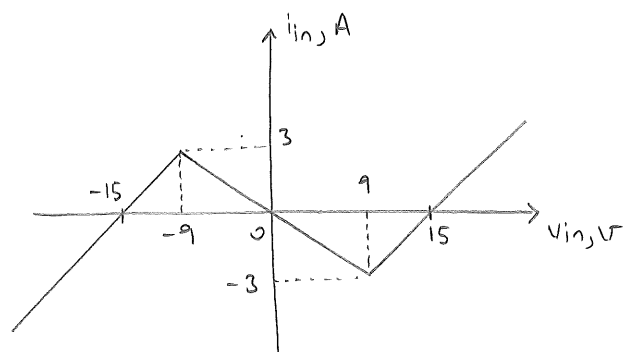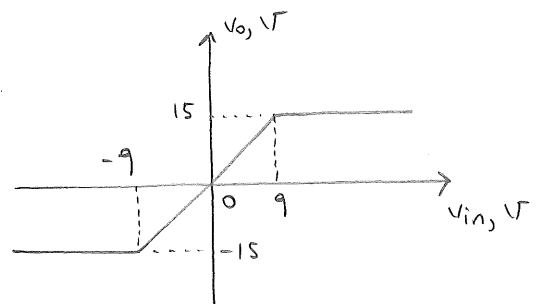
$$(3) \Rightarrow i_{in} = \frac{1}{2} (v_{in} + 15)$$




Q2.

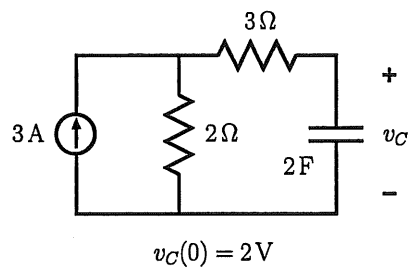


(a) Find $v_C(t)$ for $t \geq 0$.

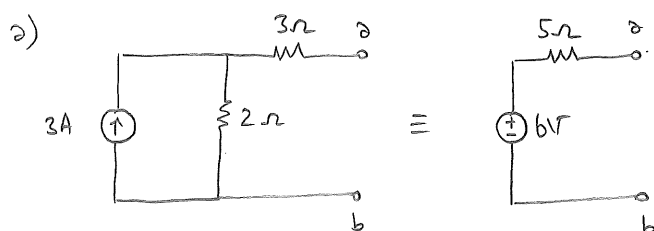(b) Find the energy stored in the capacitor in the DC steady state.



Hence we can work with

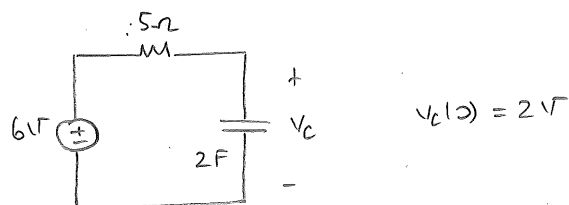

$$6 = 5i_C + v_C = 5(2Dv_C) + v_C$$

$$\Rightarrow Dv_C + \frac{1}{10}v_C = \frac{3}{5}$$

$$\Rightarrow v_C(t) = 6 + Ke^{-\frac{t}{10}}$$


$$v_C(0) = 2 \Rightarrow 6 + K = 2 \Rightarrow K = -4$$

$$\Rightarrow v_C(t) = 6 - 4e^{-\frac{t}{10}} \text{ V}$$

b) $v_C(\infty) = 6V$


$$\Rightarrow E_C = \frac{1}{2} C v_C(\infty)^2 = \frac{1}{2} \cdot 2 \cdot 6^2 = \boxed{36J}$$

Q3.

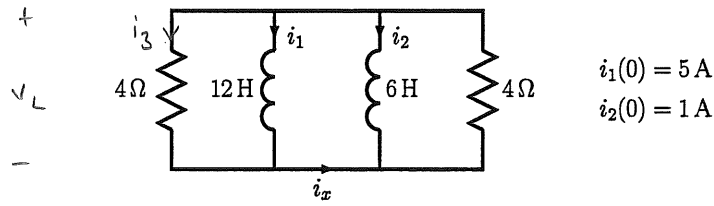

Find $i_x(t)$ for $t \geq 0$.

Equivalent circuit =

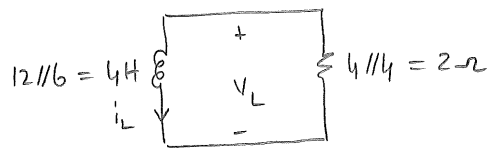

$$i_L(0) = i_1(0) + i_2(0) = 6A$$

$$\tau = \frac{L}{R} = \frac{4}{2} = 2 \text{ sec}$$

$$\Rightarrow i_L(t) = i_L(0) e^{-t/\tau} = 6 e^{-t/2} A$$

$$\begin{aligned} \Rightarrow v_L(t) &= L \frac{di_L(t)}{dt} = 4 \frac{d}{dt} \{ 6 e^{-t/2} \} \\ &= -12 e^{-t/2} V \end{aligned}$$

$$i_1(t) = i_1(0) + \frac{1}{12} \int_0^t v_L(\alpha) d\alpha$$

$$= 5 + \frac{1}{12} \int_0^t -12 e^{-\alpha/2} d\alpha$$


$$= 5 + 2 e^{-\alpha/2} \Big|_0^t = 5 + 2(e^{-t/2} - 1)$$

$$= 3 + 2e^{-t/2} A$$

$$i_3(t) = \frac{v_L(t)}{4} = -3e^{-t/2} A$$

$$i_x(t) = i_1(t) + i_3(t) = \boxed{3 - e^{-t/2} A}$$


Q4.

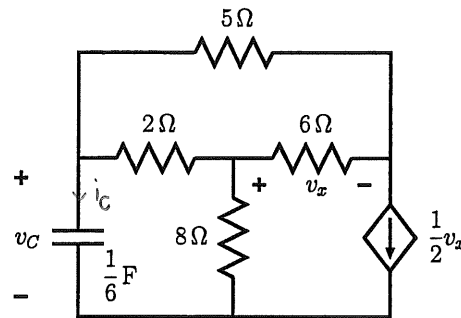


$$v_C(0) = 12 \text{ V}$$

Find $v_x(t)$ for $t \geq 0$.

First, find R_{in} :

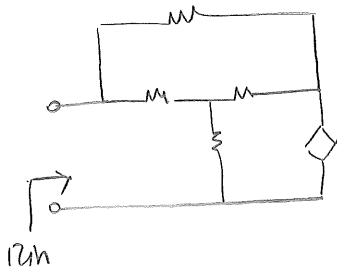

Let's connect a test source :

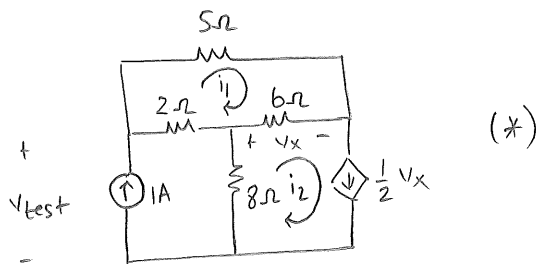

$$\text{Mesh ①: } 2(i_1 - 1) + 5i_1 + 6(i_1 - i_2) = 0$$

$$\Rightarrow 13i_1 - 6i_2 = 2 \quad (1)$$

$$\text{Constraint: } i_2 = \frac{1}{2} v_x = \frac{1}{2} \{ 6(i_2 - i_1) \} = 3i_2 - 3i_1$$

$$\Rightarrow 2i_2 - 3i_1 = 0 \quad (2)$$

$$(1) \& (2) \Rightarrow i_1 = \frac{1}{2} \text{ A} \quad \& \quad i_2 = \frac{3}{4} \text{ A}$$

$$\Rightarrow v_{test} = 2(1 - i_1) + 8(1 - i_2) = 2\left(\frac{1}{2}\right) + 8\left(\frac{1}{4}\right) = 3 \text{ V}$$


$$\Rightarrow R_{in} = \frac{v_{test}}{i_{test}} = \frac{3}{1} = 3 \Omega$$

$$\Rightarrow \tau = R_{in} C = 3 \cdot \frac{1}{6} = \frac{1}{2} \text{ sec}$$

$$\Rightarrow v_C(t) = v_C(0) e^{-t/\tau} = 12 e^{-2t} \text{ V}$$

$$\Rightarrow i_C(t) = C D v_C(t) = -4 e^{-2t} \text{ A}$$

By substitution then :

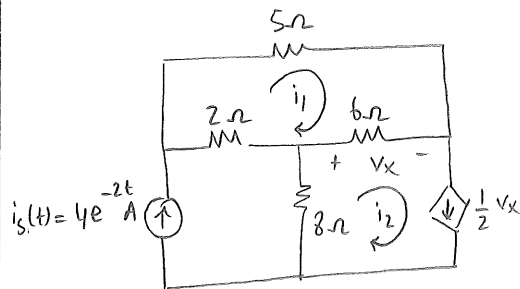

From circuit (*) we know that

$$i_1 = \frac{1}{2} i_s \quad \& \quad i_2 = \frac{3}{4} i_s$$

$$\Rightarrow v_x = 6(i_2 - i_1) = 6\left(\frac{3}{4} i_s - \frac{1}{2} i_s\right) = \frac{3}{2} i_s$$

$$\Rightarrow v_x(t) = \frac{3}{2} \{ 4e^{-2t} \} = \boxed{6e^{-2t} \text{ V}}$$