
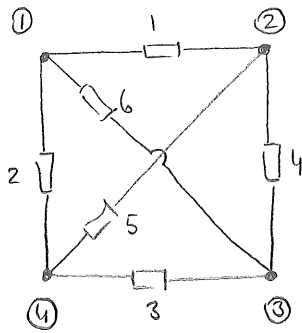


Definition A planar circuit is such that it can be drawn on plane in such a way that no two branches intersect at a point that is not a node.


Ex :

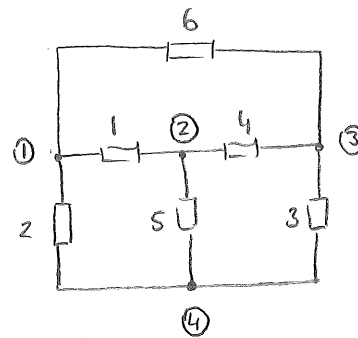

planar
because
 $\equiv$



whereas

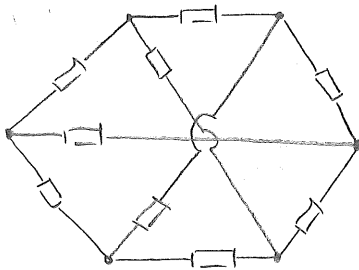

is a nonplanar circuit.


Planar circuits come with meshes and associated to each mesh there corresponds

a mesh current. (Mesh current directions are chosen clockwise by convention.)

The relation of a branch current, i_k , to mesh currents is as follows. Let the k^{th} branch touches the meshes $\textcircled{a}$ and $\textcircled{b}$. Suppose the direction of i_k is same with the mesh current $i_{\textcircled{a}}$ and opposite to the mesh current $i_{\textcircled{b}}$. Then $i_k = i_{\textcircled{a}} - i_{\textcircled{b}}$.

Let the k^{th} branch touches only the mesh $\textcircled{a}$. Then $i_k = i_{\textcircled{a}}$ if the directions are the same and $i_k = -i_{\textcircled{a}}$ if opposite.

Ex :

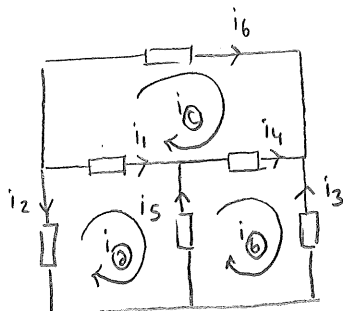

Mesh currents = $i_{\textcircled{a}}, i_{\textcircled{b}}, i_{\textcircled{c}}$

$$i_1 = i_{\textcircled{a}} - i_{\textcircled{c}}$$

$$i_4 = i_{\textcircled{b}} - i_{\textcircled{c}}$$

$$i_2 = -i_{\textcircled{a}}$$


$$i_5 = i_{\textcircled{b}} - i_{\textcircled{a}}$$

$$i_3 = -i_{\textcircled{b}}$$

$$i_6 = i_{\textcircled{c}}$$

Mesh Current Analysis

The idea is to solve for mesh currents by writing KVL at each mesh.

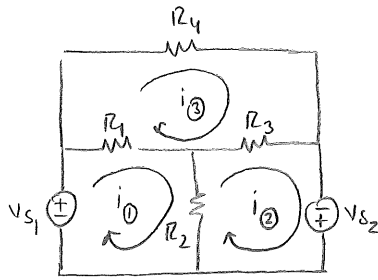Example

formulation variables i_1, i_2, i_3

KVL at mesh ① : $-v_{S1} + v_{R1} + v_{R2} = 0$

$$R_4(i_1 - i_3) \leftarrow R_1 i_1 \quad R_2 i_2 \rightarrow R_2(i_1 - i_2)$$


$$\Rightarrow -v_{S1} + R_1(i_1 - i_3) + R_2(i_1 - i_2) = 0 \quad (1)$$

KVL at mesh ② : $-v_{S2} + R_2(i_2 - i_1) + R_3(i_2 - i_3) = 0 \quad (2)$

KVL at mesh ③ : $R_4 i_3 + R_3(i_3 - i_2) + R_1(i_3 - i_1) = 0 \quad (3)$

$$(1), (2), (3) \Rightarrow \underbrace{\begin{bmatrix} R_1 + R_2 & -R_2 & -R_1 \\ -R_2 & R_2 + R_3 & -R_3 \\ -R_1 & -R_3 & R_1 + R_3 + R_4 \end{bmatrix}}_{Z_m} \underbrace{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}}_{i_m} = \underbrace{\begin{bmatrix} v_{S1} \\ v_{S2} \\ 0 \end{bmatrix}}_{v_s}$$

Z_m : mesh impedance matrix

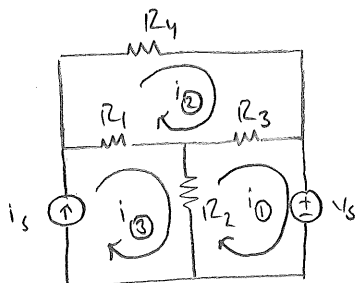Mesh Analysis with current sourcesExample

Note that $i_3 = i_S$, therefore known.


formulation var. : i_1, i_2

$$\left. \begin{aligned} \text{KVL at } ①: R_2(i_① - i_s) + R_3(i_① - i_②) + v_s &= 0 \\ \text{KVL at } ②: R_1(i_② - i_s) + R_4 i_② + R_3(i_② - i_①) &= 0 \end{aligned} \right\} \begin{bmatrix} R_2 + R_3 & -R_3 \\ -R_3 & R_1 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_① \\ i_② \end{bmatrix} = \begin{bmatrix} R_2 i_s - v_s \\ R_1 i_s \end{bmatrix}$$

Modified Mesh Analysis

When there is a current source between two meshes we cannot express its voltage in terms of mesh currents. In such a case we write KVL pretending that the two meshes (between which there is a current source) are a single mesh. Such mesh is called a supermesh.

Example

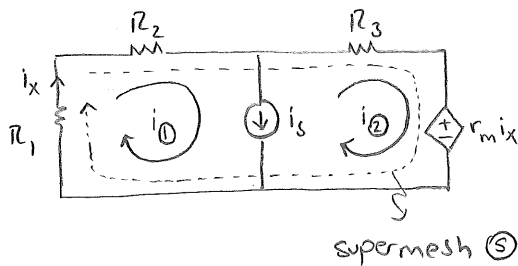

formulation var. : $i_①, i_②$

$$\left. \begin{aligned} \text{KVL at supermesh } ⑤: (R_1 + R_2) i_① + R_3 i_② + r_m i_x &= 0 \\ i_x &= i_① \end{aligned} \right\} (R_1 + R_2 + r_m) i_① + R_3 i_② = 0 \quad (1)$$


$$\text{constraint eqn. : } i_① - i_② = i_s \quad (2)$$

$$(1) \& (2) \Rightarrow \begin{bmatrix} R_1 + R_2 + r_m & R_3 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} i_① \\ i_② \end{bmatrix} = \begin{bmatrix} 0 \\ i_s \end{bmatrix} \quad (3)$$

Let $R_1 = R_2 = r_m = 1\Omega$ & $i_s = 1A$. Find $i_①, i_②$.

$$\begin{aligned} (3) \Rightarrow \begin{bmatrix} 3 & 1 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} i_① \\ i_② \end{bmatrix} &= \begin{bmatrix} 0 \\ 1 \end{bmatrix} \Rightarrow \begin{bmatrix} i_① \\ i_② \end{bmatrix} = \begin{bmatrix} 3 & 1 \\ 1 & -1 \end{bmatrix}^{-1} \begin{bmatrix} 0 \\ 1 \end{bmatrix} \\ &= \frac{1}{-4} \begin{bmatrix} -1 & -1 \\ -1 & 3 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 1/4 \\ -3/4 \end{bmatrix} \end{aligned}$$

$$\Rightarrow i_① = \frac{1}{4} A \text{ \& } i_② = -\frac{3}{4} A$$

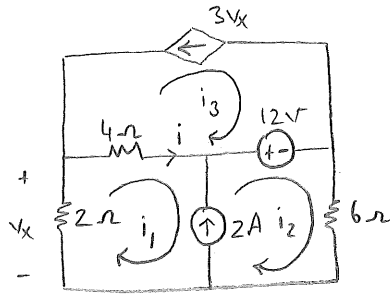ExampleFind i .Mesh current formulation

$$\text{Supermesh } ①+② : 2i_1 + 4(i_1 - i_3) + 12 + 6i_2 = 0$$


$$\Rightarrow 6i_1 + 6i_2 - 4i_3 = -12 \quad (1)$$

$$\text{Constraint 1 : } \left. \begin{array}{l} i_3 = -3v_x \\ v_x = -2i_1 \end{array} \right\} i_3 = 6i_1 \quad (2)$$

$$\text{Constraint 2 : } i_2 - i_1 = 2 \Rightarrow i_2 = i_1 + 2 \quad (3)$$

$$(1), (2), (3) \Rightarrow 6i_1 + 6(i_1 + 2) - 4(6i_1) = -12 \Rightarrow -12i_1 = -24 \Rightarrow i_1 = 2A \quad (4)$$

$$(2) \& (4) \Rightarrow i = i_1 - i_3 = i_1 - 6i_1 = -5i_1 = \boxed{-10A}$$

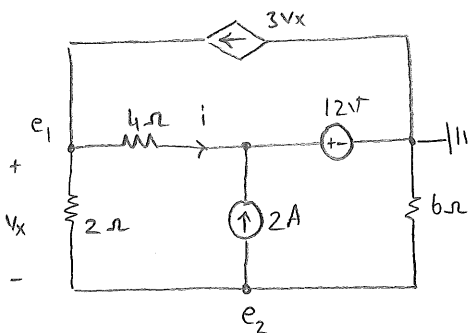Node voltage formulation

$$\text{Node ① : } \frac{e_1 - e_2}{2} + \frac{e_1 - 12}{4} - 3v_x = 0 \quad \& \quad v_x = e_1 - e_2$$

$$\Rightarrow \left(\frac{1}{2} + \frac{1}{4} - 3 \right) e_1 + \left(-\frac{1}{2} + 3 \right) e_2 = 3$$


$$\Rightarrow -\frac{9}{4}e_1 + \frac{5}{2}e_2 = 3 \quad (1)$$

$$\text{Node ② : } 2 + \frac{e_2 - e_1}{2} + \frac{e_2}{6} = 0$$

$$\Rightarrow -\frac{1}{2}e_1 + \frac{2}{3}e_2 = -2 \quad (2)$$

$$(1) \& (2) \Rightarrow \underbrace{\begin{bmatrix} -\frac{9}{4} & \frac{5}{2} \\ -\frac{1}{2} & \frac{2}{3} \end{bmatrix}}_Y \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} 3 \\ -2 \end{bmatrix} \Rightarrow \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \underbrace{\frac{1}{-\frac{3}{2} + \frac{5}{4}} \begin{bmatrix} \frac{2}{3} & -\frac{5}{2} \\ \frac{1}{2} & -\frac{9}{4} \end{bmatrix}}_{Y^{-1}} \begin{bmatrix} 3 \\ -2 \end{bmatrix} = \begin{bmatrix} -28 \\ -24 \end{bmatrix}$$

$$\text{Hence, } i = \frac{e_1 - 12}{4} = \frac{-28 - 12}{4} = \boxed{-10A}$$

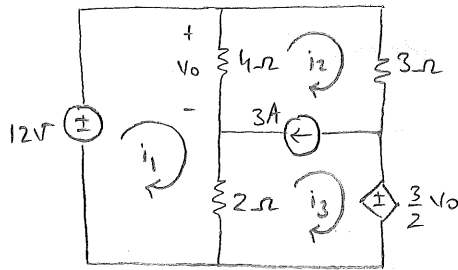Example

write mesh equations in matrix form
& find v_o .

$$\text{Mesh ① : } -12 + 4(i_1 - i_2) + 2(i_1 - i_3) = 0 \Rightarrow 6i_1 - 4i_2 - 2i_3 = 12 \quad (1)$$

$$\text{Supermesh ②+③ : } 4(i_2 - i_1) + 3i_2 + \frac{3}{2}v_o + 2(i_3 - i_1) = 0$$

$$v_o = 4(i_1 - i_2)$$

$$\Rightarrow 4(i_2 - i_1) + 3i_2 + 6(i_1 - i_2) + 2(i_3 - i_1) = 0 \Rightarrow i_2 + 2i_3 = 0 \quad (2)$$

$$\text{constraint : } i_2 - i_3 = 3 \quad (3)$$


$$(1), (2), (3) \Rightarrow \begin{bmatrix} 6 & -4 & -2 \\ 0 & 1 & 2 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 3 \end{bmatrix}$$

$$(3) \Rightarrow i_2 = i_3 + 3 \quad (4)$$

$$(2) \text{ and } (4) \Rightarrow (i_3 + 3) + 2i_3 = 0 \Rightarrow i_3 = -1A \xrightarrow{(4)} i_2 = 2A$$

$$(1) \Rightarrow 6i_1 - 4(2) - 2(-1) = 12 \Rightarrow i_1 = 3A$$

$$\Rightarrow v_o = 4(i_1 - i_2) = 4(3 - 2) = \boxed{4V}$$

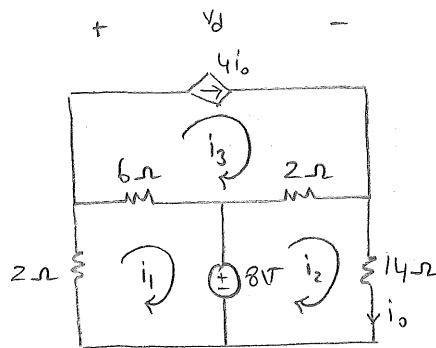Example

Find the power supplied / absorbed by the dependent source.

$$\text{Mesh ①: } 2i_1 + 6(i_1 - i_3) + 8 = 0 \Rightarrow 8i_1 - 6i_3 = -8 \quad (1)$$

$$\text{Mesh ②: } -8 + 2(i_2 - i_3) + 14i_2 = 0 \Rightarrow 16i_2 - 2i_3 = 8 \quad (2)$$

$$\text{Constraint: } \left. \begin{array}{l} i_3 = 4i_o \\ i_o = i_2 \end{array} \right\} i_3 = 4i_2 \quad (3)$$

$$(2) \& (3) \Rightarrow 16i_2 - 2(4i_2) = 8 \Rightarrow i_2 = 1A \xrightarrow{(3)} i_3 = 4A$$

$$(1) \Rightarrow 8i_1 = 6i_3 - 8 = 6(4) - 8 = 16 \Rightarrow i_1 = 2A$$

$$\text{KVL at outer loop: } v_d + 14i_2 + 2i_1 = 0 \Rightarrow v_d = -14i_2 - 2i_1 = -14 - 4 = -18V$$

$$\Rightarrow P_{\diamond} = v_d \cdot 4i_o = -18 \cdot 4(1) = -72W$$

$\Rightarrow$ Dep. source supplies 72W power.