
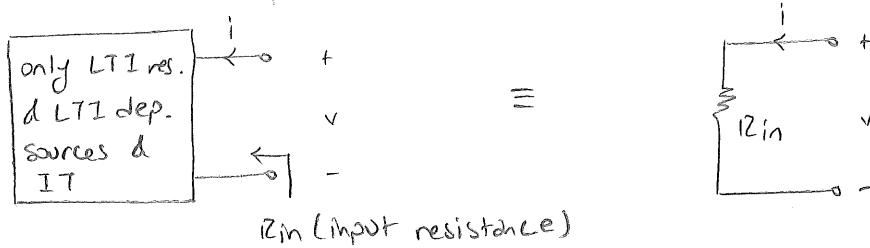
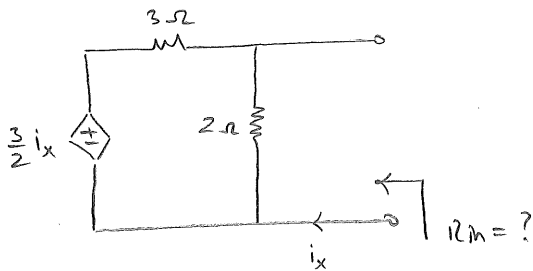
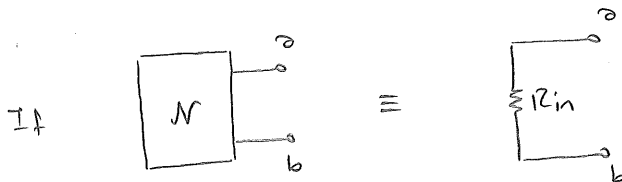
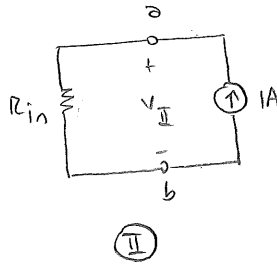


Input Resistances of LTI Resistive One-Ports


A one-port consisting only of ideal transformers, LTI resistors, and LTI dependent sources (whose control variables are within the one-port) is equivalent to a single LTI resistor.

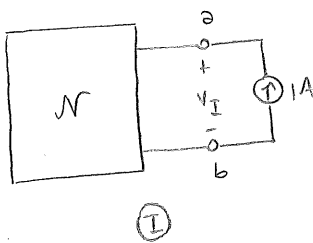ExampleIdea

then we must have $v_I = v_{II}$ for the following configurations




$R_{in} = \frac{v_{II}}{1} = v_I$ can be computed by solving the circuit in config. I
↓
unknown

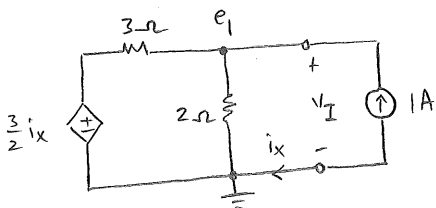Sol'n


$$\frac{e_1 - \frac{3}{2}i_x}{3} + \frac{e_1}{2} - 1 = 0 \quad \text{and} \quad i_x = -1A$$

$$\Rightarrow \frac{e_1 + 3/2}{3} + \frac{e_1}{2} - 1 = 0 \Rightarrow \frac{5}{6}e_1 = \frac{1}{2}$$

$$\Rightarrow e_1 = \frac{3}{5}V \Rightarrow v_I = \frac{3}{5}V \Rightarrow \boxed{R_{in} = \frac{3}{5} \Omega}$$

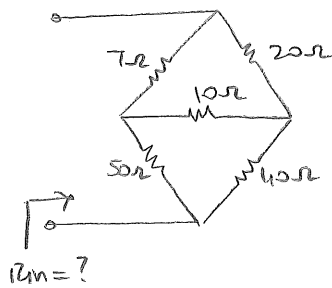Example

Sol'n Connect a test source

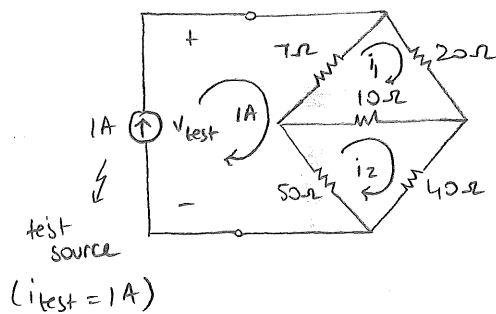

$$\text{Mesh ①: } 7(i_1 - 1) + 20i_1 + 10(i_1 - i_2) = 0$$

$$\Rightarrow 37i_1 - 10i_2 = 7 \quad (1)$$

$$\text{Mesh ②: } 50(i_2 - 1) + 10(i_2 - i_1) + 40i_2 = 0$$


$$\Rightarrow -10i_1 + 100i_2 = 50 \Rightarrow -i_1 + 10i_2 = 5 \quad (2)$$


$$(1) + (2) \Rightarrow 36i_1 = 12 \Rightarrow i_1 = \frac{1}{3}\text{A} \quad (2) \Rightarrow i_2 = \frac{8}{15}\text{A}$$

$$\text{Now, } V_{\text{test}} = 20i_1 + 40i_2 = 20 \cdot \frac{1}{3} + 40 \cdot \frac{8}{15} = 28\text{V}$$


$$\text{Then } R_{\text{in}} = \frac{V_{\text{test}}}{i_{\text{test}}} = \frac{28}{1} = \boxed{28\Omega}$$

Hence

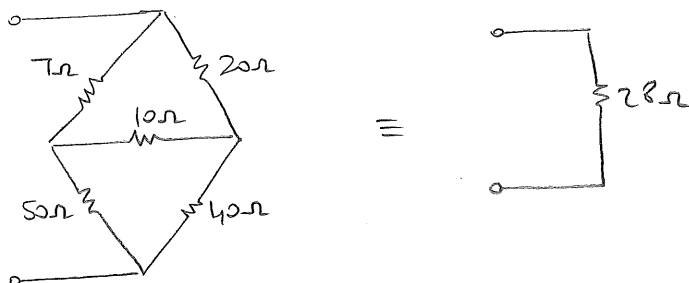

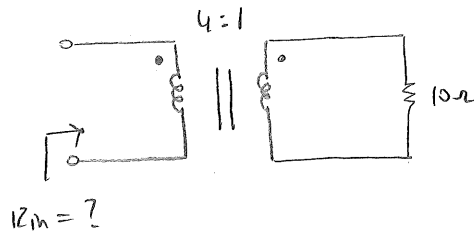
Example

Recall IT equations:

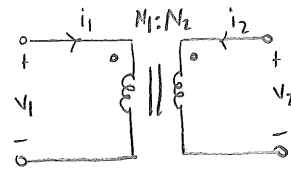

$$\frac{v_1}{N_1} = \frac{v_2}{N_2}$$

$$\& N_1 i_1 + N_2 i_2 = 0$$

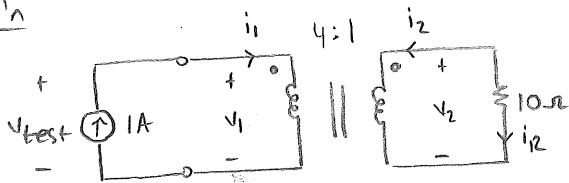Sol'n



We have $\begin{cases} \frac{v_1}{4} = v_2 & (1) \\ 4i_1 + i_2 = 0 & (2) \end{cases}$

Now, $i_1 = 1A \quad (2) \Rightarrow i_2 = -4A \Rightarrow i_2 = 4A \Rightarrow v_2 = 10i_R = 40V \quad (1) \Rightarrow v_1 = 160V$

$$\Rightarrow v_{test} = 160V$$

$$\Rightarrow R_{in} = \frac{v_{test}}{i_{test}} = \frac{160}{1} = 160\Omega$$

Here

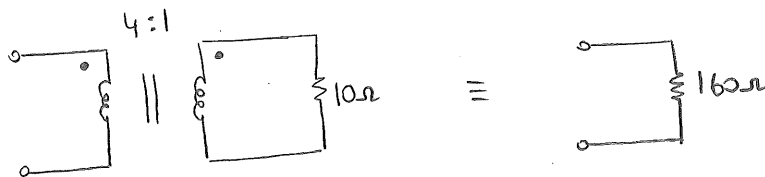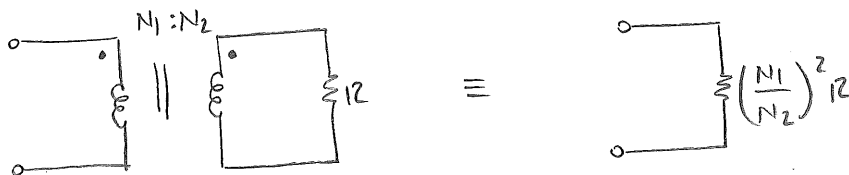
Exercise Show that in general we have

Linearity

Let $y(x_1, x_2, \dots, x_m)$ be a function of m variables $x_1, x_2, \dots, x_m$. This function is said to be linear if there exist real numbers $k_1, k_2, \dots, k_m$ such that $y(x_1, x_2, \dots, x_m) = k_1 x_1 + k_2 x_2 + \dots + k_m x_m$.

In an LTI resistive circuit each branch current/voltage is a linear function of the voltages of the ind. voltage sources and the currents of the ind. current sources.

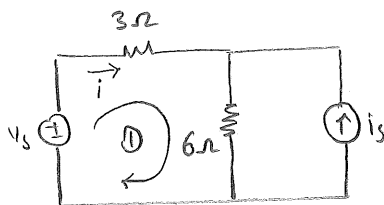Example For the below circuit find k_1 and k_2 such that




$$i = k_1 v_s + k_2 i_s$$

$$\text{KVL at } \textcircled{1} : -v_s + 3i + 6(i + i_s) = 0 \Rightarrow 9i = v_s - 6i_s \Rightarrow i = \frac{1}{9} v_s - \frac{2}{3} i_s$$

$$\Rightarrow k_1 = \frac{1}{9} \text{ and } k_2 = -\frac{2}{3}.$$

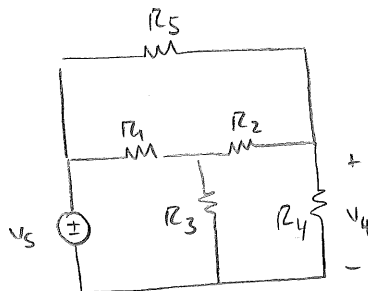Example

It has been measured that $v_4 = 9\text{V}$ when $v_s = 24\text{V}$.



Find v_4 a) when $v_s = -8\text{V}$

b) when $v_s = 36\text{V}$

Soln By linearity $v_s = -8\text{V} \Rightarrow v_4 = -3\text{V}$


& $v_s = 36\text{V} \Rightarrow v_4 = 13.5\text{V}$

Linearity allows us to solve LTI resistive circuits by superposition

Example

$$v_s = 20V$$

$$i_s = 4A$$

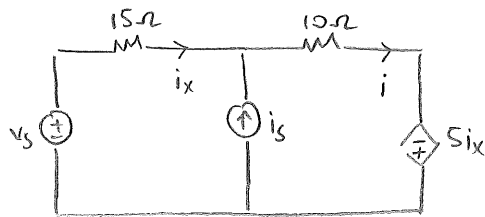

Find i by superposition (i.e. consider one ind. source at a time)


Sol'n Linearity implies $i = k_1 v_s + k_2 i_s$ (for some k_1, k_2)

$$\Rightarrow i = k_1 \cdot 20 + k_2 \cdot 4 = \underbrace{[k_1 \cdot 20 + k_2 \cdot 0]}_{i_1} + \underbrace{[k_1 \cdot 0 + k_2 \cdot 4]}_{i_2}$$


i_1 : the current passing through 10Ω resistor when $v_s = 20V$ and $i_s = 0$ (i.e. when ind. current source is killed)

i_2 : the current passing through 10Ω resistor when $i_s = 4A$ and $v_s = 0$ (i.e. when ind. voltage source is killed)

To compute i_1 , kill the current source

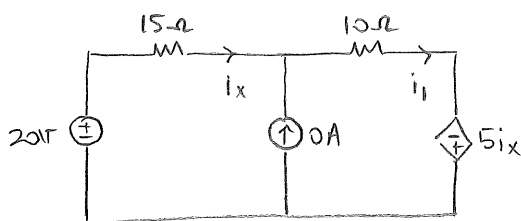

$\equiv$

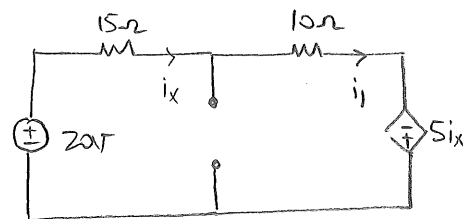


$$KVL: -20 + 15i_x + 10i_1 - 5i_x = 0 \quad (i_x = i_1)$$

$$\Rightarrow 20i_1 = 20$$

$$\Rightarrow \boxed{i_1 = 1A}$$

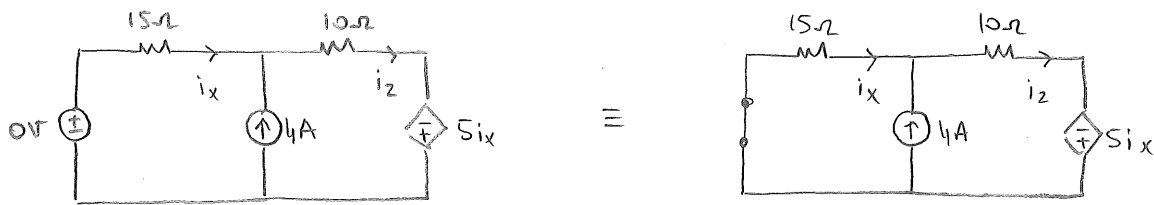To compute i_2 , kill the ind. voltage source



$$\text{KVL: } 15i_x + 10i_2 - 5i_x = 0 \quad (i_x = i_2 - 4)$$

$$\Rightarrow 20i_2 = 40$$

$$\Rightarrow \boxed{i_2 = 2\text{A}}$$


Finally, to find i we superpose i_1 and i_2 : $i = i_1 + i_2 = \boxed{3\text{A}}$

Remark killing an IVS means replacing it with short circuit.

killing an ICS means replacing it with open circuit.

Warning: Do NOT kill dependent sources!

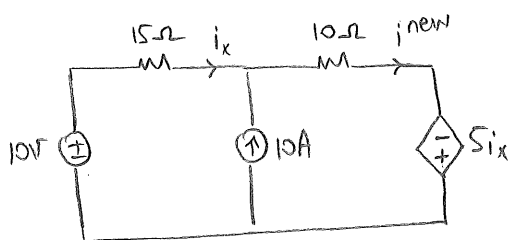Exercise Using your previous computations find i^{new}



$$\text{Answer: } i^{\text{new}} = \underbrace{i_1^{\text{new}}}_{\frac{1}{2}i_1} + \underbrace{i_2^{\text{new}}}_{\frac{5}{2}i_2} = \frac{11}{2}\text{A}$$