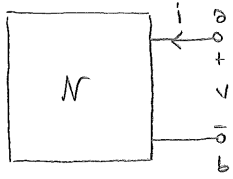


Thevenin & Norton Equivalent Circuits

Recall: two one-ports are equivalent if they have identical $i-v$ characteristics.


Thevenin's Theorem Consider the below one-port, where $\mathcal{N}$ is an LTI resistive circuit satisfying:



(A1) Any dep. source in $\mathcal{N}$ has its control var. also in $\mathcal{N}$.

(A2) One-port is both voltage- and current-controlled.

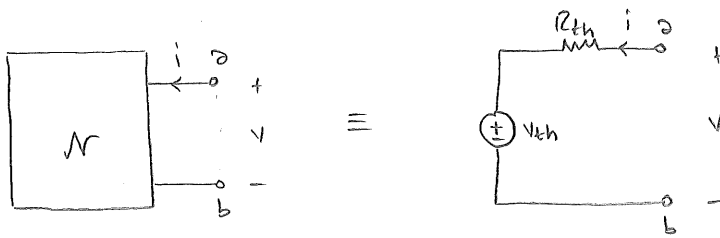
Then we can find v_{th} , R_{th} and establish the below equivalence



$i-v$ characteristics:

$$v = R_{th} i + v_{th} \quad (1)$$

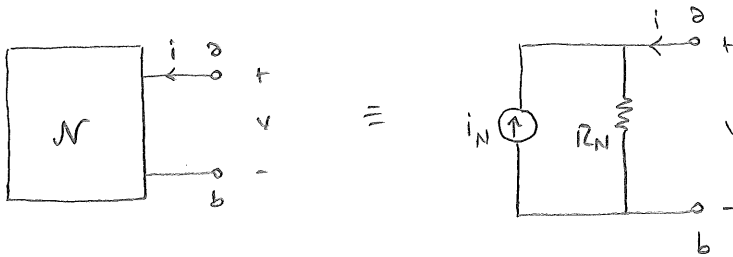Norton's Theorem Under the same conditions (A1) & (A2) we can find i_N , R_N and the below equivalence holds




$i-v$ characteristics:

$$v = R_N i + R_N i_N \quad (2)$$


Remark Since (1) $\equiv$ (2) we have to have $R_{th} = R_N$ and $v_{th} = R_{th} i_N$.

Computing v_{th} , i_N , R_{th} (for a given one-port $\mathcal{N}$)


1) Open circuit voltage equals v_{th} :

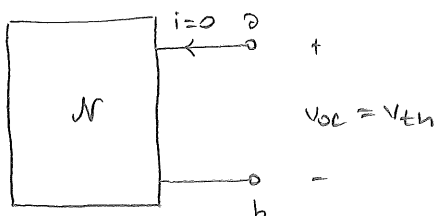


2) Short circuit current equals i_N :

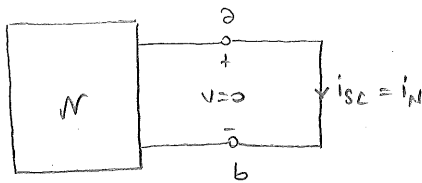

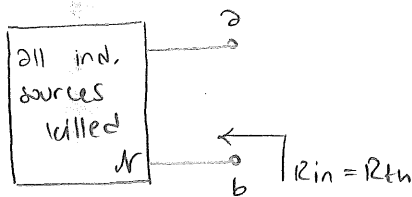3) Once v_{th} and i_N are known we have $R_{th} = v_{th}/i_N$. Another way to obtain R_{th} is to kill all independent sources within N and compute the input resistance:



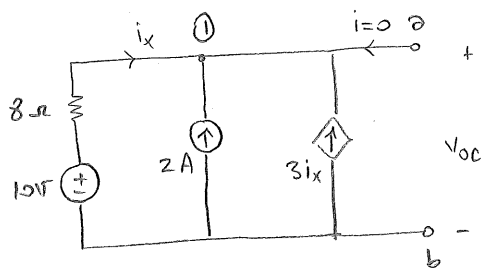Example Find the Thevenin and Norton equivalents of below one-port.




Step 1 Find the open-circuit voltage v_{oc} .

$$\text{KCL at } ①: i_x + 2 + 3i_x = 0 \Rightarrow i_x = -\frac{1}{2} \text{ A}$$

$$v_{oc} = -8i_x + 10 = 14 \text{ V}$$

$$\Rightarrow \boxed{v_{th} = 14 \text{ V}}$$

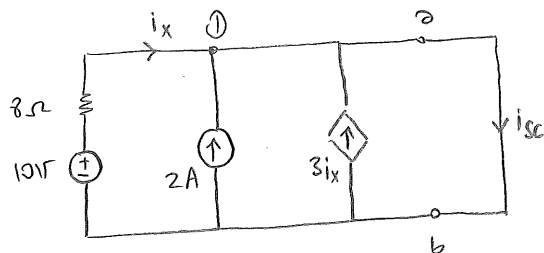Step 2 Find the short-circuit current i_{sc} .



$$\text{KVL at outer loop: } -10 + 8i_x = 0 \Rightarrow i_x = \frac{5}{4} \text{ A}$$


$$\text{KCL at } ①: i_x + 2 + 3i_x - i_{sc} = 0$$

$$\Rightarrow i_{sc} = 2 + 4i_x = 7 \text{ A}$$

$$\Rightarrow \boxed{i_N = 7 \text{ A}}$$

Step 3 Find R_{th} . $R_{th} = \frac{V_{th}}{i_N} = \frac{14}{7} \Rightarrow \boxed{R_{th} = 2\Omega}$

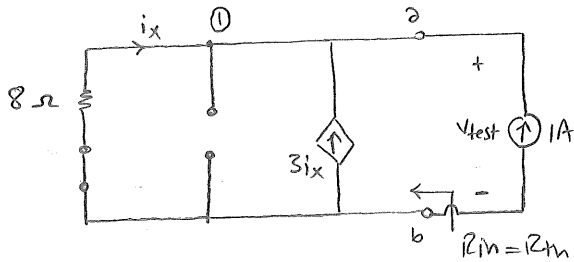Alternative way to compute R_{th} : Kill all ind. sources.




$$\text{KCL at } ①: i_x + 3i_x + 1 = 0$$

$$\Rightarrow i_x = -\frac{1}{4} \text{ A}$$


$$\Rightarrow V_{test} = -8i_x = 2 \text{ V}$$

$$\Rightarrow R_{in} = \frac{V_{test}}{1} = 2\Omega \Rightarrow R_{th} = 2\Omega$$

Therefore

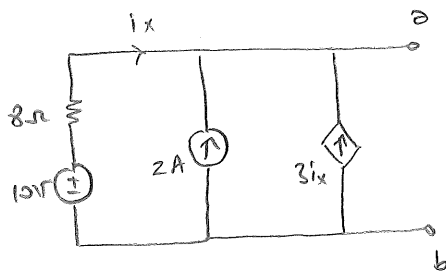


$\equiv$

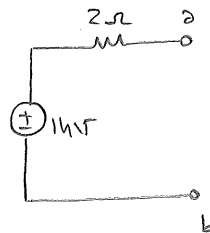

Thevenin Equiv.


$\equiv$

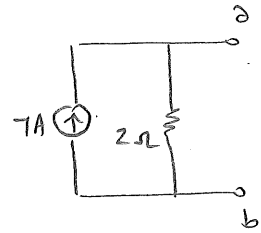


Norton Equiv.

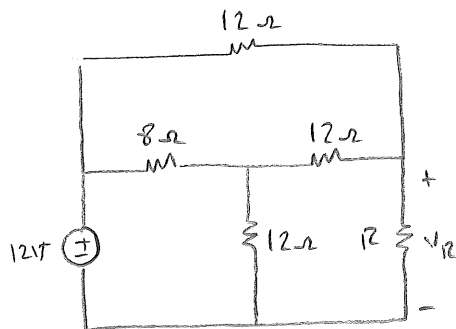Example Find the Thevenin equiv. circuit as viewed by the resistor R .

What should R be so that $V_R = 8 \text{ V}$?



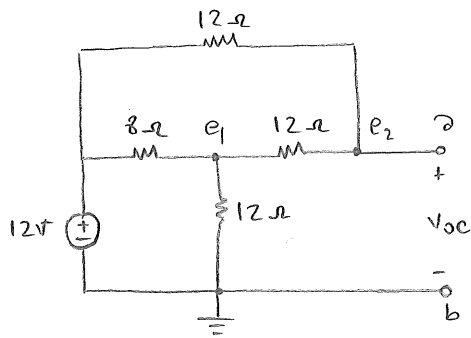Sol'n First. Remove 12Ω and find V_{oc} .



$$\text{Node ①: } \frac{e_1 - 12}{8} + \frac{e_1}{12} + \frac{e_1 - e_2}{12} = 0$$

$$\Rightarrow \frac{7}{24}e_1 - \frac{1}{12}e_2 = \frac{3}{2} \quad (1)$$


$$\text{Node ②: } \frac{e_2 - e_1}{12} + \frac{e_2 - 12}{12} = 0$$

$$\Rightarrow -\frac{1}{12}e_1 + \frac{1}{6}e_2 = 1 \quad (2)$$

$$(1) \& (2) \Rightarrow e_1 = 8V, e_2 = 10V$$

$$V_{oc} = e_2 \Rightarrow \boxed{V_{th} = 10V}$$

Then. Find i_{sc} .

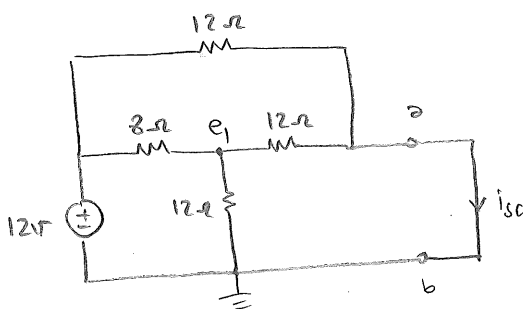


$$\text{Node ①: } \frac{e_1 - 12}{8} + \frac{e_1}{12} + \frac{e_1}{12} = 0$$

$$\Rightarrow \frac{7}{24}e_1 = \frac{3}{2} \Rightarrow e_1 = \frac{36}{7}V$$

$$\text{Node ②: } i_{sc} = \frac{e_1}{12} + \frac{12}{12} = \frac{3}{7} + 1 = \frac{10}{7}$$

$$\Rightarrow \boxed{i_N = \frac{10}{7}A} \quad \Rightarrow R_{th} = \frac{V_{th}}{i_N} = \frac{10}{10/7} = \boxed{7\Omega}$$

Finally.

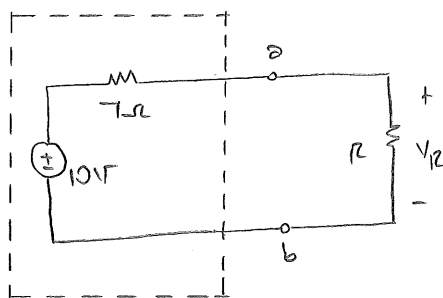

Thevenin equiv.

seen by 12Ω

Want: $V_R = 8V$.


Design parameter: R

$$V_R = \frac{R}{R + 7} \cdot 10 = 8$$

$$\Rightarrow \boxed{R = 28\Omega}$$

Maximum Power Transfer

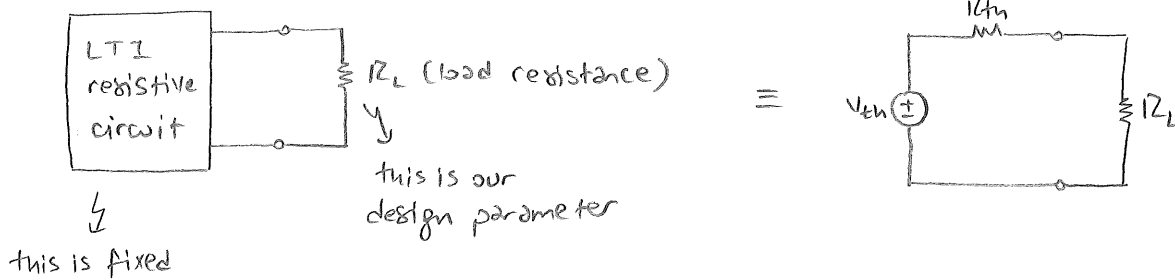There are many applications in circuit theory where it is desirable to extract maximum possible power from a given circuit.



Now, the power delivered to the load is: $P_L = R_L \left[\frac{V_{th}}{R_{th} + R_L} \right]^2$


P_L : function of R_L (since V_{th} & R_{th} are fixed)

Question: $P_{L, \max} = ?$


Answer: differentiate w.r.t. R_L .

$$\frac{dP_L}{dR_L} = \frac{V_{th}^2}{(R_L + R_{th})^2} - 2R_L \frac{V_{th}^2}{(R_L + R_{th})^3} = V_{th}^2 \left\{ \frac{(R_L + R_{th}) - 2R_L}{(R_L + R_{th})^3} \right\} = V_{th}^2 \frac{R_{th} - R_L}{(R_L + R_{th})^3}$$
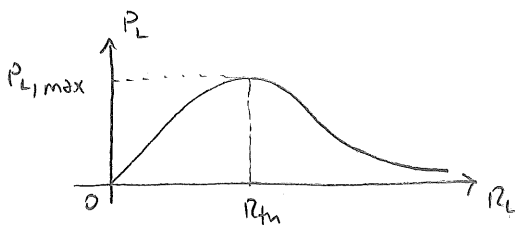
$$\frac{dP_L}{dR_L} = 0 \Rightarrow \boxed{R_L = R_{th}}$$




Conclusion For max power transfer to the load, R_L must equal R_{th} !

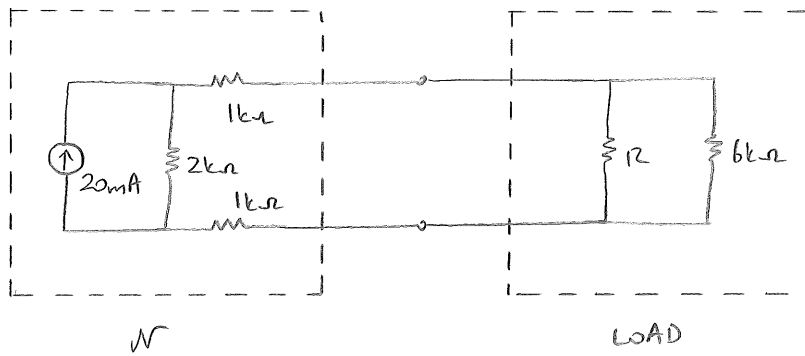Example

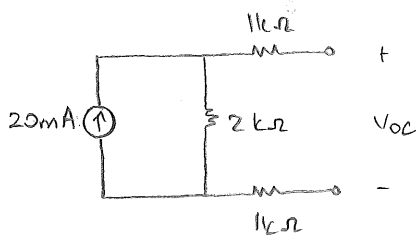
- a) Find R so that max power is delivered to the load.
 b) Find this max power.

Step 1 Find the Thevenin equiv. of the circuit N .




$$V_{oc} = (20\text{mA}) \times (2\text{k}\Omega) = 40\text{V}$$
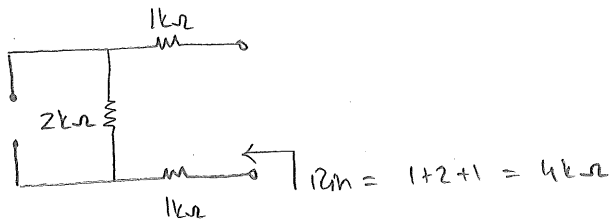
$$\Rightarrow \boxed{V_{th} = 40\text{V}}$$



$$\Rightarrow \boxed{R_{th} = 4\text{k}\Omega}$$

Step 2 Study the equiv. circuit

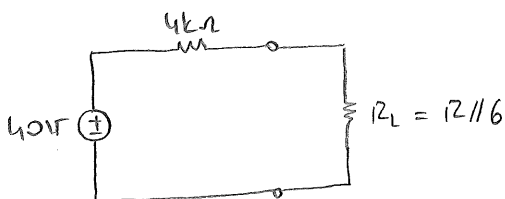

For max power transfer we need $R_L = 4\text{k}\Omega$

$$\Rightarrow \frac{1}{R} + \frac{1}{6} = \frac{1}{4} \Rightarrow \boxed{R = 12\text{k}\Omega}$$

$$P_{L, \max} = R_L \left(\frac{40}{4\text{k} + R_L} \right)^2 \bigg|_{R_L = 4\text{k}}$$

$$= 4\text{k} \left(\frac{40}{8\text{k}} \right)^2 = (4\text{k}\Omega) \times (5\text{mA})^2$$

$$= 4000 \times (5 \times 10^{-3})^2 = 0.1\text{W}$$

$$\Rightarrow \boxed{P_{L, \max} = 100\text{mW}}$$