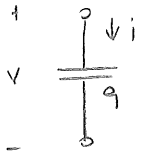



Ch. IV

First-Order Circuits


Capacitor A 2-terminal element that can store charge. The charge q it stores and the voltage v across its terminals satisfy a relation described by a curve on the q - v plane.




Ex

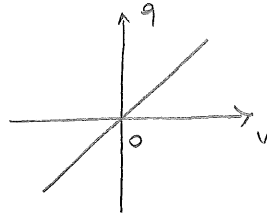

linear capacitor

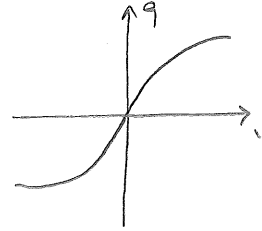

nonlinear cap.

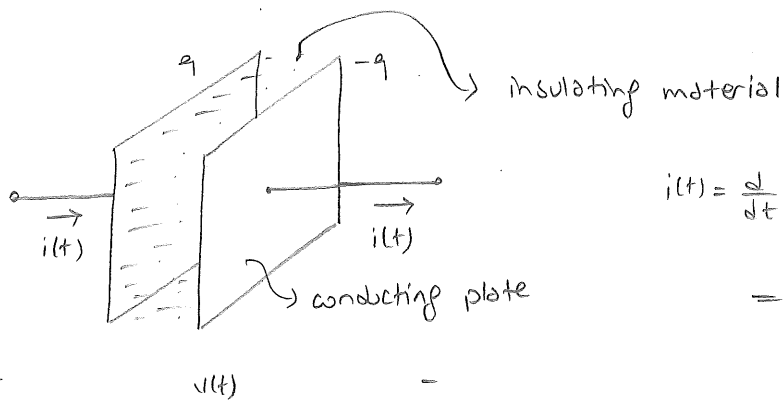

$$i(t) = \frac{d}{dt} q(t) \quad (\text{def. of current})$$

$$\Rightarrow q(t) = q(t_0) + \int_{t_0}^t i(z) dz$$

LTI Capacitor

$$q(t) = C v(t)$$

C : constant named capacitance, measured in Farads (F)

i - v relation?

$$i(t) = \frac{d}{dt} q(t) = \frac{d}{dt} \{ C v(t) \} = C \frac{dv(t)}{dt} \Rightarrow$$


$$i(t) = C \frac{dv(t)}{dt}$$

Equivalently, $v(t) = \frac{1}{C} q(t) = \frac{1}{C} \left\{ q(t_0) + \int_{t_0}^t i(z) dz \right\} \Rightarrow$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(z) dz$$

($v(t_0)$: initial voltage of the capacitor.)

Ex

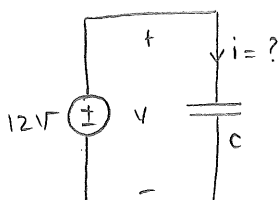

$$i = C \frac{dv}{dt} = 0$$

Therefore the capacitor behaves as open circuit under DC (constant) voltage.


power $p(t) = i(t)v(t)$

$$= C \frac{dv(t)}{dt} v(t) \quad \left\{ \quad p(t) = C v(t) \frac{dv(t)}{dt} \right.$$


stored energy ($C > 0$) $E(t) = \int_{-\infty}^t p(\tau) d\tau = \int_{v(-\infty)}^{v(t)} C v dv = \frac{1}{2} C v(t)^2$
 $\tau = 0$

Hence, the energy stored in an LTI capacitor: $E = \frac{1}{2} C v^2$

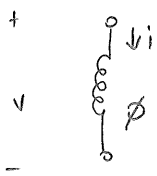
Inductor A 2-terminal element whose magnetic flux ϕ and current i satisfy a relation described by a curve on the ϕ - i plane.




Ex

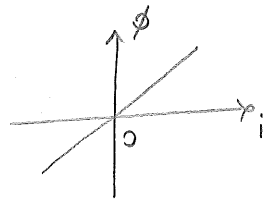

linear inductor

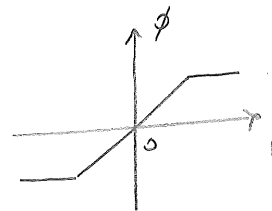

nonlinear inductor

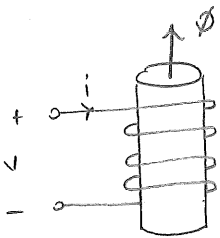

Faraday's Law: $v(t) = \frac{d}{dt} \phi(t)$

LTI inductor

$$\phi(t) = L i(t)$$

L : inductance, measured in Henries (H)

i - v relation?

$$v(t) = \frac{d}{dt} \phi(t) = \frac{d}{dt} \{ L i(t) \} = L \frac{di(t)}{dt} \Rightarrow v(t) = L \frac{di(t)}{dt}$$

Equivalently,

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

power $p(t) = v(t)i(t)$


$$= L \frac{di(t)}{dt} i(t) \quad \left\{ \quad p(t) = L i(t) \frac{di(t)}{dt} \right.$$

stored energy ($L > 0$) $E(t) = \int_{-\infty}^t p(z) dz = \int_{i(-\infty)}^{i(t)} L i di = \frac{1}{2} L i(t)^2$


$$\Rightarrow \boxed{E = \frac{1}{2} L i^2}$$

— o —

Capacitors in parallel connection

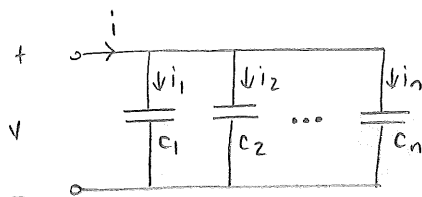

$$v(t_0) = v_0$$

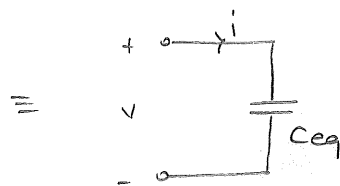

$$v(t_0) = v_0$$


$$i(t) = C_{eq} \frac{dv(t)}{dt}$$

? ?


$$i(t) = i_1(t) + i_2(t) + \dots + i_n(t) = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_n \frac{dv}{dt}$$

$$= \underbrace{[C_1 + C_2 + \dots + C_n]}_{C_{eq}} \frac{dv}{dt} \quad \Rightarrow \quad \boxed{C_{eq} = C_1 + C_2 + \dots + C_n}$$

Capacitors in series connection

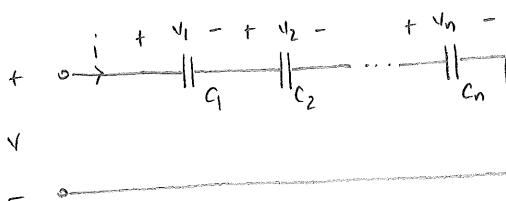
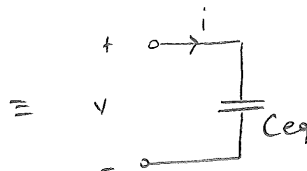
$$v_1(t_0) = v_{10}, v_2(t_0) = v_{20}, \dots, v_n(t_0) = v_{n0}$$



$$v(t_0) = v_1(t_0) + v_2(t_0) + \dots + v_n(t_0)$$


$$v(t) = v(t_0) + \frac{1}{C_{eq}} \int_{t_0}^t i(z) dz$$

? ?


$$v(t) = v_1(t) + v_2(t) + \dots + v_n(t) = \left\{ v_1(t_0) + \frac{1}{C_1} \int_{t_0}^t i(z) dz \right\} + \dots + \left\{ v_n(t_0) + \frac{1}{C_n} \int_{t_0}^t i(z) dz \right\}$$

$$= \underbrace{\{v_{10} + v_{20} + \dots + v_{n0}\}}_{v(t_0)} + \underbrace{\left[\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right]}_{\frac{1}{C_{eq}}} \int_{t_0}^t i(z) dz$$

$$\Rightarrow \boxed{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$

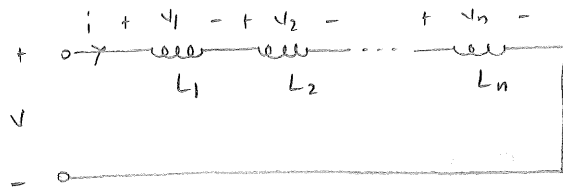Inductors in series connection

$$i(t_0) = I_0$$

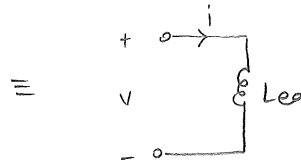


$$i(t_0) = I_0$$


$$V = L_{eq} \frac{di(t)}{dt}$$

$$V = V_1 + V_2 + \dots + V_n$$

$$= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_n \frac{di}{dt} = \underbrace{[L_1 + L_2 + \dots + L_n]}_{L_{eq}} \frac{di}{dt} \Rightarrow \boxed{L_{eq} = L_1 + L_2 + \dots + L_n}$$

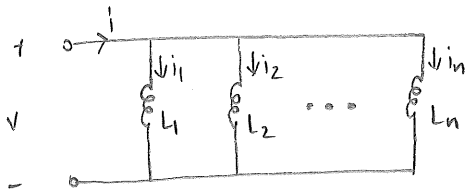Inductors in parallel connection
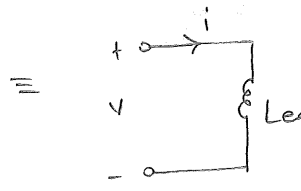
$$i_1(t_0) = I_{10}, \dots, i_n(t_0) = I_{n0}$$



$$i(t_0) = I_{10} + I_{20} + \dots + I_{n0}$$

$$i(t) = i(t_0) + \frac{1}{L_{eq}} \int_{t_0}^t v(z) dz$$

$$i(t) = i_1(t) + i_2(t) + \dots + i_n(t)$$


$$= \left\{ I_{10} + \frac{1}{L_1} \int_{t_0}^t v(z) dz \right\} + \dots + \left\{ I_{n0} + \frac{1}{L_n} \int_{t_0}^t v(z) dz \right\}$$

$$= \{ I_{10} + \dots + I_{n0} \} + \left[\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right] \int_{t_0}^t v(z) dz$$

$$\underbrace{\left[\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right]}_{\frac{1}{L_{eq}}}$$

$$\Rightarrow \boxed{\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}}$$

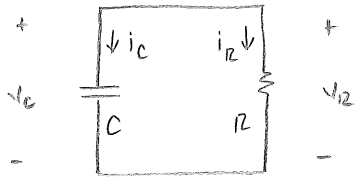Zero input response response of a circuit to initial conditions only. (No input.)



$$v_c(0) = V_0$$

$$v_c(t) = ? \text{ for } t \geq 0$$

$$(\text{Notation: } Df := \frac{d}{dt} f(t))$$

$$i_c = C Dv_c$$

$$\Rightarrow Dv_c = \frac{1}{C} i_c \quad \left. \begin{array}{l} \text{KCL} \end{array} \right\}$$

$$= -\frac{1}{C} i_R \quad \left. \begin{array}{l} \text{terminal eqn.} \end{array} \right\}$$

$$= -\frac{1}{C} \frac{v_R}{R} \quad \left. \begin{array}{l} \text{KVL} \end{array} \right\}$$

$$= -\frac{1}{RC} v_c$$

$$\Rightarrow Dv_c + \frac{1}{RC} v_c = 0 \quad (1)$$

Eqn. (1) is a first-order homogeneous (i.e. the right-hand side is zero) differential equation. (The right-hand side is zero because we have no input.) Solution to (1) is of the form $v_c(t) = Ke^{st}$ where K and s are to be determined.


$$\frac{d}{dt} \{ Ke^{st} \} + \frac{1}{RC} \{ Ke^{st} \} = 0 \Rightarrow sKe^{st} + \frac{1}{RC} Ke^{st} = 0$$

$$\Rightarrow \left[s + \frac{1}{RC} \right] Ke^{st} = 0 \Rightarrow s = -\frac{1}{RC} : \text{"natural frequency"}$$

Then $v_c(t) = Ke^{-t/RC}$ for $t \geq 0$. How about K ?

$$\text{Initial cond. constraint: } V_0 = v_c(0) = Ke^{-t/RC} \Big|_{t=0} = K \Rightarrow K = V_0$$

Hence
$$v_c(t) = V_0 e^{-t/RC}$$

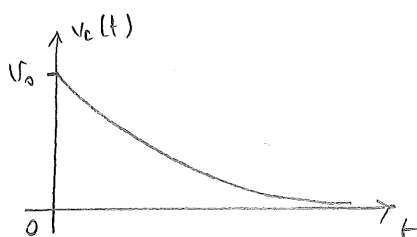



Remark $\tau = RC$ is sometimes called the "time constant." Note that the smaller the time constant the faster the response.

How about $i_L(t)$, $i_R(t)$?


$$i_L(t) = C \frac{d}{dt} v_C(t) = C \frac{d}{dt} \left\{ v_0 e^{-t/\tau} \right\} = -\frac{v_0}{\tau} e^{-t/\tau}$$

$$i_R(t) = \frac{v_R(t)}{R} = \frac{v_C(t)}{R} = \frac{v_0}{R} e^{-t/\tau}$$

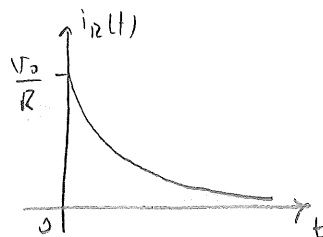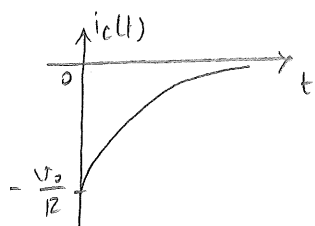Note that $i_L(t) + i_R(t) = 0$ (KCL) as expected.



Example Find $i_L(t)$ for $t \geq 0$.

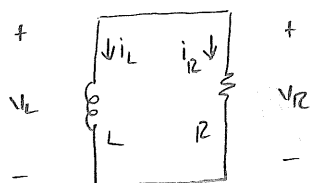

$$i_L(0) = I_0$$

$$v_L = \frac{1}{L} \int i_L dt = \frac{1}{L} \int i_R dt = \frac{1}{L} R i_R = -\frac{R}{L} i_L$$

$$\Rightarrow D i_L + \frac{R}{L} i_L = 0$$

Natural freq. $s = -\frac{R}{L} \Rightarrow i_L(t) = K e^{-\frac{R}{L}t}$, $K = ?$

Init. cond. constraint: $i_L(0) = I_0 \Rightarrow K = I_0$

$$\Rightarrow i_L(t) = I_0 e^{-\frac{R}{L}t}$$


(Sometimes we write $i_L(t) = I_0 e^{-t/\tau}$ where $\tau = \frac{L}{R}$ is the time constant.)

— o —

Zero-state response Response of a circuit with zero init. cond. to an input.

Example [constant input]

For $t > 0$ we can write

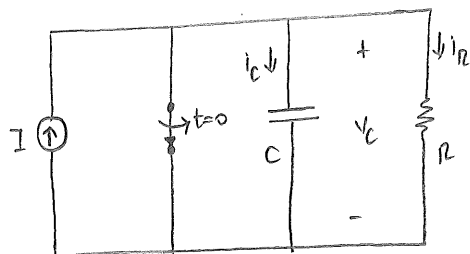

$$\left. \begin{aligned} v_C &= \frac{1}{C} \int i_C dt \\ &= \frac{1}{C} (I - i_R) \\ &= \frac{1}{C} \left(I - \frac{v_C}{R} \right) \end{aligned} \right\} v_C + \frac{1}{RC} v_C = \frac{I}{C} \quad (*)$$

input term

Solution to (*) is of the form: $v_C(t) = v_h(t) + v_p(t)$

homogeneous solution particular solution

Note that $v_C(0) = 0$

"zero initial condition"

To find $v_h(t)$ ignore the right-hand side (i.e. consider the homogeneous diff. eqn.)

$$DV_c + \frac{1}{RC} v_c = 0 \Rightarrow \underbrace{v_h(t) = K e^{-t/RC}}_{\text{hmp. solution (K to be determined later)}}$$

$$\text{Natural freq.} = -\frac{1}{RC} \quad (\text{time constant} = RC)$$

to find $v_p(t)$ v_p has the same "form" as input. [ex input constant $\Rightarrow v_p$ constant]

Hence let $v_p(t) = A$ (constant)

Substitute $v_p(t)$ in the diff. eqn.

$$\frac{d}{dt} v_p(t) + \frac{1}{RC} v_p(t) = \frac{1}{C} \quad \bigg|_{v_p(t)=A} \Rightarrow \frac{A}{RC} = \frac{1}{C} \Rightarrow A = 1R$$

$$\Rightarrow v_p(t) = 1R$$

Now, the overall solution: $v_c(t) = v_h(t) + v_p(t) = K e^{-t/RC} + 1R$ (K yet unknown)

To find K, use the init. cond. constraint:

$$K e^{-t/RC} + 1R \bigg|_{t=0} = v_c(0) = 0 \Rightarrow K = -1R$$

Finally, $\boxed{v_c(t) = 1R(1 - e^{-t/RC})}$

