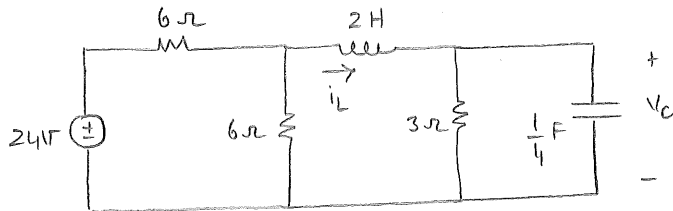


Definition A circuit is said to be in DC steady state if all its branch currents and branch voltages are constant.

Example The following circuit has reached DC steady state. Find v_C and i_L .




Sol'n Observe that in DC steady state

$$i_L(t) = \text{constant} \Rightarrow v_L(t) = L \frac{di_L(t)}{dt} = 0$$

$$v_C(t) = \text{constant} \Rightarrow i_C(t) = C \frac{dv_C(t)}{dt} = 0$$

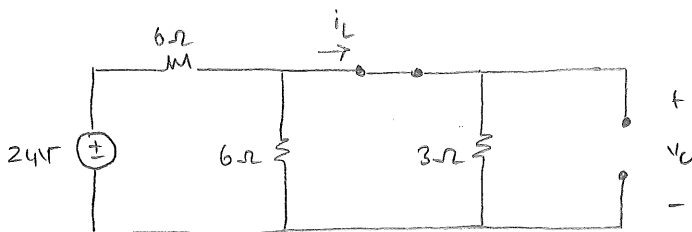Therefore we can consider the following circuit.




$$\Rightarrow i_L(t) = 2A \quad \text{and} \quad v_C(t) = 6V$$

in DC steady state.


Remark In DC steady state inductors behave as short circuit and capacitors as open circuit.

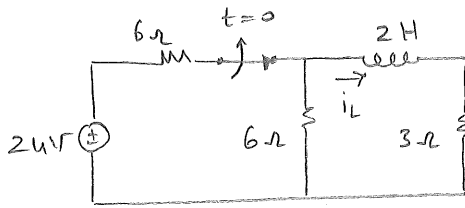Example The circuit is initially (switch closed) in DC steady state. Find $i_L(t)$ for $t > 0$ (switch open).



Sol'n $i_L(0) = 2A$ (from previous example)

For $t > 0$ we have

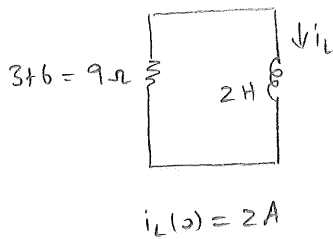


$$i_L(t) = i_L(0) e^{-t/\tau}$$


$$\text{time constant } \tau = \frac{L}{R} = \frac{2}{9} \text{ s}$$

$$\Rightarrow i_L(t) = 2e^{-9t/2} \text{ A}$$


Example Find $i_L(t)$ for $t \geq 0$.

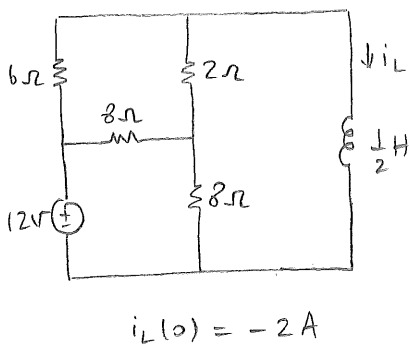

Step 1 Find Thevenin / Norton equiv.

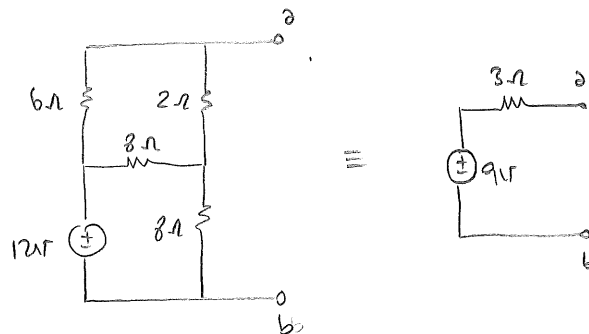

Step 2 Consider the equiv. circuit

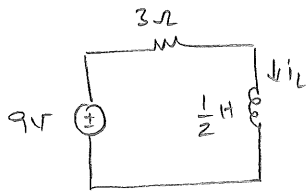

$$i_L(0) = -2A$$

$$9 = 3i_L + \frac{1}{2} \frac{di_L}{dt} \Rightarrow \frac{di_L}{dt} + 6i_L = 18 \quad (1)$$

$$\Rightarrow \text{not. freq. } s = -6$$

$$\Rightarrow \text{hmf: sol'n } i_h(t) = Ke^{-6t}$$

$$i_p(t) = ? \quad i_p(t) = \text{constant} \quad (\text{because the right-hand side of (1) is constant})$$


$$(1) \Rightarrow \cancel{\frac{d}{dt}} i_p + 6i_p = 18 \Rightarrow i_p(t) = 3$$

$$\Rightarrow i_L(t) = i_p(t) + i_h(t) = 3 + Ke^{-6t}$$

$$\underline{K = ?} \quad i_L(0) = -2 \Rightarrow 3 + Ke^{-6t} \Big|_{t=0} = -2 \Rightarrow K = -5$$

$$\Rightarrow i_L(t) = 3 - 5e^{-6t} \text{ A}$$

Step 2 (Alternative)

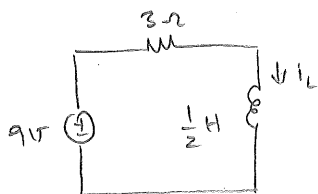

$$i_L(0) = -2 \text{ Amps}$$


$$i_L(t) = A + Be^{-t/\tau} \quad (A, B, \tau = ?)$$

$$\tau = \frac{L}{R} = \frac{1/2}{3} = \frac{1}{6} \text{ s}$$

$$\Rightarrow i_L(t) = A + Be^{-6t}$$

Note that as $t \rightarrow \infty$ $i_L(t) \rightarrow A \Rightarrow i_L(t)$ becomes constant $\Rightarrow$ circuit reaches DC steady state

$t = \infty$

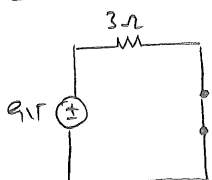


$$i_L(\infty) = 3 \text{ Amps} \Rightarrow A = 3 \Rightarrow i_L(t) = 3 + Be^{-6t}$$

finally find B by using init. cond. constraint


$$i_L(0) = -2 \text{ Amps} \Rightarrow 3 + Be^{-6t} \Big|_{t=0} = -2 \Rightarrow B = -5 \Rightarrow i_L(t) = 3 - 5e^{-6t} \text{ Amps}$$

Example Find $i_x(t)$ for $t \geq 0$.

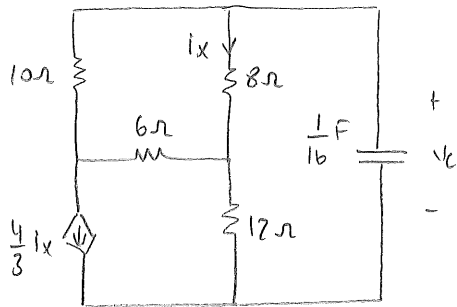


$$v_c(0) = 6V$$

Step 1 Find R_{Th} .

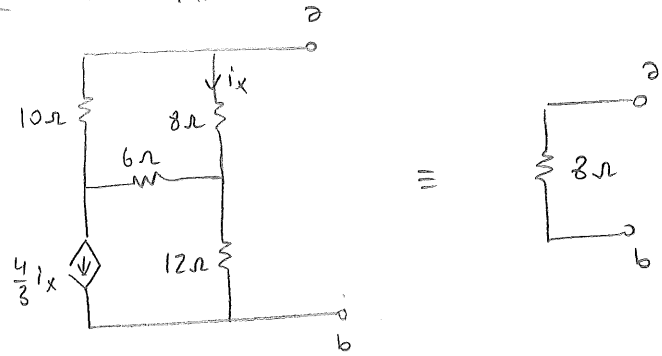

Step 2 Solve the RC circuit

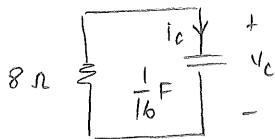


$$v_c(0) = 6V$$

$$\Rightarrow v_c(t) = v_c(0) e^{-t/RC} = 6 e^{-2t} V$$

$$\Rightarrow i_c(t) = C \frac{dv_c(t)}{dt} = \frac{1}{16} \{-12 e^{-2t}\} = -\frac{3}{4} e^{-2t} A$$

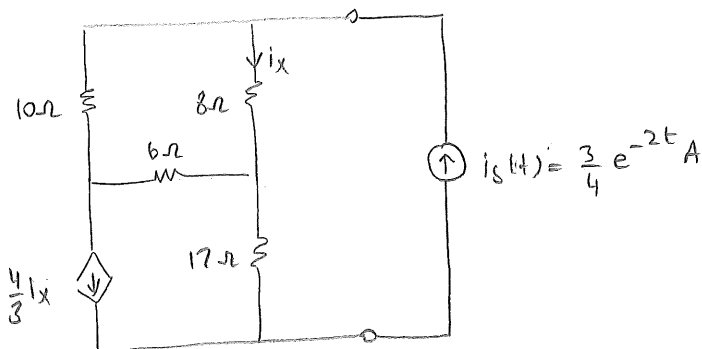
Step 3 Substitute capacitor with an ind. source and solve for i_x .



$$\Rightarrow i_x = \frac{1}{2} i_s$$


$$\Rightarrow i_x(t) = \frac{3}{8} e^{-2t} A$$

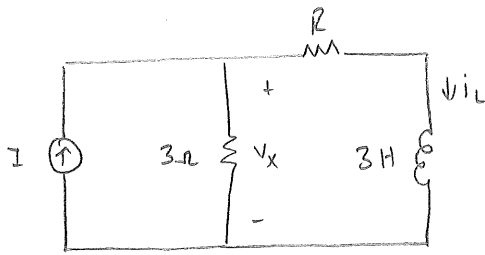Example Consider the below circuit where I is constant. Find $i_L(0)$, I , R .



$$v_x(t) = 12 - 9e^{-3t} \text{ V} \quad (1)$$

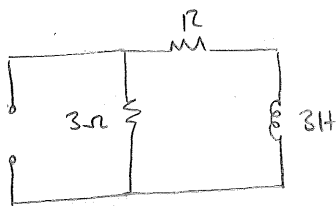Sol'n Note that (1) $\Rightarrow \tau = \frac{1}{3} \text{ s}$. Since the time constant τ does not depend on the input consider the input-free circuit. (I.e. kill the current source.)




$$\equiv R+3 \quad \Rightarrow \quad \tau = \frac{3}{R+3} = \frac{1}{3}$$

$$\Rightarrow \boxed{R = 6 \Omega}$$

This circuit & the original circuit have the same τ

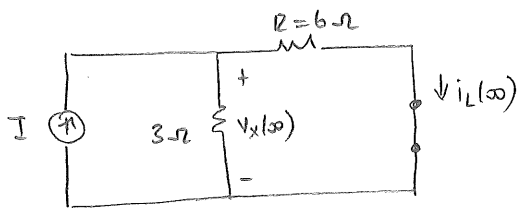$t = \infty$ At $t = \infty$ circuit reaches DC steady state. (I.e. inductor becomes short circuit.)




$$(1) \Rightarrow v_x(\infty) = 12 \text{ V}$$

$$v_x(\infty) = I \times (6 \parallel 3) = 2I$$

$$\Rightarrow \boxed{I = 6 \text{ A}}$$

$t = 0$

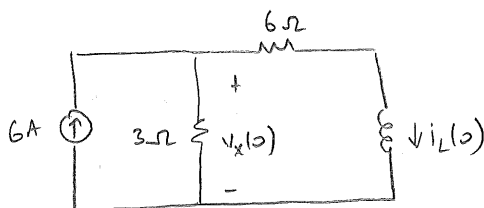

$$\text{KCL} \Rightarrow 6 = \frac{v_x(0)}{3} + i_L(0)$$

$$\Rightarrow \boxed{i_L(0) = 5 \text{ A}}$$

$$(1) \Rightarrow v_x(0) = 3 \text{ V}$$