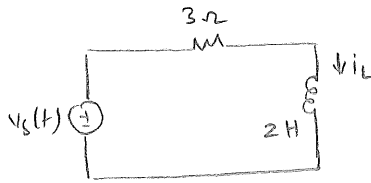


Ch. 17

Sinusoidal Steady State AnalysisExample (revisited)

$$v_s(t) = 10 \cos 2t \text{ V}$$

$$i_L(0) = 0$$

$$\text{Diff. eqn. } \frac{di_L}{dt} + \frac{3}{2} i_L = 5 \cos 2t, \quad \text{Nat. freq. } s = -\frac{3}{2}$$

$$\text{Sol'n } i_L(t) = -\frac{6}{5} e^{-\frac{3}{2}t} + \frac{6}{5} \cos 2t + \frac{8}{5} \sin 2t \text{ A}$$

$\underbrace{\hspace{10em}}$
 transient part (hmf. sol'n) sinusoidal steady state part (particular sol'n)

Question : Can we compute SSS solution without solving the diff. eqn?

Answer : YES!

— o —

Consider an LTI circuit such that

→ Each natural freq. $\lambda_i = \alpha_i + j\omega_i$ satisfies $\text{Re}\{\lambda_i\} = \alpha_i < 0$. This implies that the hmf. sol'n always decays to zero, regardless of the init. cond.

→ The inputs are sinusoidal signals at the same frequency ω rad/sec.

In such a circuit the response converges to the particular solution which is also a sinusoid with frequency ω (the freq. of the inputs). This solution is called the sinusoidal steady state (SSS) solution.

Some useful identities

1) $e^{j\phi} = \cos\phi + j\sin\phi$ (Euler's identity)

2) $\text{Re}\{z_1 + z_2\} = \text{Re}\{z_1\} + \text{Re}\{z_2\}$

3) $\text{Re}\{Df(t)\} = D\text{Re}\{f(t)\}$


4) Let $\omega \neq 0$ be real. If $\text{Re}\{x_1 e^{j\omega t}\} = \text{Re}\{x_2 e^{j\omega t}\}$ for all $t \in \mathbb{R}$ then $x_1 = x_2$.

proof $t=0 \Rightarrow \text{Re}\{x_1\} = \text{Re}\{x_2\} \quad (*)$

$t = \frac{3\pi}{2\omega} \Rightarrow \text{Re}\{-jx_1\} = \text{Re}\{-jx_2\} \Rightarrow \text{Im}\{x_1\} = \text{Im}\{x_2\} \quad (**)$

$(*) \& (**) \Rightarrow x_1 = x_2$

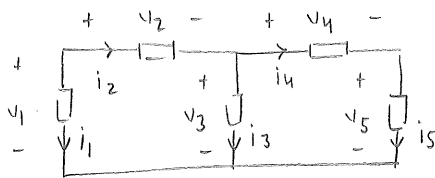consider a circuit in sinusoidal steady state



(input frequency = ω rad/sec)

Since the circuit is in SSS, each voltage/current signal should look like

$$x_k(t) = A_k \cos(\omega t + \phi_k) \text{ for some magnitude } A_k \text{ and phase } \phi_k.$$

Definition For a signal $x_k(t) = A_k \cos(\omega t + \phi_k)$, the complex number


$X_k := A_k e^{j\phi_k}$ is called the phasor of $x_k(t)$.

Note that given the pair (X_k, ω) we can reconstruct the signal $x_k(t)$ as


$\swarrow \quad \searrow$
 phasor of $x_k(t)$ the operating freq. of the circuit

$$x_k(t) = \operatorname{Re}\{X_k e^{j\omega t}\} = A_k \cos(\omega t + \phi_k)$$

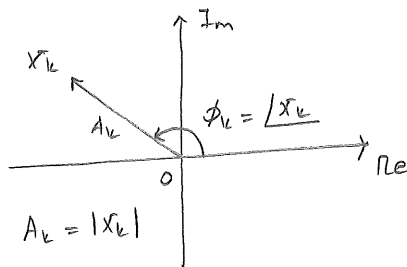Phasor diagram contains the vector representation of X_k on the complex plane:



Example [circuit in SSS]

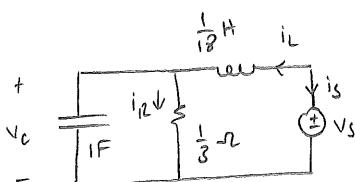

$$v_s(t) = \cos 3t \text{ V}$$

Signals

$$i_L(t) = 6 \cos 3t \text{ A}$$

$$i_R(t) = 3\sqrt{2} \cos(3t - \frac{\pi}{4}) \text{ A}$$

$$i_C(t) = 3\sqrt{2} \cos(3t + \frac{\pi}{4}) \text{ A}$$

$$i_S(t) = -6 \cos 3t \text{ A}$$

$$v_L(t) = -\sin 3t = \cos(3t + \frac{\pi}{2}) \text{ V}$$

$$v_R(t) = \sqrt{2} \cos(3t - \frac{\pi}{4}) \text{ V}$$

$$v_C(t) = \sqrt{2} \cos(3t + \frac{\pi}{4}) \text{ V}$$

$$v_S(t) = \cos 3t \text{ V}$$

Phasors

$$I_L = 6e^{j0} = 6 \text{ A}$$

$$I_R = 3\sqrt{2} e^{-j\frac{\pi}{4}} = 3 - j3 \text{ A}$$

$$I_C = 3\sqrt{2} e^{j\frac{\pi}{4}} = 3 + j3 \text{ A}$$


$$I_S = 6e^{j\pi} = -6 \text{ A}$$

$$V_L = e^{j\frac{\pi}{2}} = j \text{ V}$$


$$V_R = \sqrt{2} e^{-j\frac{\pi}{4}} = 1 - j \text{ V}$$

$$V_C = \sqrt{2} e^{j\frac{\pi}{4}} = 1 + j \text{ V}$$

$$V_S = e^{j0} = 1 \text{ V}$$

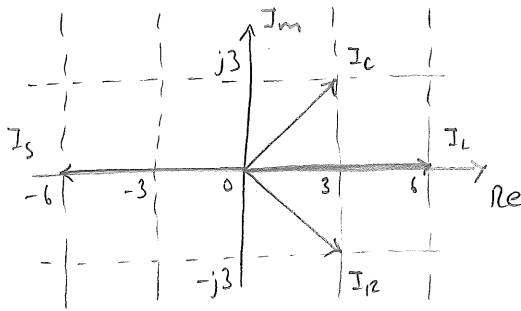Phasor Diagram

Note: $I_L = I_{L1} + I_{L2}$ (KCL?)

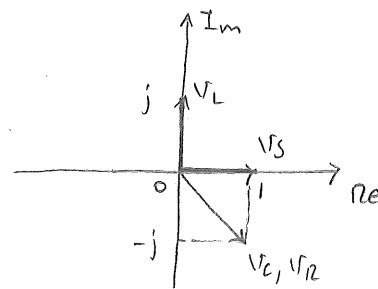

Note: $V_S = V_L + V_R$ (KVL?)

Claim Phasors of currents obey KCL.

Proof Let some currents satisfy KCL: $i_1(t) + i_2(t) + \dots + i_n(t) = 0$


$$\Rightarrow \operatorname{Re}\{I_1 e^{j\omega t}\} + \operatorname{Re}\{I_2 e^{j\omega t}\} + \dots + \operatorname{Re}\{I_n e^{j\omega t}\} = 0$$

$$\Rightarrow \operatorname{Re}\{I_1 e^{j\omega t} + I_2 e^{j\omega t} + \dots + I_n e^{j\omega t}\} = 0$$

$$\Rightarrow \operatorname{Re}\{(I_1 + I_2 + \dots + I_n) e^{j\omega t}\} = 0$$

$$\Rightarrow I_1 + I_2 + \dots + I_n = 0 \quad \square$$

Likewise, phasors of voltages obey KVL.

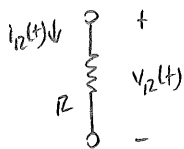Terminal Equations in PhasorsResistor

(belongs to a circuit in SSS)
at freq. ω rad/sec

$$v_R(t) = \operatorname{Re}\{V_R e^{j\omega t}\}, \quad V_R: \text{phasor of } v_R(t)$$

$$i_R(t) = \operatorname{Re}\{I_R e^{j\omega t}\}, \quad I_R: \text{phasor of } i_R(t)$$


$$\underline{V_R \sim I_R?}$$

$$v_R(t) = R i_R(t)$$


$$\Rightarrow \operatorname{Re}\{V_R e^{j\omega t}\} = R \cdot \operatorname{Re}\{I_R e^{j\omega t}\}$$

$$= \operatorname{Re}\{R I_R e^{j\omega t}\} \Rightarrow \boxed{V_R = R I_R}$$

phasor diagram:

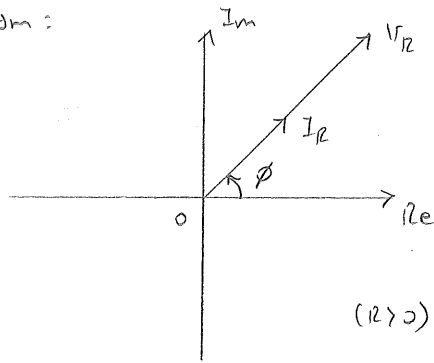

Both V_R and I_R have the same phase (ϕ). Such signals are said to be in phase.

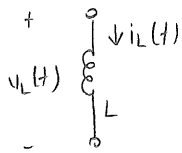Inductor

$$v_L(t) = \text{Re}\{V_L e^{j\omega t}\}$$


$$i_L(t) = \text{Re}\{I_L e^{j\omega t}\}$$

$$v_L(t) = L \frac{di_L(t)}{dt} \Rightarrow \text{Re}\{V_L e^{j\omega t}\} = L \frac{d}{dt} \text{Re}\{I_L e^{j\omega t}\}$$


$$= \text{Re}\{L I_L j\omega e^{j\omega t}\}$$

$$= \text{Re}\{j\omega L I_L e^{j\omega t}\}$$
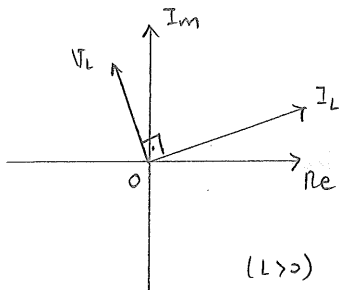
$$\Rightarrow \boxed{V_L = j\omega L I_L}$$




The current phasor I_L lags the voltage phasor V_L by 90° . (or voltage leads current by 90° .)

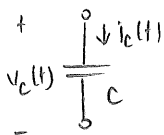Capacitor

$$v_C(t) = \text{Re}\{V_C e^{j\omega t}\}$$

$$i_C(t) = \text{Re}\{I_C e^{j\omega t}\}$$
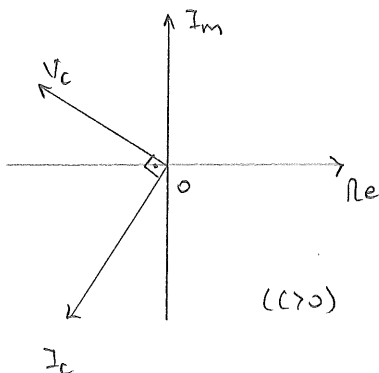
$$\text{Dual of inductor} \Rightarrow \boxed{I_C = j\omega C V_C}$$




The current leads the voltage by 90° .
(or, voltage lags current by 90° .)

Impedance & Admittance

Consider a one-port that

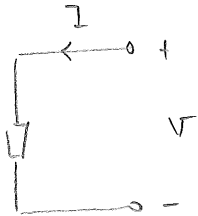- is part of a circuit in SSS
- contains no independent sources
- contains the control variables of its dependent sources



(I, V : phasors)

we define:

Impedance $Z := \frac{V}{I} = |Z|e^{j\theta_Z} = |Z| \angle \theta_Z$ (measured in ohms)

admittance $Y := \frac{I}{V} = \frac{1}{Z}$ (measured in mhos Ω^{-1})

Remark Impedance is the generalization of resistance in phasor domain. It is a function of the operating frequency ω .

Impedance Z in rectangular form : $Z = R + jX$

$R = \operatorname{Re}\{Z\}$: resistance

$X = \operatorname{Im}\{Z\}$: reactance

Likewise, $Y = G + jB$


$G = \operatorname{Re}\{Y\}$: conductance

$B = \operatorname{Im}\{Y\}$: susceptance


Note : $R \neq \frac{1}{G}$ & $X \neq \frac{1}{B}$ in general!

We have



Component	Impedance	Admittance
R	$Z_R = R$	$Y_R = \frac{1}{R}$
L	$Z_L = j\omega L$	$Y_L = \frac{1}{j\omega L}$
C	$Z_C = \frac{1}{j\omega C}$	$Y_C = j\omega C$

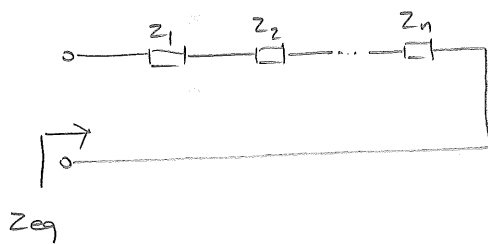Series & parallel connections

$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n$$

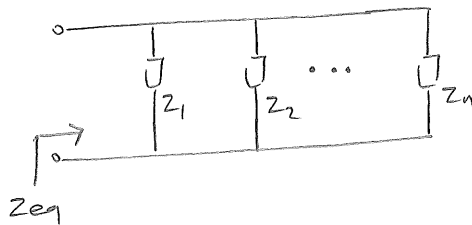


$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$

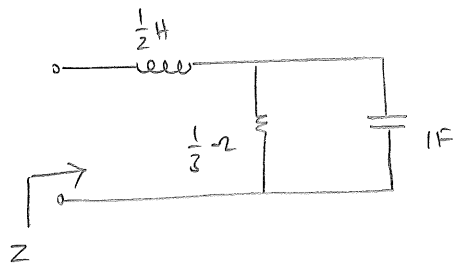
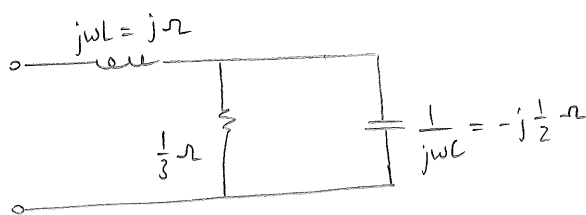
ExampleFind Z for $\omega = 2 \text{ rad/sec}$ Sol'n

$$\begin{aligned} & \left[j2 \right] \parallel \left[\frac{1}{3} \parallel -j\frac{1}{2} \right] = \frac{1}{\frac{1}{3+j2}} \\ & = \frac{3}{13} - j\frac{2}{13} \Omega \end{aligned}$$



$$\equiv \left[j2 \right] \parallel \left[\frac{3}{13} - j\frac{2}{13} \right] = \frac{3}{13} + j\frac{11}{13} \Omega$$

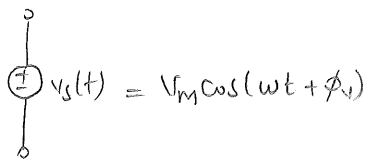Independent Sources (in SSS)

in phasor
domain $\rightarrow$

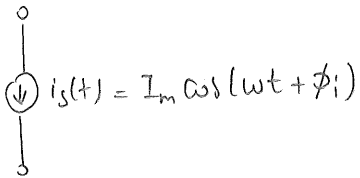
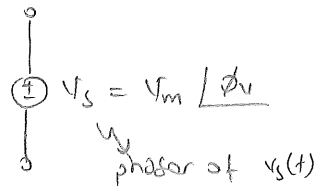


P.D. $\rightarrow$

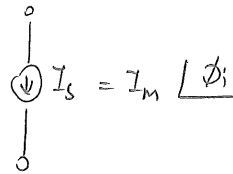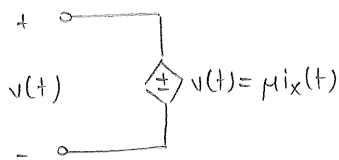
Dependent Sources

i_x : control current

P.D. $\rightarrow$

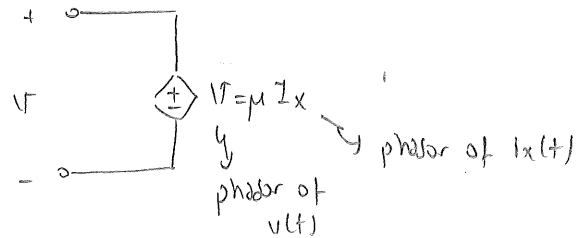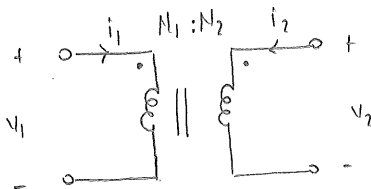Ideal transformer

P.D. $\rightarrow$

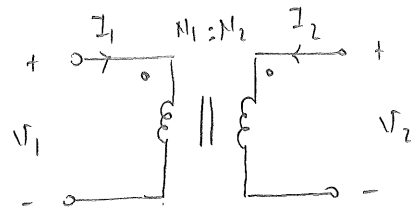

$$\frac{v_1}{N_1} = \frac{v_2}{N_2} \quad \& \quad N_1 i_1 + N_2 i_2 = 0$$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \quad \& \quad N_1 I_1 + N_2 I_2 = 0$$