

Phasor Domain Analysis


[Goal: Solve the circuit in sinusoidal steady state.]

Step 1 Transform the circuit into phasor domain by representing the input and circuit variables as phasors and passive circuit elements by their impedances.

Step 2 Solve the phasor domain circuit treating it like an LTI resistive circuit. That is, obtain the phasors of the asked variables.


Step 3 Transform the phasors (obtained in step 2) into their time domain representations.

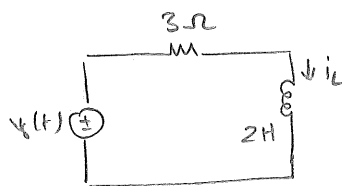Example (Revisited) Find $i_L(t)$ in steady state.




$$v_s(t) = 10 \cos 2t \text{ V}$$

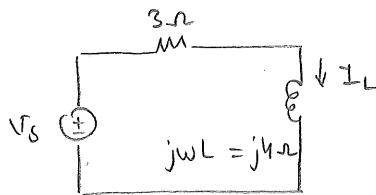Sol'n Phasor domain circuit: ($\omega = 2 \text{ rad/sec}$)



$$v_s = 10 \angle 0^\circ = 10 \text{ V}$$
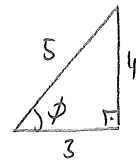
$$I_L = \frac{v_s}{3 + j4} = \frac{10}{5 \angle \phi} = 2 \angle -\phi \text{ A (1)}$$





$$(1) \Rightarrow i_L(t) = 2 \cos(2t - \phi) = \boxed{2 \cos(2t - 2 \tan^{-1} \frac{4}{3}) \text{ A}}$$

$$= 2 \{ \cos \phi \cos 2t + \sin \phi \sin 2t \} = 2 \{ 0.6 \cos 2t + 0.8 \sin 2t \}$$

$$= 1.2 \cos 2t + 1.6 \sin 2t \text{ A}$$

Example

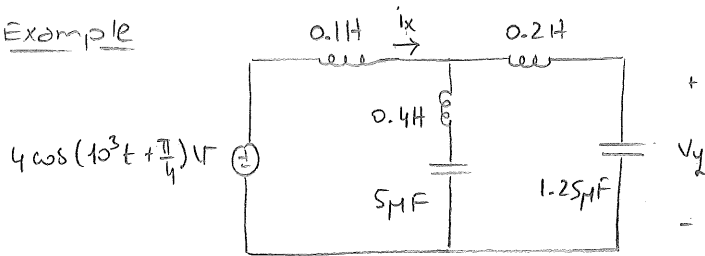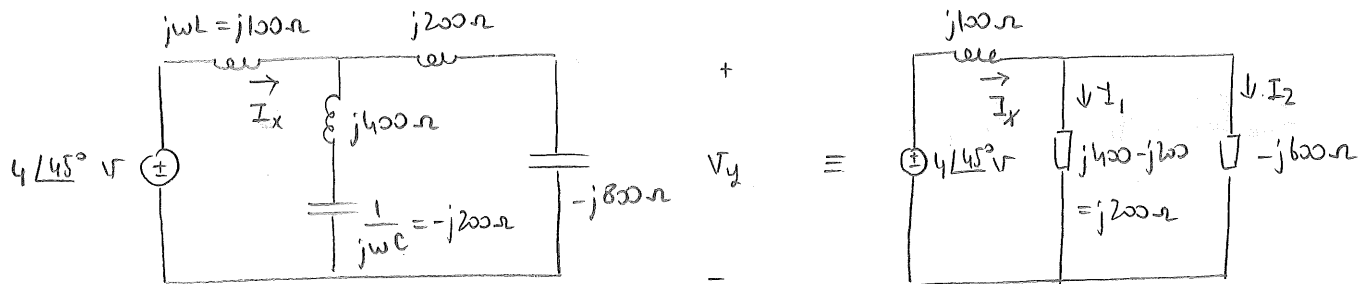Find $i_x(t)$ & $v_y(t)$ in steady state.Sol'n Equivalent circuit in phasor domain at freq. $\omega = 10^3 \text{ rad/sec}$:

$$\Rightarrow \text{Equivalent circuit: } 4 \angle 45^\circ \text{ V source in series with } j100 \Omega \text{ inductor, looking into a load } Z.$$

$$Z = \left\{ \frac{1}{j200} + \frac{1}{-j600} \right\}^{-1} = \frac{j200(-j600)}{j200 - j600} = \frac{200 \times 600}{-j400} = j300 \Omega$$


$$\Rightarrow I_x = \frac{4 \angle 45^\circ}{j100 + j300} = \frac{4 \angle 45^\circ}{400 \angle 90^\circ} = \frac{1}{100} \angle -45^\circ \text{ A} \quad (1)$$

$$\text{Current division} \Rightarrow I_2 = \frac{j200}{j200 - j600} \cdot I_x = -\frac{1}{2} I_x = -\frac{1}{200} \angle -45^\circ = \frac{1}{200} \angle 135^\circ \text{ A}$$


$$\Rightarrow V_y = -j600 I_2 = 600 \angle -90^\circ \cdot \frac{1}{200} \angle 135^\circ = 4 \angle 45^\circ \text{ V} \quad (2)$$

$$(1) \Rightarrow i_x(t) = \text{Re}\{I_x e^{j\omega t}\} = \boxed{10 \cos(1000t - \frac{\pi}{4}) \text{ mA}}$$

$$(2) \Rightarrow v_y(t) = \boxed{4 \cos(1000t + \frac{\pi}{4}) \text{ V}}$$

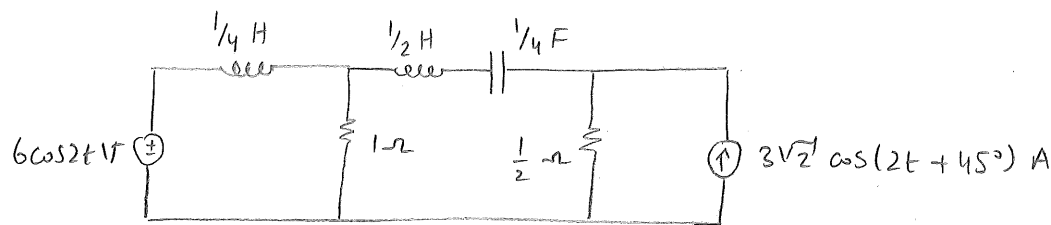Example [Node analysis]

Find the steady state voltage across the 1Ω resistor.

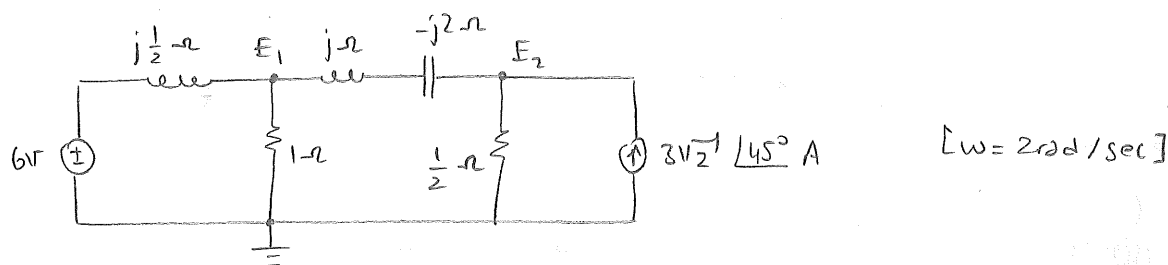Sol'n

$$\text{Node ①: } \frac{E_1 - 6}{j\frac{1}{2}} + \frac{E_1}{1} + \frac{E_1 - E_2}{-j} = 0 \quad (1)$$

$$\text{Node ②: } \frac{E_2 - E_1}{-j} + \frac{E_2}{\frac{1}{2}} - 3\sqrt{2} \angle 45^\circ = 0 \quad (2)$$

$$(1) \Rightarrow \{-j2 + 1 + j\} E_1 - j E_2 = -j12 \Rightarrow (1-j) E_1 - j E_2 = -j12 \Rightarrow E_2 = -(1+j) E_1 + 12 \quad (3)$$


$$(2) \Rightarrow -j E_1 + (2+j) E_2 = 3+j3 \quad (4)$$

$$(3) \& (4) \Rightarrow -j E_1 + (2+j) \{12 - (1+j) E_1\} = 3+j3$$

$$\Rightarrow -\{j + (1+j)(2+j)\} E_1 = -12(2+j) + 3+j3$$


$$\Rightarrow -(1+j4) E_1 = -21-j9 \Rightarrow E_1 = \frac{21+j9}{1+j4} = \frac{57-j75}{17} = \frac{3}{17} (19-j25) \quad (5)$$

$$\text{Finally, } (5) \Rightarrow e_1(t) = \frac{3}{17} \sqrt{19^2 + 25^2} \cos(2t - \tan^{-1}(25/19)) \text{ V}$$

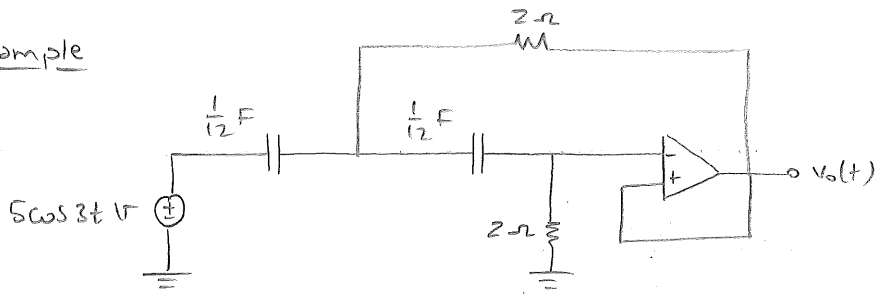Example

Assume: OPAMP is in
linear region & the
circuit is in SSS.

Find $v_o(t)$.

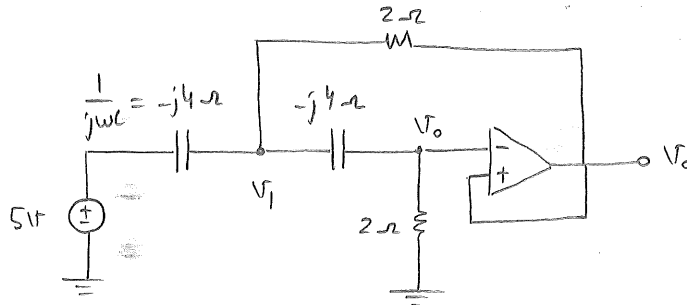Sol'n

$\omega = 3 \text{ rad/sec}$


$$\frac{v_1 - 5}{-j4} + \frac{v_1 - v_o}{-j4} + \frac{v_1 - v_o}{2} = 0 \Rightarrow \left\{ \frac{1}{2} + j\frac{1}{2} \right\} v_1 - \left\{ \frac{1}{2} + j\frac{1}{4} \right\} v_o = j\frac{5}{4} \quad (1)$$

$$\frac{v_o - v_1}{-j4} + \frac{v_o}{2} = 0 \Rightarrow \left\{ \frac{1}{2} + j\frac{1}{4} \right\} v_o - j\frac{1}{4} v_1 = 0 \Rightarrow v_1 = (1 - j2) v_o \quad (2)$$

$$(1) \& (2) \Rightarrow \left[\left(\frac{1}{2} + j\frac{1}{2} \right) (1 - j2) - \left(\frac{1}{2} + j\frac{1}{4} \right) \right] v_o = j\frac{5}{4} \Rightarrow \left(1 - j\frac{3}{4} \right) v_o = j\frac{5}{4}$$

$$\Rightarrow \frac{5}{4} \angle -\tan^{-1} \frac{3}{4} \quad v_o = \frac{5}{4} \angle 90^\circ \Rightarrow v_o = 1 \angle 90^\circ + \tan^{-1} \left(\frac{3}{4} \right) \text{ V} \quad (3)$$


$$(3) \Rightarrow \boxed{v_o(t) = \cos\left(3t + 90^\circ + \tan^{-1} \frac{3}{4}\right) \text{ V}}$$

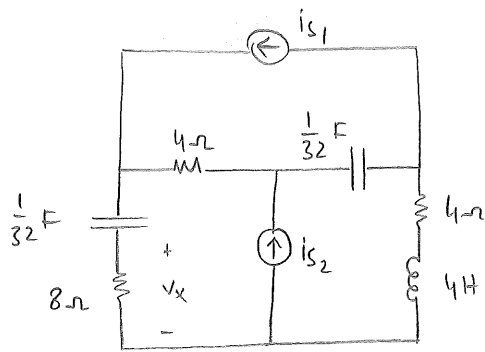Example [Mesh Analysis]

Given : $\rightarrow i_{s1}(t) = 6\cos 4t \text{ A}$
 $\rightarrow i_{s2}(t) = 2\cos 4t \text{ A}$
 $\rightarrow$ circuit is in SSS

Find $v_x(t)$.

Sol'n $[\omega = 4\text{rad/sec}]$

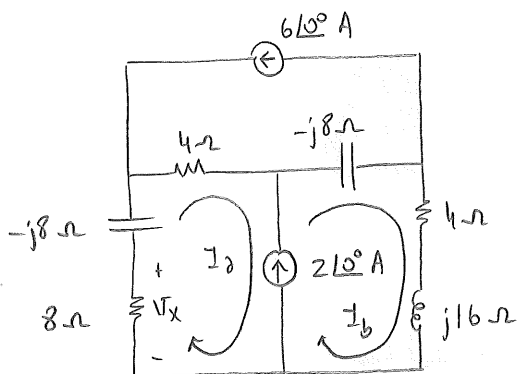

Supermesh :

$$(8-j8)I_a + 4(I_a+I_b) - j8(I_b+I_a) + (4+j16)I_b = 0 \quad (1)$$

$$\text{constraint : } I_b - I_a = 2 \Rightarrow I_b = I_a + 2 \quad (2)$$

$$(1) \& (2) \Rightarrow (8-j8+4)I_a + (-j8+4+j16)(I_a+2) = -24+j48$$


$$\Rightarrow (12-j8)I_a + (4+j8)I_a = -24+j48 - 2(4+j8)$$

$$\Rightarrow 16I_a = -32+j32 \Rightarrow I_a = -2+j2 \text{ A}$$


$$\Rightarrow v_x = -8I_a = 16-j16 = 16\sqrt{2} \angle -45^\circ \text{ V}$$

$$\Rightarrow \boxed{v_x(t) = 16\sqrt{2} \cos(4t - \frac{\pi}{4}) \text{ V}}$$

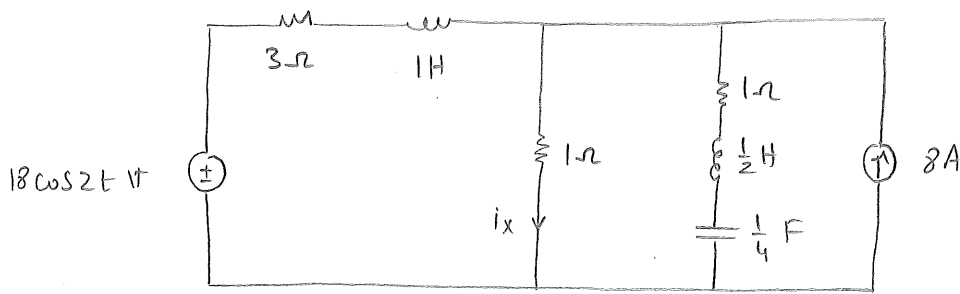Example [Superposition] Find $i_x(t)$ in the steady state.



Step 1 Kill DC source.

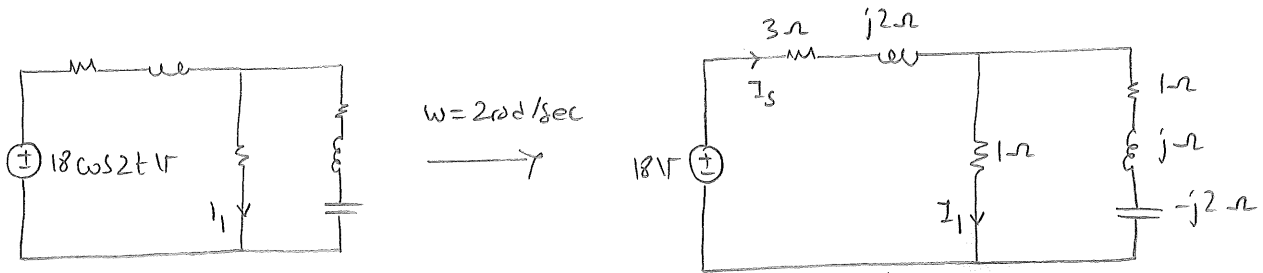


$$I_s = \frac{18}{(3+j2) + (1 \parallel (1-j))} = \frac{18}{3.6 + j1.8} = 4-j2$$

$$\Rightarrow I_1 = \frac{1-j}{1+(1-j)} \cdot I_s = \frac{3-j}{5} (4-j2) = 2-j2 = 2\sqrt{2} \angle -45^\circ \text{ A}$$

$$\Rightarrow i_1(t) = 2\sqrt{2} \cos(2t - 45^\circ) \text{ A}$$

Step 2 Kill AC source.

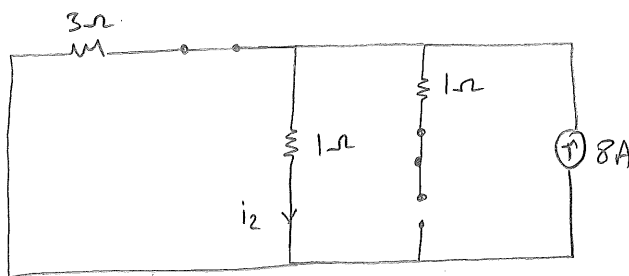


$$i_2(t) = 6 \text{ A}$$


Step 3 Superpose. $i_x(t) = i_1(t) + i_2(t) = 6 + 2\sqrt{2} \cos(2t - 45^\circ) \text{ A}$

Thevenin / Norton Equivalent Circuits

Just like in the LTI resistive case.

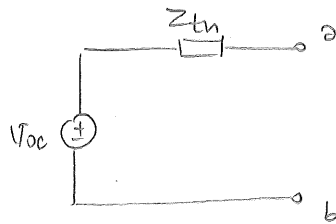


Thevenin Equivalent
in phasor domain

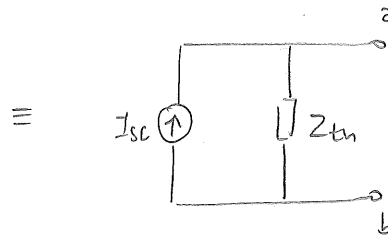

Norton Equivalent

$$Z_{th} = \frac{V_{oc}}{I_{sc}}$$

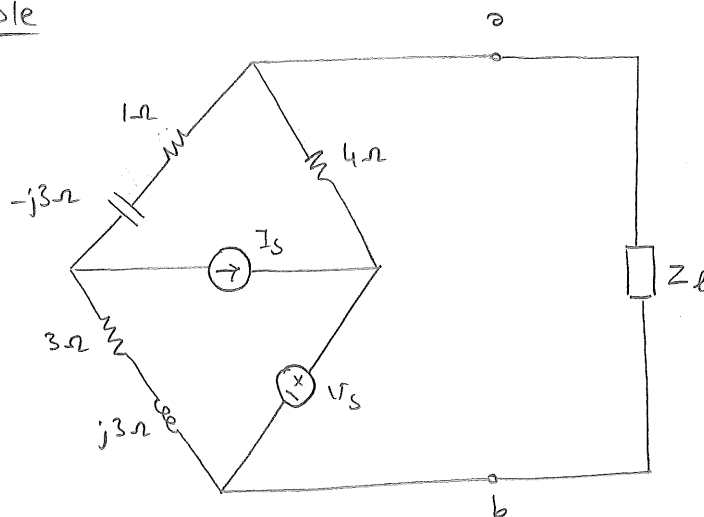
Example

$$I_s = \sqrt{2} \angle -45^\circ \text{ A}$$

$$V_s = 8 \angle 0^\circ \text{ V}$$

Find the Thevenin equiv.
circuit seen by the
load Z_L .

Sol'n First, find V_{oc} .

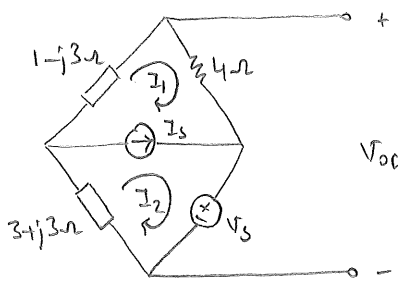

$$\text{Supermesh: } (1-j3)I_1 + 4I_1 + V_s + (3+j3)I_2 = 0$$

$$\Rightarrow (5-j3)I_1 + (3+j3)I_2 = -8 \quad (1)$$


$$\text{Constraint: } I_2 - I_1 = I_s \Rightarrow I_2 = I_1 + (1-j) \quad (2)$$

$$(1) \& (2) \Rightarrow (5-j3)I_1 + (3+j3)\{I_1 + (1-j)\} = -8 \Rightarrow 8I_1 = -8 - (3+j3)(1-j) = -14$$

$$\Rightarrow I_1 = -\frac{7}{4} \text{ A}$$

$$\Rightarrow V_{oc} = 4I_1 + V_s = 4\left(-\frac{7}{4}\right) + 8 = \underline{1V}$$

Now, find I_{sc} .

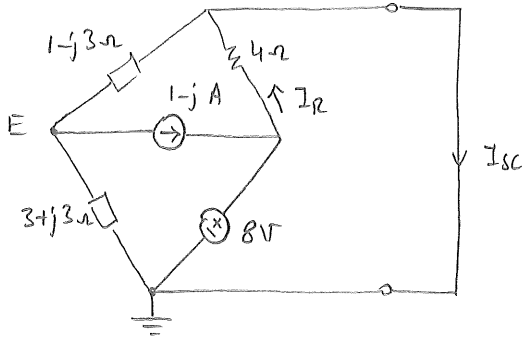

$$\frac{E}{3+j3} + (1-j) + \frac{E}{1-j3} = 0$$

$$\Rightarrow \left(\frac{1}{3+j3} + \frac{1}{1-j3} \right) E = -1+j$$



$$\Rightarrow \frac{4+j2}{15} E = -1+j \Rightarrow E = -\frac{3}{2} + j\frac{9}{2} \text{ V}$$

$$\& I_R = \frac{8}{4} = 2 \text{ A}$$


$$\Rightarrow I_{sc} = \frac{E}{1-j3} + I_R = -\frac{3}{2}(1-j3) \cdot \frac{1}{1-j3} + 2 = \boxed{\frac{1}{2} \text{ A}}$$

$$\text{Hence } Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{1}{1/2} = \boxed{2 \Omega}$$

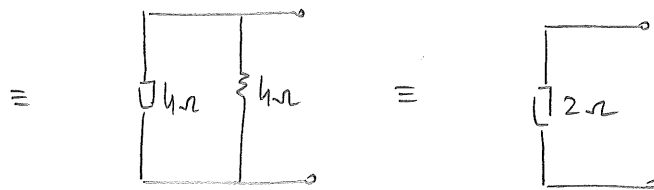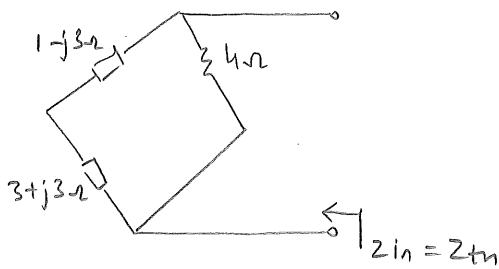
Alternatively, we can compute Z_{th} by killing the ind. sources:



Finally, Z_L sees:

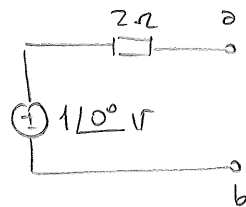


Thev. Equiv.

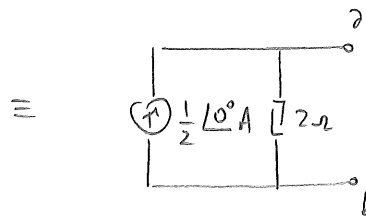

Norton Equiv.

Example

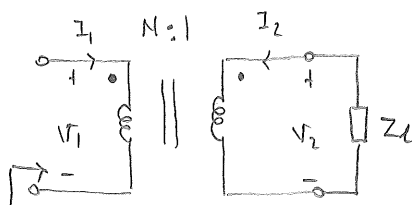

$Z_{in} = ?$

$$Z_{in} = \frac{V_1}{I_1} = \frac{N V_2}{-I_2/N} = \frac{N(-I_2 Z_L)}{-I_2/N} = N^2 Z_L$$

$$\Rightarrow \boxed{Z_{in} = N^2 Z_L}$$