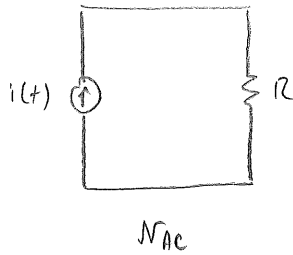
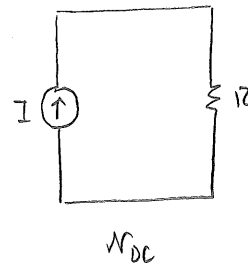


Effective (RMS) value

Consider two circuits

 $i(t+T) = i(t)$, periodic signalinstantaneous power dissipated on the resistor: $p(t) = Ri(t)^2$ average power: $P_{av} = \frac{1}{T} \int_0^T p(t) dt$  $I > 0$, constant $p(t) = P_{av} = RI^2$ Suppose: The average powers are equal for N_{AC} and N_{DC} .Question: what does the above condition imply?

$$\Rightarrow \frac{1}{T} \int_0^T Ri(t)^2 dt = RI^2 \quad \Rightarrow \quad \frac{1}{T} \int_0^T i(t)^2 dt = I^2$$


$$\Rightarrow \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt} = I$$

This motivates the following definition.

Definition Given a periodic signal $i(t) = i(t+T)$ the effective or RMS (root mean square) value $I_{eff} > 0$ is defined via

$$I_{eff} = \left[\frac{1}{T} \int_0^T i(t)^2 dt \right]^{1/2}$$

Remark For $i(t) = A \cos(\omega t + \phi)$ ($A > 0$) we have $I_{eff} = \frac{A}{\sqrt{2}}$.

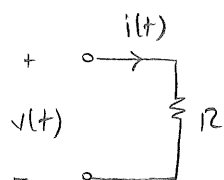Instantaneous & average power in SSSResistor


Let $i(t) = I_m \cos(\omega t + \phi)$, period $T = \frac{2\pi}{\omega}$ sec, $I_{eff} = \frac{I_m}{\sqrt{2}}$

$$\begin{aligned} \Rightarrow p(t) &= i(t)v(t) \\ &= RI_m \cos(\omega t + \phi) I_m \cos(\omega t + \phi) \\ &= \frac{1}{2} RI_m^2 (1 + \cos[2(\omega t + \phi)]) \end{aligned} \quad \left\{ \cos^2 \alpha = \frac{1}{2} [1 + \cos 2\alpha] \right.$$

Hence inst. power: $p(t) = \frac{1}{2} RI_m^2 (1 + \cos(2\omega t + 2\phi))$, periodic with T

$$\text{aver. power: } P_{av} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} RI_m^2 \left\{ \underbrace{\frac{1}{T} \int_0^T dt}_{=1} + \underbrace{\frac{1}{T} \int_0^T \cos(2\omega t + 2\phi) dt}_{=0} \right\}$$

$$\Rightarrow P_{av} = \frac{1}{2} RI_m^2 = \boxed{RI_{eff}^2}$$

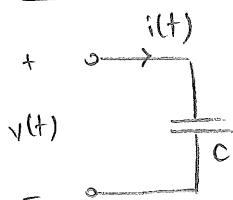Capacitor

Let $v(t) = V_m \cos(\omega t + \phi)$, period $T = \frac{2\pi}{\omega}$ sec, $V_{eff} = \frac{V_m}{\sqrt{2}}$

$$\Rightarrow I = j\omega C V = j\omega C V_m \angle \phi = \omega C V_m \angle \phi + \frac{\pi}{2}$$

$$\Rightarrow i(t) = \omega C V_m \cos(\omega t + \phi + \frac{\pi}{2})$$


$$\begin{aligned} \Rightarrow p(t) &= i(t)v(t) = \omega C V_m^2 \cos(\omega t + \phi) \cos(\omega t + \phi + \frac{\pi}{2}) \\ &= \frac{1}{2} \omega C V_m^2 \cos(2\omega t + 2\phi + \frac{\pi}{2}) \end{aligned} \quad \left\{ \cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha + \beta) + \cos(\alpha - \beta)] \right.$$

$$\Rightarrow \boxed{P_{av} = 0} \quad \text{because } p(t) \text{ is purely sinusoidal.}$$

How about stored energy?

$$e(t) = \frac{1}{2} C v(t)^2 = \frac{1}{2} C V_m^2 \cos^2(\omega t + \phi), \text{ periodic with } T$$

$$\Rightarrow E_{av} = \frac{1}{T} \int_0^T e(t) dt = \frac{1}{4} C V_m^2 = \boxed{\frac{1}{2} C V_{eff}^2}$$

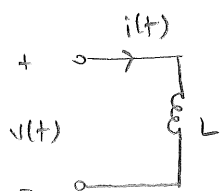
Inductor

Let $i(t) = I_m \cos(\omega t + \phi)$, period $T = \frac{2\pi}{\omega}$, $I_{eff} = \frac{I_m}{\sqrt{2}}$

By duality we can write

$$p(t) = \frac{1}{2} \omega L I_m^2 \cos(2\omega t + 2\phi + \frac{\pi}{2}) \Rightarrow \boxed{P_{av} = 0}$$

$$e(t) = \frac{1}{2} L I_m^2 \cos^2(\omega t + \phi) \Rightarrow \boxed{E_{av} = \frac{1}{4} L I_m^2 = \frac{1}{2} L I_{eff}^2}$$

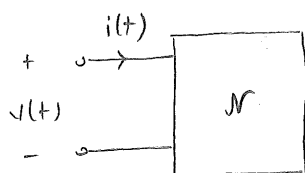Power into one-port

Let $i(t) = I_m \cos(\omega t + \phi_i)$

$v(t) = V_m \cos(\omega t + \phi_v)$

$$\Rightarrow p(t) = i(t)v(t)$$

$$= I_m V_m \cos(\omega t + \phi_i) \cos(\omega t + \phi_v)$$

$$= \frac{1}{2} I_m V_m \cos(\phi_v - \phi_i) + \frac{1}{2} I_m V_m \cos(2\omega t + \phi_i + \phi_v)$$

purely sinusoidal term, i.e.,
has zero average

$$\Rightarrow \boxed{P_{av} = \frac{1}{2} I_m V_m \cos(\phi_v - \phi_i) = I_{eff} V_{eff} \cos(\phi_v - \phi_i)}$$


The term " $\cos(\phi_v - \phi_i)$ " is called the power factor when N is passive and md. source free.

Now, suppose N contains no md. sources and therefore can be represented by an impedance Z . That is, $V = ZI$.

Observe: $Z = \frac{V_m \angle \phi_v}{I_m \angle \phi_i} = \frac{V_m}{I_m} \angle \phi_v - \phi_i = |Z| \angle \phi_v - \phi_i$

$$\begin{aligned} \text{Then } P_{av} &= \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) = \frac{1}{2} I_m \{ I_m |Z| \} \cos(\phi_v - \phi_i) \\ &= \frac{1}{2} I_m^2 \{ |Z| \cos(\phi_v - \phi_i) \} \end{aligned}$$

$$\text{Hence } \boxed{P_{av} = \frac{1}{2} I_m^2 \operatorname{Re}\{Z\} = I_{eff}^2 \cdot \operatorname{Re}\{Z\}}$$

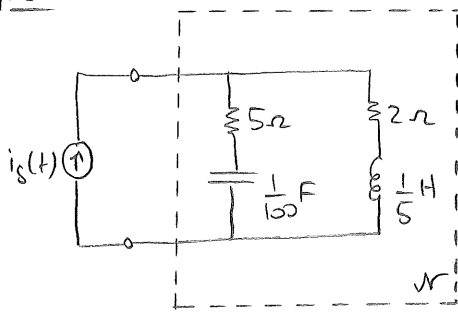
Example

$$i_s(t) = 5 \cos(20t) \text{ A}$$

The circuit is in SSS. Find:

- The average power delivered to N .
- The aver. power dissipated on 5Ω resistor.
- The aver. power dissipated on 2Ω resistor.
- The aver. stored energy in the inductor.

Sol'n a)

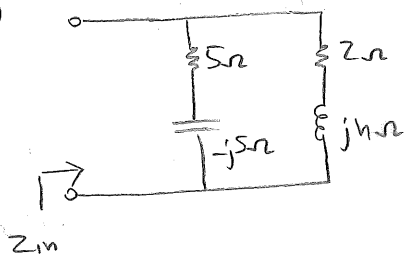


$$\frac{1}{Z_{in}} = \frac{1}{5-j5} + \frac{1}{2+j4} = \frac{5+j5}{50} + \frac{2-j4}{20}$$

$$= \frac{1+j}{10} + \frac{1-j2}{10} = \frac{2-j}{10}$$

$$\Rightarrow Z_{in} = \frac{10}{2-j} = \frac{2 \sqrt{5}(2+j)}{5} = 4+j2 \Omega$$

$$\Rightarrow P_w = I_{s,eff}^2 \cdot \text{Re}\{Z_{in}\} = \left(\frac{5}{\sqrt{2}}\right)^2 \cdot 4 = \boxed{50 \text{ W}}$$

b/c)

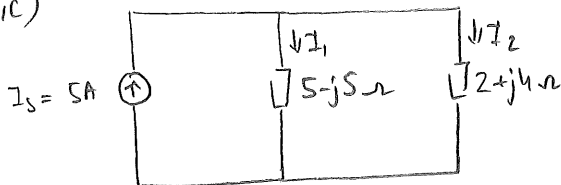

$$I_1 = \frac{Z_2}{Z_1 + Z_2} I_s = \frac{2+j4}{7-j} \cdot 5 = 1+j3 \text{ A}$$

$$\Rightarrow I_2 = I_s - I_1 = 4-j3 \text{ A}$$

$$\Rightarrow I_1 = \sqrt{10} \angle \tan^{-1} 3 \text{ A} \quad \text{and} \quad I_2 = 5 \angle -\tan^{-1} 3/4 \text{ A}$$

$$\Rightarrow P_{5\Omega} = I_{1,eff}^2 \cdot 5 = \left(\frac{\sqrt{10}}{\sqrt{2}}\right)^2 \cdot 5 = \boxed{25 \text{ W}} \quad \text{and} \quad P_{2\Omega} = I_{2,eff}^2 \cdot 2 = \boxed{25 \text{ W}}$$

Note that $P_w = P_{5\Omega} + P_{2\Omega}$!

$$d) E_L = \frac{1}{2} \cdot \frac{1}{5} \cdot I_{2,eff}^2 = \frac{1}{10} \cdot \left(\frac{5}{\sqrt{2}}\right)^2 = \frac{25}{20} = \boxed{\frac{5}{4} \text{ J}}$$