
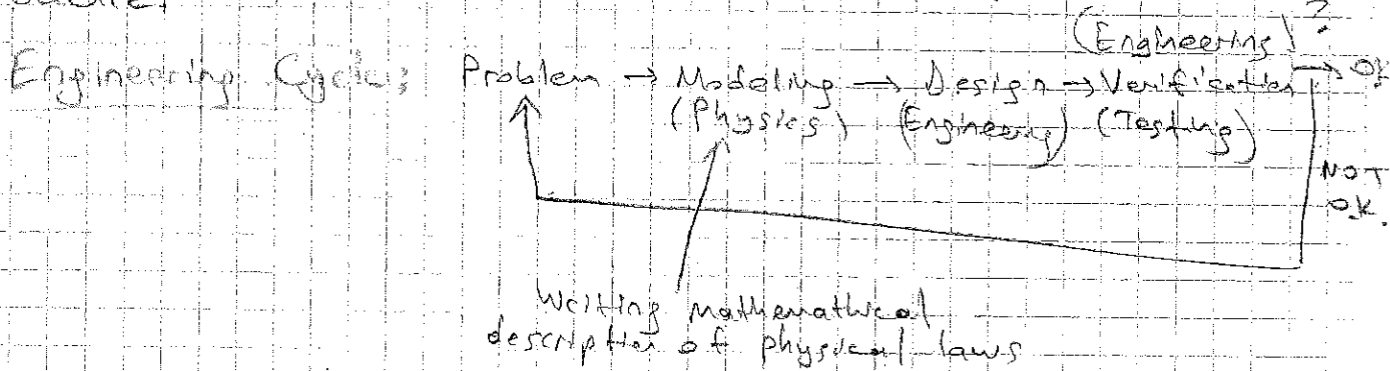


EE 201 Section 2.3 (Circuit Fundamentals)

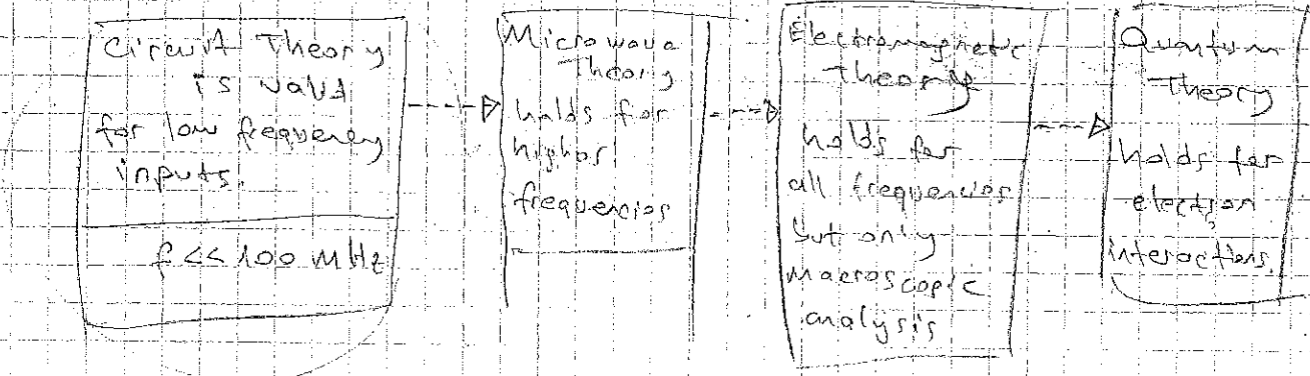
Goals: Analyzing / designing systems/equipment such that we have something valuable that is making human life safer, more convenient, healthier etc, and of value to the general public and science.





Modeling: Modeling requires expressing physical laws or objects in terms of mathematical equations. All models are somewhat approximate, but if the model works, we, as engineers are happy and enjoy the results.



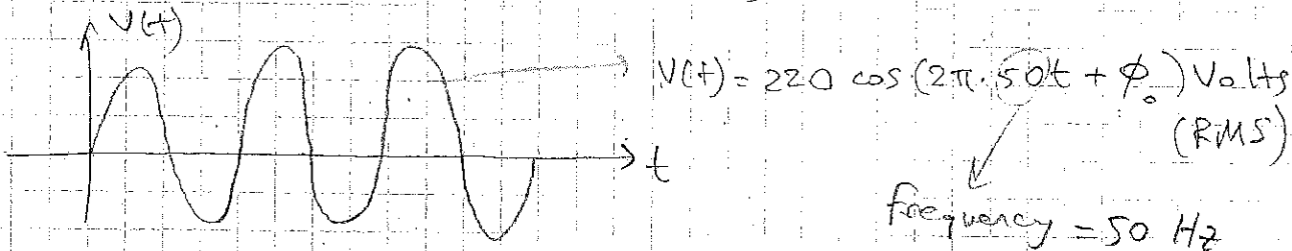Frequency of power line in Turkey is 50 Hz



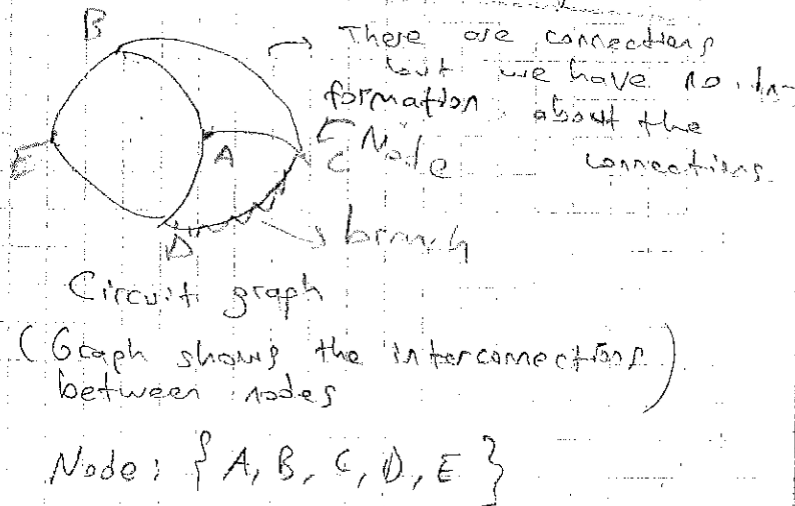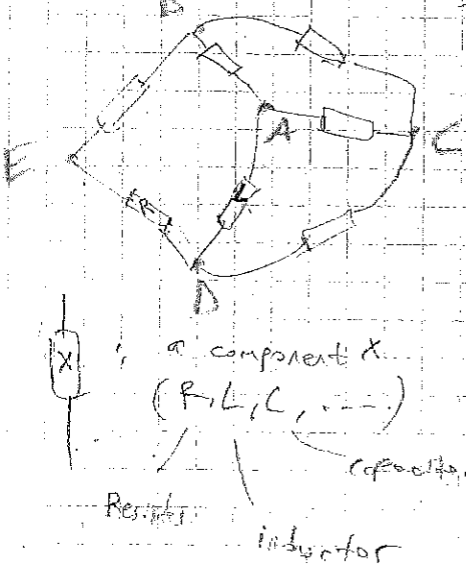EE 201 deals with lumped circuits with lumped components.



Lumped Circuit: If the propagation delay in the circuit is negligible in comparison to the changes in the circuit we call such circuits lumped circuits.


voltage and current, however

In other words, the components are assumed to be instantaneously informed about the circuit variable variations (current/voltage) in the circuit.


If $\lambda \gg$ (circuit diameter) then circuit is assumed to be lumped circuit.

$$\lambda = \frac{c}{f_{max}} \rightarrow c: \text{speed of light } (3 \times 10^8 \text{ m/sec})$$

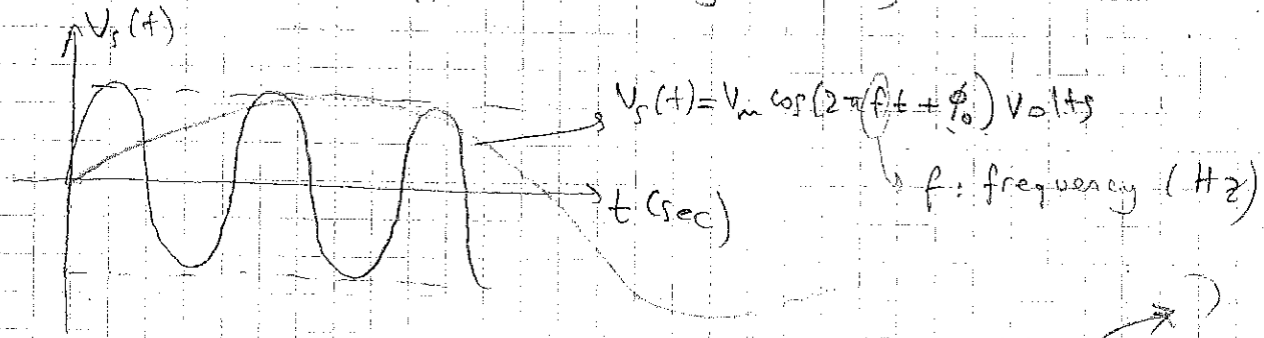wavelength f_{max} : max operating frequency



DC circuits are low frequency.

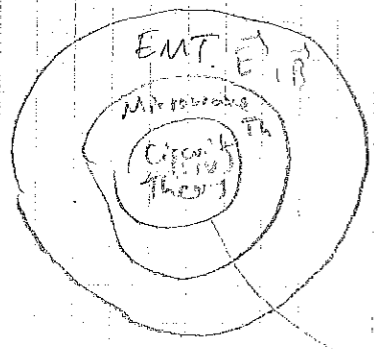

low frequency approximation of EMT

If lumped circuit condition ($\lambda \gg$ circuit diameter) is not satisfied, we call such circuits distributed circuits. (They are the topic of 4th year courses).

Ex: High frequency circuits are distributed circuits.

② Turkey's A.C. Power Grid $f: 50 \text{ Hz}$ (In Turkey)



Circuit diameter $\approx 1500 \text{ km}$

$$\lambda = \frac{c}{f} = \frac{3 \cdot 10^8 \text{ m/s}}{\frac{10}{2} \text{ 1/s}}$$


$$= 6 \cdot 10^6 = 6000 \text{ km}$$

1500 km is not much smaller than 6000 km. There should be at least 1 order of magnitude for us to use lumped theory.

Lumped Component: Component dimensions are negligible in effect in circuit analysis. That is, we never need the physical dimensions such as volume of the component, base area of the component in circuit analysis. Lumped components can be considered as points (dimensionless) in 3-D space.

As a summary, In EE 201 and EE 202 we focus on circuits whose physical attributes does not affect the circuit analysis results.

For this reason,

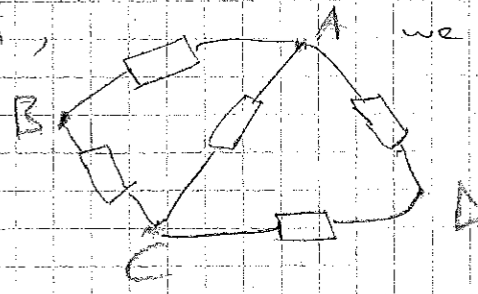


we never indicate the length of connectors or size of components in this course.

Circuit Variables:

Charge, Current, Voltage

Charge: Unit: Coulomb (C)

Charges are countable.

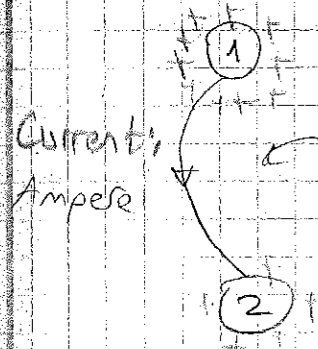


Charge transfer from ① to ②

$Q_2(t)$: Total amount of charge in ② at time "t"

I can transfer charges from ① to ② at a rate 1 C/sec.

Current at time t $\rightarrow \frac{Q_2(t+h) - Q_2(t)}{h}$


$$i(t) = \lim_{h \rightarrow 0} \frac{Q_2(t+h) - Q_2(t)}{h} = i'(t) = \left. \frac{dQ(t)}{dt} \right|_{t=t_x}$$

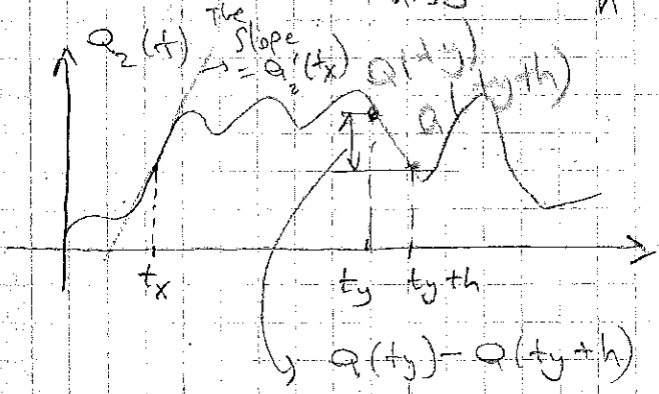

As a summary, current is rate of transfer of charge from ① to ②.

Voltage: Voltage difference is the potential difference between two points in space.

Volts

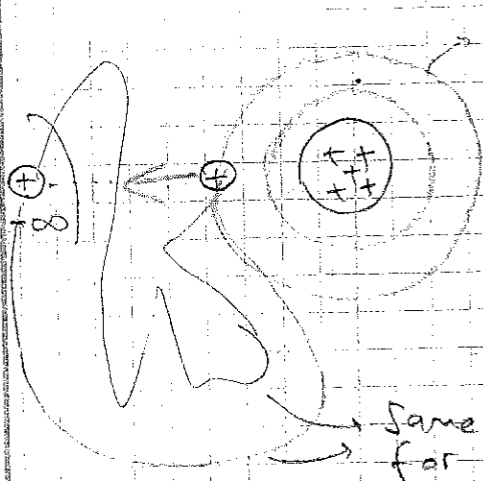


$$W = q \cdot \Delta V$$

Work

Potential difference


It is path-independent.

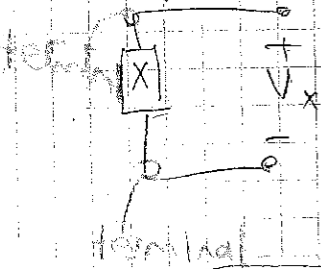Note that voltage difference (or voltage itself) is always referenced to another point.




V_X is the voltage difference between component terminals.

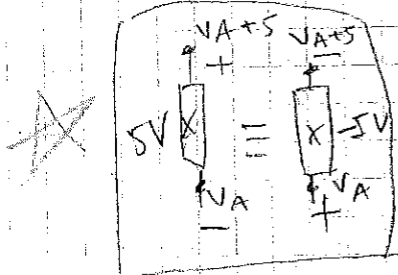Also, voltage has a polarity that + and - terminals are important.



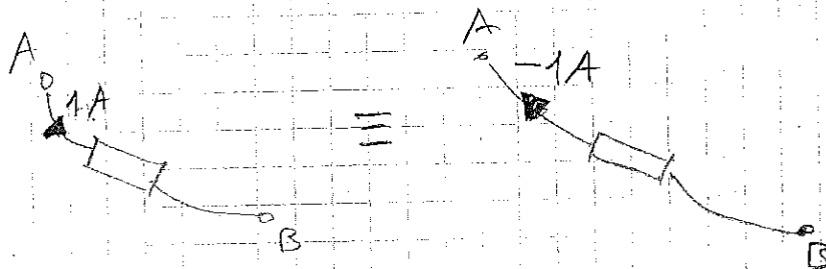Similarly, current has a direction and magnitude indicating transfer rate.



You may consider that current direction shows the direction of moving positive charges.

$1A = 1 \text{ Coulomb/sec}$ transfer rate.

Since $i(t) = \lim_{h \rightarrow 0} \frac{q(t+h) - q(t)}{h}$

Work and Power

$W \triangleq$ Energy required to do something

$$W = q \cdot \Delta V$$


Joules
the rate of change of work/energy at time "t"

Electrostatics fact

$$P(t) = \frac{dW(t)}{dt}$$

Power at time "t"

Parallel plates

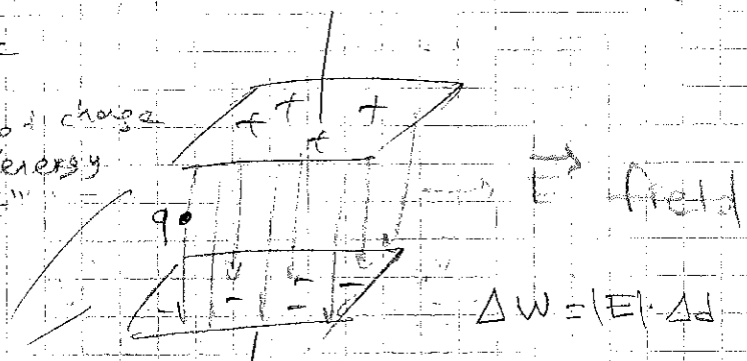

$$P(t) = \frac{d}{dt} (q \cdot \Delta V) = \left(\frac{d}{dt} q(t) \right) \Delta V = i(t) \cdot \Delta V$$


$$P(t) = i(t) \cdot V(t)$$

Power Watts


Conservation Laws and Kirchhoff's (Voltage/Current Laws)

1) Conservation of Charge

KCL (Kirchhoff's Current Law)

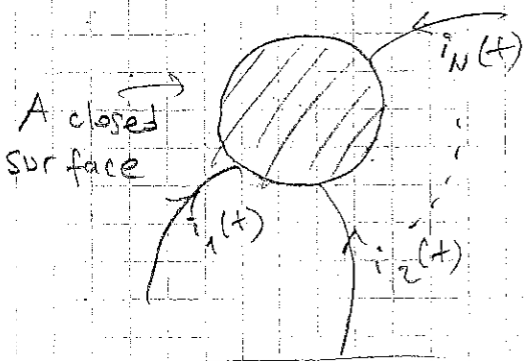

$$\sum_{k=1}^N i_k(t) = 0$$

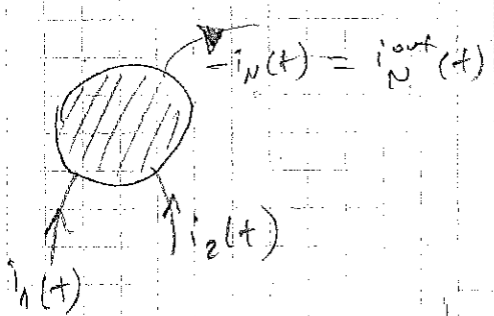


$$\sum_{k=1}^{N-1} i_k(t) + i_N(t) = 0$$

$$-i_N^{\text{out}}(t)$$

$$\sum_{k=1}^{N-1} i_k(t) = i_N^{\text{out}}(t)$$

$$\sum_{k \in \{\text{incoming currents}\}} i_k(t) = \sum_{k \in \{\text{outgoing currents}\}} i_k(t)$$

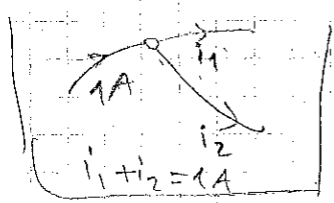
Sum of incoming currents is equal to sum of outgoing currents.



② Conservation of Energy and KVL

(or energy difference)

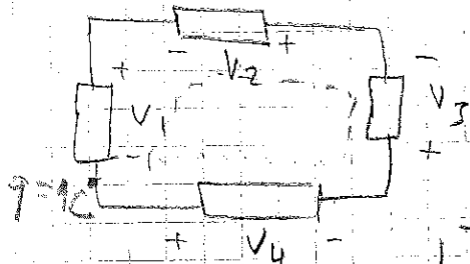
Work done by a moving q charge in the loop




$$0 = qV_1 + qV_2 + qV_3 + qV_4$$

$$\sum V_k = 0$$

KVL
KE branches in a loop

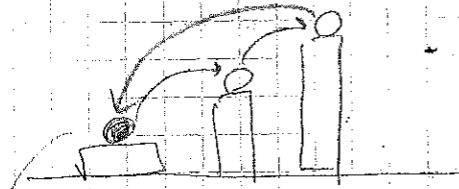

At the end $W=0$

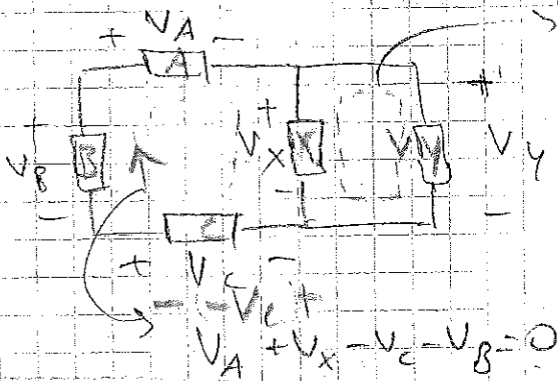

$$V_Y - V_X = 0$$




$$V_Y = V_X$$

$$V_A + V_X - V_C - V_B = 0$$

Last lecture:

Conservation Laws / KCL / KVL

KVL

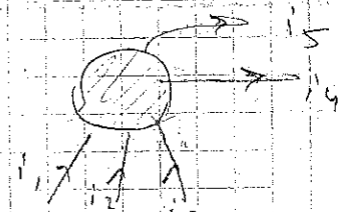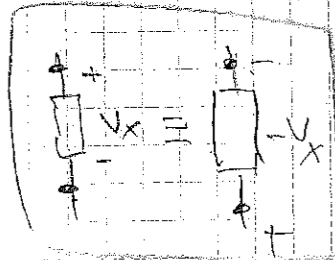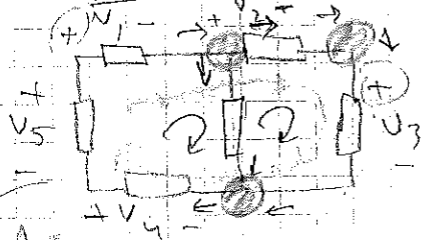

KCL

$$i_1 + i_2 + i_3 = i_4 + i_5$$

$$i_1 + i_2 + i_3 - i_4 - i_5 = 0$$

Summation of voltage drops across the loop:

$$V_1 + V_2 + V_3 - V_4 - V_5 = 0$$




Write the sign of the component to the equations, while traveling in the loop.

→ we have 3 loops. Conservation of energy is true for all 3 loops.
KVL, KCL is true for all loops, nodes in the circuit.

Circuit Components

Basic Component

R, L, C

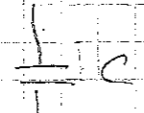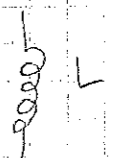
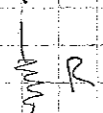


(Ohm's Law)
 $V_R = I_R R$


$$V_L(t) = L \frac{dI_L(t)}{dt}$$

$$I_C(t) = C \frac{dV_C(t)}{dt}$$

Unit: Ω (ohm)

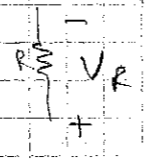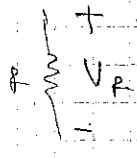


→ which terminal is at higher potential?

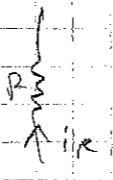




We have a convention (accepted rule)

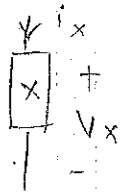Passive sign convention for circuit components




Passive sign convention assumes I_x enters into \oplus polarity of V_x voltage.

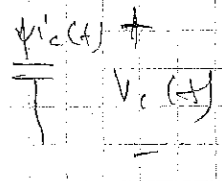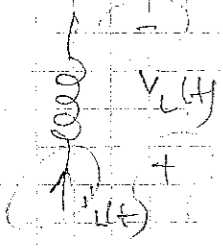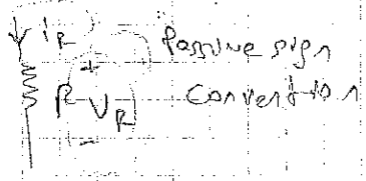All circuit components (R, L, C etc.) have terminal equations mapping currents to branch voltages (and vice versa) written according to the passive sign convention.



Some definitions

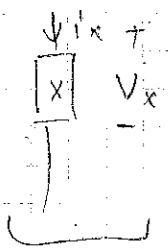

1-Port



Ex: R, L, C






2-Port

Ex: transformer, amplifier, equivalent circuits...

Degree of freedom: 2

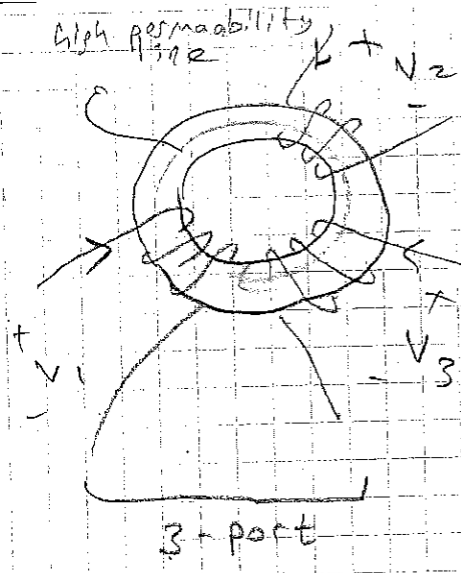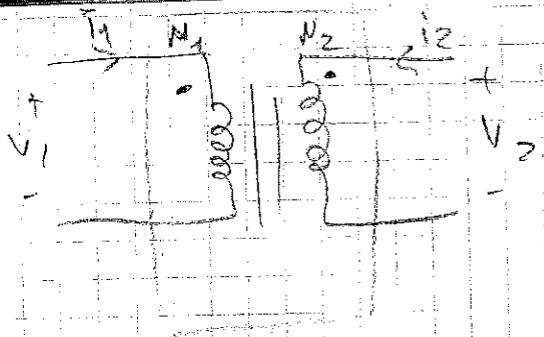


Terminal

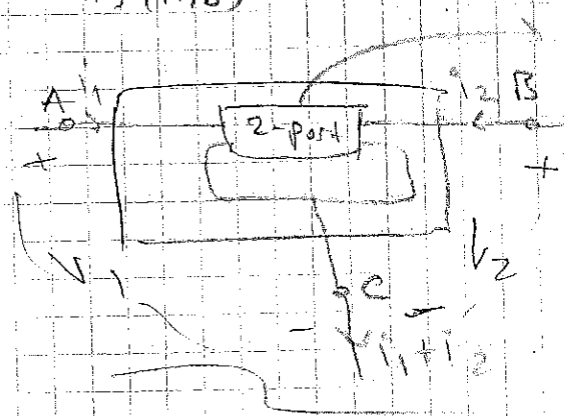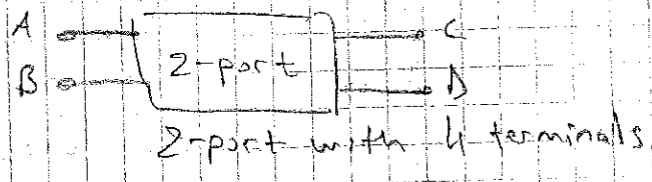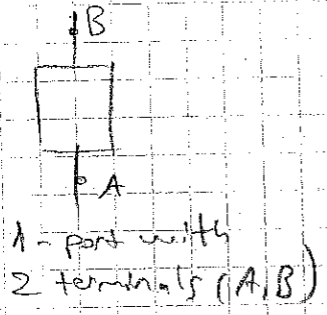

2-port with 4 terminals


~~AC~~ kVL
 kCL can be applied here as well

2-port with 3 terminals

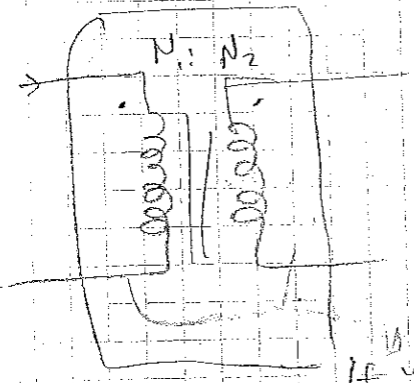

If we connect them there is no decoupling.

Resistor network (circuit with 2 ports)

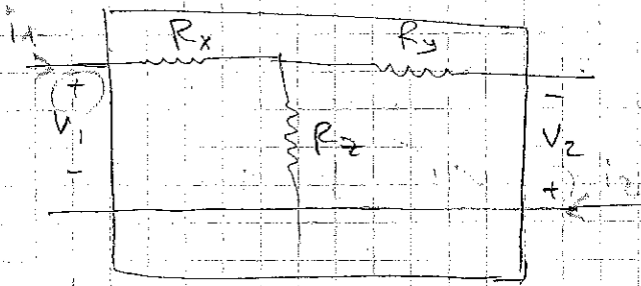


(i_1, V_1) and (i_2, V_2)


directions and polarity obey the passive sign convention.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$


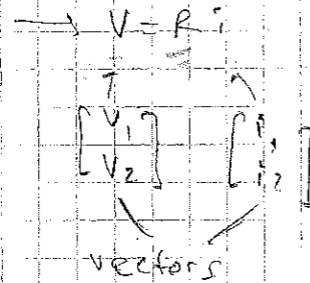
If we know any 2 we can find the 3rd one.



Ideal Voltage / Current Source

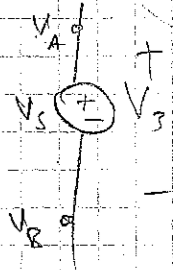


Always: $V_A - V_B = V_S$

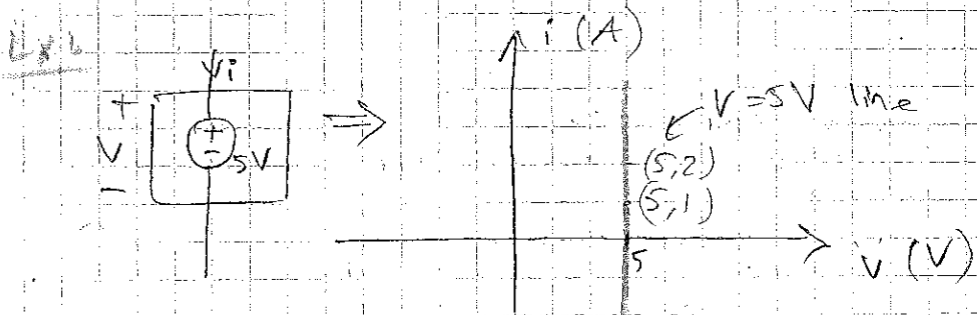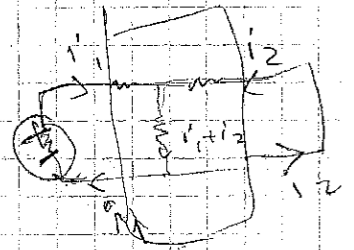

Locus of allowed (i, V) pairs
geometrically


Current Source

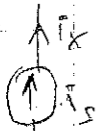

Always: $i_x = i_s$

Ideal current source provides i_s amount of Amperes as branch current no matter what.

EX:

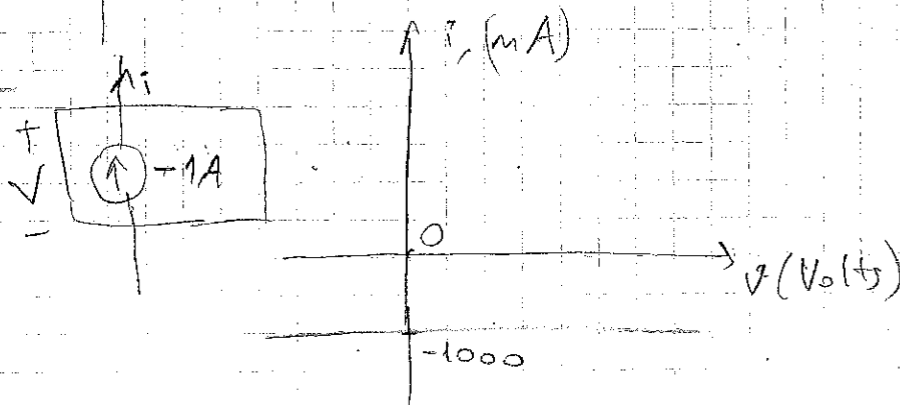


caution: ideal current source of i Amperes, does NOT mean that

the branch voltage is 0 Volts.





If this were the case power of ideal current source would be

$$P = V i = 0 \text{ watts all the time!!}$$

EX


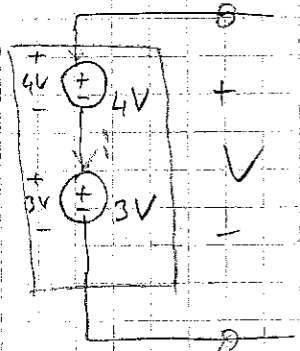


\equiv

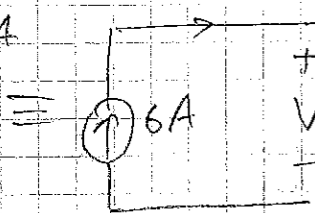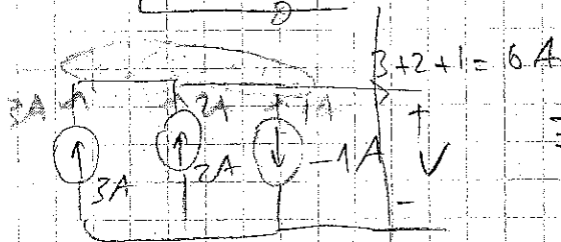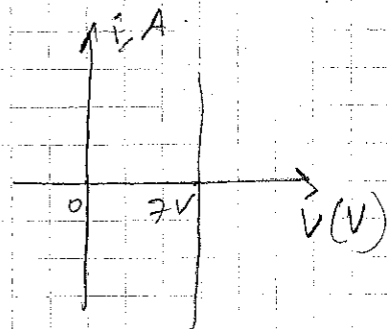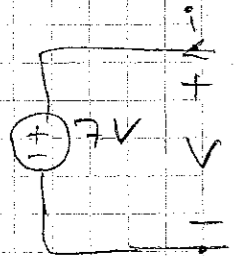


Pathological Combinations

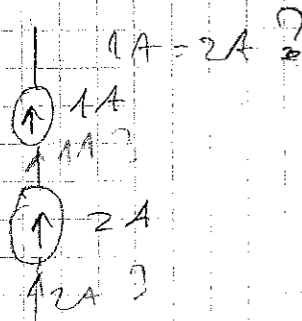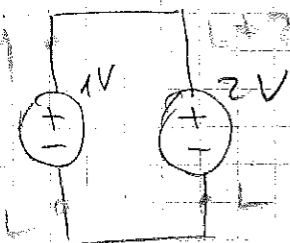Some source combinations are not possible with ideal sources. These combinations are called pathological combinations.




Pathological connection $\rightarrow x + 2 = x$

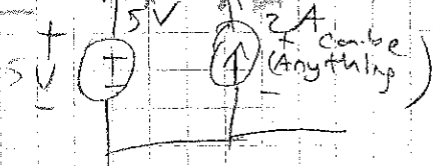
Ex 6 (can be anything) \rightarrow (Can be anything) too




\equiv

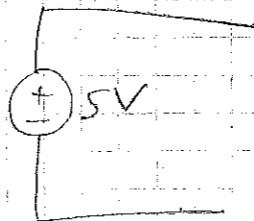

Not a pathological connection.

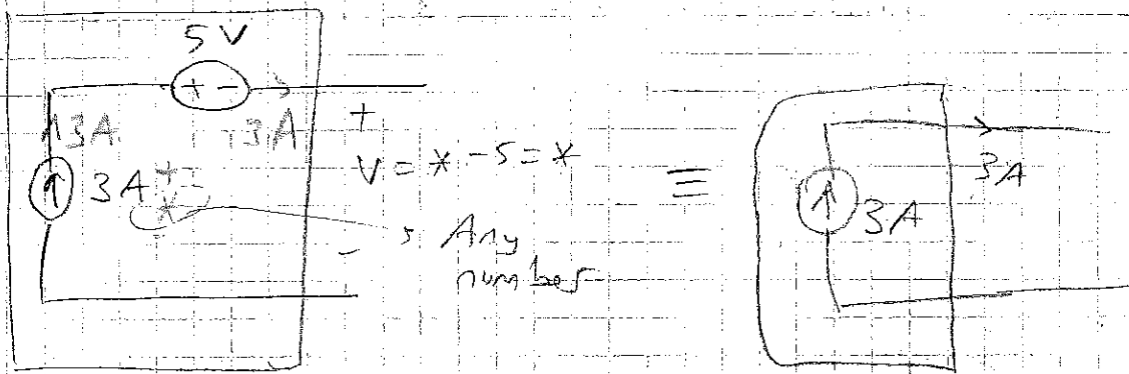

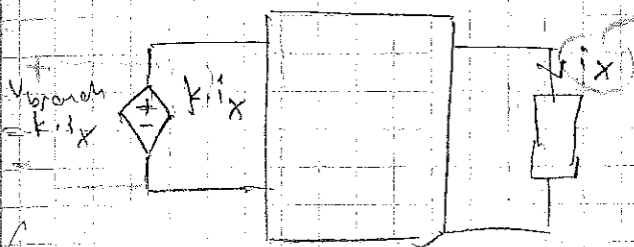Dependent Sources or Dependent Components



controlling variable for dependent source.

Dependent sources are denoted with \diamond (diamond) symbols.




\diamond is dependent voltage source.

k is a scalar proportionality constant. (for this case k has units Ω (ohms))


\uparrow is dependent current source.

An example of a current controlled voltage source (CCVS)

4 types

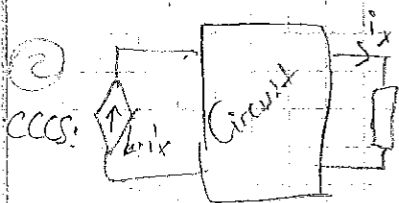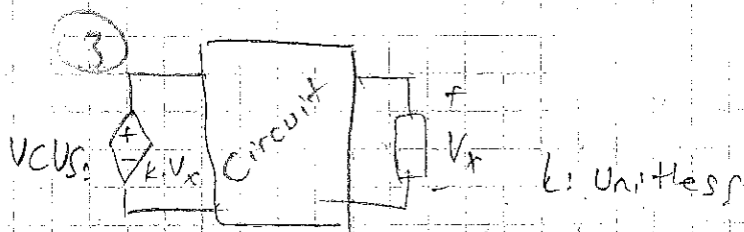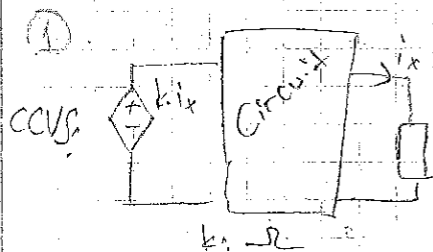



$k: \text{unitless}$

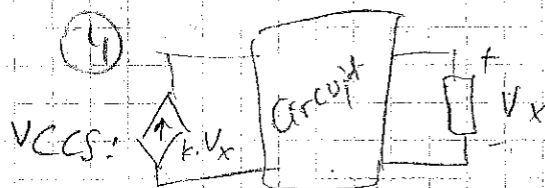



$k: \frac{1}{\Omega} = \mathcal{S} = \text{Siemens} = \text{mho}$

Circuit Components (continued)

Telexor:

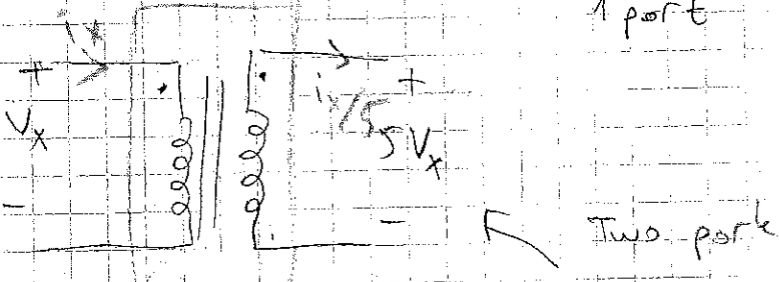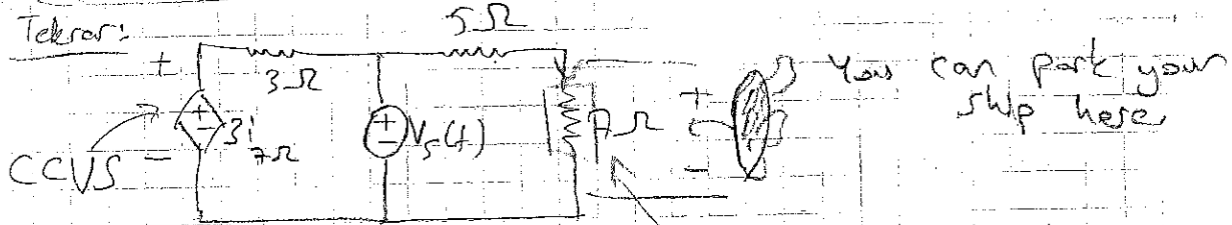


Resistors:

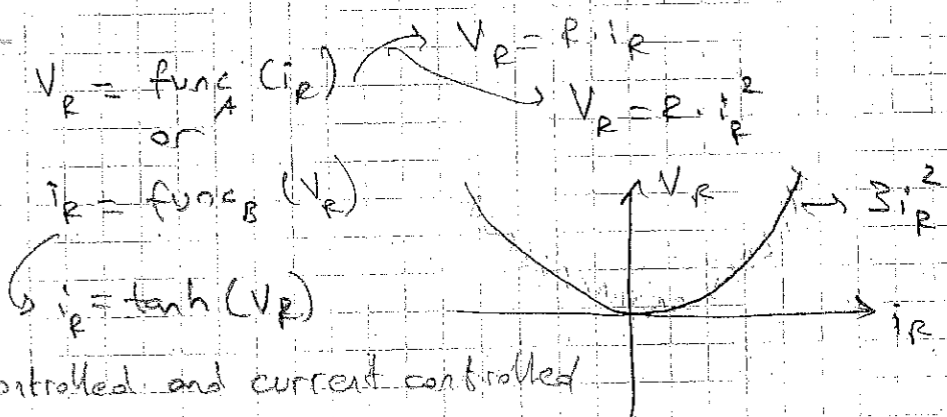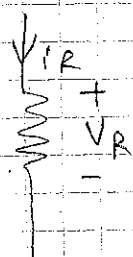


Defn: Voltage controlled and current controlled components:

Voltage controlled: If branch current of a component can be written as a function of its branch voltage then component is voltage controlled.

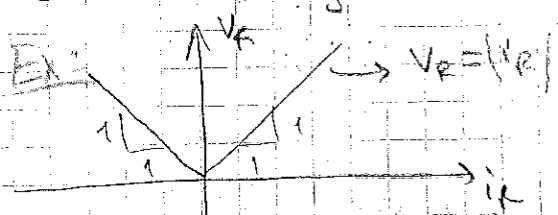
Current controlled: Branch current uniquely specifies the branch voltage.



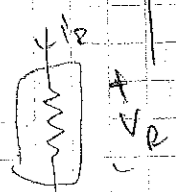
A resistor whose $(V_R - i_R)$ characteristic is given. Determine if the resistor is voltage/current controlled.



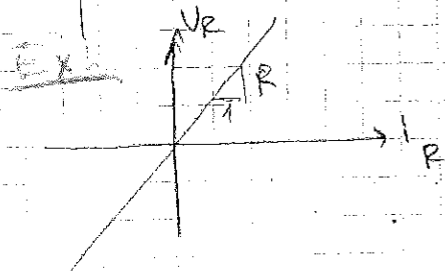It is current controlled since for every current value, there is a unique voltage.




→ Both voltage and current controlled.

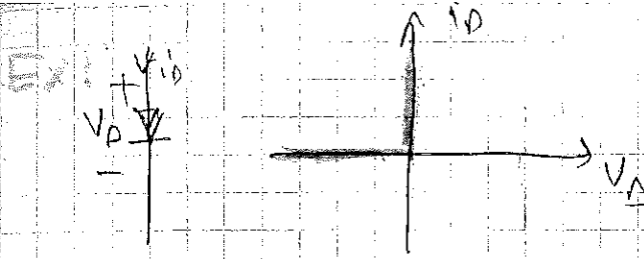

→ Neither voltage nor current controlled.

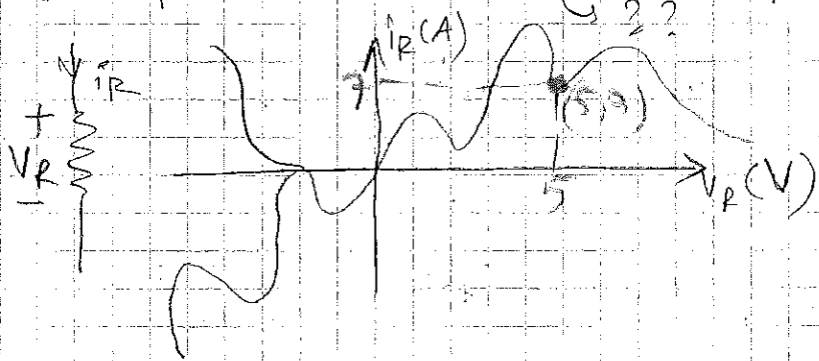In EE 201/202 resistors are components which map branch currents to branch voltages (current controlled resistor) or branch voltages to branch currents (voltage controlled resistor) or they just have a focus of operating points in the (i, v) plane associated to the component (neither voltage nor current controlled).




Diode is also a resistor (non-linear resistor)

Passive and Active Components

A component is passive if it cannot deliver energy/power to the other components; hence it only absorbs or stores energy.

A component which is not passive → active component.

Ex: $V_R = R \cdot i_R$

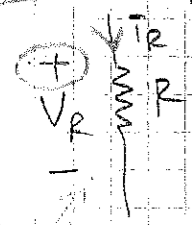


$$P_R(t) = V_R(t) \cdot i_R(t) = R \cdot (i_R(t))^2$$

Since $P_R(t) = R \cdot (i_R(t))^2 \geq 0$


↑
power absorbed or delivered by the component at time "t"
= instantaneous power

↳ Component absorbs power (R > 0)
↓ Component is passive.

passive component

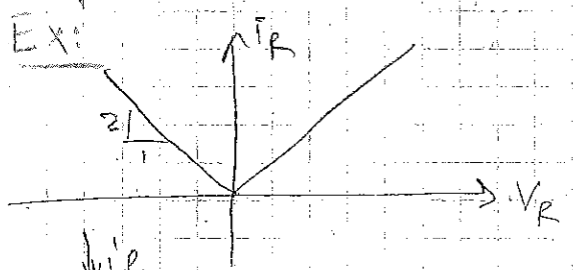

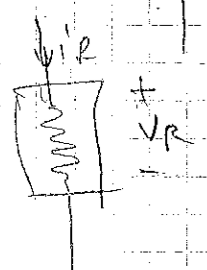→ Does the (i, v) char. belong to a passive or active component?




Check the power of the resistor and see whether power of resistor can be negative valued or not.

$$P_R = i_R \cdot V_R$$


If $V_R = -5$ Volts → $i_R = 10$ Amperes from the (i, v) char.

then $P_R = (-5) \cdot (10) = -50$ watts → At this operating point, the component delivers power to the other components.



Linear and non-linear components

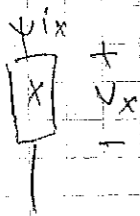

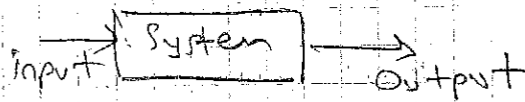
Assume your input is i_x and you are interested in the output v_x .



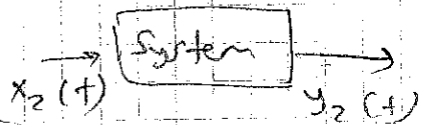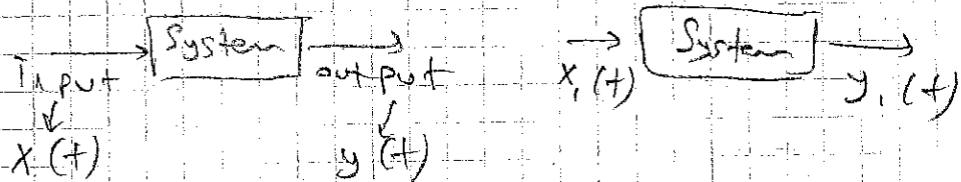
If a system satisfies the following conditions it is said to be a linear system:




Condition 1 (homogeneity)

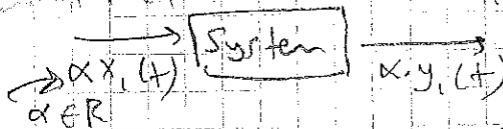

Condition 2 (additivity)

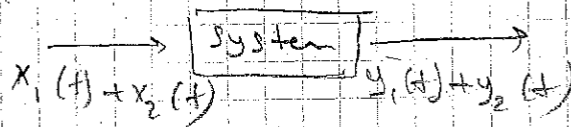


Ex 1

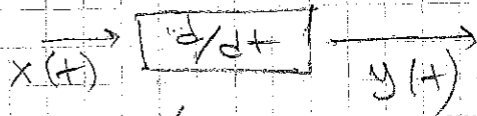

It is a linear system.

The system takes derivatives of input.

Ex 2

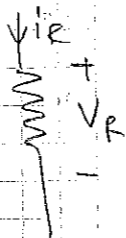

$$V_R = R \cdot i_R \text{ (Ohm's Law)}$$

If input: i_R , output: V_R , then is the simple resistor linear or not?

$$V_R(t) = R \cdot i_R(t) \text{ (Not derivative)}$$

① Homogeneity: $i_R'(t) = \alpha \cdot i_R(t)$

$$V_R'(t) = R (i_R'(t)) = R \alpha i_R(t)$$

$$= \alpha \cdot V_R(t)$$

② Additivity can be checked similarly.


A simple resistor is a linear component.

Ex 1: $V_x(t) = (i_x(t))^2 \rightarrow X$ (Both conditions are not satisfied)

$V_x(t) = i_x(t) + 1 \rightarrow X$ Homogeneity not satisfied.


$V_x(t) = i_x(t) \frac{di_x(t)}{dt} \rightarrow X$ Linearity and Homogeneity are not satisfied.

$2 \cdot V_x \neq V_{2x}$

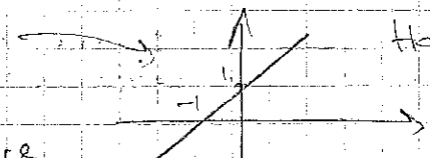


Hint: If the system is linear zero input should result in zero output.

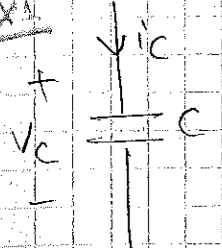Ex 2: $V_c(t) = C \frac{dV_c(t)}{dt} \rightarrow$ This is linear. ✓



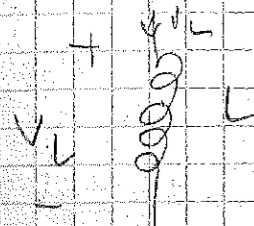$V_L(t) = L \frac{dI_L(t)}{dt} \rightarrow$ Linear ✓



Passive/active discussion:

If a resistor ever operates in power delivery region, then it is active. That is, if a resistor always absorbs ($p(t) \geq 0$) power \rightarrow passive.



Then if a memoryless component has an $i-v$ characteristic limited to 1st and 3rd quadrants \rightarrow passive component.

If it has a single operating point in 2nd or 4th quadrants then it is an active component.

Memoryless Component: A component whose branch current and voltage depend only on instantaneous values of the branch variables.

Ex 1: $V_x(t) = R \cdot I_x(t) \rightarrow$ Source, $V_x(t)$ depends only on the input at time t .

$V_L(t) = L \frac{dI_L(t)}{dt} \rightarrow$ Not memoryless (only to and $L(t_0)$ wait to enough)

$V_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau \rightarrow X$ Not memoryless/a component with memory

Time invariant + time varying components


Time invariant: The mathematical rule connecting input and output that does not depend on time \rightarrow Time-invariant system.

Time varying: Not time-invariant.

Ex:
$$V_p(t) = \begin{cases} 3 i_R(t) & t \geq 10 \\ 2 i_R(t) & t < 10 \end{cases} \quad \times \rightarrow \text{Time-varying}$$

Then mathematical rule connecting input $i(t)$ to output $V_p(t)$ depends on time, i.e. there is an 'if' statement in the mathematical rule depending on time.

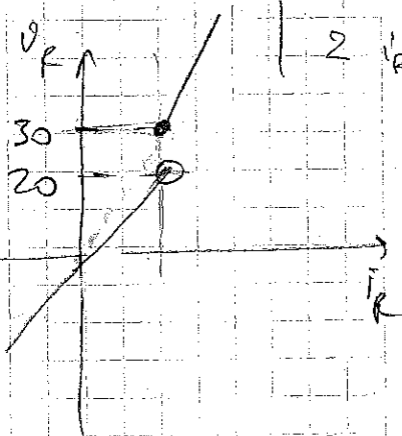
Ex:
$$V_p(t) = \begin{cases} 3 i_R(t), & i_R(t) \geq 10 \\ 2 i_R(t), & i_R(t) < 10 \end{cases}$$




\rightarrow Passive, non-linear, time-invariant, current controlled.

Dynamic and resistive circuits

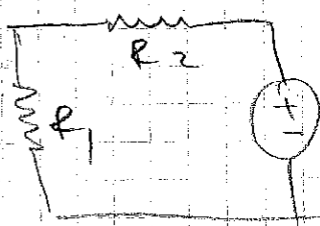If a circuit is composed purely of memoryless (resistors) components \rightarrow resistive circuits.



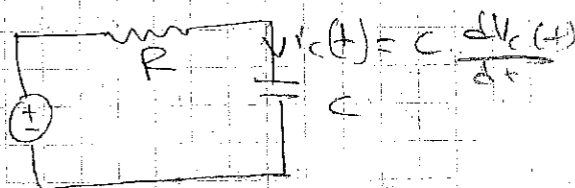
Dynamic Circuits: The circuit contains components which depend on the rate of change of circuit variables \rightarrow dynamic circuits.



HWK Please check ZPS-I and examine problems on the components, their classification and simple KVL/KCL applications.

In ZPS-I $\begin{matrix} \uparrow \\ V_c \\ \downarrow \\ C \end{matrix}$ $Q_c(t) = C \cdot V_c(t)$
 $\hookrightarrow \frac{d}{dt} \rightarrow i_c(t) \rightarrow C \frac{dV_c(t)}{dt}$

$Q = V \cdot C$

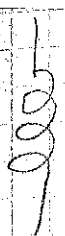

$$\phi(t) = L \cdot i(t)$$


$$\frac{d}{dt} \rightarrow V_c(t) = L \cdot \frac{di(t)}{dt}$$

Components:

- * Linear / Non-linear
- * Memoryless / Dynamic
- * Time-invariant / Time-varying
- * Passive / Active

Classification of Components

Unilateral / Bilateral Component:

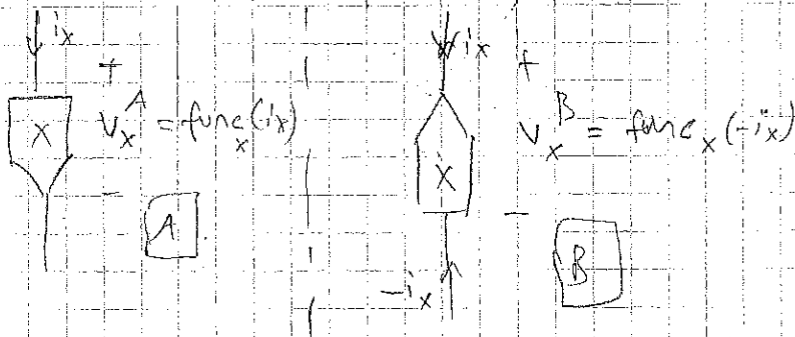

If component orientation & which side is up) does not matter \rightarrow bilateral component;
 (if it matters \rightarrow unilateral component.)

Then, for the same i_x , if I get the same V_x for components shown in **A** and **B**.

From Fig. **B**, $\rightarrow V_x^B = -func_x(-i_x)$ } So, $V_x^A = V_x^B (V_{i_x})$
 $\Leftrightarrow func_x(i_x) = -func_x(-i_x)$


Fig **A**, $\rightarrow V_x^A = func_x(i_x)$

Bilateral !!!

Ex: Ohm's Law


- $V_x = R \cdot i_x \rightarrow$ Bilateral
- $V_x = R \cdot i_x^2 \rightarrow$ Unilateral
- $V_x = R \cdot i_x^3 \rightarrow$ Bilateral

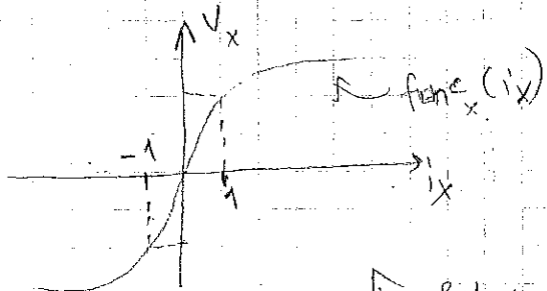A component whose (i, V) char. is symmetric with respect to origin is bilateral.



Bilateral


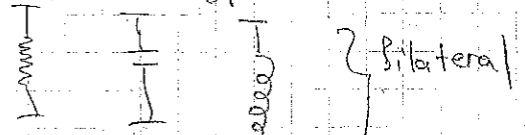
$$i_c(t) = C \cdot \frac{dV_c(t)}{dt} \rightarrow \text{Bilateral}$$



Unilateral



Not symmetric w.r.t. origin

Circuits / Electrical Networks

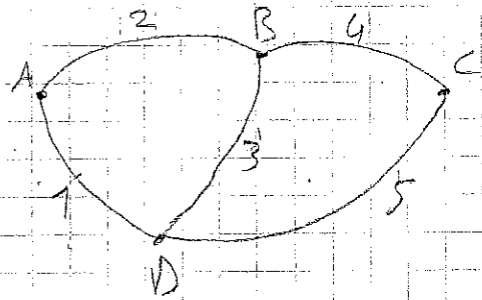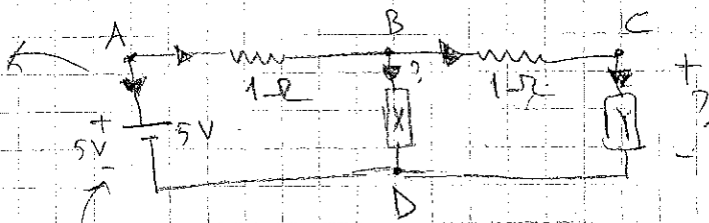

Notation for DC sources = $\oplus 5V$

Directed graph of the circuit

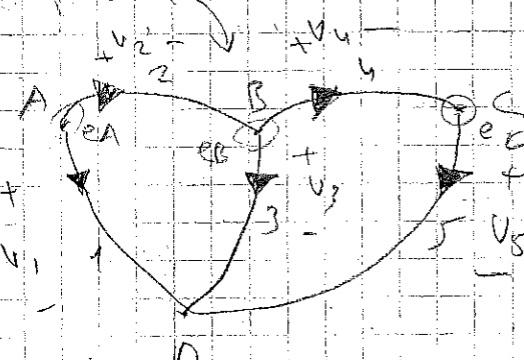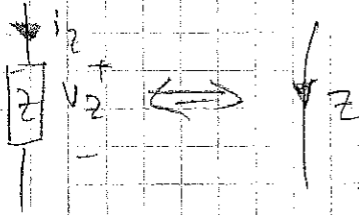

Graph of the circuit

Incidence matrix

$$A = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\ \begin{matrix} A \\ B \\ C \\ D \end{matrix} & \begin{bmatrix} 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 \\ -1 & 0 & -1 & 0 & -1 \end{bmatrix} \end{matrix}$$

Branch #5 leaves node C.
" " enters into node D.

Observation :

① About KCL: KCL at every node can be written:

$$\begin{matrix} 1^{st} \text{ Row} \rightarrow \\ A_a \end{matrix} \begin{bmatrix} 1 & 1 & 0 & 0 & 0 \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ \vdots & \vdots & \vdots & \vdots & \vdots \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \\ J_3 \\ J_4 \\ J_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \Rightarrow 1^{st} \text{ Row} \Rightarrow J_1 + J_2 = 0$$

Question: Is the equation system $A_a J = 0$

(4 equations with 5 unknowns for this example) redundant?

That is, are the equations independent?

$$\begin{aligned} x + y &= 2 \\ x - y &= -2 \\ 2x + 3y &= 5 \end{aligned}$$

$$\begin{bmatrix} 1 & 1 \\ 1 & -1 \\ 2 & 3 \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} 2 \\ -2 \\ 5 \end{bmatrix}$$

(or $3x + 4y = 7$)
we don't need this equation.

Rank of this matrix = 2
(smallest square matrix inside it)

Answer: $A \cdot J = 0$ equation system contains a single redundant equation.

$$A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 \end{bmatrix} \rightarrow A \cdot J = 0$$

Reduced Incidence Matrix

No redundant equations.

Comment: In general, we select a node (Node D in this example) as a reference node / Datum node / Ground Node and do not write KCL equations for this node, since it would be a redundant equation.

② About Branch Voltages

$$V = \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_5 \end{bmatrix}$$

Branch Volt. Vector

$$e = \begin{bmatrix} e_A \\ e_B \\ e_C \end{bmatrix}$$

Node Voltage Vector

Voltage between a node and datum / ground / reference node.

$$V = A^T \cdot e \rightarrow V = \begin{bmatrix} 1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & -1 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} e_A \\ e_B \\ e_C \end{bmatrix}$$

③ Conservation of Power (Tellegen's Theorem):

Branches

$$\sum_{k=1} V_k J_k = 0$$

Conservation of power statement.

$$P_k(t)$$

instantaneous power absorbed by k^{th} branch.

Proof:


branches

branches

$$\sum_{k=1} P_k(t) = \sum_k V_k(t) J_k(t) = [V_1 \ V_2 \ \dots \ V_k] \begin{bmatrix} J_1 \\ J_2 \\ \vdots \\ J_k \end{bmatrix} = V \cdot J = (A^T \cdot e) \cdot J = (e^T \cdot A) \cdot J = e^T (A \cdot J) = e^T \cdot 0 = 0$$

So, conservation of power is verified.

④ Mesh Matrix and Mesh Currents

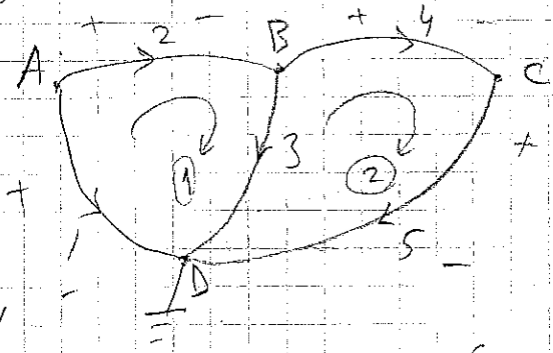

About KVL:

$$\text{Mesh}_1: +V_2 + V_3 - V_1 = 0$$

$$\text{Mesh}_2: V_4 + V_5 - V_3 = 0$$

$$\text{Outer mesh: } V_2 + V_4 + V_5 - V_1 = 0$$

Passive sign convention:

$$M_{ij} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Outer mesh KVL equation is redundant, so we focus on individual meshes

Mesh matrix

$$M \cdot V = 0$$

$$\begin{bmatrix} -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix}$$

Mesh currents!

$$\begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_m \end{bmatrix} = i$$

mesh current vector

$$\begin{aligned} J_1 &= -i_1 \\ J_2 &= i_1 \\ J_3 &= i_1 - i_2 \\ J_4 &= i_2 \\ J_5 &= i_2 \end{aligned}$$

$$J = M^T \cdot i$$

branch current vector

mesh current vector

this i_1 and i_2 are imaginary values, we can't measure them.

Dual Circuits/Variables/Graphs etc.

Previously we have expressed a circuit in terms of node voltages or mesh currents, To do that we have used KCL and KVL equations and we have observed that the theory is very similar for both cases.

Node Analysis

$$A \cdot J = 0$$

$$V = A^T \cdot e$$

branch current vector

branch voltages

node voltage

Mesh Analysis

$$M \cdot V = 0$$

$$J = M^T \cdot i$$

branch voltage vector

branch current

mesh current

Dual component

A dual component is a component whose math. description is achieved by the interchange of current (i) and voltage of the original component.

Ex: $v = 2(i)^2 \xleftrightarrow{\text{Dual}} i = 2(v)^2 \leftarrow \text{Interchange } i \leftrightarrow v$

$v_{(i)} = k \frac{di(t)}{dt} \xleftrightarrow{\text{Dual}} i(v) = k \frac{dv(t)}{dt}$

(k Henry Inductor)

(k Farad capacitor)

$v = R \cdot i \xleftrightarrow{\text{Dual}} i = R \cdot v$

(R resistor)

(R resistor)

Dual Variables

Duals Components

flux \leftrightarrow charge
Volt \leftrightarrow current

R \leftrightarrow $\frac{1}{R}$
k F (cap.) \leftrightarrow k H (inductor)


Volt source \leftrightarrow Current source

Dual Equations

KVL \leftrightarrow KCL


Dual circuit

ON Wednesday

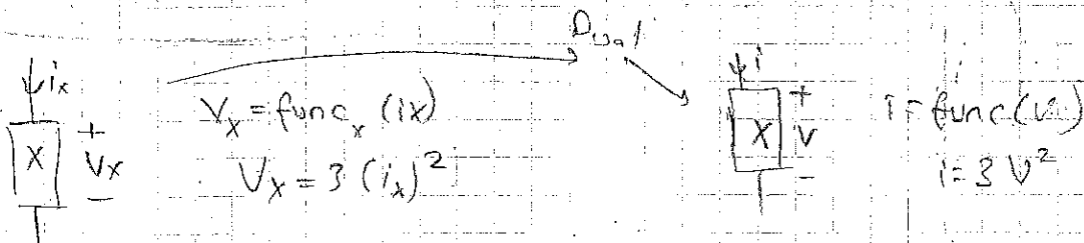

Alam asosiyonlu
★★

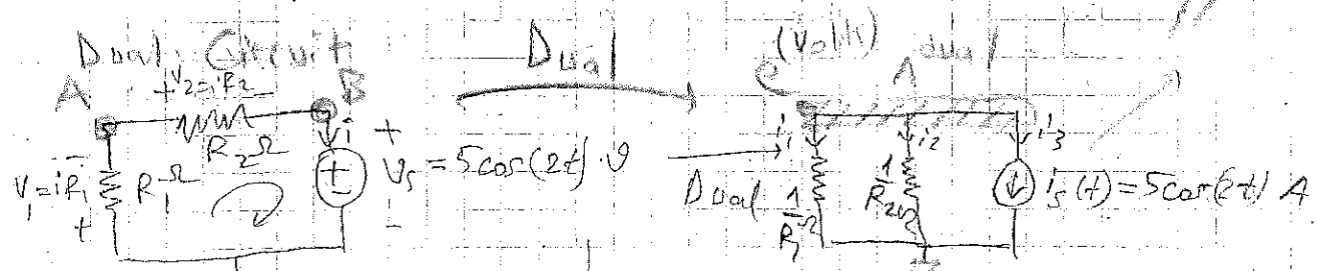Ex: $i(t) = k \frac{dv(t)}{dt} \xleftrightarrow{\text{Dual}} v(t) = k \frac{di(t)}{dt}$ C \leftrightarrow L Dual




KVL: $+v_1 + v_2 + v_3 = 0$
 $iR_1 + iR_2 + 5\cos 2t = 0$
 $i = -\frac{5\cos 2t}{R_1 + R_2} A$

KCL at A: $i_1 + i_2 + i_3 = 0$
 $\frac{e}{R_1} + \frac{e}{R_2} + 5\cos(2t) = 0$
 $e = -\frac{5\cos(2t)}{R_1 + R_2} \text{ Volts}$

Circuits A and B are duals of each other if branch voltages of say circuit A is identical to the branch currents of circuit B.


How to find dual circuit?

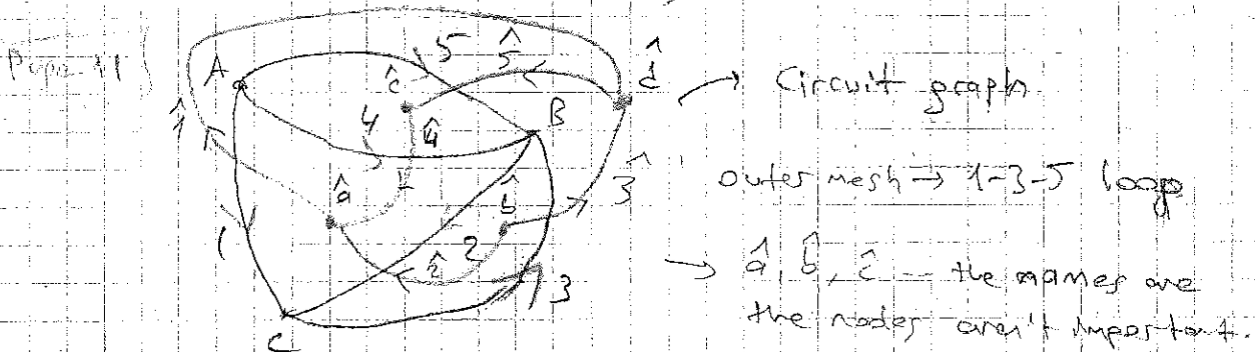- ① Map components to their dual components.
- ② Map circuit configuration to the dual configuration. (Parallel \leftrightarrow Series)





How to find dual graph?

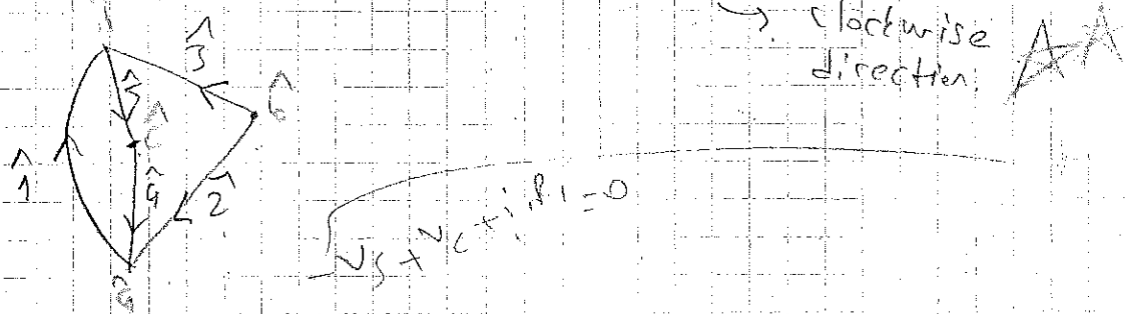- ① Place a node at the center of each mesh including outer mesh.
- ② Every branch is now in between two nodes that we put.
- ③ Connect the nodes we put and rotate the direction of the link in the circuit graph by 90° .



Ex

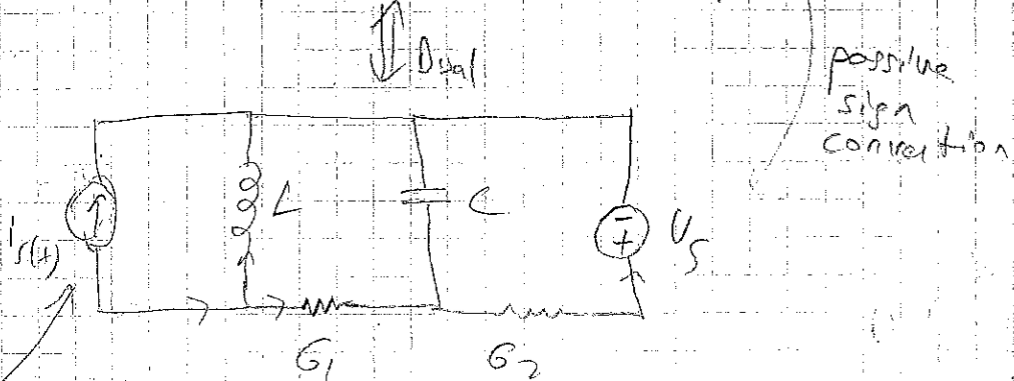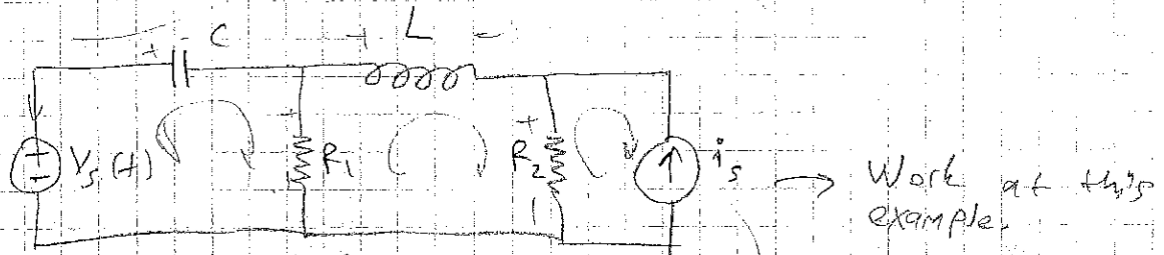


wrong direction


Series and Parallel Combination

Circuit Simplification

Our only focus

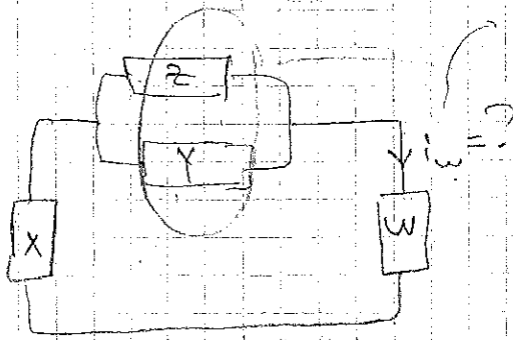

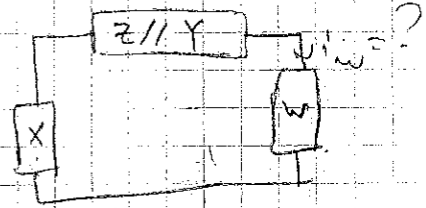Simplify two components into an equivalent single component.



Series combination of LTI resistors

LTI (Linear Time-Invariant) Resistor $\rightarrow V = iR$



$$V_{R1} = R_1 \cdot i_x$$

$$V_{R2} = R_2 \cdot i_x$$


$$+ \quad V_x$$

|||

$$V_x = V_{R1} + V_{R2}$$


$$= R_1 \cdot i_x + R_2 \cdot i_x$$

$$V_x = (R_1 + R_2) i_x$$

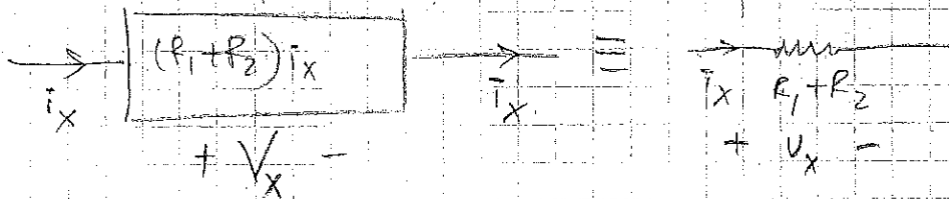


Parallel Combination

Passive Sign Conventions

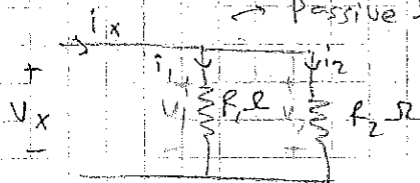

\Leftrightarrow

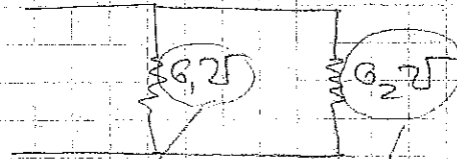

$$i_x = i_1 + i_2$$

$$= \frac{V_x}{R_1} + \frac{V_x}{R_2}$$

$$G_1 V_x = \frac{1}{R_1} V_x$$

$$\frac{1}{R_2} V_x$$



$$i_x = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_x \rightarrow V_x = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} i_x$$

The box is equivalent to resistance $\left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$ or $(G_1 + G_2)^{-1}$

$$G_1 = \frac{1}{R_1}$$

Conductance of a resistor.

Source Transformation

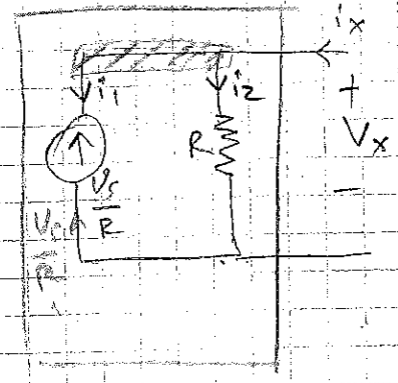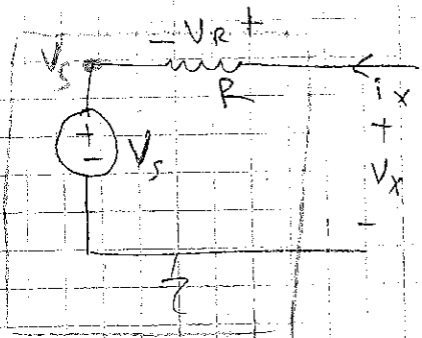

$$V_R = V_x - V_s$$


$$i_R = \frac{V_R}{R} = \frac{V_x - V_s}{R}$$

$$i_x = i_1 + i_2$$

$$i_x = \frac{-V_s}{R} + \frac{V_x}{R}$$



$$i_x = \frac{V_x - V_s}{R}$$

The same

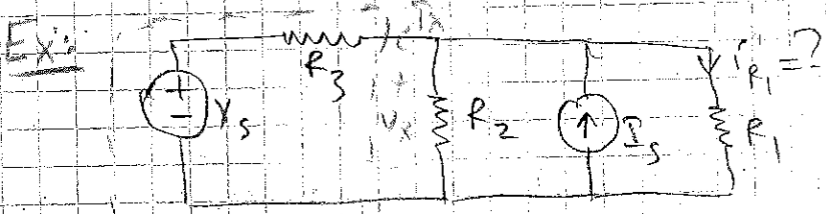


Find i_{R_1}
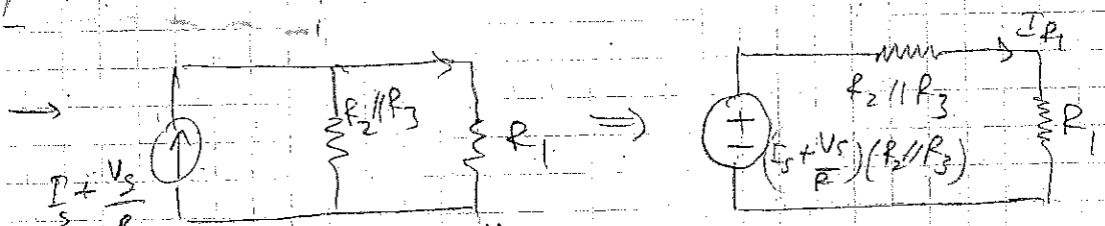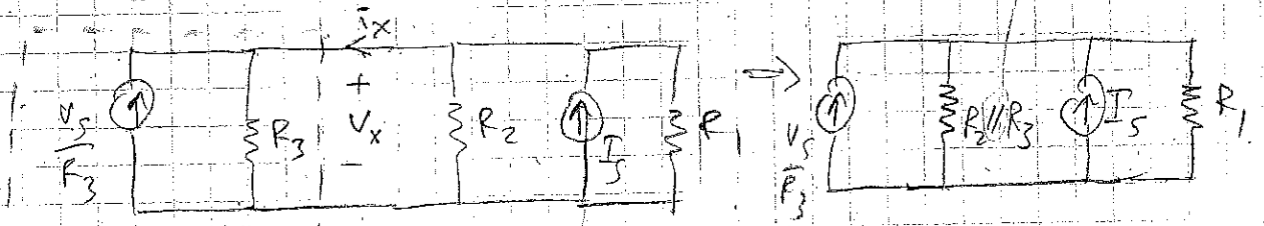
$$R_2 // R_3 = \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$


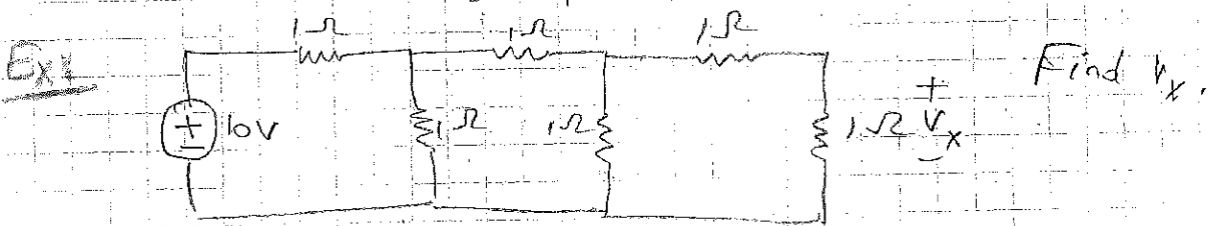
$$I_{R_1} = \frac{\left(I_s + \frac{V_s}{R_3} \right) (R_2 // R_3)}{R_2 // R_3 + R_1}$$




Find V_x

Ladder Network

I will use linearity of the circuit, that is all components in the circuit is linear, hence the relation between input (10V source) and output V_x .

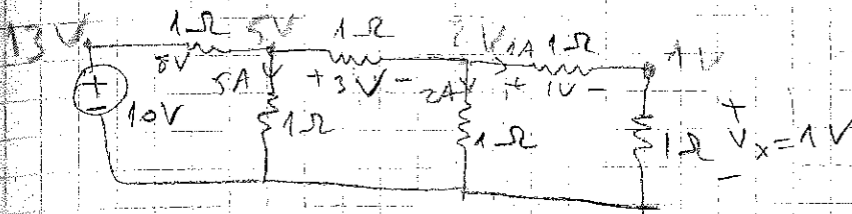Let's make a guess on V_x . Let $V_x = 1V$




Then if V_5 were 13V
 $\rightarrow V_x$ would be 1V.
 But I know $V_5 = 10V$
 and circuit is linear.

$$\frac{13}{10} = \frac{1}{V_x} \quad V_x = \frac{10}{13} V$$

Solution is achieved by making use of linearity of the circuit.

Node Analysis Method

Ex1

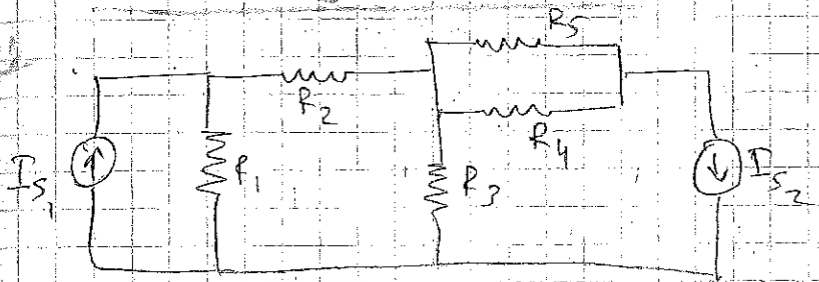

Find branch voltages and branch currents.

Circuit Analysis: Goal: finding branch currents and voltages such that;

- ① All component equations (terminal equations) should be satisfied,
- ② KCL equations should be satisfied, \leftarrow # of independent KCL equations = # of nodes - 1
- ③ KVL " " " " " "

\leftarrow # of independent KVL equations = # of meshes (Not counting outer mesh)
 (only valid for planar circuits)


From ① 7 branch currents/voltages should be set such that each branch component's $i-v$ relation is satisfied.

- ② 3 independent KCL equations (constraints) $\rightarrow i_1 + i_2 - i_3 = 0$ (constraint)
- ③ 4 " " KVL constraints.

Apply Node Analysis (Nodal Analysis)

Procedure

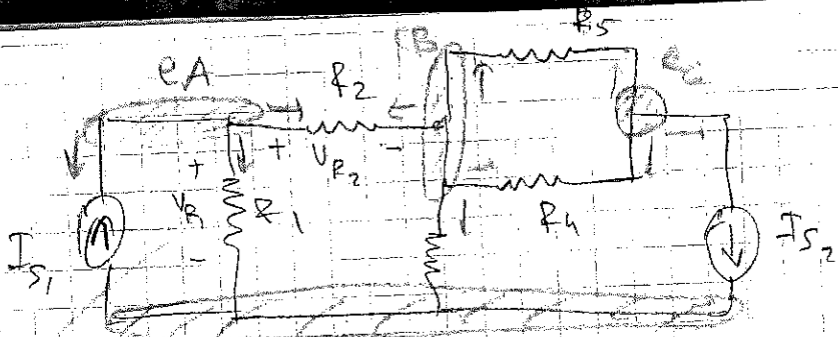- ① Select a datum node
- ② Assign node voltages to the remaining nodes (e_1, e_2, \dots), (e_A, e_B, \dots)
- ③ Write KCL at every node except reference/datum using node voltages.
- ④ Solve KCL equations \rightarrow find node voltages \rightarrow find branch voltages \rightarrow find branch currents.



0 Volts

KCL at e_A : $-I_{S1} + \frac{e_A}{R_1} + \frac{e_A - e_B}{R_2} = 0$

$V_{R1} = e_A - 0 = e_A$

KCL at e_B : $\frac{e_B}{R_3} + \frac{e_B - e_C}{R_4} + \frac{e_B - e_C}{R_5} + \frac{e_B - e_A}{R_2} = 0$

KCL at e_C : $\frac{e_C - e_B}{R_4} + \frac{e_C - e_B}{R_5} + I_{S2} = 0$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} & 0 \\ -\frac{1}{R_2} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} & -\frac{1}{R_4} - \frac{1}{R_5} \\ 0 & \frac{1}{R_4} - \frac{1}{R_5} & \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} e_A \\ e_B \\ e_C \end{bmatrix} = \begin{bmatrix} I_{S1} \\ 0 \\ -I_{S2} \end{bmatrix}$$

↳ Solve for e_A, e_B, e_C

Then, since any branch is between two nodes, the branch voltages can be found immediately from node voltages.


$V_{R1} = e_A - 0 = e_A$, $V_{R4} = e_B - e_C$, ...

Then, every branch voltage is known, from component equations, branch currents can be immediately calculated.

$I_{R4} = \frac{V_{R4}}{R_4}$, ...

Node analysis aims to find node voltages (e_A, e_B, \dots) and unknowns of node analysis should be only node voltages.

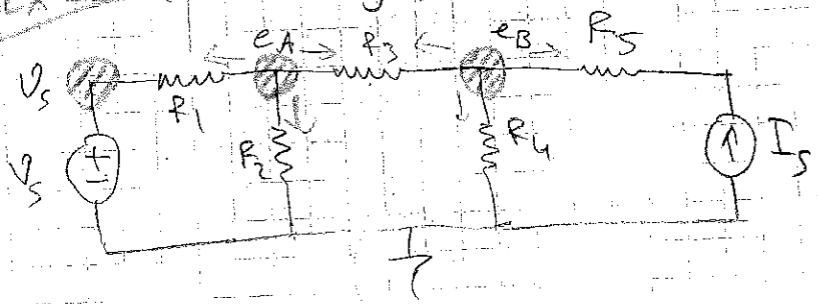Ex 2 (Node analysis with voltage sources)




50V (important!)

$$\text{KCL at } e_A: \frac{e_A - v_s}{R_1} + \frac{e_A}{R_2} + \frac{e_A - e_B}{R_3} = 0$$

$$\text{KCL at } e_B: \frac{e_B}{R_3} + \frac{e_B - e_A}{R_3} - I_s = 0$$

2 equations and 2 unknowns
solve for e_A and e_B

Ex: (Super-node)

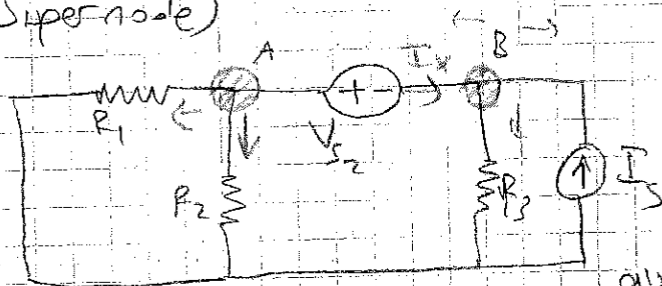

$$\text{KCL at } e_A: \frac{e_A}{R_1} + \frac{e_A}{R_2} + I_x = 0 \quad \text{(I)}$$

$$\text{KCL at } e_B: \frac{e_B}{R_3} - I_s - I_x = 0 \quad \text{(II)}$$

2 equations
3 unknowns

$$\text{Auxiliary Equation: } e_A - e_B = v_{s2} \quad \text{(III)}$$

3rd equation

Let's solve for e_A and e_B ($e_A - v_{s2}$)

$$\text{(I)} + \text{(II)} \rightarrow \frac{e_A}{R_1} + \frac{e_A}{R_2} + \frac{e_B}{R_3} - I_s = 0$$


$$\text{(III)} \rightarrow e_A - e_B = v_{s2}$$

$$\text{(I)} \quad e_A = \frac{I_s + \frac{v_{s2}}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \text{ Volts}$$

$$\text{(II)} \quad e_B = e_A - v_{s2} \text{ Volts}$$


(III)

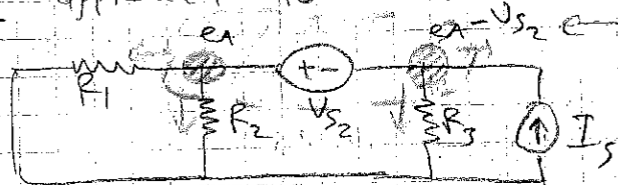Instead of introducing auxiliary variable I_x , we may use supernode approach to shorten the solution.



$$\text{KCL at supernode: } \frac{e_A}{R_1} + \frac{e_A}{R_2} + \frac{e_A - v_{s2}}{R_3} - I_s = 0$$

Ex. EPS-2
Pt. 3f

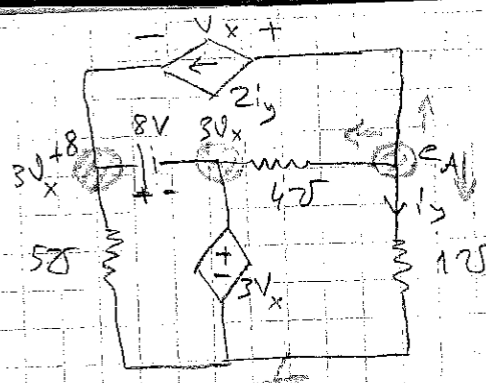

Apply node analysis and find branch currents & voltages.

KCL at eA:

$$\frac{eA}{1} + \frac{eA - 3V_x}{4} + 2iy = 0$$

iy in terms of node voltages

$$iy = \frac{eA}{1}$$

$$V_x = e_A - (3V_x + 8)$$

$$V_x = \frac{e_A - 8}{4}$$


$$e_A + \frac{e_A - \frac{3}{4}(e_A - 8)}{1/4} + 2e_A = 0$$

$$e_A + 4e_A - 3e_A + 24 + 2e_A = 0$$

$$4e_A = -24$$

$$e_A = -6A$$

$$V_x = \frac{7}{2} \text{ Volts}$$

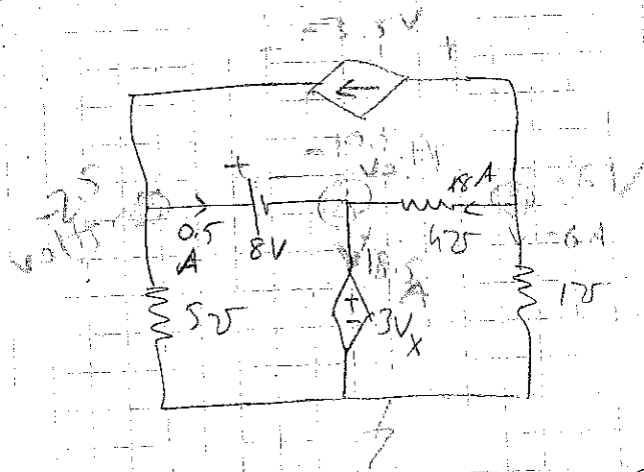

Power of 8V source =

$$P_{8V} = V(+).i(+)$$

$$= 8 \times \frac{1}{2} = 4 \text{ watts}$$

4 Watts absorbed

$$P_{3V_x} = (18.5) \times (-10.5) = -194.25 \text{ watts}$$

absorbed

$$= 194.25 \text{ watts}$$

delivered

$$P_{2iy} = (-3.5)(-12) = 42 \text{ watts}$$

absorbed

$$P_{1\Omega} = \frac{V^2}{R} = 36 \text{ watts}$$

$$P_{5V} = I^2 R = (12.5)^2 \cdot \frac{1}{5} = (2.5)(12.5) = 31.25 \text{ watts}$$


$$P_{4V} = I^2 R = 18^2 \cdot \frac{1}{4} = 81 \text{ watts}$$

Let's check whether power is conserved

$$P_{30V} + P_{21V} + P_{5V} + P_{5V} + P_{4V} + P_{12V} \stackrel{?}{=} 0$$

$$-194.25 + 42 + 4 + 31.25 + 81 + 36 = 0 \quad \checkmark$$


Gives me absorbed power in watts

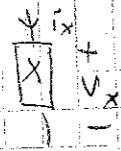

Also check Alexander-Sadiku for Node and Mesh analysis


for a planar circuit, the possible analysis is the mesh analysis.
Planar circuit: A circuit whose graph can be drawn on two dimensional surface, i.e. drawn on paper.

Non-planar graph:

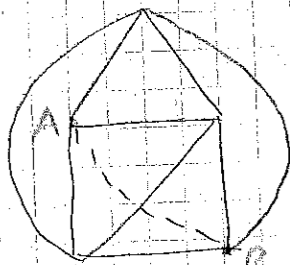

Non-planar graph

positive sign convention

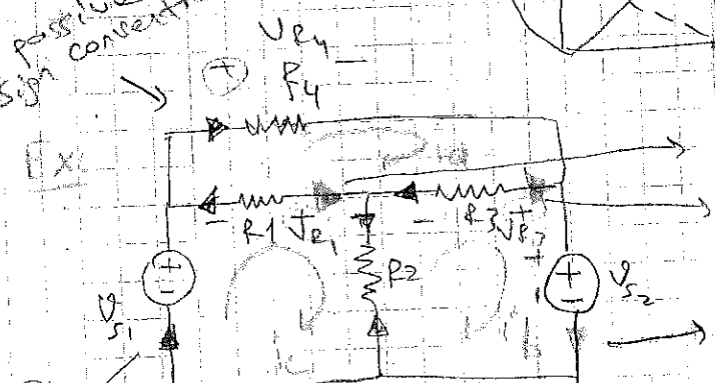

A ↔ B connection cannot be made on a 2-D plane.

Branch current of $R_1 = i_{R_1} = i_1 - i_3$
 $i_{R_2} = i_2 - i_3$
 $i_{R_3} = i_3 - i_1$

Since circuit is planar, mesh analysis is applicable. To do mesh analysis:

- 1) Introduce mesh currents in each mesh,
- 2) Write KVL equations using mesh currents as unknowns.
- 3) Solve for mesh currents → get branch currents → get branch voltages from component equations

KVL around i_a : $V_{R_4} + V_{R_3} + V_{R_1} = 0$

$$R_4 (i_a) + R_3 (i_a - i_b) + R_1 (i_a - i_c) = 0$$

KVL around i_b : $R_2 (i_b - i_c) + R_3 (i_b - i_a) + V_{S_2} = 0$


KVL around i_c mesh: $-V_{S_1} + R_1 (i_c - i_a) + R_2 (i_c - i_b) = 0$

Every branch voltage can be found $V_{R_3} = i_{R_3} R_3$ every branch current can be found $i_{R_3} = i_b - i_a$ solve for i_a, i_b, i_c

3 eqns 3 unknown

(Previous question) $3V_x$

Ex 1

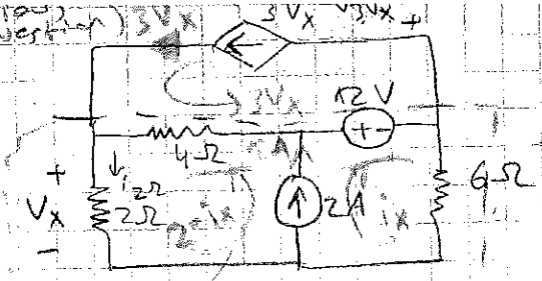

? $i_x = 2$
 ? $= 2 - i_x$

Supermesh

$$V_x = 2 \cdot i_2 \cdot \Omega = 2(2 - i_x)$$

KVL: $4(3V_x) + i_x \cdot 2 + 12 + 6i_x + 2(i_x - 2) = 0$
 $6(2 - i_x)$

$$i_x = \frac{-40 - 12 + 4}{-20 + 6 + 2}$$

$$i_x = \frac{-48}{-12} = 4A$$

KVL for V_{3V_x} : $-12 + 4(2 - i_x - 3V_x) - V_{3V_x} = 0$


$$V_{3V_x} = -12 + 4 \cdot 10$$

$$V_{3V_x} = 28V$$

1 KVL equation
 # of meshes
 - # of CS = 1

Analyze the circuit.

Ex 2

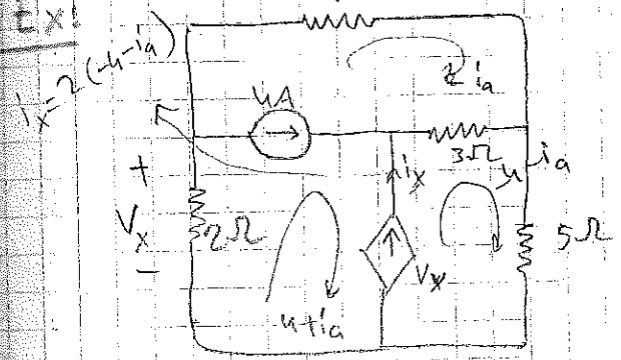

Mesh Analysis

Only one unknown i_a
 Outer mesh is supermesh


Node Analysis

e_a, e_b, e_c 3 unknowns to solve

★ General comment on # of equations for Node/Mesh analysis.

- (1) Mesh analysis: # unknowns = # meshes - # of current sources (dependent or independent)
- (2) Node analysis: # of unknowns = # of nodes - # of voltage sources (dependent or independent)

Ex 1

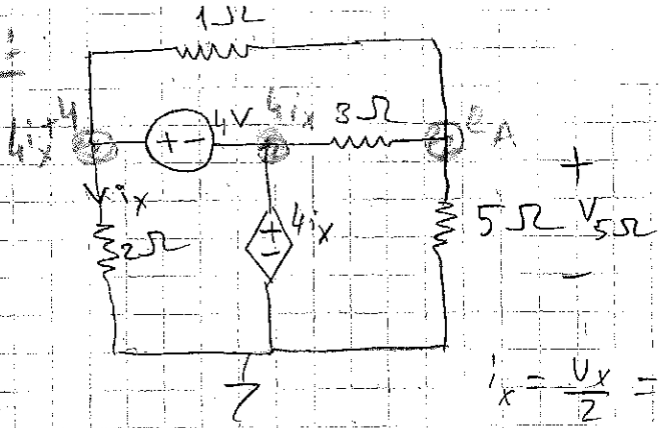

Analyze the circuit and find $V_{5\Omega}$


$$i_x = \frac{V_x}{2} = \frac{4i_x + 4}{2} \rightarrow i_x = -2A$$

KCL at e_A :

$$\frac{e_A}{9} + \frac{e_A - (-8)}{3} + \frac{e_A - (-4)}{1} = 0$$

$$\rightarrow e_A = \frac{-40 - 60}{3 + 5 + 1} = \frac{-100}{9} \text{ Volts}$$

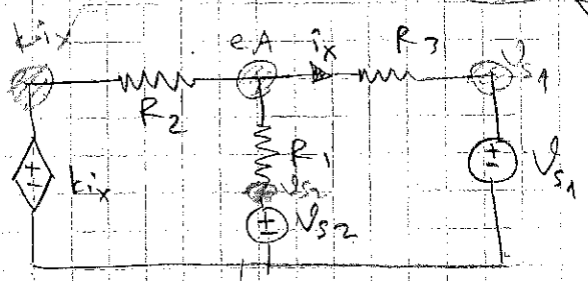Circuits with multiple (inputs) (independent sources)



Analyze using node analysis


KCL at e_A :

$$\frac{e_A - V_{s2}}{R_1} + \frac{e_A - kix}{R_2} + \frac{e_A - V_{s1}}{R_3} = 0$$

$$i_x = \frac{e_A - V_{s1}}{R_3}$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} - \frac{k}{R_2 R_3} + \frac{1}{R_3} \right) e_A = \frac{1}{R_1} V_{s2} - \frac{k}{R_2 R_3} V_{s1} + \frac{1}{R_3} V_{s1} \quad (I)$$

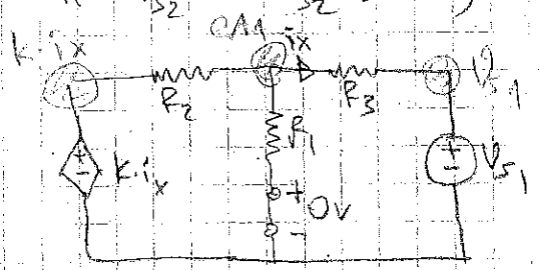If $V_{s2} = 0$ (V_{s2} is OFF) and $V_{s1} \neq 0$ (V_{s1} is ON)




KCL at e_{A1}

$$\frac{e_{A1}}{R_1} + \frac{e_{A1} - kix}{R_2} + \frac{e_{A1} - V_{s1}}{R_3} = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} - \frac{k}{R_2 R_3} + \frac{1}{R_3} \right) e_{A1} = \frac{-k V_{s1}}{R_2 R_3} + \frac{V_{s1}}{R_3} \quad (A_1)$$

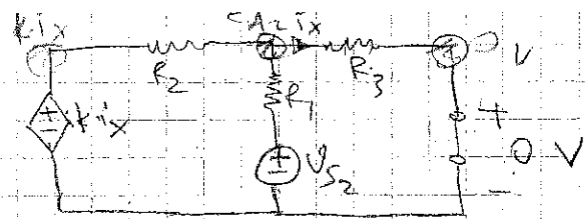(★₂) Take $V_{S1} = 0$ (OFF)
 $V_{S2} = ON$



Relate e_{A2} :

$$\left(\frac{e_{A2} - V_{S2}}{R_1} \right) + \frac{e_{A2} - kix}{R_2} + \frac{e_{A2}}{R_3} = 0$$

$$i_x = \frac{e_{A2}}{R_3}$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} - \frac{k}{R_2 R_3} + \frac{1}{R_3} \right) e_{A2} = -\frac{1}{R_1} V_{S2} \quad (\star_2)$$

If $V_{S1} = ON$, $V_{S2} = ON$, can I use (★₁) and (★₂) solutions to find the solution (general solution for $V_{S1} \neq 0, V_{S2} \neq 0$)?

A: $e_A = e_{A1} + e_{A2}$

Solution of ★₁

Solution of ★₂

$$A \cdot e = b_1 \cdot V_{S1} + b_2 \cdot V_{S2}$$



$$e = \begin{bmatrix} e_A \\ e_B \end{bmatrix}$$

$$e = A^{-1} (b_1 V_{S1} + b_2 V_{S2})$$

$$= (A^{-1} b_1 V_{S1}) + (A^{-1} b_2 V_{S2})$$

Superposition

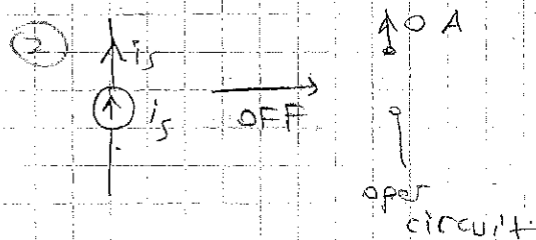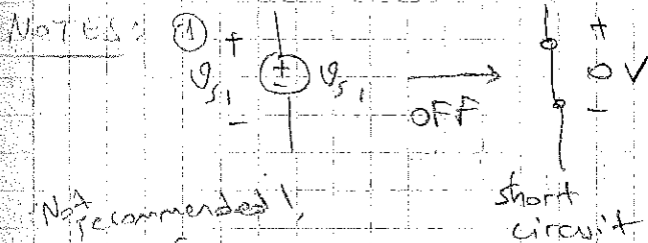
Principle: For linear circuits, the output can be calculated by individually turning off/on the independent sources and summing the response to each ON/OFF configuration.




Not recommended!

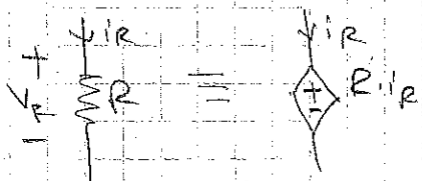(3) Never try to turn ON/OFF dependent sources (dependent components).

A dependent source is just another component; it is not an input to the circuit; hence like all components it affects LHS of node/mesh equation. Always remember that a simple resistor can also be described as a dependent source.



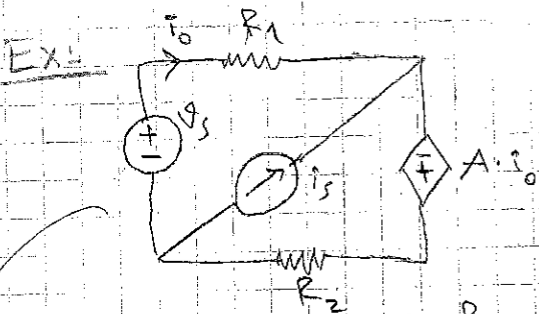


Find i_0 (Apply Superposition)

$$i_0 = \left(\begin{matrix} ? \\ - \\ ? \end{matrix} \right) V_s + \left(\begin{matrix} ? \\ - \\ ? \end{matrix} \right) I_s$$

\uparrow a scalar \uparrow a scalar

(I) V_s : OFF
 I_s : ON

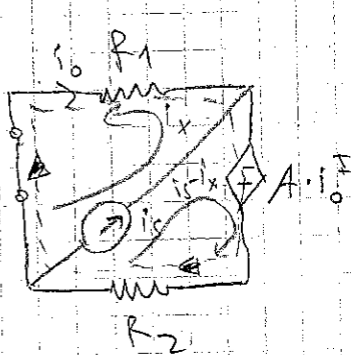


$$R_1(-i_x) - A i_0 + R_2(i_s - i_x) = 0$$

$$i_x = \frac{-R_2}{-R_1 + A - R_2} i_s$$

$$i_0^I = \frac{R_2}{A - R_1 - R_2} \cdot i_s$$

$$i_x(A - R_1 - R_2) + R_2 i_s = 0$$

(II) V_s : ON
 I_s : OFF

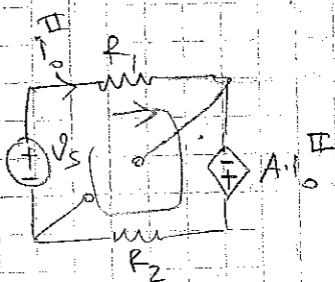

KVL:



$$-V_s + R_1 i_0^II - A i_0^II + R_2 i_0^II = 0$$

$$i_0^II = \frac{1}{R_1 + R_2 - A} V_s$$

When V_s : ON
 I_s : ON $\rightarrow i_0 = i_0^I + i_0^II$

$$i_0(t) = \left(\frac{R_2}{A - R_1 - R_2} \right) i_s(t) + \left(\frac{-1}{A - R_1 - R_2} \right) V_s(t)$$

Δ -Y Transformation


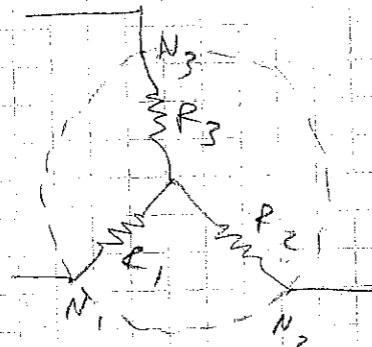
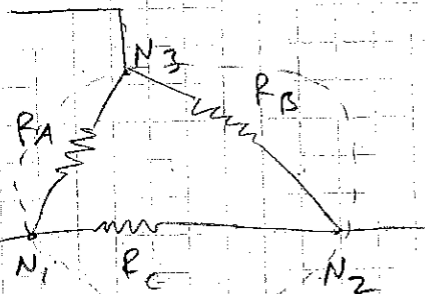


Δ -connection

Y-connection

$$Y \rightarrow \Delta \begin{cases} R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3} \\ R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2} \\ R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1} \end{cases}$$
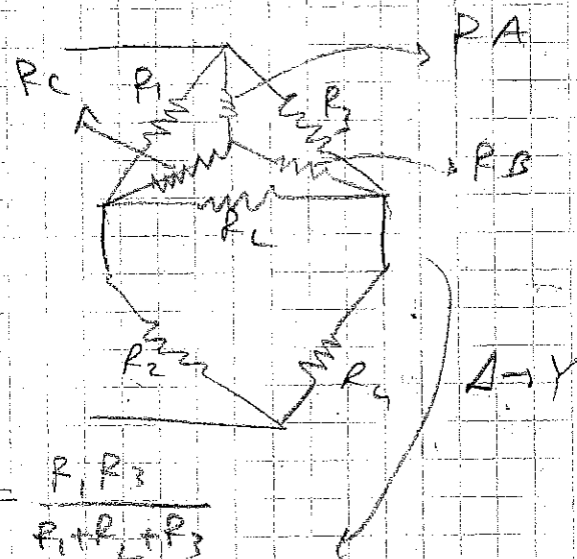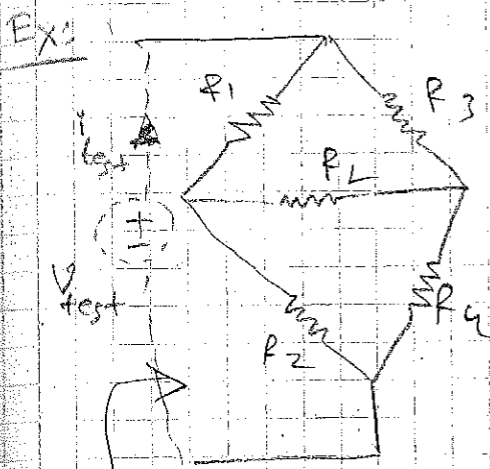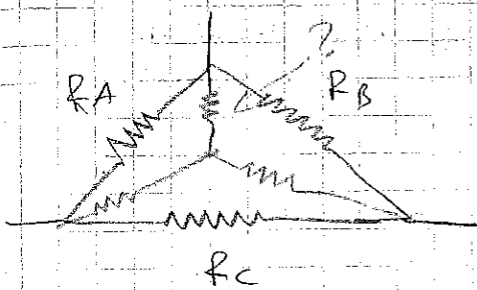
$$\Delta \rightarrow Y \begin{cases} R_1 = \frac{R_A R_C}{R_A + R_B + R_C} \\ R_2 = \frac{R_B R_C}{R_A + R_B + R_C} \\ R_3 = \frac{R_A R_B}{R_A + R_B + R_C} \end{cases}$$




$$R_A = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$



$$R_B = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$


$$R_{in} = \frac{V_{test}}{I_{test}}$$

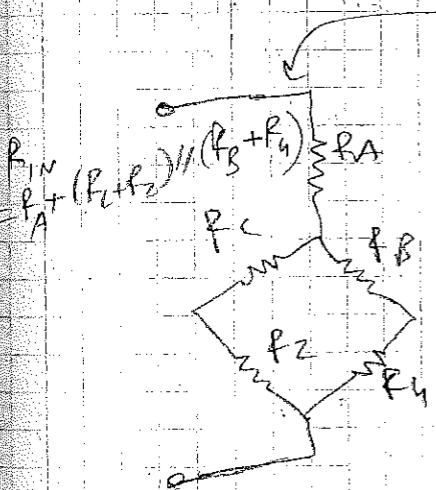

Input Resistance Calculation

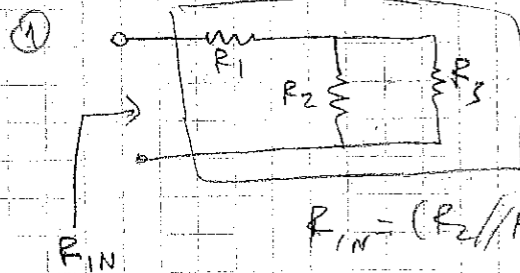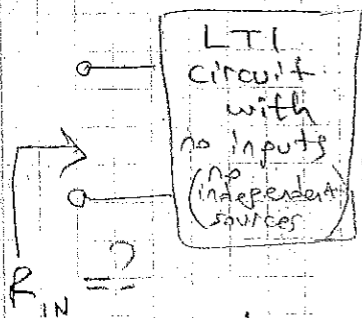

$$R_{in} = (R_2 // R_3) + R_1$$

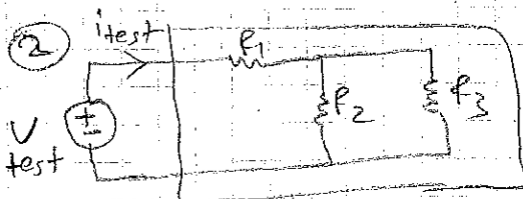


$$R_{in} = \frac{V_{test}}{I_{test}}$$

← Voltage applied
← Current measured (calculated)

So to find R_{in} I can apply V_{test} to the terminals of the box, and then "check" I_{test} . R_{in} is equal to $\frac{V_{test}}{I_{test}}$.


(or i_{test})

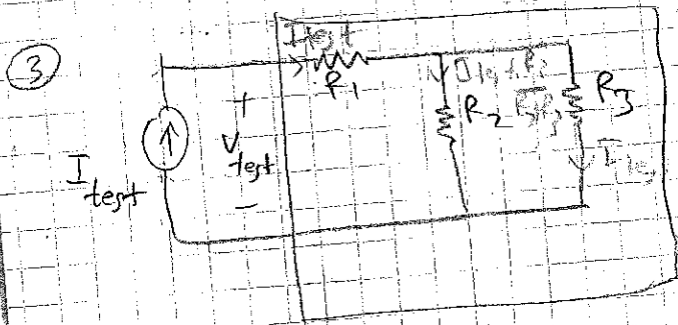

$$V_{test} = I_{test} R_1 + I_{test} \frac{R_2 R_3}{R_2 + R_3}$$

$$R_{in} = \frac{V_{test}}{I_{test}} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

Transformers:

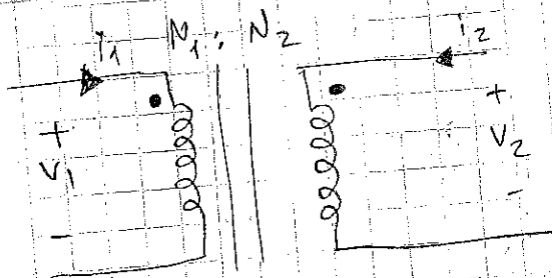


Transformer is a 2-part component. N_1, N_2 are called turns-ratios.


Transformer operates only the principle of rate of change of flux is proportional to the voltage (Faraday's Law).

Hence, transformers operate only with A.C. signals, but in EE 201 we introduce (assume) a hypothetical transformer which also operates with DC voltages.

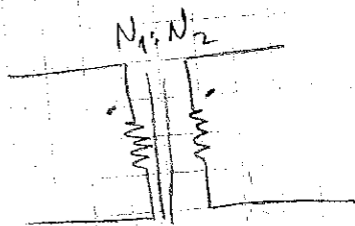This is the reason in problem sets of EE 201, the transformers are also shown as:



Terminal relations for transformer?

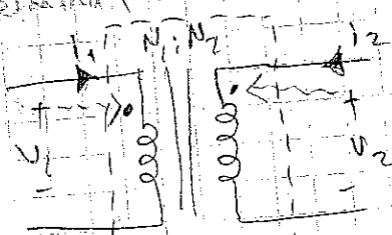


$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

(Voltages are proportional to turns ratio)


$$\frac{I_1}{I_2} = -\frac{N_2}{N_1}$$

(Currents are inversely proportional to turns ratio)

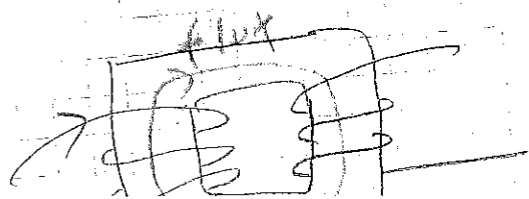These equations are correct for this dot configuration.



Power of a 2-port

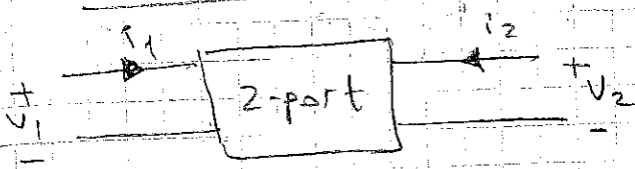

$$P_{2\text{-part}} = V_1 i_1 + V_2 i_2$$

For transformer:



$$P_{\text{Transformer}} = V_1 i_1 + V_2 i_2 = 0$$

$$= \frac{N_1}{N_2} i_1$$


Transformer doesn't consume energy

Please note the dots in the transformer symbol and how they define polarity of V_1, V_2 and direction of i_1, i_2 .

Thevenin - Norton Equivalents

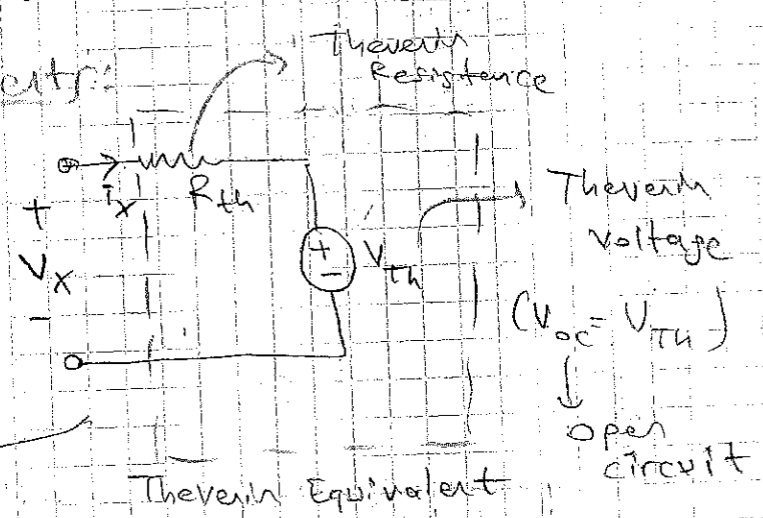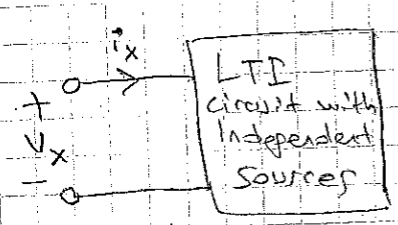

Thevenin Equivalent

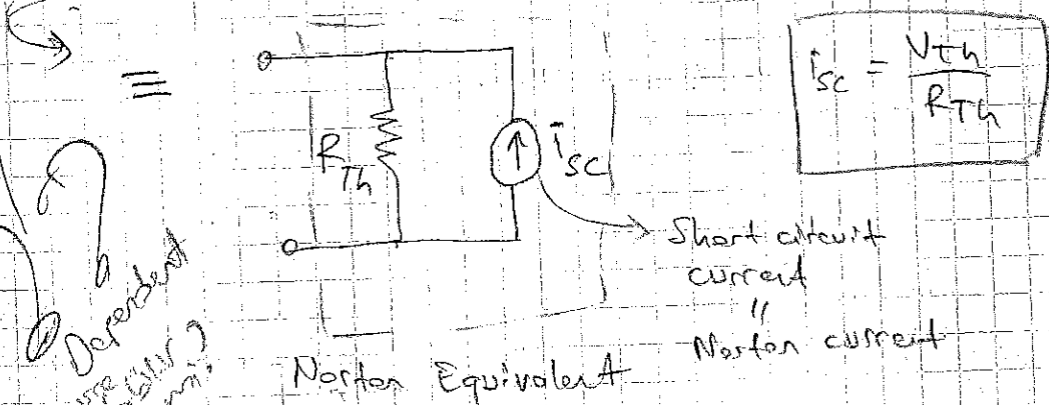

Norton Equivalent

Procedure for finding Thevenin - Norton Equivalents

- Procedure 1:
- (A) Find V_{oc}
 - (B) Find R_{th}


To find R_{th} :

(1) Turn-off all independent sources and find equivalent resistance seen from terminals of the box.

(2) Turn-off all independent source and apply V_{test} and

calculate I_{test} . $R_{th} = \frac{V_{test}}{I_{test}}$

Procedure ②: * V_{oc} (as before)

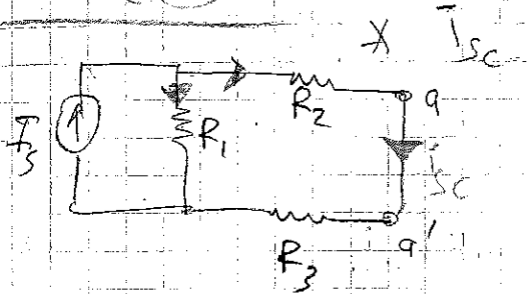


$$I_{sc} = I_s \cdot \frac{R_1}{R_1 + R_2 + R_3}$$


$$(V_{oc} = R_1 \cdot I_s)$$

$$\left. \begin{aligned} R_{Th} &= \frac{V_{oc}}{I_{sc}} \\ &= R_1 + R_2 + R_3 \end{aligned} \right\}$$

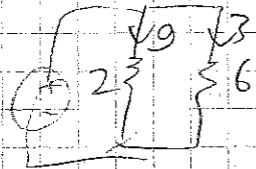Note: Pay attention to V_{oc} and I_{sc} signs and direction




Current Division:

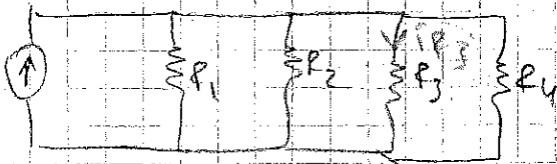


$$I_{R3} = \frac{\frac{1}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} I_s$$

G_3 (conductance)

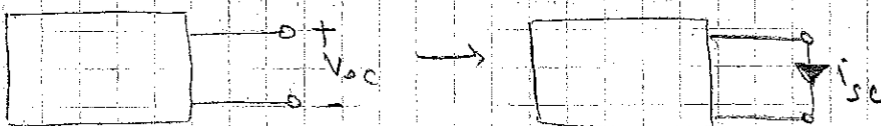
V_{oc} polarity and its relation with I_{sc} current:



Ex:

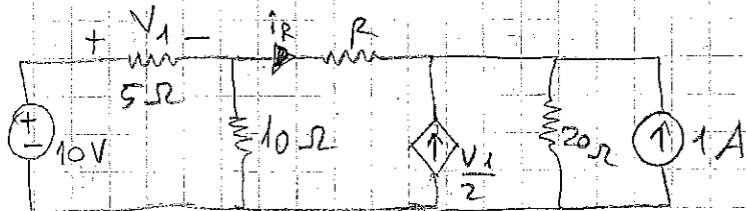

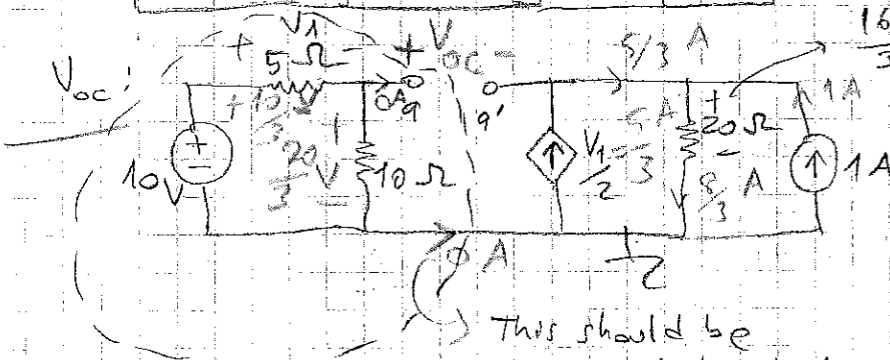Find i_R by finding Thevenin equivalent seen by R.




$$V_1 = \frac{10}{3} \cdot \frac{160}{17}$$

$$V_{a1} = \frac{160}{3} \text{ Volts}$$

$$V_{a2} = \frac{20}{3} \text{ Volts}$$

This should be zero or well by KCL.
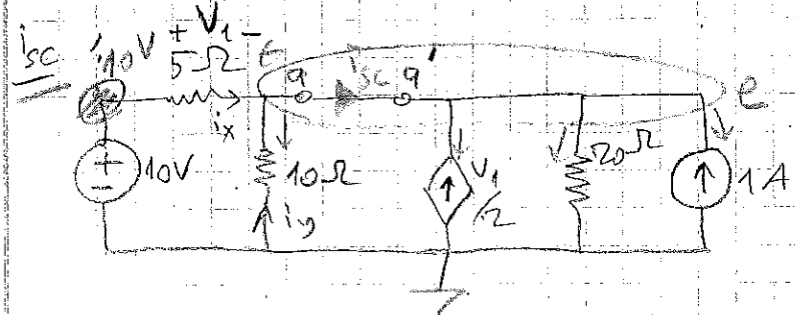
$$V_a - V_{a1} = V_{oc} = -\frac{140}{3} \text{ Volts}$$




KCL at e:

$$\frac{e-10}{5} + \frac{e}{10} - \frac{V_1}{2} + \frac{e}{20} - 1 = 0$$

$$e = \frac{40 + 100 + 20}{4 + 2 + 10 + 1} = \frac{160}{17} \text{ Volts}$$


$$I_{sc} = i_x + i_y = \frac{10 - e}{5} - \frac{e}{10} = 2 - \frac{3e}{10} = 2 - \frac{48}{17} = \frac{-14}{17} \text{ A}$$
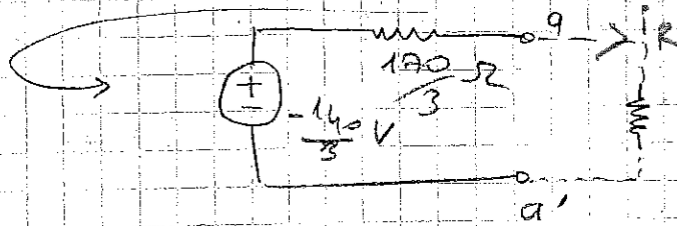
$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{-140/3}{-14/17} = \frac{170}{3} \Omega$$



Procedure (1):

Both using V_{test} method

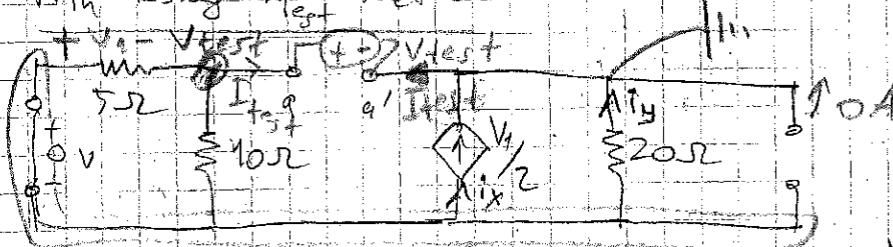


$$\text{KCL at } e: \frac{e - V_{test}}{5} + \frac{e - V_{test}}{10} + \frac{V_1}{2} + \frac{e}{20} = 0$$

$$\Rightarrow e = \frac{4 + 2 + 10}{4 + 2 + 10 + 1} V_{test} = \frac{16}{17} V_{test}$$

$$i_{test} = i_x + i_y = \frac{V_1}{2} + \frac{e}{20} = \frac{e - V_{test}}{2} + \frac{e}{20} = \frac{11e}{20} - \frac{V_{test}}{2}$$


$$= \frac{11}{20} \cdot \frac{16}{17} V_{test} - \frac{1}{2} V_{test} = \frac{88}{170} - \frac{85}{170} = \frac{3}{170} V_{test}$$
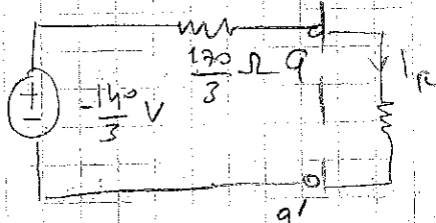
$$R_{Th} = \frac{V_{test}}{i_{test}} = \frac{V_{test}}{\frac{3}{170} V_{test}} = \frac{170}{3} \Omega$$




$$I_R = \frac{-140/3}{\frac{170}{3} + R} \text{ A}$$

Maximum Power Transfer

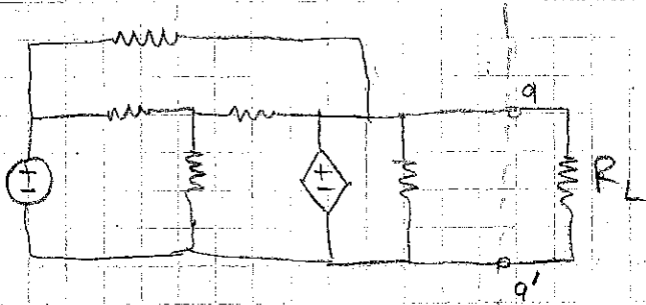

$$P_{R_L} = (i_{R_L})^2 \cdot R_L = \frac{V^2}{R_L}$$

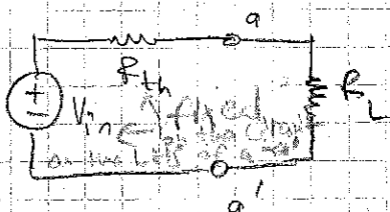→ Find the Thevenin equivalent of Left hand side (LHS) of a-a' line!



derivative = 0 (max. min problem)


$$\frac{d}{dR_L} P(R_L) = \left(V_{Th}^2 \cdot \left(\frac{1}{R_{Th} + R_L} \right)^2 \cdot R_L \right)' = V_{Th}^2 \cdot \left[\frac{1}{(R_{Th} + R_L)^2} - \frac{2R_L}{(R_{Th} + R_L)^3} \right] = 0$$

$$R_{Th} + R_L = 2R_L$$

$$R_{Th} = R_L$$



~~$R_{Th} = R_L$~~ can't be possible

A:

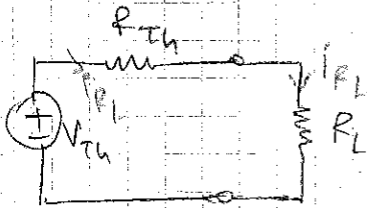

So efficiency is 50%!


Ex:

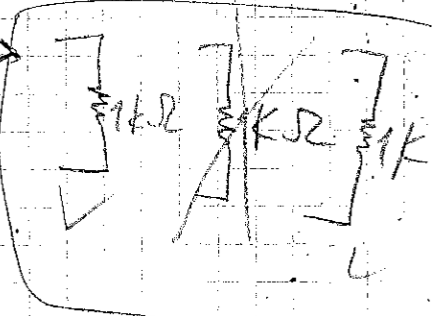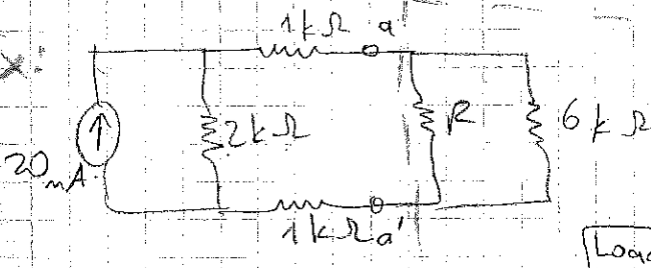


Q: Find R such that P_{Load} (Load is combination of R and $6k\Omega$) is maximized.

A: The resistance seen by the load should be identical to the load resistance for max. power transfer.

Thevenin equivalent of LHS of a-a':

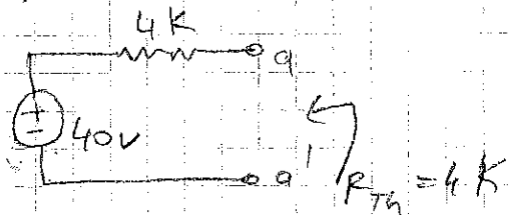


Thevenin Eq. of RHS of a-a':

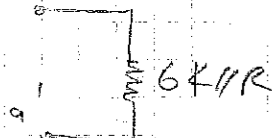


Then for max. power $4k = 6k || R$
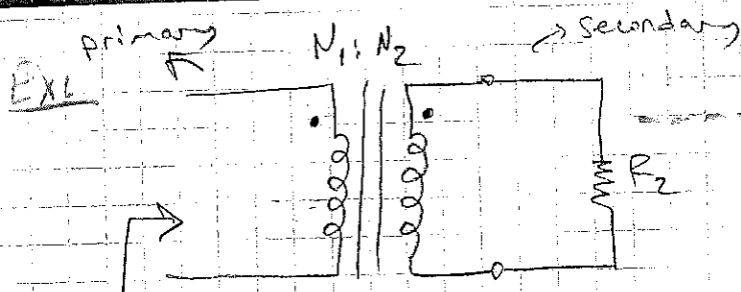
$$2 \cdot 4 = \frac{6R}{6+R} \quad 8R = 12 + 2R \quad \boxed{R = 12k}$$



Let's apply V_{test}

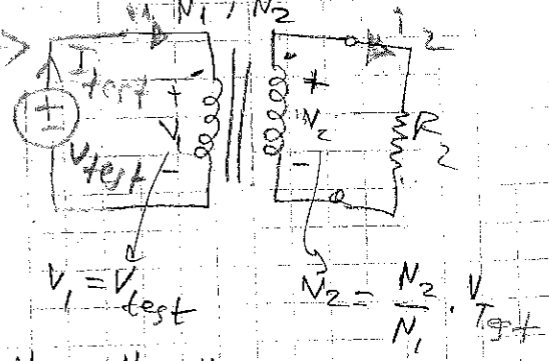

$R_1 = ?$ Resistance seen from primary side of transformer.

$$i_1 = \frac{N_2}{N_1} i_2$$


$$i_2 = \frac{V_2}{R_2} = \frac{N_2}{N_1} \frac{V_{test}}{R_2}$$

$$R_{in} = \frac{V_{test}}{i_{test}} = \frac{V_{test}}{\frac{N_2^2}{N_1^2} \frac{1}{R_2} V_{test}}$$

$$= R_2 \cdot \left(\frac{N_1}{N_2}\right)^2$$

(Resistance Reflection Rule)

Ex:

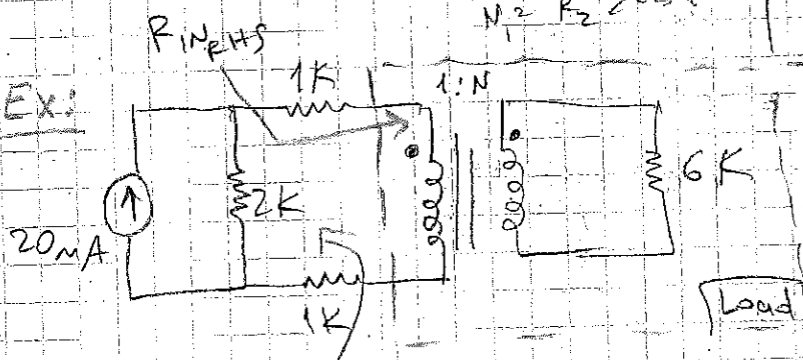


Find N (turns ratio) such that P_{Load} is maximum.

$R_{in, LHS} = 4K$


$R_{in, RHS} = (6K) \cdot \frac{1}{N^2}$

$4K = 6K \cdot \frac{1}{N^2}$


$N = \sqrt{\frac{3}{2}}$

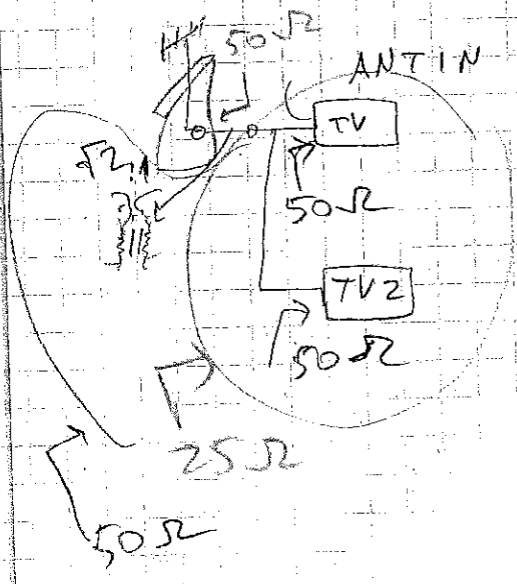


Two-Ports

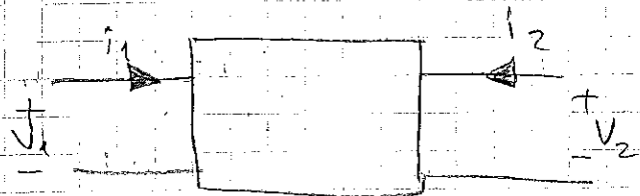

1-Port

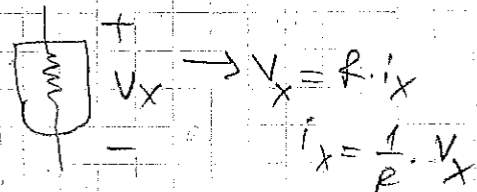

Simple 2-ports:

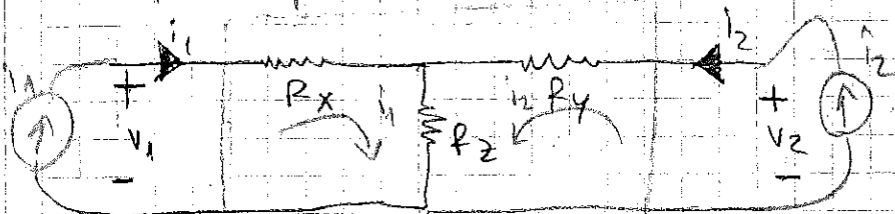

Assume that $\begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$ as the input, and then $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$ as the output.

So after the connection of i_1, i_2 sources; we need to solve the circuit and find V_1 and V_2 .

$$V_1 = R_x i_1 + R_2 (i_1 + i_2)$$

$$V_2 = V_{Ry} + R_2 = R_y i_2 + R_2 (i_1 + i_2)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_x + R_2 & R_2 \\ R_2 & R_y + R_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Calculated output

input

$$V = R \cdot i$$

Resistance Parameters \rightarrow Good at series connection

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

r_{ij} has the unit of R

$$V = R \cdot i$$

Conductance Parameters

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Note: $G = R^{-1}$

Calculated outputs

$$i = G \cdot V$$

Inputs

Hybrid-I parameter set:

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}}_H \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$

Hybrid-II parameter set:



$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = H^{-1} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

ABCD parameters (Transfer parameters) → Like a transformer

Advantages in cascade two-ports (multiple)

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$


Please note the sign.

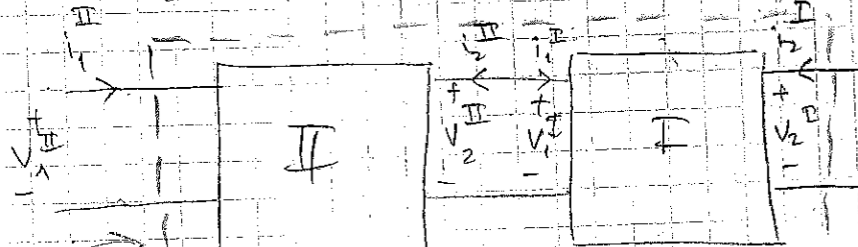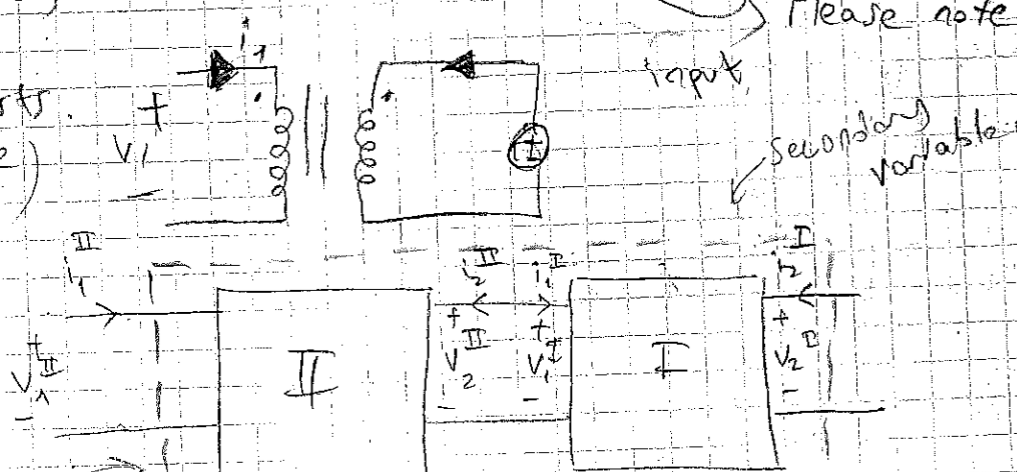


Primary variables

$$(ABCD)_{\text{cascade}} = (ABCD)_I \times (ABCD)_II$$

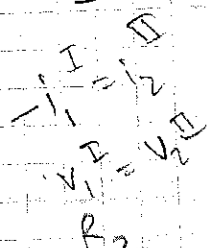ABCD representation of the 2-ports I and II cascade.



Ex:

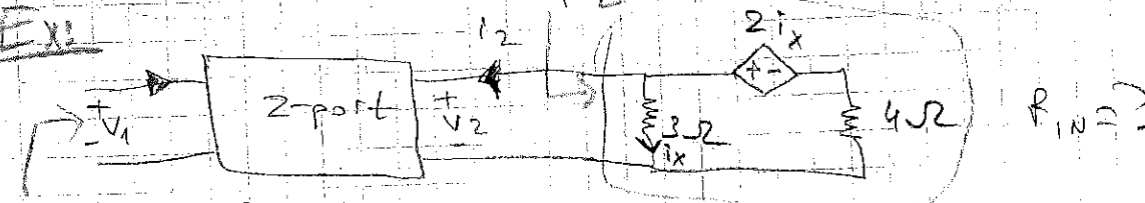


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3 & 2 \\ 2 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

2-port parameters

terminated 2-port one side of 2-port is connected with load.

Let's find R_2 first
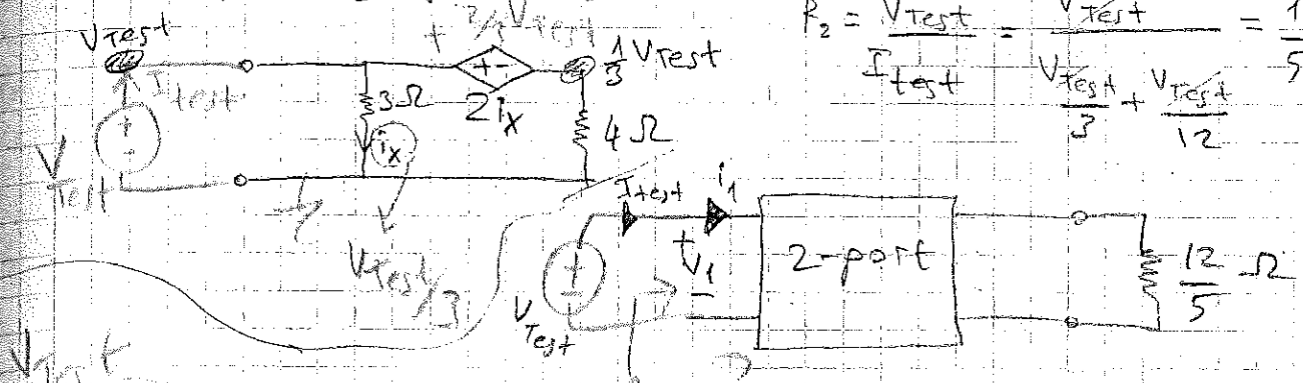
$$R_2 = \frac{V_{test}}{I_{test}} = \frac{V_{test}}{\frac{V_{test}}{3} + \frac{V_{test}}{12}} = \frac{12}{5} \Omega$$



due to termination

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3 & 2 \\ 2 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Need to express i_2 in terms of V_{test}, I_{test}

$$V_2 = 2I_{test} + 4i_2$$

$$V_2 = -\frac{12}{5}i_2$$

$$\frac{-12}{5}i_2 = 2I_{test} + 4i_2$$

From the first row of the 2-port part equation:

$$V_{test} = 3I_{test} + 2i_2$$


$$= 3I_{test} - \frac{2}{3.2}I_{test}$$

$$= \left(\frac{4.8 - 1}{1.6}\right)I_{test}$$

$$i_2 = \frac{-2}{6.4}I_{test} = \frac{-1}{3.2}I_{test}$$

$$R_{in} = \frac{V_{test}}{I_{test}} = \frac{38}{16} = \frac{19}{8} \Omega$$


T- Network:

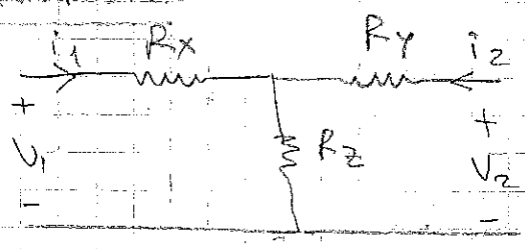


$$R = \begin{bmatrix} R_x + R_z & -R_z \\ R_z & R_y + R_z \end{bmatrix}$$

$V = R \cdot i$
Let's go back to the original problem:

Ex:

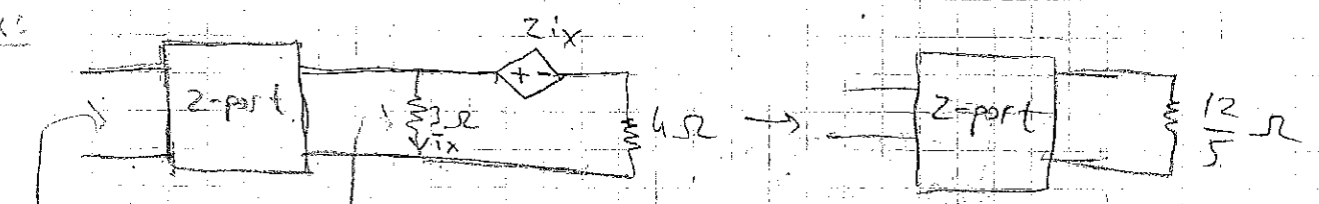
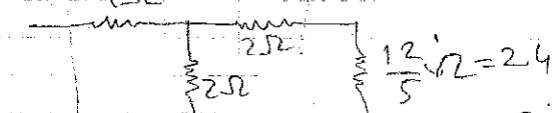
$$R = \begin{bmatrix} 3 & 2 \\ 2 & 4 \end{bmatrix} \rightarrow \begin{bmatrix} 1\Omega & & \\ & 2\Omega & \\ & & 2\Omega \end{bmatrix}$$




$$R_{in} = 1 + 2 // \frac{12}{5} = \frac{19}{8} \Omega$$

The replacement with T network is applicable when R is symmetric.


$$A = A^T$$

π -Network

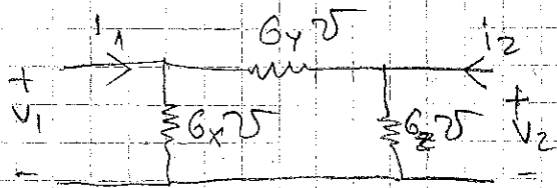

$G = ?$
conductance matrix.
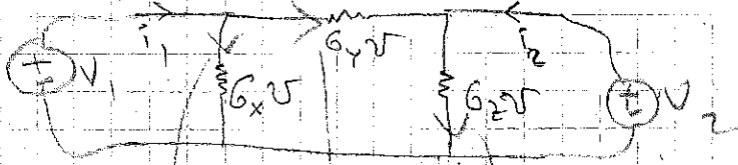
$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = G \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



$$\begin{aligned} i_1 &= V_1 \cdot G_x + (V_1 - V_2) G_y \\ i_2 &= V_2 \cdot G_z - (V_1 - V_2) G_y \end{aligned}$$

$$V_1 \cdot G_x$$

$$(V_1 - V_2) G_y$$

$$V_2 \cdot G_z$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} G_x + G_y & -G_y \\ -G_y & G_y + G_z \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{matrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{matrix}$$

$$G$$


(Note: $G = G^T$ for π network i.e. symmetric matrix)

- a 2nd method to find parameters:

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


Let's find only g_{11} !

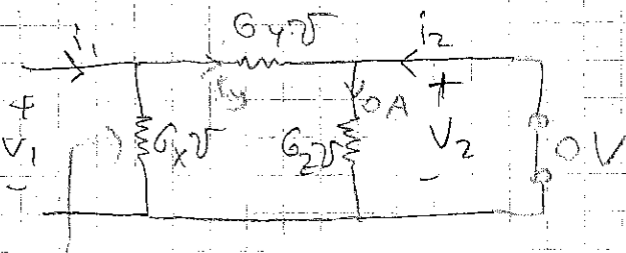Set $V_2 = 0$ and find $\frac{i_1}{V_1} = g_{11}$, Let's apply this method to π -network.



$$\frac{i_1}{V_1} = G_x + G_y$$

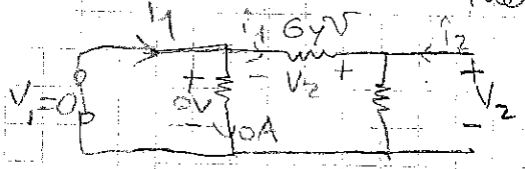
$g_{12} = ?$ Set $V_1 = 0 \rightarrow$ then $\frac{i_1}{V_2} = ?$



$$V_2 = \frac{1}{G_Y} (-i_1)$$

$$\frac{i_1}{i_2} = -\frac{1}{G_Y}$$

Find Γ_{11} of π -network

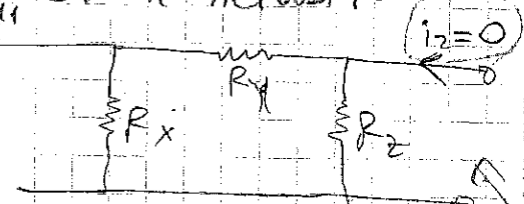

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \Gamma_{11} & \Gamma_{12} \\ \Gamma_{21} & \Gamma_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



$$R_x = \frac{1}{G_x}, \quad R_y = \frac{1}{G_y}, \quad R_z = \frac{1}{G_z}$$

$$\Gamma_{11} = R_x \parallel (R_y + R_z) = \frac{R_x R_y + R_x R_z}{R_x + R_y + R_z}$$

open circuit

Remember $\Delta \rightarrow Y$ conversion

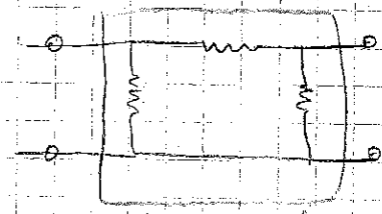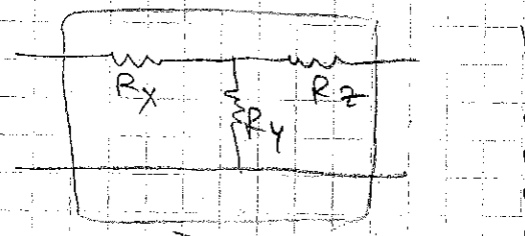The proof of $\Delta \rightarrow Y$ conversion formulas is simply:



Y-connection

Δ -connection

$Y \rightarrow \Delta$: Find R parameters of T network


$\rightarrow G = R^{-1} \rightarrow$ Draw T network from G (conductance) parameter

$\Delta \rightarrow Y$: Find G from π -network


$\rightarrow R = G^{-1} \rightarrow$ Draw T network by inspection from R matrix

Series

Interconnection of 2-parts

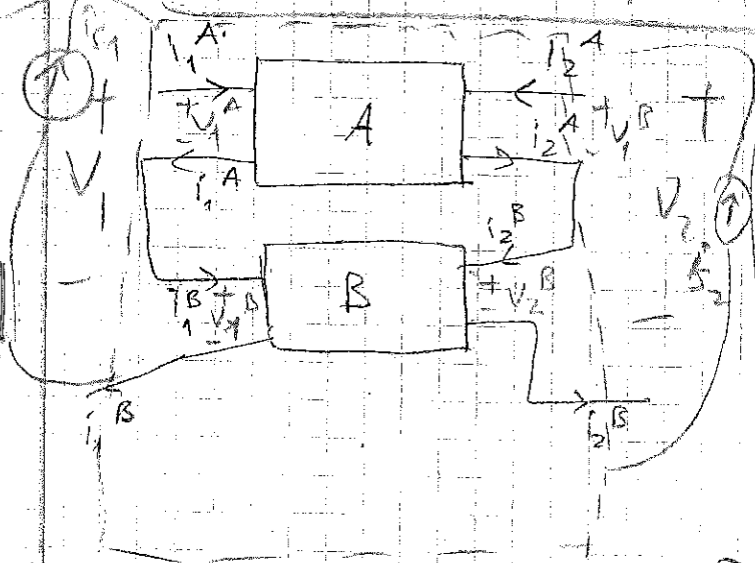

Validity condition for 2-port network

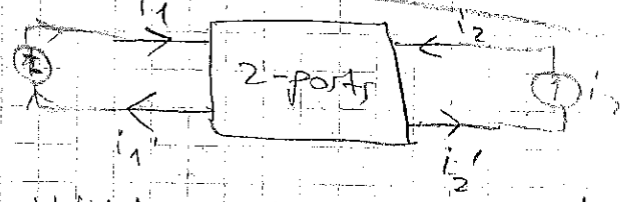


Validity conditions: $i_1 = i_1'$
 $i_2 = i_2'$

R of series combination?

(Matrix)

$$\begin{bmatrix} V_1^{\text{series}} \\ V_2^{\text{series}} \end{bmatrix} = \begin{bmatrix} V_1^A + V_1^B \\ V_2^A + V_2^B \end{bmatrix} = \begin{bmatrix} V_1^A \\ V_2^A \end{bmatrix} + \begin{bmatrix} V_1^B \\ V_2^B \end{bmatrix} = R_A \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} + R_B \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$
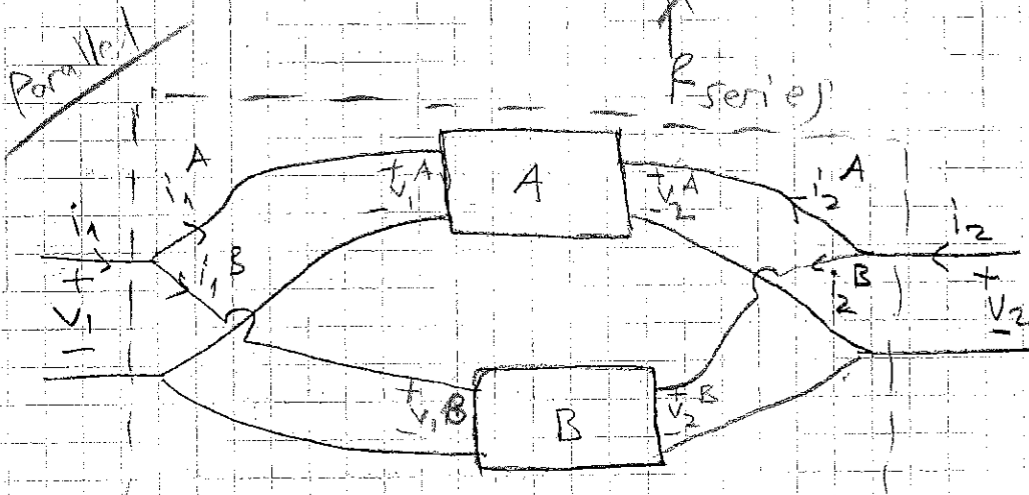
$$R_{\text{series}} = \underline{\underline{(R_A + R_B)}} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$




Due to parallel comb. $V_1 = V_1^A = V_1^B$
 $V_2 = V_2^A = V_2^B$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} i_1^A \\ i_2^A \end{bmatrix} + \begin{bmatrix} i_1^B \\ i_2^B \end{bmatrix}$$

$$= \underline{\underline{(G_A + G_B)}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


G matrix of the 2-port

Remark:

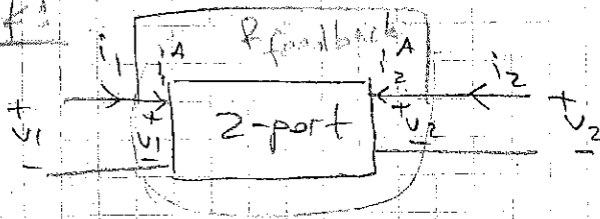

Two port parameters, if given for the above configuration, can be utilized for finding a relation between i_1, i_2, V_1, V_2 , but not i_1, i_2, V_1, V_2


3-terminal 2-port

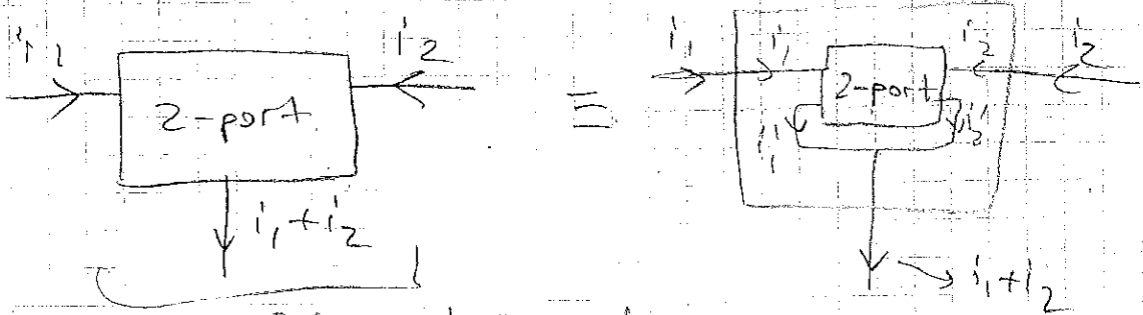

3-terminal 2-port



Ex: 2PS-II
P.10
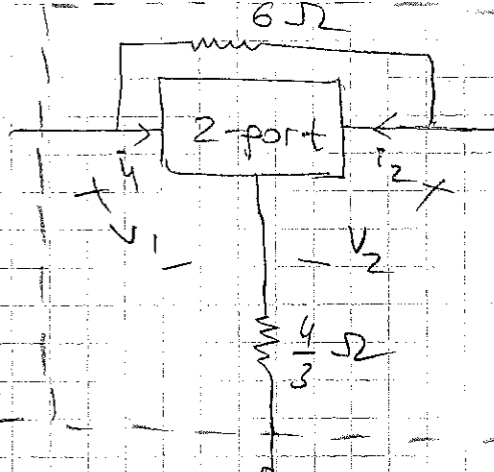
$$\begin{bmatrix} 8 & 6 \\ 6 & 10 \end{bmatrix}$$





$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 8 & 6 \\ 6 & 10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Find 2-parameters of the combination.

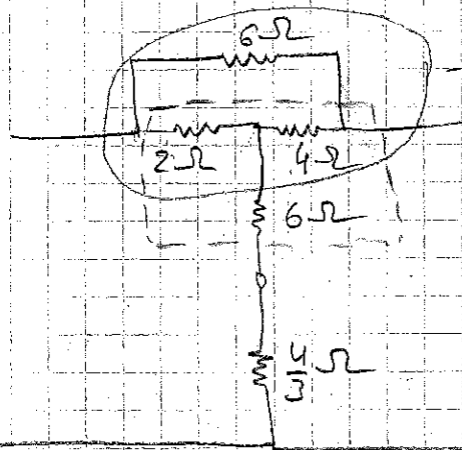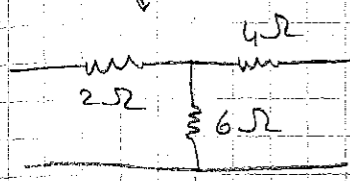


∇(π) network

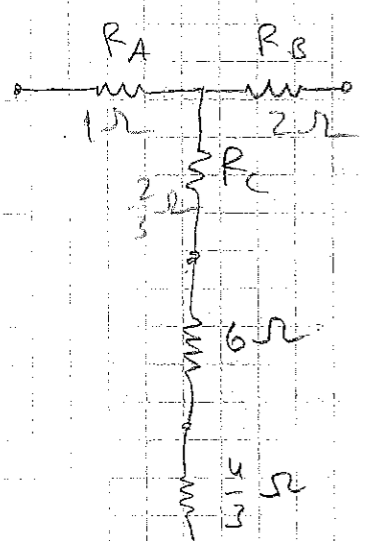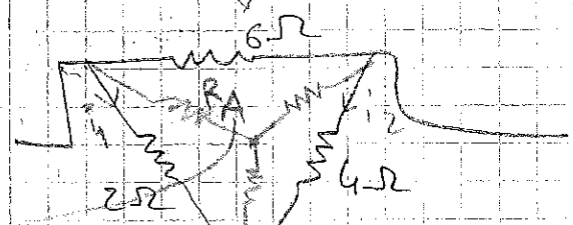


$$R_A = \frac{6 \times 2}{6 + 4 + 2} = 1\Omega$$

$$R_B = \frac{2 \times 4}{2 + 4 + 6} = \frac{8}{12} = \frac{2}{3}\Omega$$
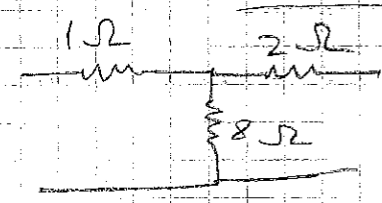
$$R_C = \frac{6 \times 4}{6 + 4} = \frac{24}{10} = 2.4\Omega$$


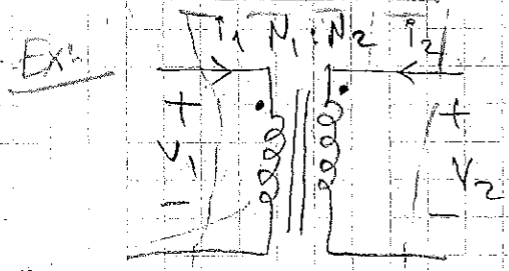
$$P = \begin{bmatrix} 9 & 8 \\ 8 & 10 \end{bmatrix}$$




$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \quad \frac{i_1}{i_2} = -\frac{N_2}{N_1}$$

ABCD parameters of transformer:

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -i_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} \frac{N_1}{N_2} & 0 \\ 0 & \frac{N_2}{N_1} \end{bmatrix} \begin{bmatrix} V_2 \\ -i_2 \end{bmatrix}$$


★ Sometimes it is drawn like this

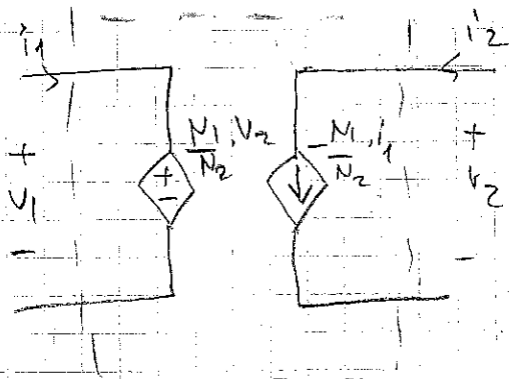

2-ports (continued)


Today: Reciprocity and Symmetry in 2-port Circuits

T Networks

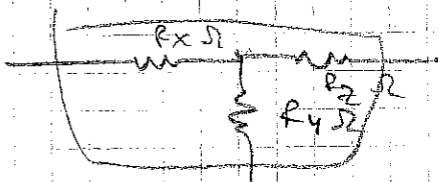

$$R = \begin{bmatrix} R_x + R_y & R_y \\ R_y & R_y + R_z \end{bmatrix}$$

π Networks

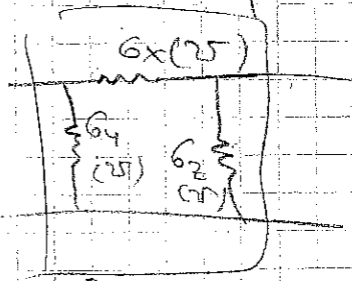

$$G = \begin{bmatrix} G_x + G_y & -G_y \\ -G_y & G_y + G_z \end{bmatrix}$$


Pls note that R and G matrices for T and π network are symmetric.

Reciprocity: If a 2-port doesn't contain any dependent sources, that is, it is composed of only resistances, then its R matrix or G matrix is guaranteed to be symmetric, that is:

$$r_{12} = r_{21} \quad \text{or} \quad g_{12} = g_{21} \quad \left(\text{Such networks are called reciprocal networks} \right)$$

For such networks, some special operations involving exchange of input and output results in the same mappings.


① Since $r_{12} = r_{21}$,

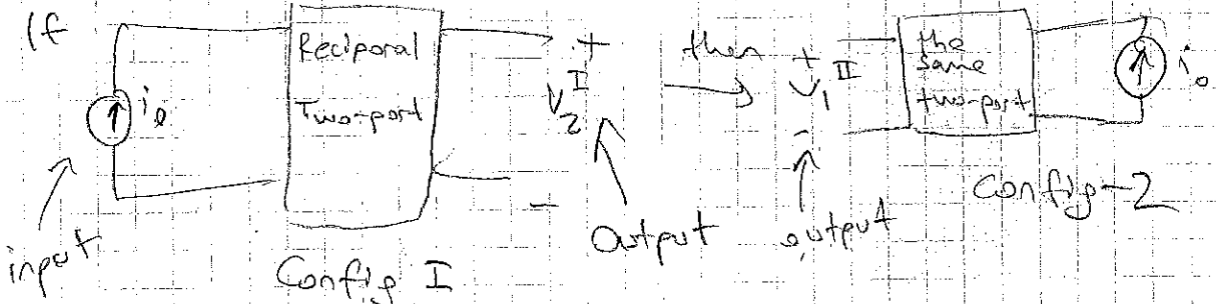


→ Since the 2-port is reciprocal,

$$v_1^{\text{II}} = v_2^{\text{I}}$$

(2) Since $g_{12} = g_{21}$,

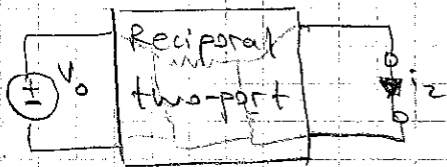

Config-2


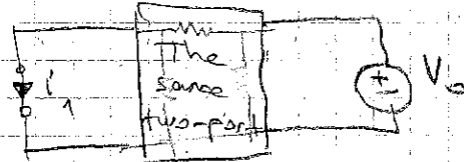


Config-1 Due to reciprocity ($g_{12} = g_{21}$)

$$i_1 = i_2$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

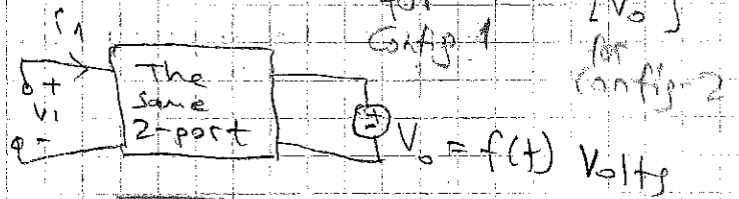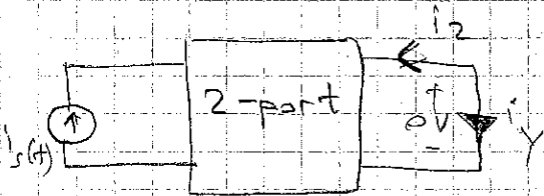(3) $h_{12} = -h_{21}$ (for reciprocal 2-ports)



$$i_2(t) = f(t) \text{ A}$$

a function



For reciprocal 2-ports:

$$v_1 = i_2$$

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

negatives of each other

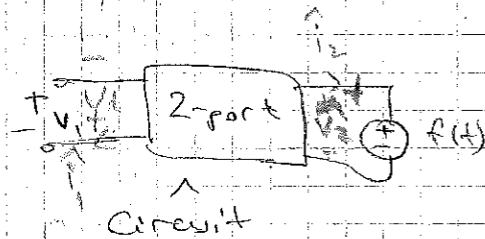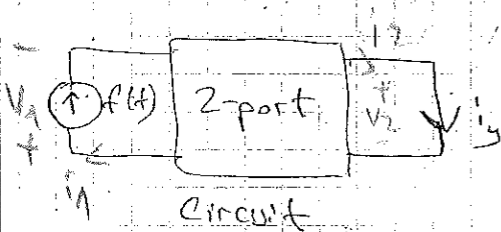Let's give a proof for the 3rd case involving h parameters.



We will use Tellegen's theorem to show the reciprocity case.

$$\sum_{k=1}^N \hat{v}_k \hat{i}_k = \sum_{k=1}^N \hat{v}_k \hat{i}_k = 0$$

Then since 2-part is reciprocal, I can assume that it contains only LTI resistors.

$$v_1 \hat{i}_1 + v_2 \hat{i}_2 + \sum_{k=3}^N \hat{v}_k \hat{i}_k = \hat{v}_1 i_1 + \hat{v}_2 i_2 + \sum_{k=3}^N \hat{v}_k i_k$$

all branches of 2-part


$$v_1 \hat{i}_1 + v_2 \hat{i}_2 = \hat{v}_1 i_1 + \hat{v}_2 i_2$$

$$v_1 \cdot 0 + 0 \cdot \hat{i}_2 = (-v_1) f(t) + f(t) i_1$$

$$v_1 = i_1$$

Ex 1


(Circuit 1)

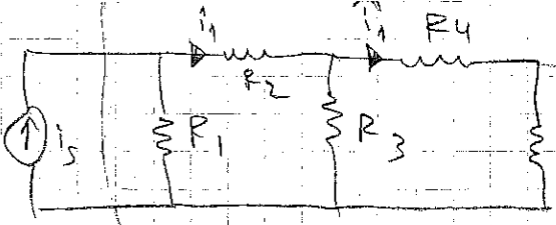

$i_1 = 0.6 \text{ A}$
 $i_2 = 0.3 \text{ A}$

Our important

C2:

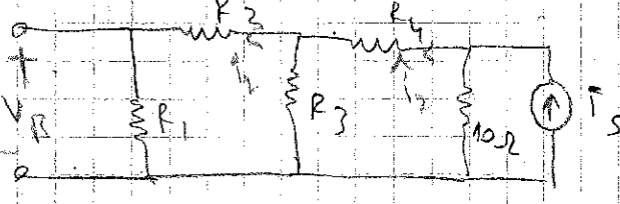

$i_2 = 0.2 \text{ A}$
 $i_1 = 0.5 \text{ A}$


Find R_1 from measurements from circuits C_1 and C_2 .

By reciprocity ($r_{12} = r_{21}$)

$\rightarrow V_A = V_B$
 $10 \cdot i_1 = R_1 \cdot i_2$
 $10 (0.3 \text{ A}) = R_1 (0.2 \text{ A})$

$R_1 = 15 \Omega$


Symmetric Circuits

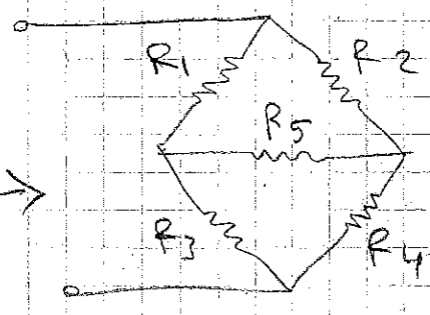

$R_{IN} = ?$

Case 1:



$R_1 = R_2$
 $R_3 = R_4$

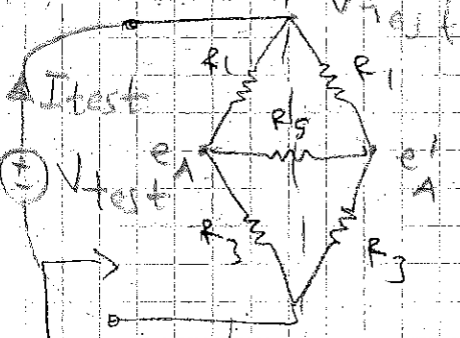

$R_{IN} = ?$




Symmetric axis

By symmetry $e_A = e_A'$

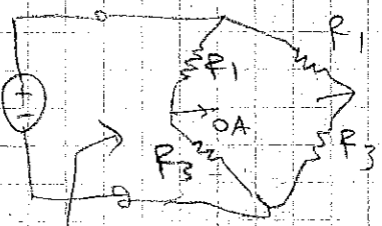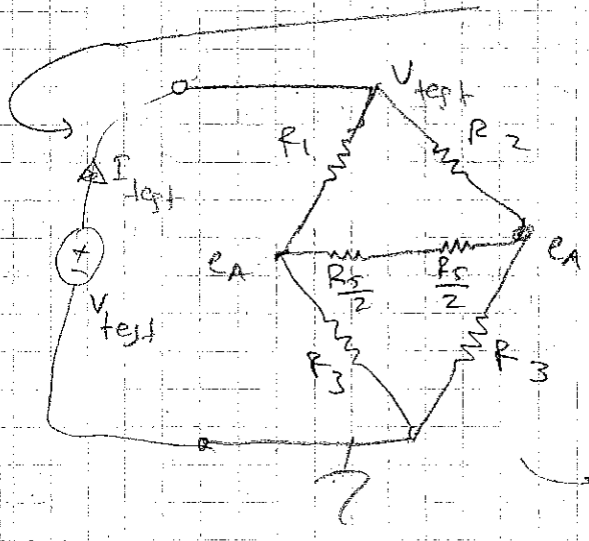

$R_{IN} = (R_1 + R_3) \parallel (R_1 + R_3)$
 $= \frac{R_1 + R_3}{2}$


Case 2: $R_1 = R_3$
 $R_2 = R_4$

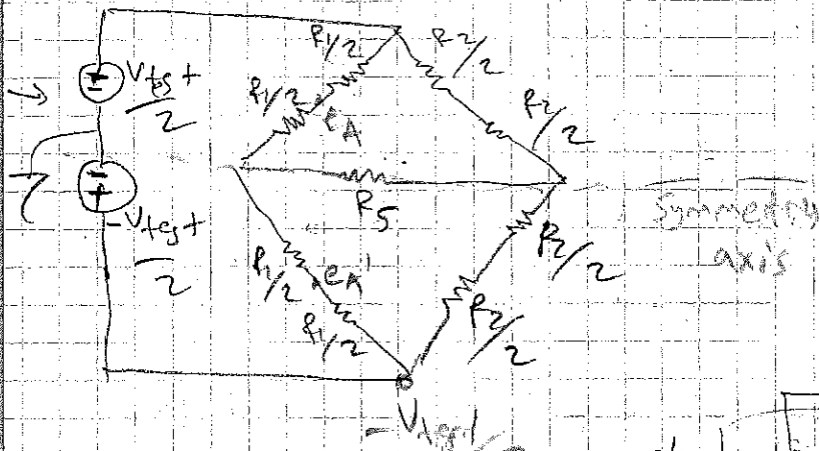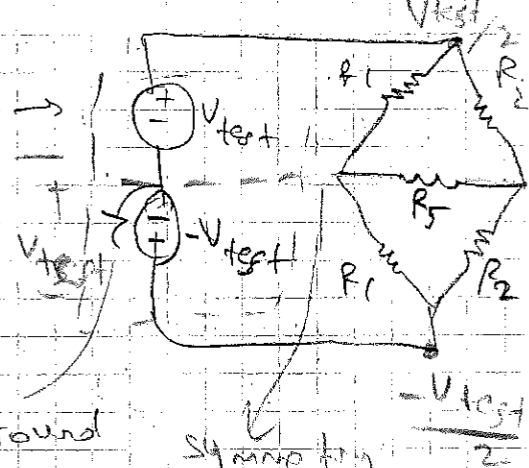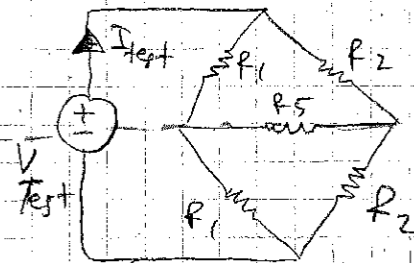

Ground


Symmetry axis

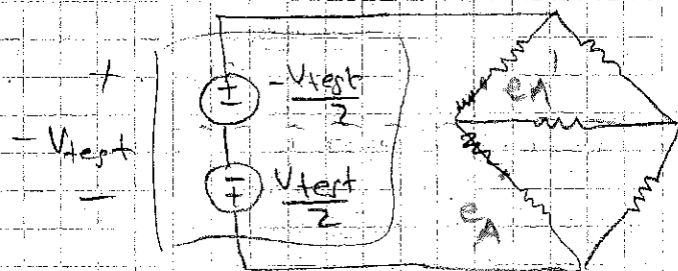By folding upper part to bottom and lower part to top we get



$e_x = e_x'$ but
 $e_x = -e_x'$
 $\rightarrow e_x = 0$

Node x is on symmetry axis

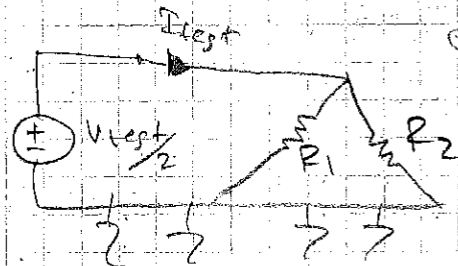


$e_x = -e_x'$

$$I_{test} = \frac{V_{test}/2}{R_1 \parallel R_2}$$



$$\frac{V_{test}}{I_{test}} = 2(R_1 \parallel R_2)$$

Node Ground above


EX1

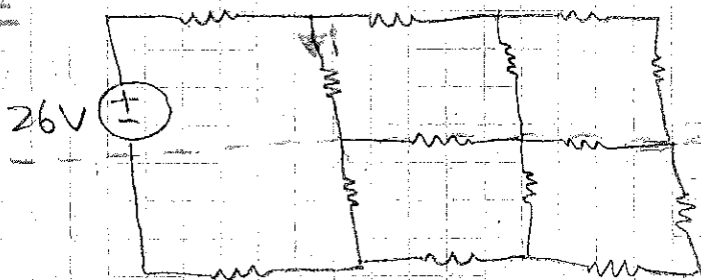

All resistors are 1Ω. Find i_1

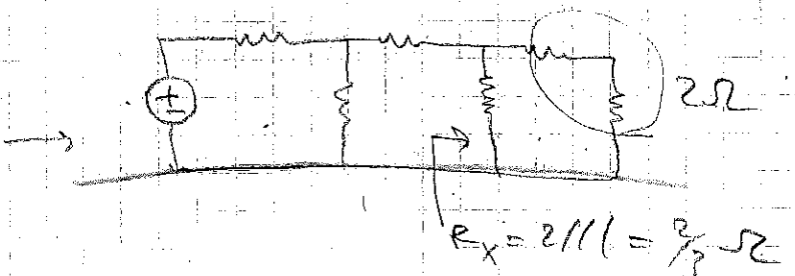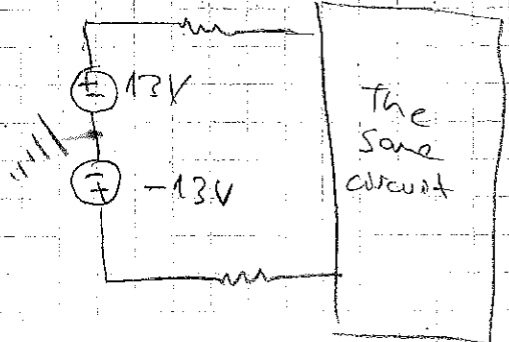

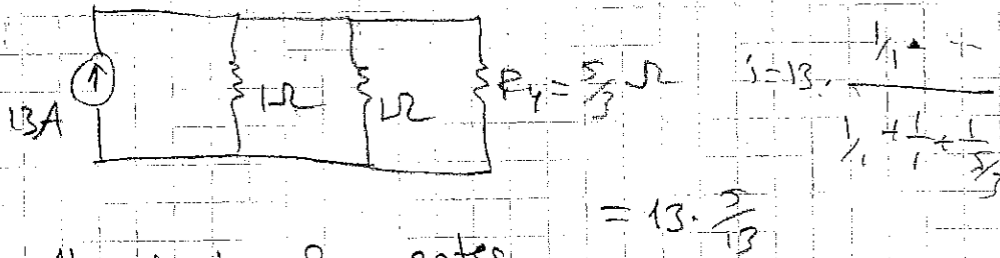
$$R_x = 2 \parallel 1 = \frac{2}{3} \Omega$$




Also check notes for another application of symmetry

$= 5A$

ZPS!!

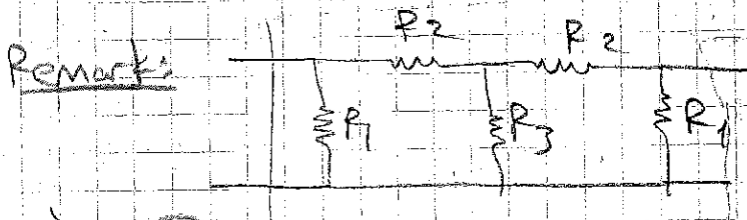


Find R parameters.

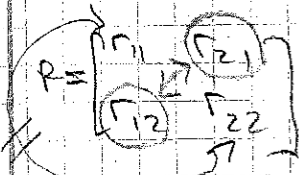

Comment (1): 2-port is reciprocal then $r_{12} = r_{21}$


Comment (2): 2-port has symmetry across the axis. The labeling of primary and secondary ports for 2-port is arbitrary.

$r_{11} = r_{22}$

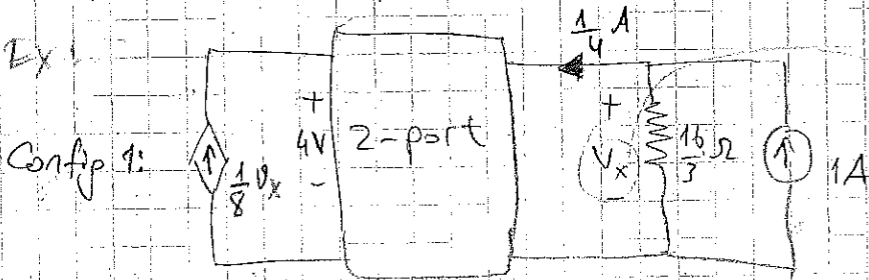


Dummy Variables


They do not have same

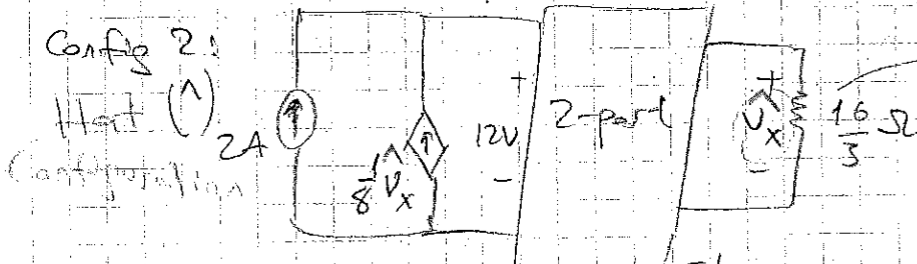

let's say it is V_b

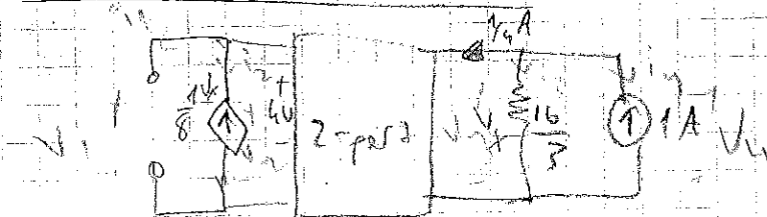Find V_x of circuit 2. (2-port consist of LTI (reciprocal))
 Apply Tellegen's Theorem.



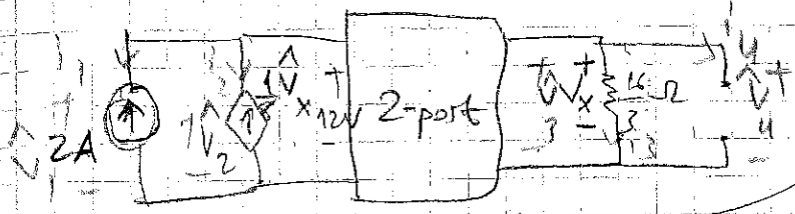

of branches $\sum_{k=1}^2 V_k \cdot i_k = \sum_{k=1}^2 V_k \cdot i_k = 0$


$$V_1 \cdot i_1 + V_2 \cdot i_2 + V_3 \cdot i_3 + V_4 \cdot i_4 + \sum_{k=5}^{\text{# of branches}} (R_k) i_k = V_1 i_1 + V_2 i_2 + V_3 i_3 + V_4 i_4 + \sum_{k=5}^{\text{# of branches}} (R_k) i_k$$

$$4(-2) + 4 \cdot \left(-\frac{1}{8} \hat{V}_x\right) + 4 \left(\frac{\hat{V}_x}{16/3}\right) + 4 \cdot 0 = 12 \cdot 0 + 2 \left(\frac{1}{2}\right) + \dots$$



$$-2 - \frac{1}{8} \hat{V}_x + \frac{3}{16} \hat{V}_x = \frac{-3}{2} + \hat{V}_x \cdot \frac{3}{16} - \frac{0}{4}$$

$\hat{V}_x = 4V$ Note! Don't confuse the branch numbers of the 2-part.

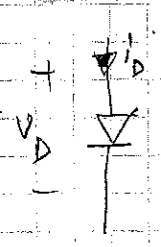Ideal Diodes and Introduction to Non-linear Components




possible sign Conventions

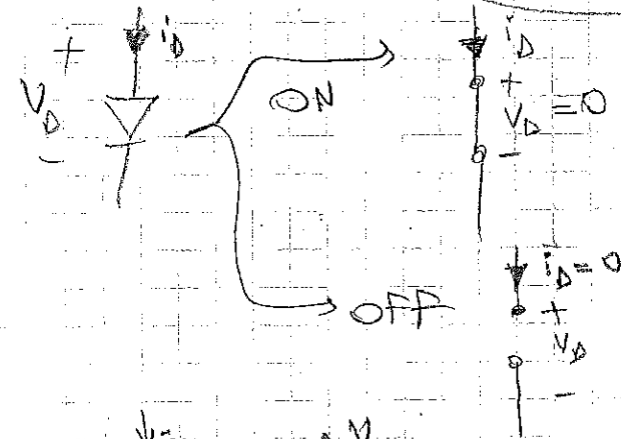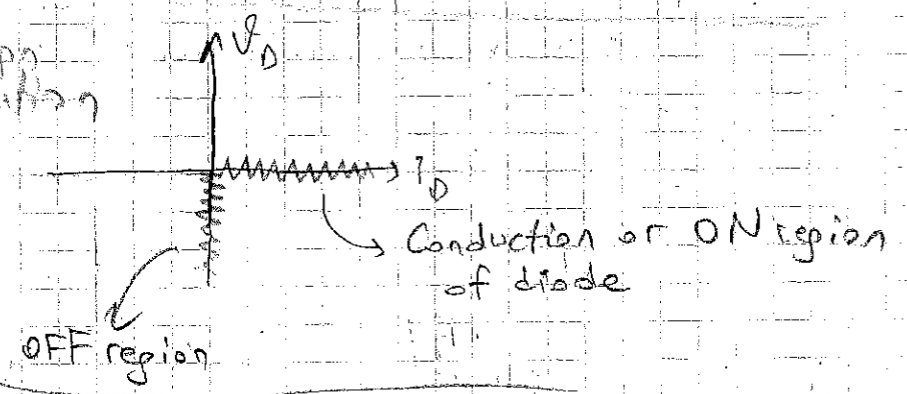


provided that $i_D \geq 0$

provided that $V_D \leq 0$

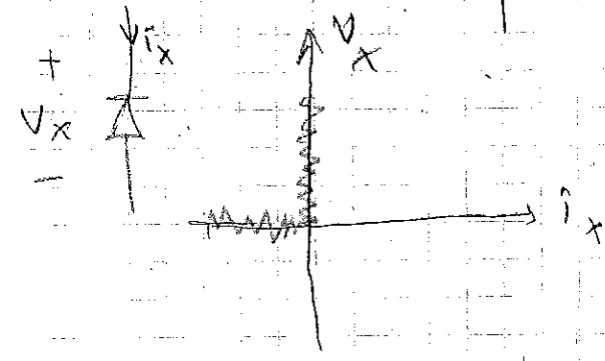

Remark: Ideal diodes have i-v characteristics whose one leg is in (+) part of the axis and other one in the (-) part of the axis.


EX1

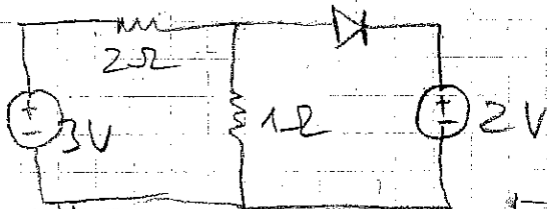

Analyze the circuit

Assume the diode is ON!


(Requires $i_D \geq 0$)

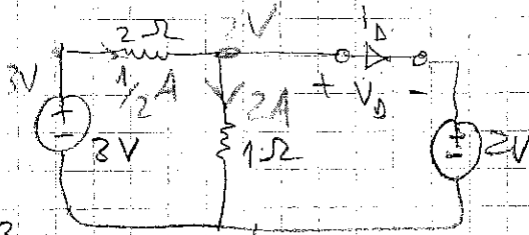

$$i_D = -\frac{3}{2} \text{ A}$$

The assumption is not correct since the ON condition is NOT satisfied.

Assume the diode is OFF:

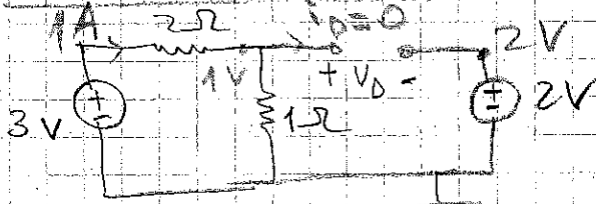

Condition: $V_D < 0$




$$V_D = 1 - 2 = -1 \text{ Volt}$$

Assumption is satisfied.

What if a circuit has 50 diodes?


Series and Parallel combinations through Graphical Analysis

Series

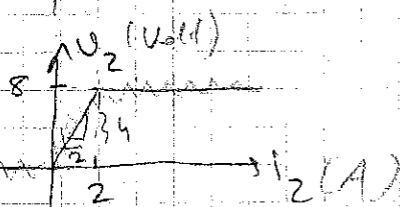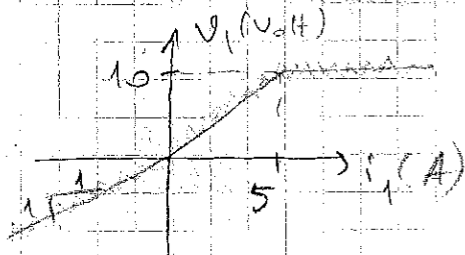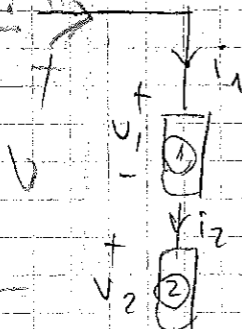

the slope = 2
the slope = 6

the slope = 1

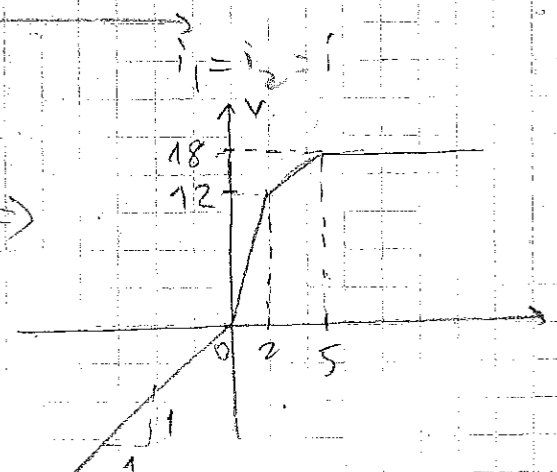



$$i_1 = i_2 = i$$

Series combination: For the same current value, we


add the voltages.

In this example, the voltage addition is the vertical addition of two graphs.


Nodes:

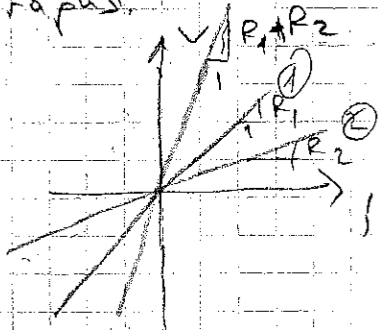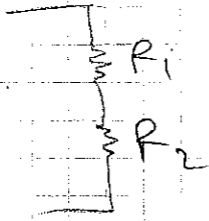

Parallel:

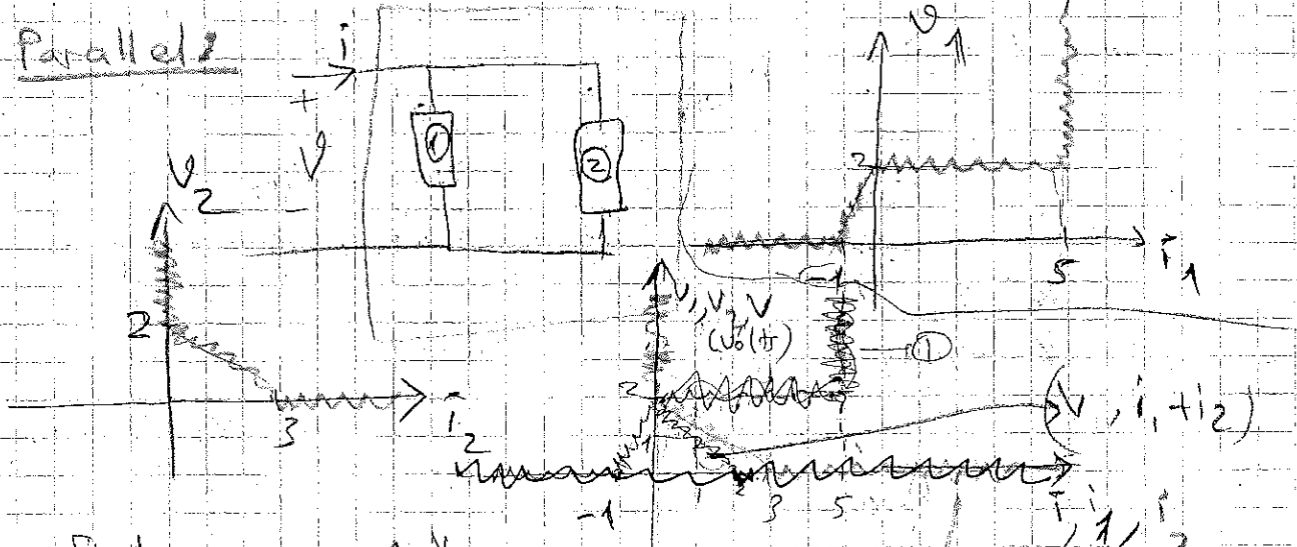

Final answer:

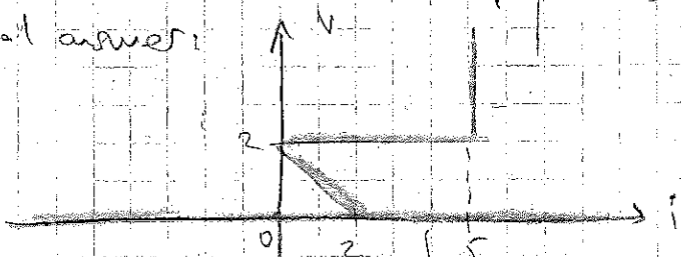


i_1 can be any negative number < -1
 i_2 can be any positive number > 1
 EX: $-5 + 6 = 1$




Parallel combination: We add current values for the same voltage, $i = i_1 + i_2$ for the fixed $V = V_1 = V_2$.

For this example, adding currents is the horizontal addition of graphs.



Ex:

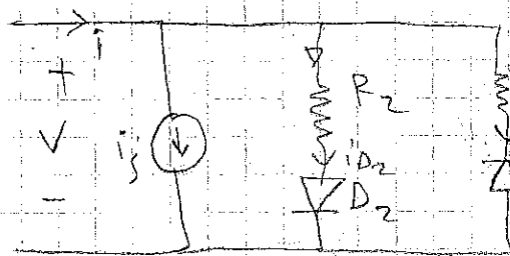

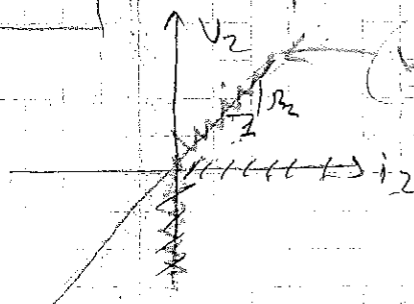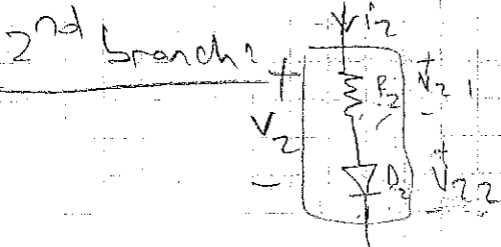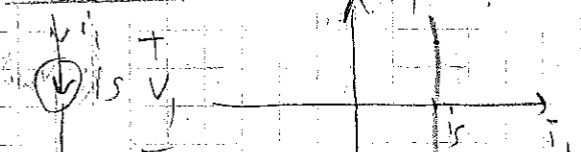
Find (i, V) characteristics for branches:





3rd Branch:

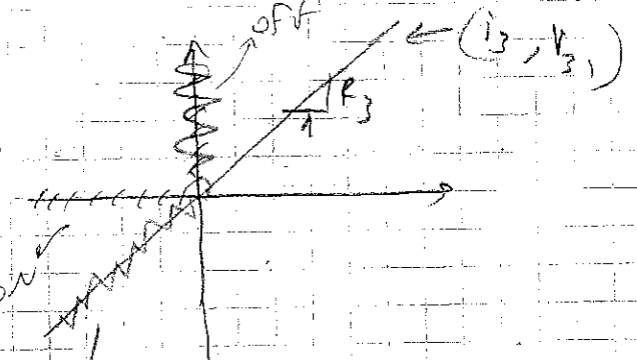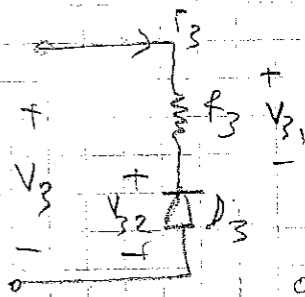

Finally:

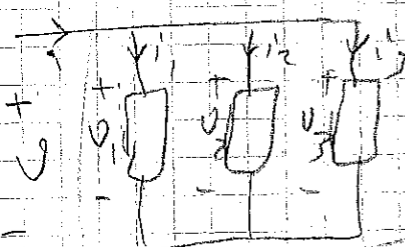



$(i_3, V_3) = (1.0, 1.0)$

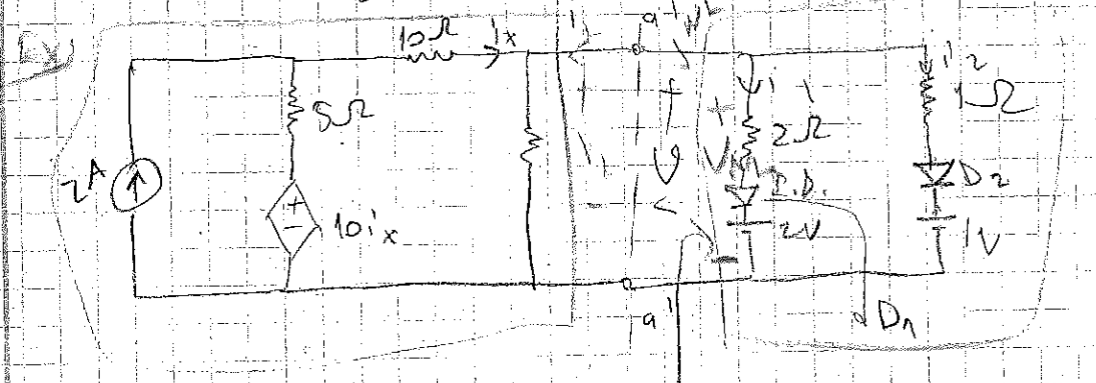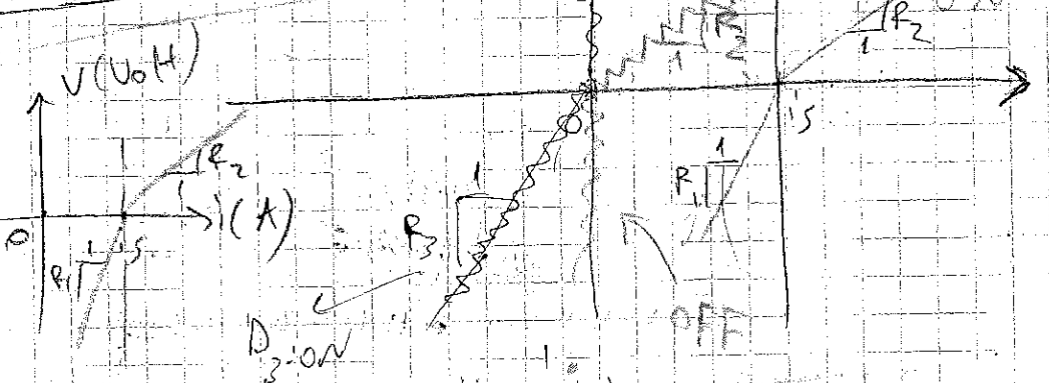


Ans: V_s

To simplify the solution let's first find Thevenin equivalent of LHS of a-a' line.


Thevenin Eqn

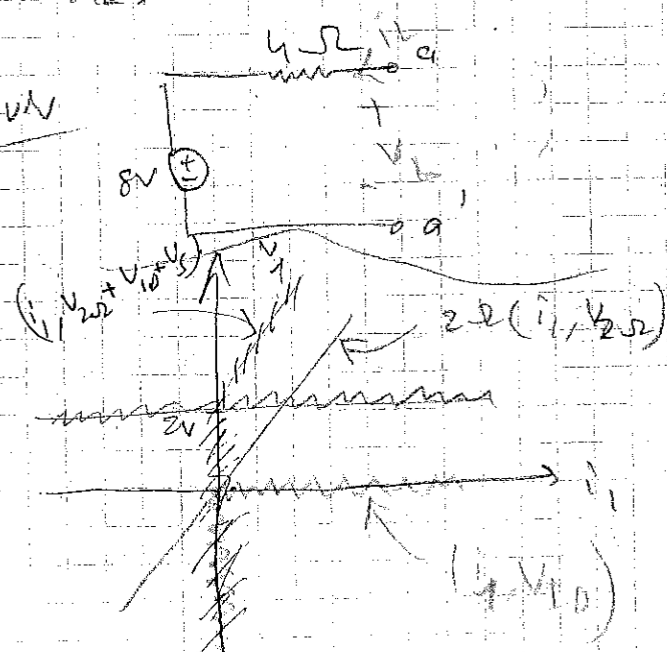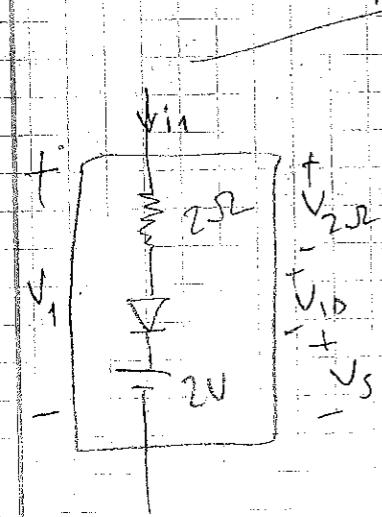

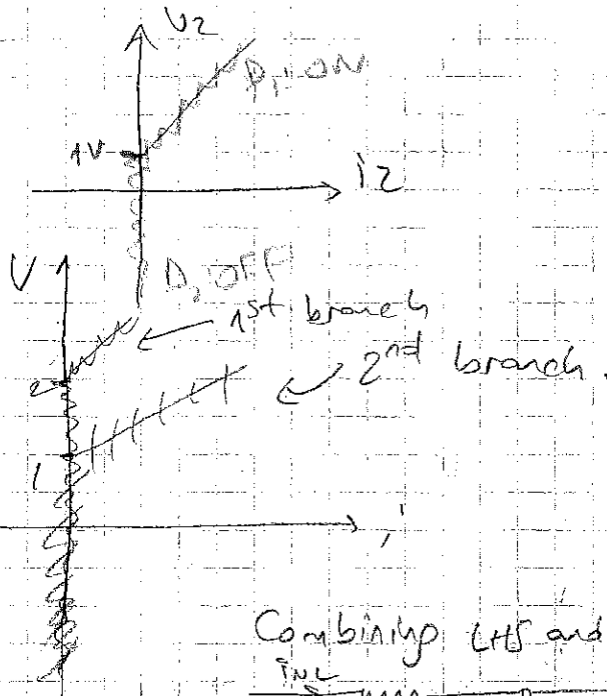


Note: Ideal transformer is a reciprocal component, since its h-parameter representation is:

$$h_{12} = -h_{21}, \text{ so}$$

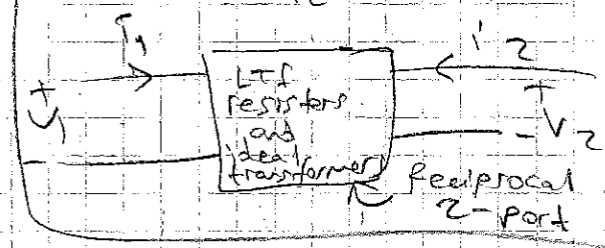


Combining LHS and RHS of a-a' line:

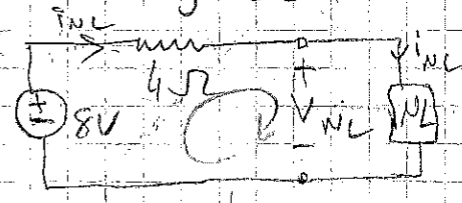

$$\text{KVL: } -8 + 4i_{NL} + V_{NL} = 0$$

$$V_{NL} = 8 - 4i_{NL} \leftarrow \text{load line}$$

Solution by load line (graphical method)

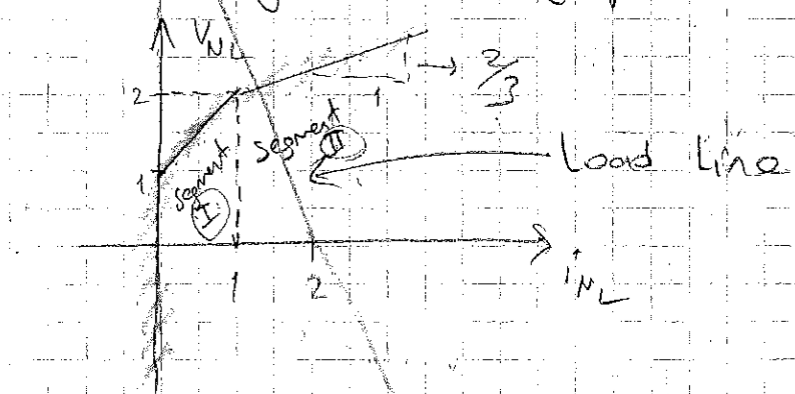

Operating point is the intersection of the load line and the NL characteristic.

Assume operating point (the intersection) is in segment I:

$$\left. \begin{aligned} \text{I: } i_{NL} V_{NL} &= i_{NL} + 1 \\ \text{Load Line: } V_{NL} &= 8 - 4i_{NL} \end{aligned} \right\} i_{NL} = \frac{7}{5} \text{ A} \quad \times \quad \left. \begin{aligned} V_{NL} &= \frac{12}{5} \text{ Volts} \\ & \times \end{aligned} \right.$$

This assumption is wrong since segment I is valid for $0 < i_{NL} < 1$.

Assume that op. point is in segment II.

$$\left. \begin{aligned} \text{II: } V_{NL} &= \frac{2}{3} i_{NL} + \frac{4}{3} \\ \text{Load Line: } V_{NL} &= 8 - 4i_{NL} \end{aligned} \right\} i_{NL} = \frac{10}{7} \text{ A} \quad V_{NL} = \frac{16}{7} \text{ V}$$

So $(i_{NL}, V_{NL}) = (\frac{10}{7} \text{ A}, \frac{16}{7} \text{ V})$ is the operating point.

Q: Assume that the 2A source is replaced with a 3A source. What is the new solution?



Load line: $V_{NL} = 12 - 4i_{NL}$

Q2: Assume the source is 2A but the NL component is expressed as

$$V_{NL} = \begin{cases} 4(i_{NL})^2 + 5 & i_{NL} > 0 \\ 0 & i_{NL} < 0 \end{cases}$$

Find the solution.

Answer of Q2:

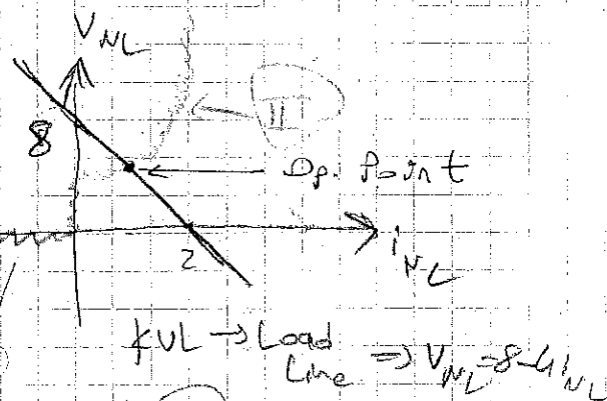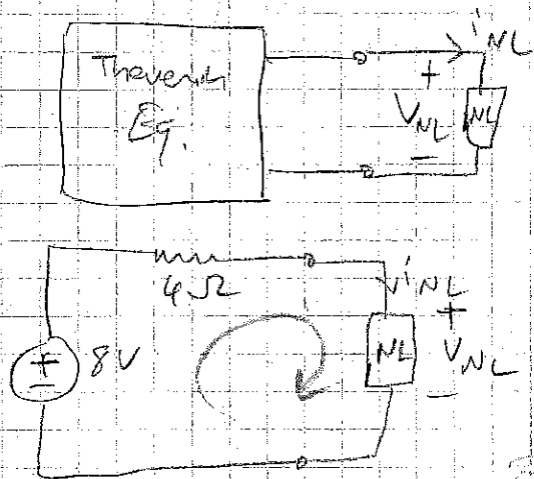

Assume the solution is in segment (II):


load line $\Rightarrow V_{NL} = 8 - 4i_{NL}$

NL load $\Rightarrow V_{NL} = 4(i_{NL})^2 + 5$

$$4(i_{NL})^2 + 4i_{NL} - 3 = 0$$

$$i_{NL} = \left\{ \frac{1}{2}, -\frac{3}{2} \right\}$$

Small Signal Analysis

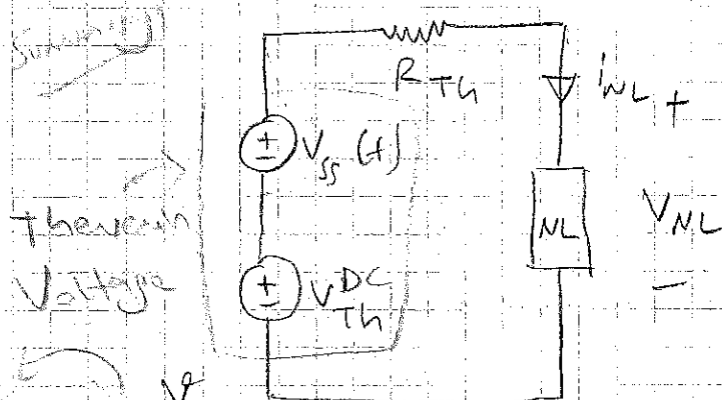


$V_{SS}(t)$ = Small signal voltage waveform (A.C.)



V_{DC_Th} : DC part of the thevenin voltage.

Small signal assumption:

$$|V_{SS}(t)| \ll V_{Th}$$

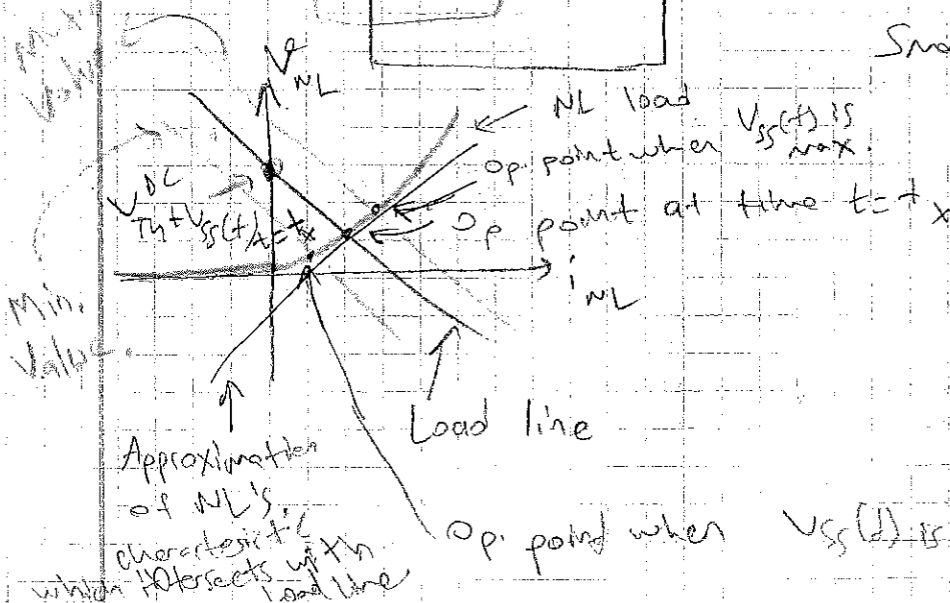

Ex

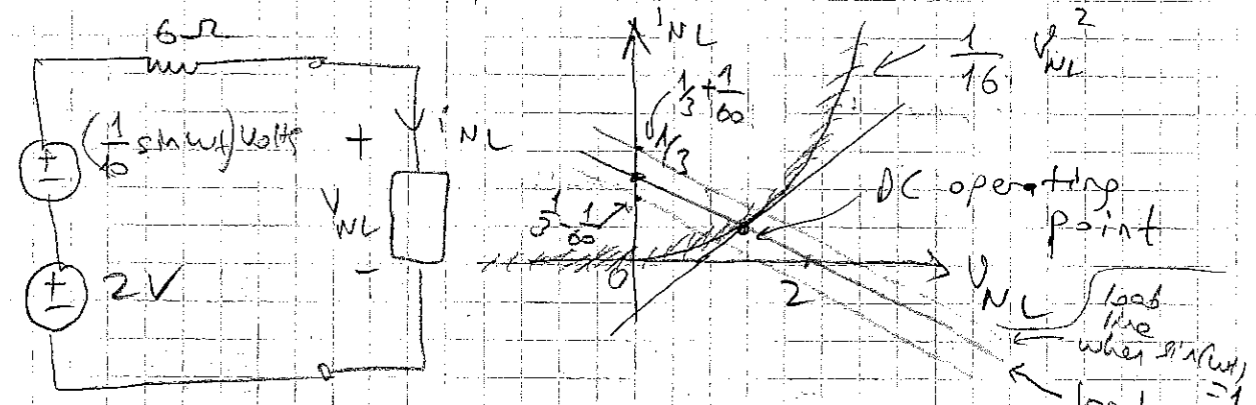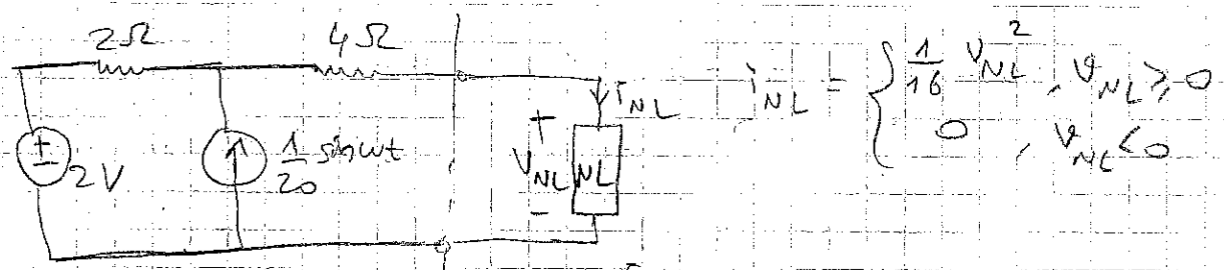

Load line (KVL): $V_{NL} = (2 + \frac{1}{10} \sin(\omega t)) - 6 i_{NL}$

$i_{NL} = [\frac{1}{3} + \frac{1}{60} \sin(\omega t)] - \frac{V_{NL}}{6}$

Finally DC operating point:

Load Line: $i_{NL} = \frac{1}{3} + \frac{1}{60} \sin(\omega t) - \frac{V_{NL}}{6}$

for DC operating point AC part is not taken into account.

NL Load $i_{NL} = \begin{cases} \frac{1}{16} V_{NL}^2, & V_{NL} \geq 0 \\ 0, & \text{otherwise} \end{cases}$

Assume $V_{NL} \geq 0 \rightarrow \frac{1}{16} V_{NL}^2 = \frac{1}{3} - \frac{V_{NL}}{6}$

$V_{NL} = \frac{4}{3} V$ is the DC operating point. $\rightarrow i_{NL} = \frac{1}{9} A$

$\frac{1}{3} - \frac{2}{9} = \frac{3-2}{9} = \frac{1}{9}$

$(V_{NL}^{DC}, i_{NL}^{DC}) = (\frac{4}{3} V, \frac{1}{9} A)$

Approximating NL with a straight line:

$i_{NL} = \frac{1}{16} V_{NL}^2$

① Taylor Series around DC op. point

$f(V_{NL}) = f(V_{NL}^{DC}) + f'(V_{NL}^{DC}) \cdot (V_{NL} - V_{NL}^{DC}) + \frac{f''(V_{NL}^{DC}) (V_{NL} - V_{NL}^{DC})^2}{2!}$

$f(V_{NL}) = \frac{1}{16} V_{NL}^2, \quad V_{NL}^{DC} = \frac{4}{3}$

$f(V_{NL}) = \frac{1}{9} + f'(\frac{4}{3}) (V_{NL} - \frac{4}{3}) + \dots$



$f'(V_{NL}^{DC}) = \frac{2}{16} V_{NL} \Big|_{V_{NL} = V_{NL}^{DC} = \frac{4}{3}} = \frac{1}{6}$

$$f(v_{NL}) \approx \frac{1}{9} + \frac{1}{6} (v_{NL} - \frac{4}{3})$$

$$\frac{1}{46} v_{NL}^2$$


approximation around DC op. point.

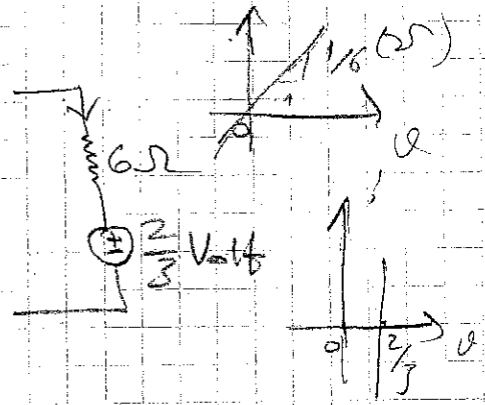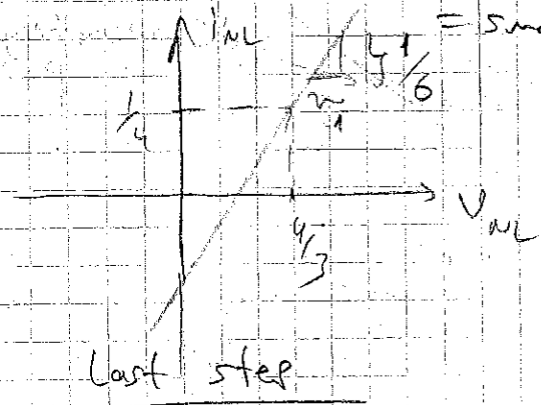(2) You can find the tangent line at (a straight line) DC operating point.




Last step

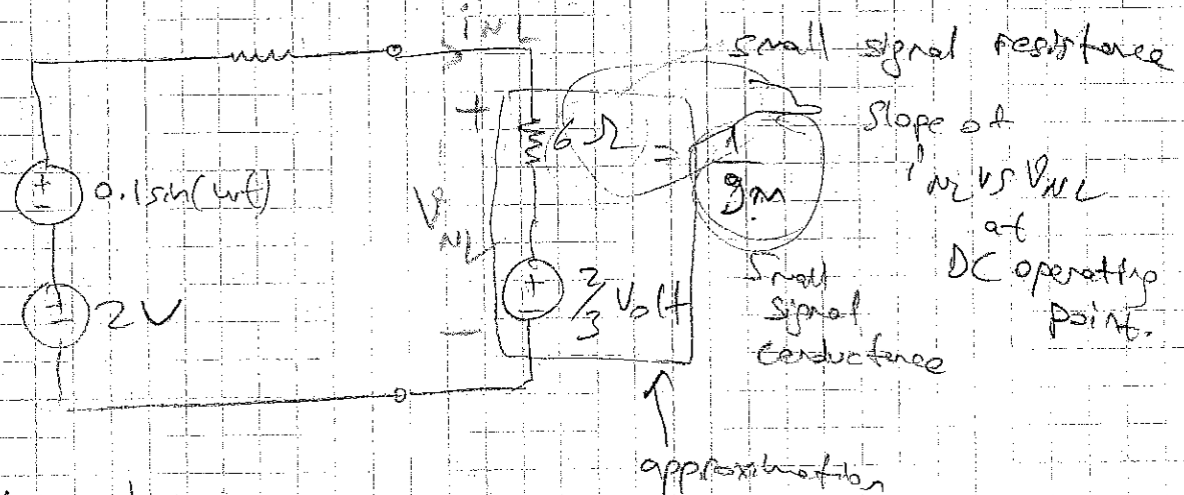Replace the NL component with the approximation:




AC part: (small signal circuit)

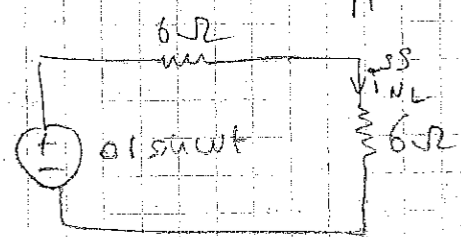

$$i_{NL}^{SS}(t) = \frac{0.1 \sin(\omega t)}{12} A$$

DC part:

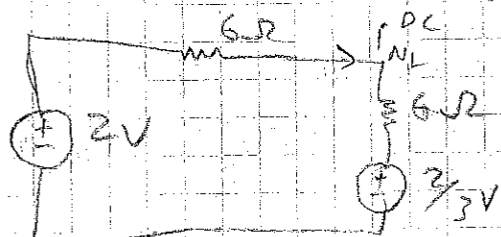


$$i_{NL}^{DC} = \frac{2 - \frac{2}{3}}{12} = \frac{1}{9} A$$

$$i_{NL}(t) \approx i_{NL}^{DC} + i_{NL}^{SS} = \frac{1}{9} + \frac{0.1}{12} \sin(\omega t) A$$


Ex: 2PS-3
Pr. 46

Find i_1 by small signal approximation
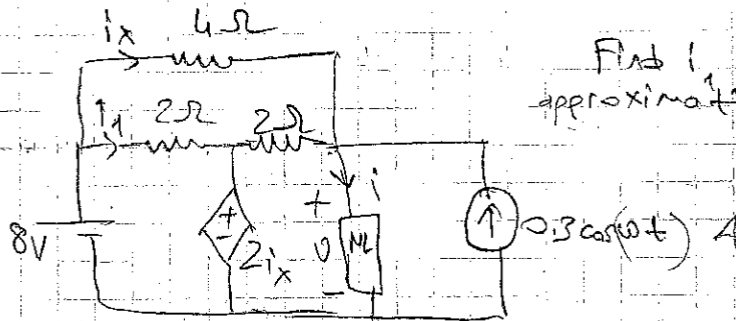
$$i_2 = \begin{cases} \frac{1}{2} V^2, & V > 0 \\ 0, & \text{otherwise} \end{cases}$$



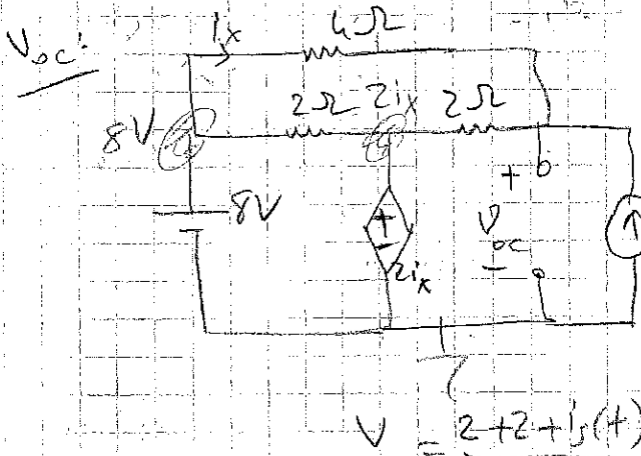I need to find D.C. operating point. To do that, Thevenin equivalent will be utilized.




We need node (or mesh) analysis to find Thevenin eq.

KCL at V_{oc}

$$\frac{V_{oc} - 8}{2} + \frac{V_{oc} - 8}{4} - \frac{1}{5} = 0$$

$$V_{oc} = \frac{2+2 + \frac{1}{5}}{\frac{1}{2} + \frac{1}{4} + \frac{1}{5}}$$


$$i_x = \frac{8 - V_{oc}}{4}$$

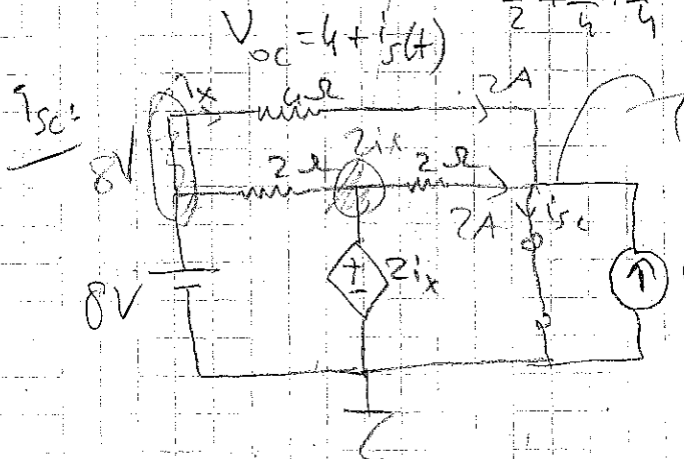

$$i_x = 2A$$

$$i_{sc} = 2 + 2 + \frac{1}{5} = 4 + \frac{1}{5} A$$
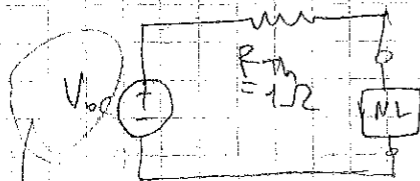
$$R_{Th} = \frac{V_{oc}}{i_{sc}} = 1\Omega$$



Let's find D.C. operating point:

KVL: $-4 + i_{NL} \times 1 + V_{NL} = 0$

$\frac{1}{2} V_{NL}^2$ (provided that $V_{NL} > 0$)


$4 + 0.3 \cos(\omega t) \rightarrow$ Very small!
More than 10 times smaller.

Then D.C. operating point is $(V_{NL}^{DC}, i_{NL}^{DC}) = (2V, 2A)$

$$V_{NL}^2 + 2V_{NL} - 8 = 0$$

$$(V_{NL} + 4)(V_{NL} - 2) = 0$$

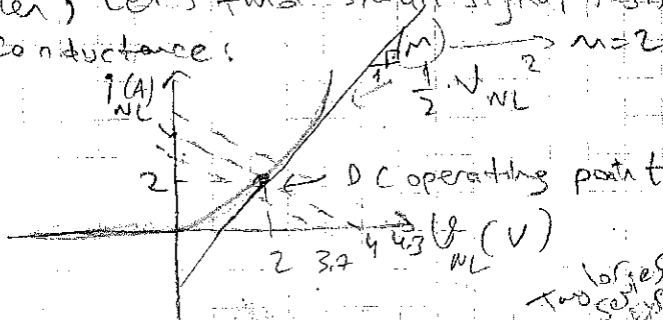Then, let's find small signal resistance/conductance:



$$f(V_{NL}) = \frac{1}{2} V_{NL}^2$$

then slope of $f(\cdot)$ is at DC op. point is

$$\frac{df(V_{NL})}{dV_{NL}} = \frac{2}{2} V_{NL} \Big|_{V_{NL} = V_{NL}^{DC} = 2} = 2$$

$g_m = 20 \rightarrow r_m = \frac{1}{2} \Omega$
 the small signal conductance \rightarrow the small signal resistance


Then to find the AC part of the solution,

$$v_w^{SS} = \frac{0.3 \cos(\omega t)}{3}$$

$$v_w^{SS} = 0.1 \cos(\omega t)$$

$$i_{NL}^{SS}(t) = 0.2 \cos(\omega t)$$


AC Component of v_{oc}

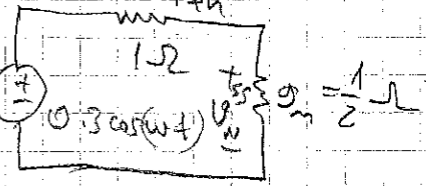


Normally we can't use superposition in non-linear circuits but we make a linear approximation here.

$$v_{NL}(t) \approx v_{NL}^{DC} + v_{NL}^{SS}(t) = 2 + 0.1 \cos(\omega t) \text{ V}$$
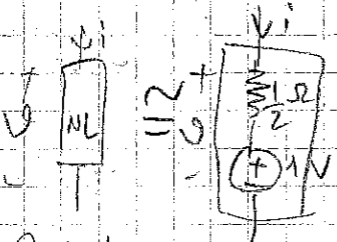
$$i_{NL}(t) \approx i_{NL}^{DC} + i_{NL}^{SS}(t) = 2 + 0.2 \cos(\omega t) \text{ A}$$



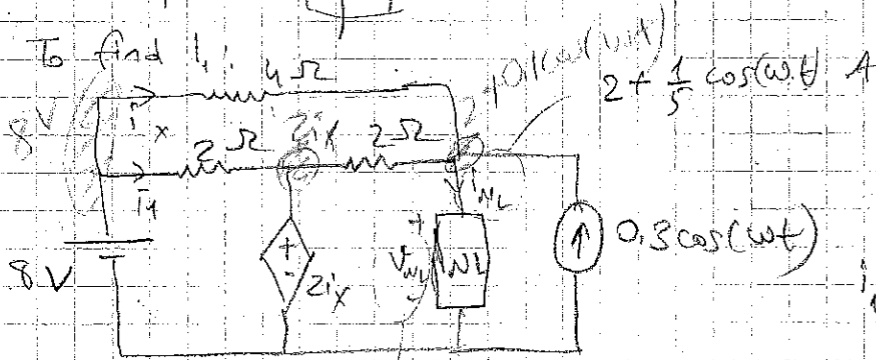We approximated the non-linear component around D.C. operating point.



$$i_1 = \frac{5}{2} + \frac{1}{40} \cos(\omega t) \text{ A}$$

$$2 + \frac{1}{10} \cos(\omega t) \text{ V}$$

Again we do analysis:

$$i_1 = \frac{8 - 2i_x}{2} = 4 - i_x$$


$$i_x = \frac{8 - (2 + 0.1 \cos(\omega t))}{4}$$

$$i_1 = \frac{3}{2} + \frac{1}{40} \cos(\omega t)$$


Diodes: Analysis and Synthesis

Analysis: Given the circuit \rightarrow find (i, v) characteristic

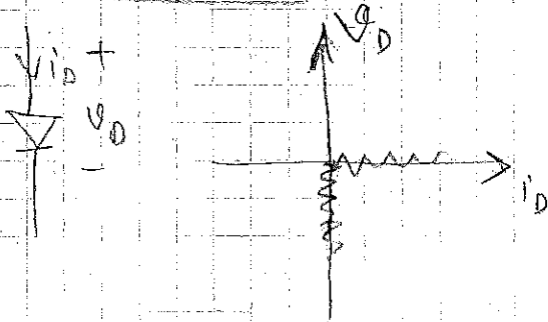
Synthesis (Design): Given (i, v) char. \rightarrow Design a circuit realizing (i, v) char.



Analysis example:

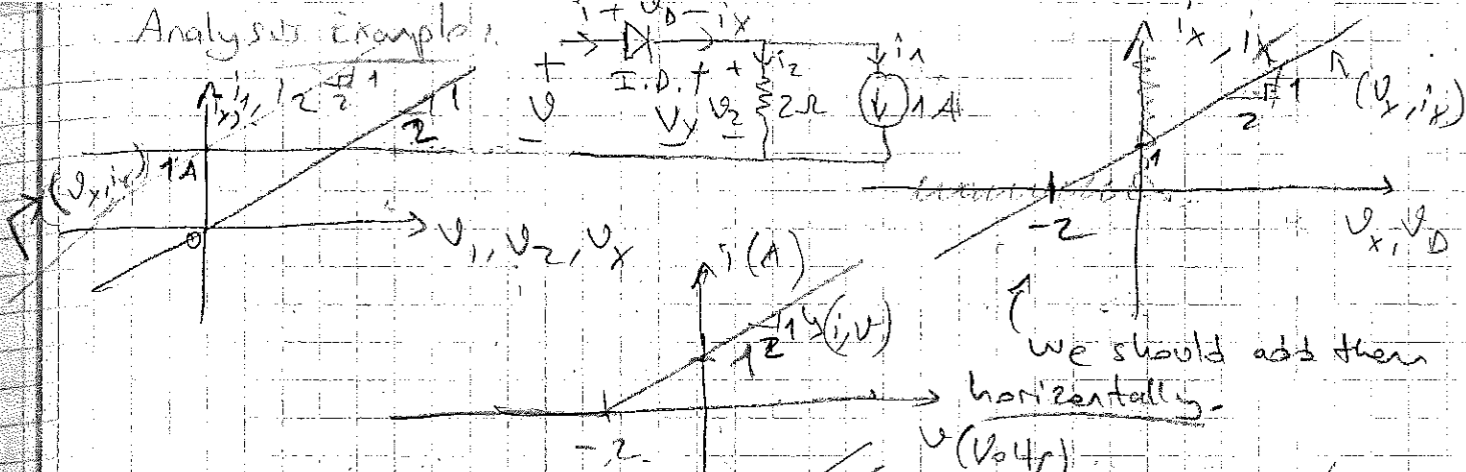


Design Example:

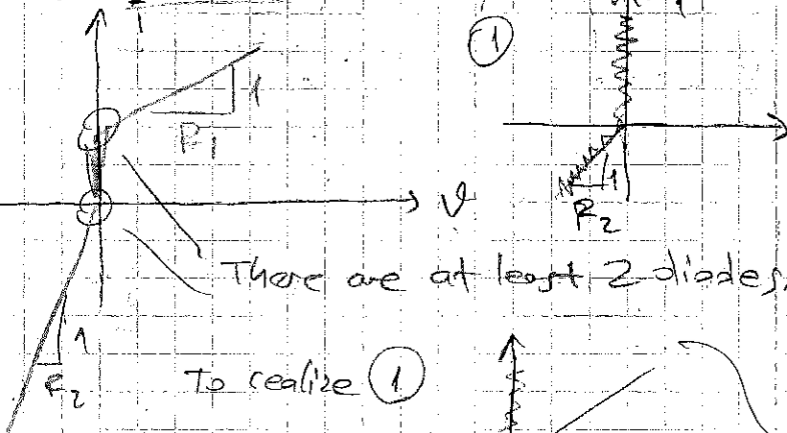


To realize ①





To realize ②:

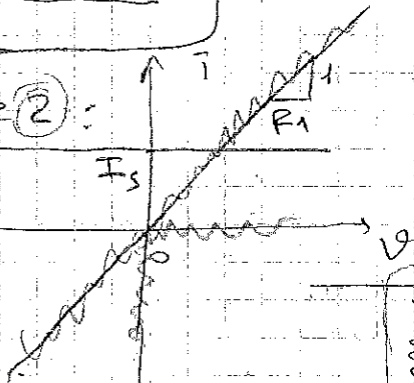


Vertical addition gives ②

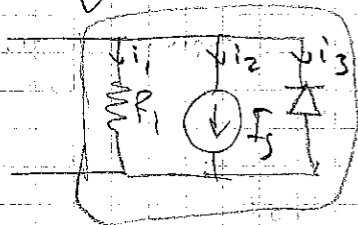


Final design:

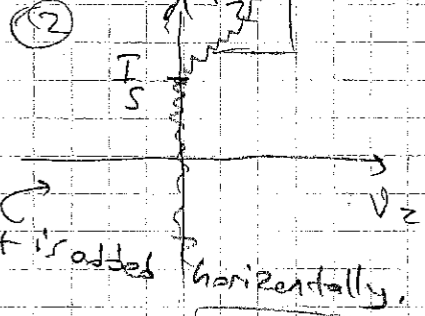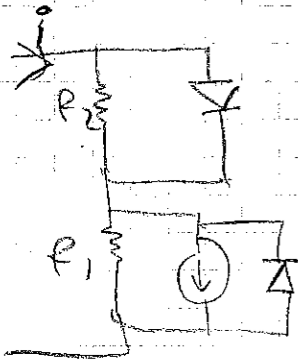

Vertical addition: i.e. parallel combination (for the same voltage add currents)

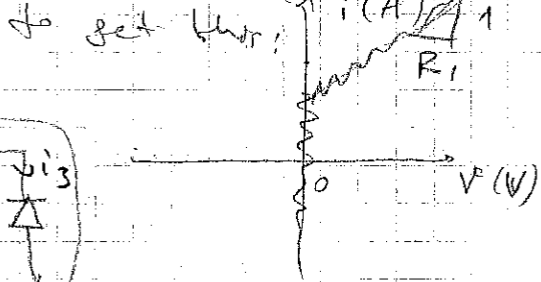





Ex 11

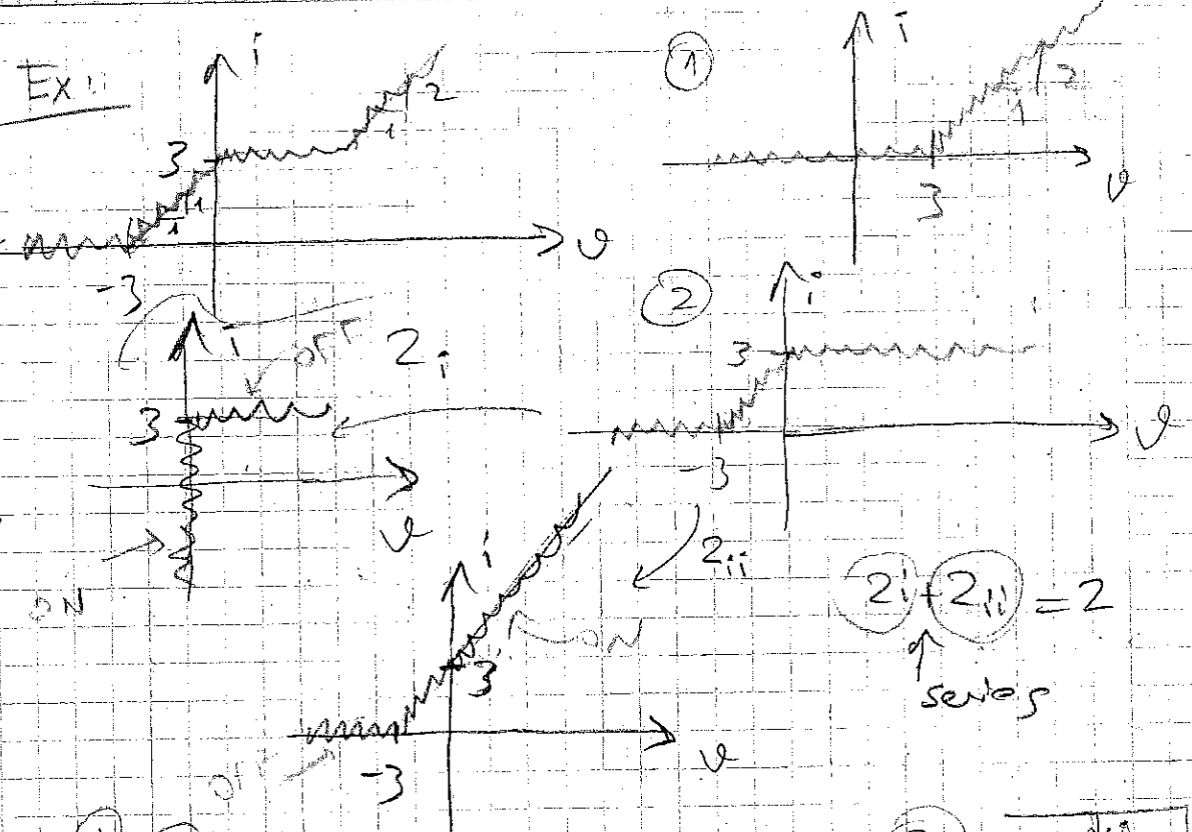


(1) / (2) is the final design

$$(2) = (2i) + (2ii)$$

for the same voltage values we add currents.

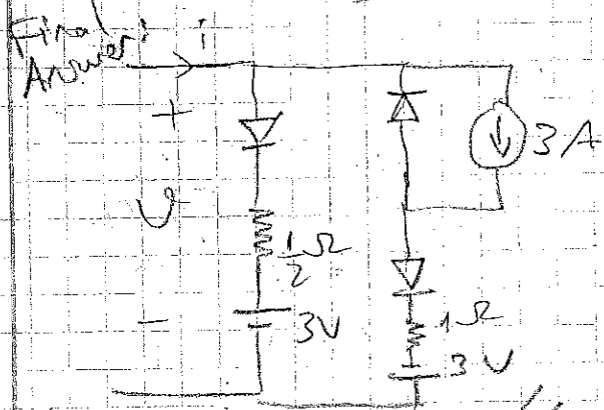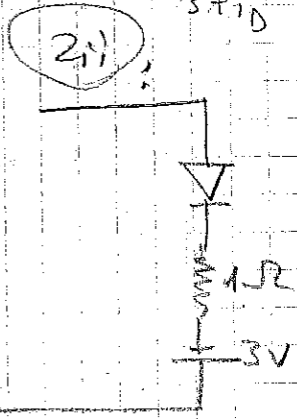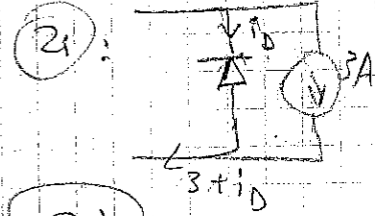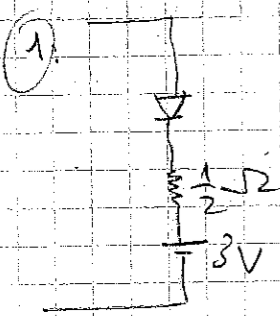

(around 1968)

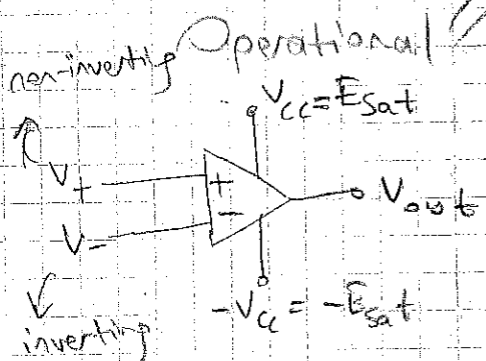

op-amp is an integrated chip in EE311 we will be studying op-amps further.

Ideal Op-Amp Model



$$V_d = V_+ - V_-$$

Differential voltage


For ideal op-amp:

$$\begin{pmatrix} A = \infty \\ r_{out} = 0 \\ R_{in} = \infty \end{pmatrix}$$

It is like a Comparator.

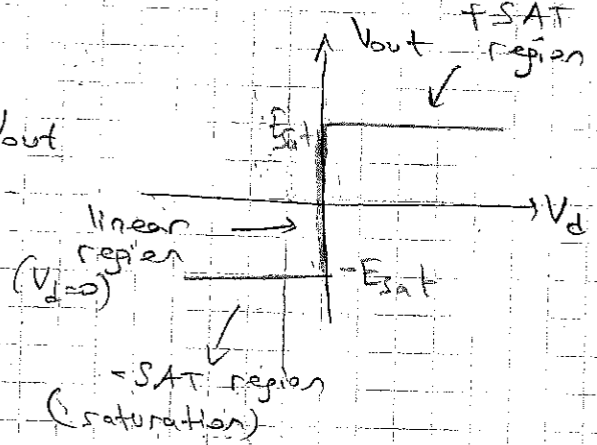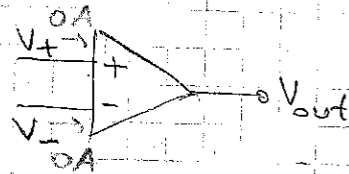

Inverting Amplifier

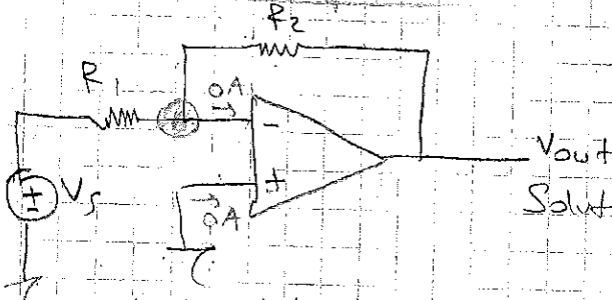



Assume op-amp is ideal and in linear region, find V_{out} in terms of V_s .

- Solution:
- In linear region, $V_d = 0 \rightarrow V_+ = V_-$
 - $I_+ = I_- = 0A$ Ideal op-amp in linear region

KCL at V_- terminal:

$$\frac{0 - V_s}{R_1} + \frac{0 - V_{out}}{R_2} = 0$$

$$V_{out} = -\frac{R_2}{R_1} V_s$$

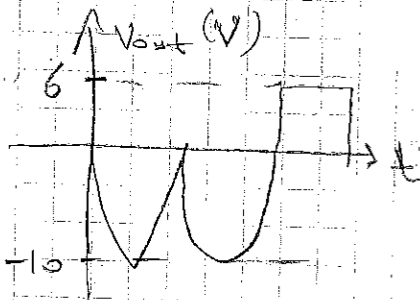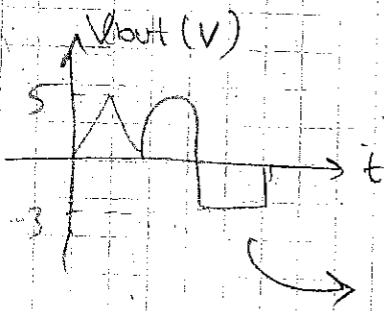


Ideal op-amp Transfer characteristic in linear region

$$I_{in} = \frac{V_s}{R_1} A$$

(output vs input)

Non-inverting Amplifier

Ideal op-amp linear region


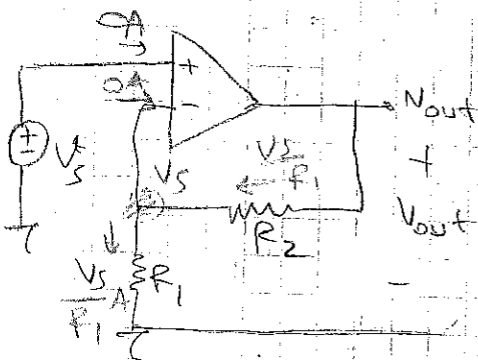


$$V_{out} = V_s + \frac{V_s}{R_1} R_2 = V_s \left(\frac{R_1 + R_2}{R_1} \right)$$


$$\frac{R_1 + R_2}{R_1} = \text{amplification constant} = 1 + \frac{R_2}{R_1}$$

Improved Model (Finite Gain Model)

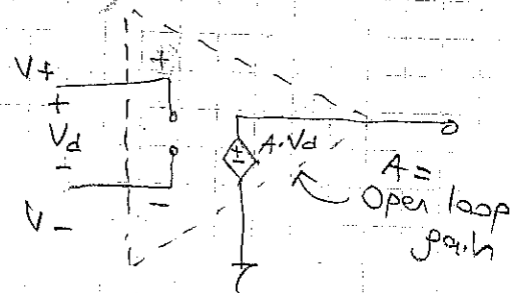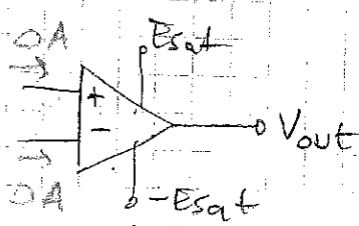
$$\begin{pmatrix} A: \text{finite} \\ r_{out} = 0 \\ R_{in} = \infty \end{pmatrix}$$



the slope is A.

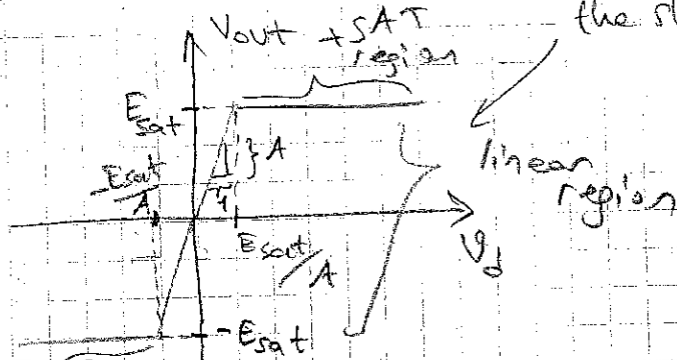

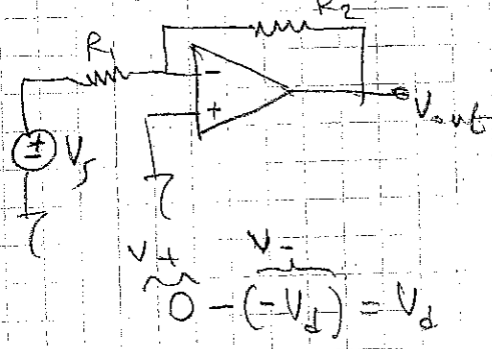Let's analyze inverting amplifier with finite gain model:



KCL at V_- :

$$\frac{-V_d - V_s}{R_1} + \frac{-V_d - V_{out}}{R_2} = 0$$


$$V_d = \frac{-R_2}{R_1 A + R_1 + R_2} V_s$$

Model for linear region

Validity condition

$$|V_d| < \frac{E_{sat}}{A}$$
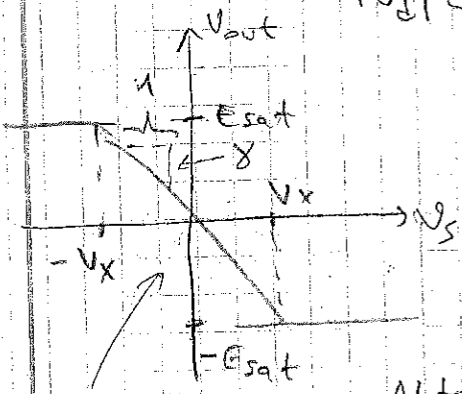
$$V_{out} = A \cdot V_d = \frac{-A \cdot R_2}{A \cdot R_1 + R_1 + R_2} V_s$$



$$|V_d| < \frac{E_{sat}}{A} \rightarrow \frac{-R_2}{R_1 A + R_1 + R_2} V_s < \frac{E_{sat}}{A}$$


$$|V_s| < \frac{E_{sat}}{A} \cdot \frac{R_1 A + R_1 + R_2}{R_2} = V_x$$

$$\gamma = \frac{-A R_2}{R_1 A + R_1 + R_2}$$


Note: As $A \rightarrow \infty$,

$$V_{out} = \frac{-R_2}{R_1} V_s, \quad V_x = E_{sat} \cdot \frac{R_1}{R_2}$$

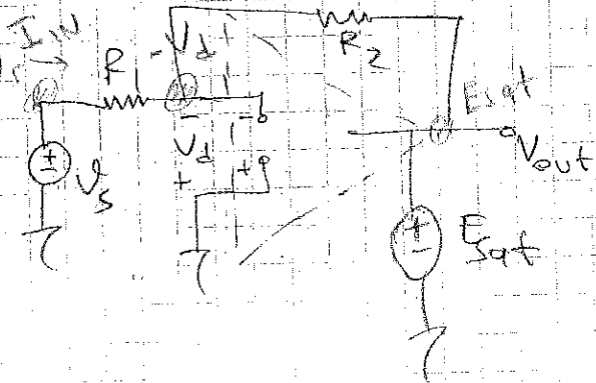$V_{out} = E_{sat}$ provided that $V_d > \frac{E_{sat}}{A}$



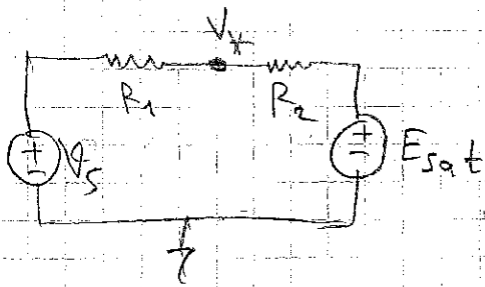$V_{out} = E_{sat}$
Let's find V_s interval for which op-amp is in +SAT region.



from linearity

$$V_x = \frac{R_2}{R_1 + R_2} V_s + \frac{R_1}{R_2 + R_1} E_{sat}$$



$$V_d = - \left(\frac{R_2 V_s + R_1 E_{sat}}{R_1 + R_2} \right)$$

$$V_d > \frac{E_{sat}}{A} \rightarrow \frac{R_2 V_s + R_1 E_{sat}}{R_1 + R_2} < \frac{-E_{sat}}{A}$$

Similarly, when op-amp is in -SAT region;

$$V_s < \frac{-E_{sat} \left(\frac{R_1 + R_2}{A} \right) - R_1 E_{sat}}{R_2}$$

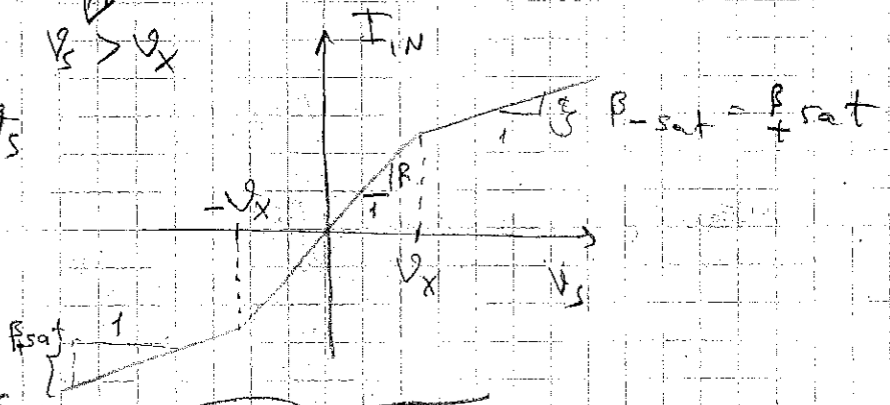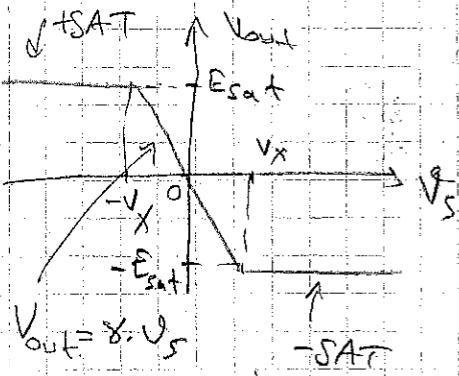$V_{out} = -E_{sat}$ and $V_d < -\frac{E_{sat}}{A}$



transfer characteristic of the circuit

Input characterization

$$I_{IN} = \frac{V_s - (-V_d)}{R_1}$$

Linear region

$$V_d = \frac{-R_2}{R_1 A + R_1 + R_2} V_s$$


$$I_{IN} = \frac{V_s}{R_1} \left(1 - \frac{R_2}{R_1 A + R_1 + R_2} \right)$$

$$= \frac{V_s}{R_1} \left(\frac{R_1 A + R_1}{R_1 A + R_1 + R_2} \right)$$


+SAT $V_d = - \left(\frac{R_2 V_s + R_1 E_{sat}}{R_1 + R_2} \right)$

$$I_{IN} = \frac{V_s}{R_1} - \frac{R_2}{(R_1 + R_2)} \frac{V_s}{R_1} - \frac{R_1}{(R_1 + R_2)} \frac{E_{sat}}{R_1}$$
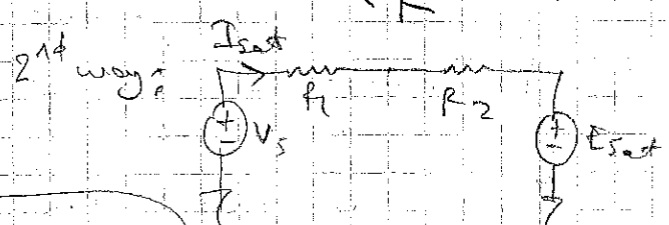
$$I_{IN} = \left(\frac{1}{R_1 + R_2} \right) V_s - \frac{1}{R_1 + R_2} E_{sat}$$



Integrator

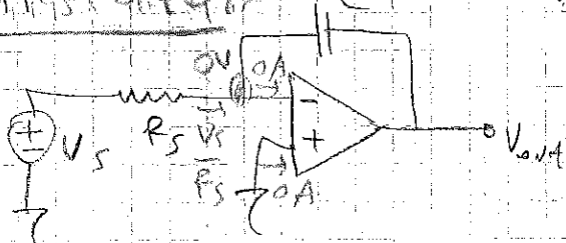

Ideal op-amp in linear region



$$V_{out} = - \int i_c dt$$

$$= - \frac{1}{C} \int i_c(t) dt$$

$$V_{out}(t) = - \frac{1}{R_s C} \int_{-\infty}^t V_s(\tau) d\tau$$


Op-amp's (cont'd)

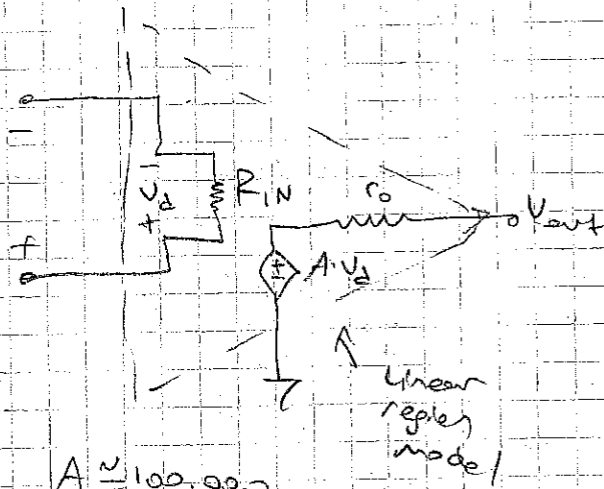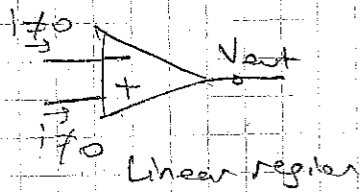Improved model for op-amp: (A : finite, $r_o \neq 0$, $r_{in} \neq \infty$)



$A \approx 100,000$
 $R_{in} \approx 1M\Omega$
 $r_o \approx 10\Omega$

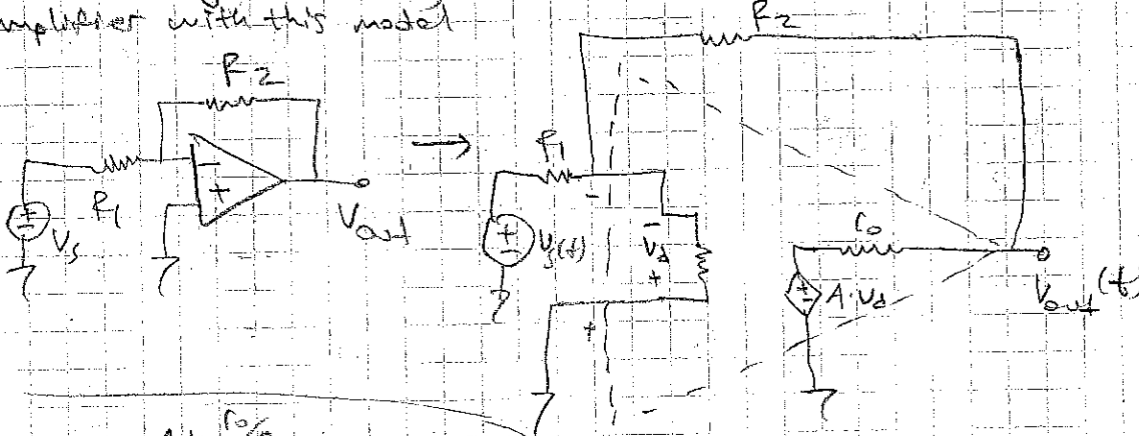Let's analyze inverting amplifier with this model



$$V_{out} = \frac{-A + r_o/R_2}{\frac{R_1}{R_2} (1 + A + \frac{r_o}{R_{in}}) + (\frac{R_1}{R_{in}} + 1) + \frac{r_o}{R_2}} V_s$$

Linear resistor model
 Finding V_{out} as a function of $V_s(t)$.

Let's check what happens as;

① ($A \rightarrow \infty$) \rightarrow ($V_{out} \rightarrow -\frac{R_2}{R_1} V_s$)

② A is finite; and I would like to design an amplifier with gain -10 , that is from ideal op-amp model $-\frac{R_2}{R_1} = -10$

$$\frac{R_2}{R_1} = 10$$


Design rule

So, by selecting R_1 and R_2 as much larger than r_o and at the same time much smaller than R_{in} , I can have a reliable design.

$R_k \gg r_o$
 $R_k \ll R_{in}$
 Select $R_k \approx 10k\Omega$

$k = \{1, 2\}$
 if $R_{in} \approx 1M\Omega$
 $r_o \approx 10\Omega$

Differentiator R_F

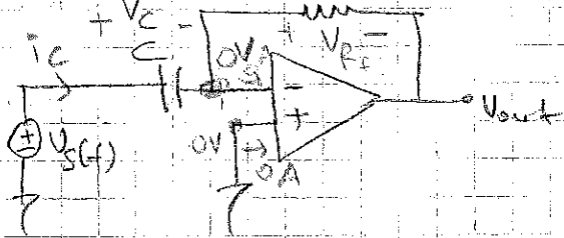

Ideal op-amp, linear region

$$(D^2 + D + 1) V_{out}(t) = V_s(t)$$

$$V_{out}(0) = 0$$

$$V_o(0) = 0$$

(derivative)

$$i_c(t) = C \frac{d}{dt} V_c(t)$$


$$i_c(t) = C \frac{d}{dt} V_s(t) = C \cdot \dot{V}_s(t)$$

$$V_{R_F} = R_F \cdot i_c$$

$$V_{out} = 0 - V_{R_F} = -R_F \cdot C \frac{d}{dt} V_s(t)$$

Some examples for ideal op-amp analysis


Ex:

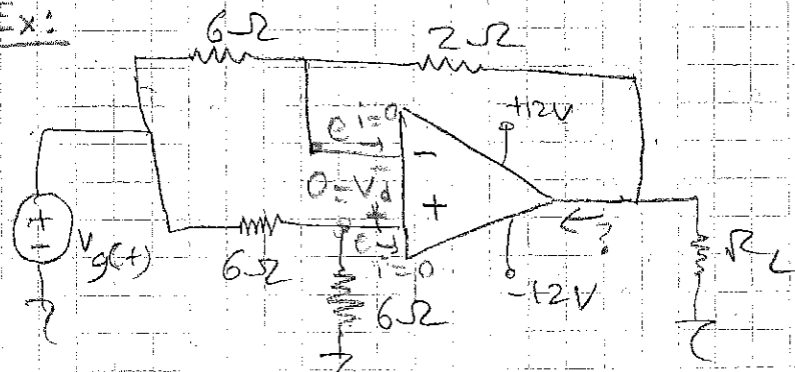

KCL at V_- : $\frac{e - V_g}{6} + \frac{e - V_{out}}{2} = 0$

KCL at V_+ : $\frac{e - V_g}{6} + \frac{e}{6} = 0 \rightarrow e = \frac{-V_g}{2}$

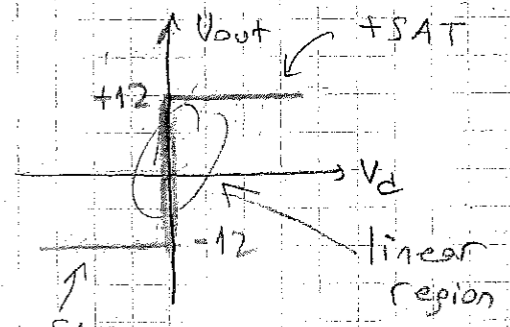Find V_{out} (Assume ideal op-amp in linear region)




(*) $4e - 3V_{out} - V_g = 0$
 $\rightarrow V_g = 3V_{out}$

$$V_{out} = \frac{V_g}{3}$$

Caution: Do NOT write a KCL equation at V_{out} since with ideal op-amp model you cannot calculate I_{out} since we do not know A_{oc} or R_o values.

Ex:

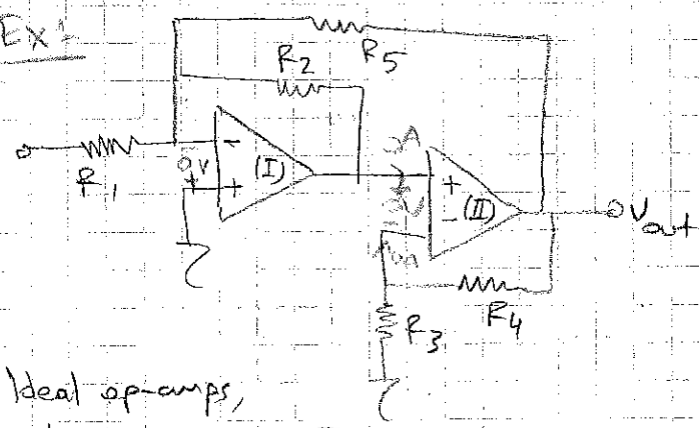

Ideal op-amps, in linear region; Find V_{out} .

Don't write KCL at V_{out} .

We almost always use negative feedback.

KCL at V_- terminal of (II):
 $\frac{e}{R_3} + \frac{e - V_{out}}{R_4} = 0 \rightarrow e = \frac{R_3}{R_3 + R_4} V_{out}$

KCL at V_- terminal of (I):
 $\frac{0 - V_s}{R_1} + \frac{0 - V_{out}}{R_2} + \frac{0 - e}{R_2} = 0$

$$V_{out} = \frac{-R_5 R_2 (R_3 + R_4)}{[R_2 (R_3 + R_4) + R_2 R_5] R_1} V_s$$


This analysis is only valid when op-amp **I** is in linear region:

$|V_{out}| < E_{sat} \rightarrow |e| < E_{sat}$
 op-amp **II** is in linear region!

$|V_{out}^{II}| < E_{sat} \rightarrow |V_{out}| < E_{sat}$ $|V_s| < Y$

Assume ideal op-amp
 Find V_{out} vs. V_{IN}, I_{IN} vs. V_{IN}
 for all 3 regions of op-amp.

$|V_s| < X$
 $|V_s| \leq \min(X, Y)$

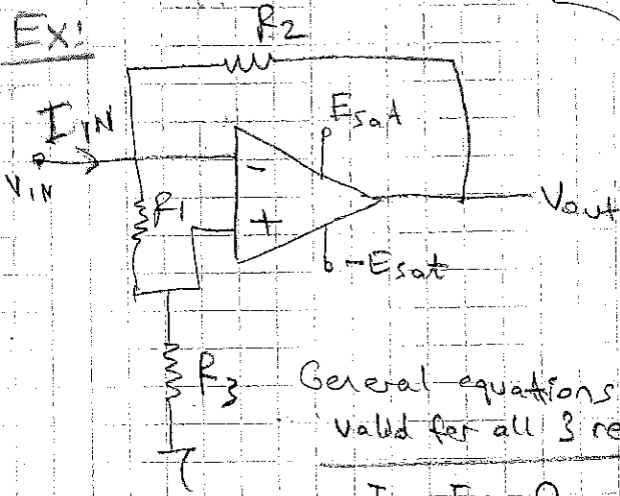

General equations valid for all 3 regions!


$$I_+ = I_- = 0$$

KCL at V_+ :

$$\frac{V_+}{R_3} + \frac{V_+ - V_{IN}}{R_1} = 0 \rightarrow V_+ = \frac{R_3}{R_3 + R_1} V_{IN} \quad V_- = V_{IN}$$

① Linear region

$V_d = 0$
 $|V_{out}| < E_{sat}$
 $V_d = 0 \rightarrow V_+ = V_- \rightarrow V_{IN} = 0$ **A**

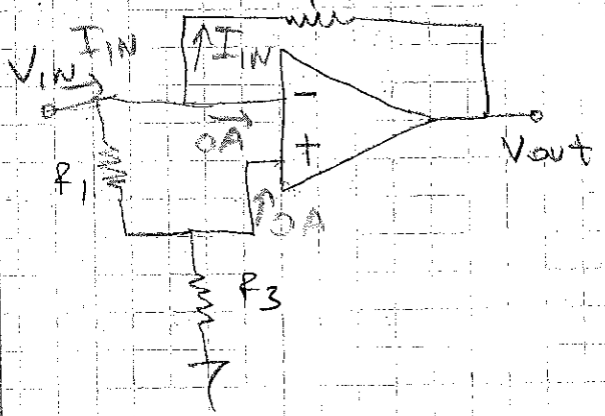


$$V_{out} = -I_{IN} R_2$$

Condition $|V_{out}| < E_{sat} \rightarrow |I_{IN}| < \frac{E_{sat}}{R_2}$ **B** **C**

② +SAT region

$V_{out} = +E_{sat}$
 $V_d > 0 \rightarrow V_+ > V_- \rightarrow V_{IN} < 0$ **D**

$$V_{out} = +E_{sat} \quad \text{E}$$

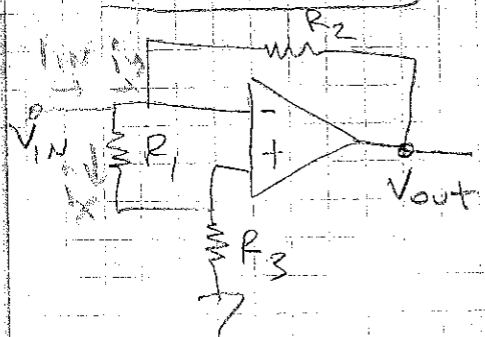

$$I_{IN} = i_x + i_y = \frac{V_{IN}}{R_1 + R_3} + \frac{V_{IN} - E_{sat}}{R_2} \quad \text{F}$$



③ -SAT region

$$V_{out} = -E_{sat} \quad \left. \begin{array}{l} V_d < 0 \end{array} \right\}$$

$$V_{out} = -E_{sat} \quad \text{A}$$


$$V_{IN} > 0 \quad \text{B}$$
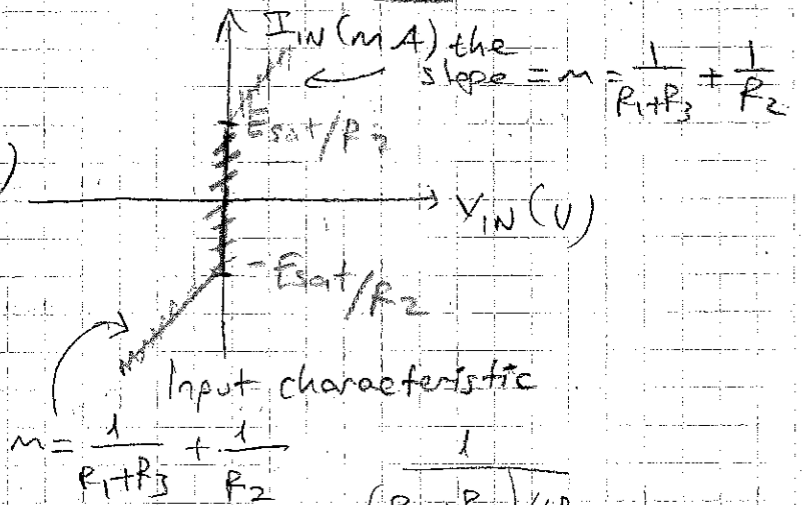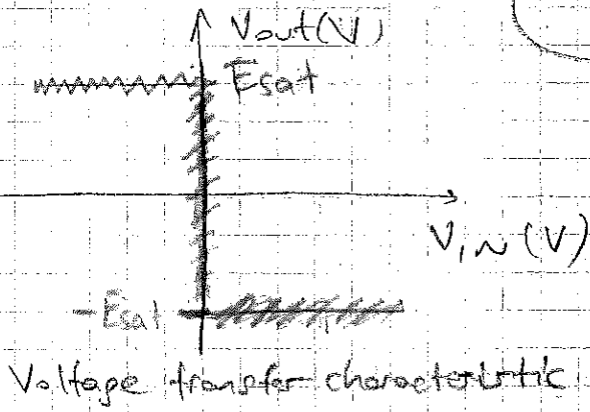
$$I_{IN} = \frac{V_{IN}}{R_1 + R_3} + \frac{V_{IN} + E_{sat}}{R_2} \quad \text{C}$$



Op-Amps (cont'd)

CMRR (Common Mode Rejection Ratio)

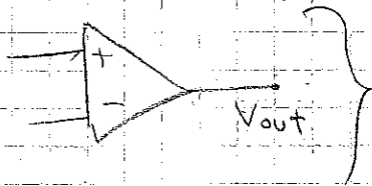

Ideally, in linear region

$$V_{out} = A(V_+ - V_-)$$

V_d open-loop gain/finite gain
means there is no feedback

But in practice

$$V_{out} = A_+ V_+ - A_- V_-$$

finite gain of inverting terminal (V_-)

$$V_{com} = \frac{V_+ + V_-}{2} \quad V_d = V_+ - V_-$$

$$V_+ = V_{com} + \frac{V_d}{2}$$

$$V_- = V_{com} - \frac{V_d}{2}$$

$$V_{out} = A_+ V_+ - A_- V_-$$

$$= A_+ \left(V_{com} + \frac{V_d}{2} \right) - A_- \left(V_{com} - \frac{V_d}{2} \right)$$

$$= V_{com} (A_+ - A_-) + V_d \left(\frac{A_+ + A_-}{2} \right)$$

A_{com}
Common mode
voltage gain

A_d
Differential mode gain

$$CMRR \Rightarrow \left(\frac{A_d}{A_c} \right) \rightarrow \left(\frac{A_d}{A_c} \right)_{dB}$$


$$= 20 \log_{10} \left(\frac{A_d}{A_c} \right)$$

A_{com}

Ideally, $CMRR = \infty$, that is, $A_+ = A_- \Rightarrow \begin{cases} A_{com} = 0 \\ A_d = A_+ = A_- = A \end{cases}$

dB = decibell, Graham Bell


Positive and Negative Feedback

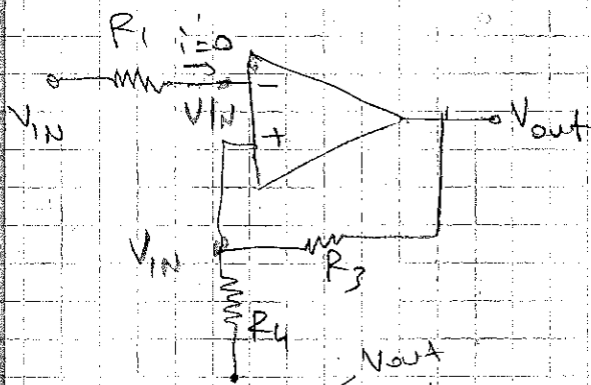

Assume linear region, ideal opamp

$$V_{out} = \frac{R_3 + R_4}{R_4} V_{in}$$

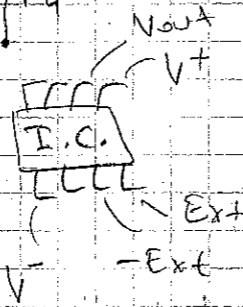
The difference with negative feedback is there isn't a minus sign.




The propagation delay isn't zero!

$$t=0, 0.1 \text{ Volts} \rightarrow V_{out}(0^+) = A \cdot V_{in}(0)$$

It amplifies until saturation

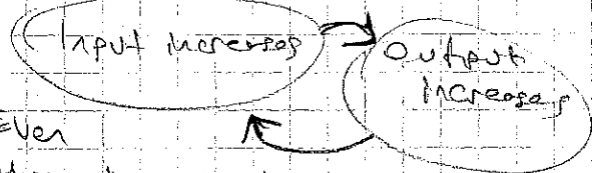

Even if there is a little noise,

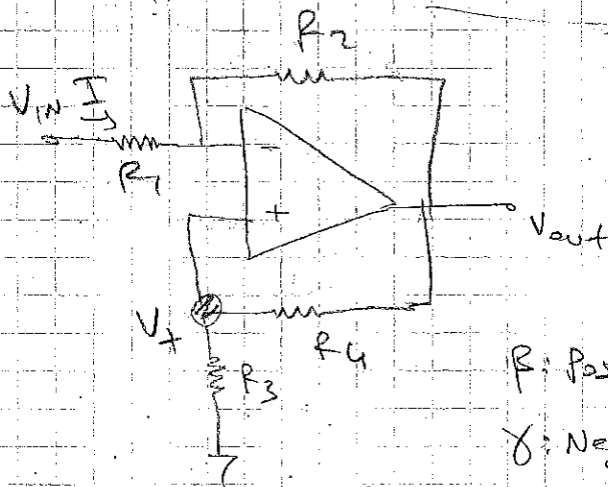

$$V_+ = \frac{R_3}{R_3 + R_4} V_{out}$$

$$V_- = \frac{R_2}{R_1 + R_2} V_{in} + \frac{R_1}{R_1 + R_2} V_{out}$$

β : Positive feedback coef.


γ : Negative feedback coef.

Depending on $\beta > \gamma$, $\beta < \gamma$, $\beta = \gamma$

we have different V_{out}/V_{in} characteristics


Waveforms

① Unit Step Function

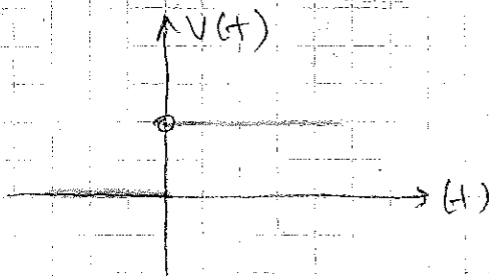


$$V(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases}$$

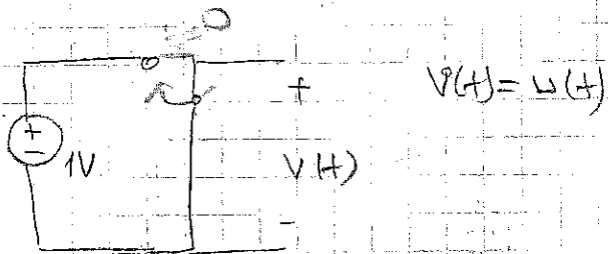$V(0) \triangleq \frac{1}{2}$ (Not critical in EE201 but defined as $V(0) = \frac{1}{2}$ in EE301 for Fourier Series discussion)



Switch moves from A to B at $t=0$

(2) Ramp Function

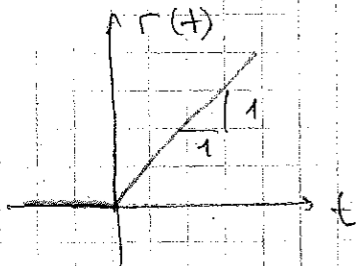


$$r(t) = \begin{cases} t, & t \geq 0 \\ 0, & t < 0 \end{cases}$$

$$r(t) = tu(t)$$




Combining elementary waveforms to synthesize other waveforms

Ex: $V(t) = f(t)$

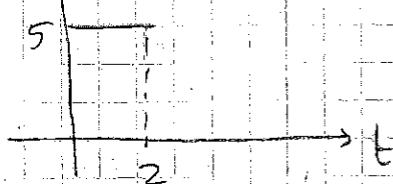


Express $V(t)$ as a linear combination of $u(t)$ and its shifted versions

$$f(t) = 5u(t) - 5u(t-2)$$

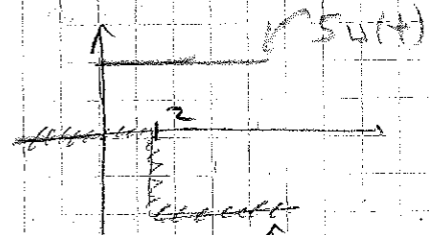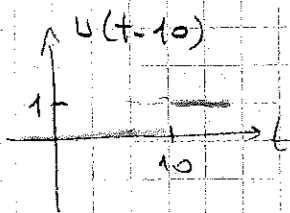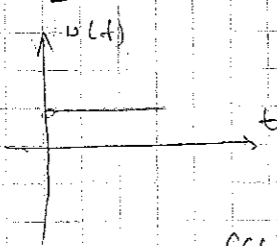

$$f(t) = 5u(t) - 5u(t-2)$$

Ex: Sketch $u(t^2-2t)$ vs t .

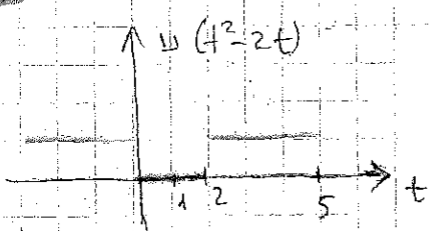


$$f \circ g(x) = f(g(x))$$

$$g(t) = t^2 - 2t = t(t-2)$$


$$g(t) > 0 \text{ or } < 0 \text{ ?}$$

$$g(t) = 0 \Rightarrow t = \{0, 2\}$$

$$g(t) < 0 \Rightarrow t \in (0, 2)$$

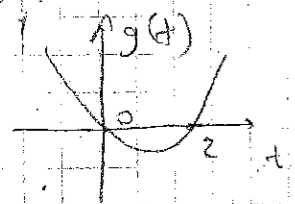


Ex:


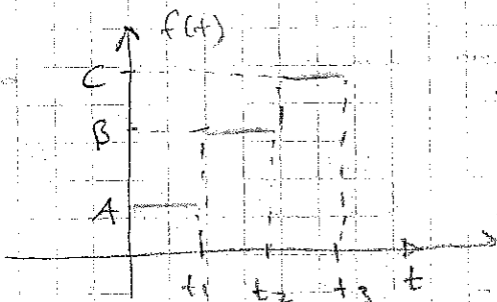


$$f(t) = Au(t) + (B-A)u(t-t_1) + (C-B)u(t-t_2) + (-C)u(t-t_3)$$


Exc

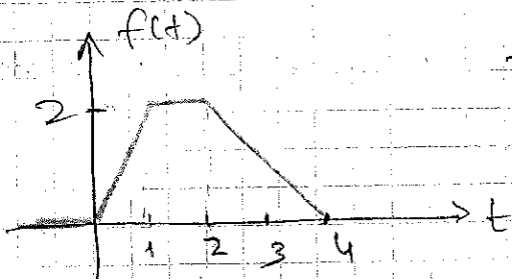
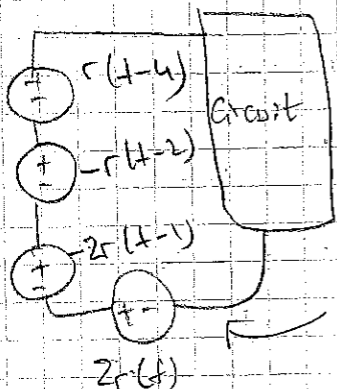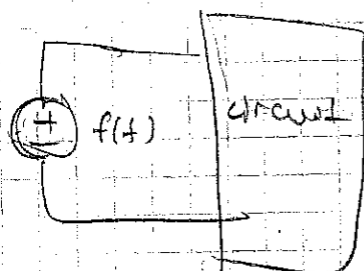
$$f(t) = 2r(t) - 2r(t-1) - r(t-2) + r(t-4)$$



we will use linearity later.

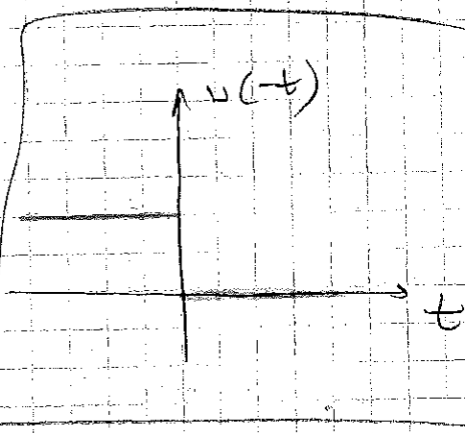


3 Impulse Function


(Generalized function, not a regular calculus function)

Definition: $\int_{-\infty}^{\infty} f(t) \delta(t-t_0) dt \triangleq f(t_0)$ for all continuous $f(t)$




impulse at $t=t_0$

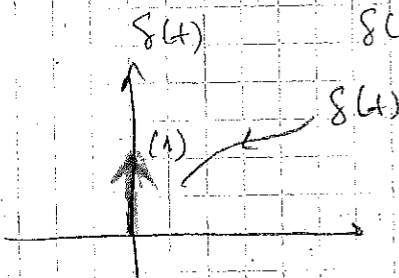

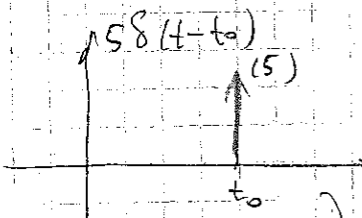$\delta(t)$: Unit weight Impulse Function



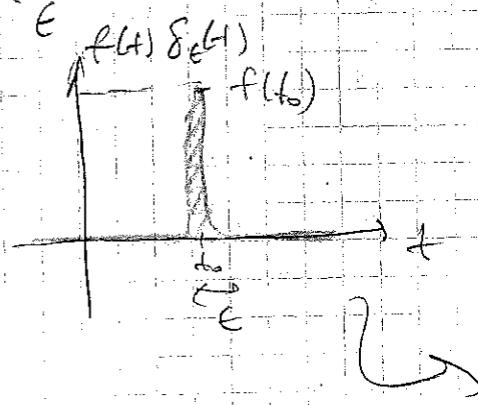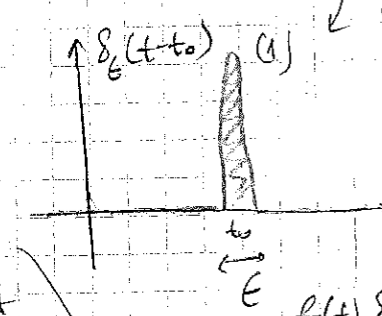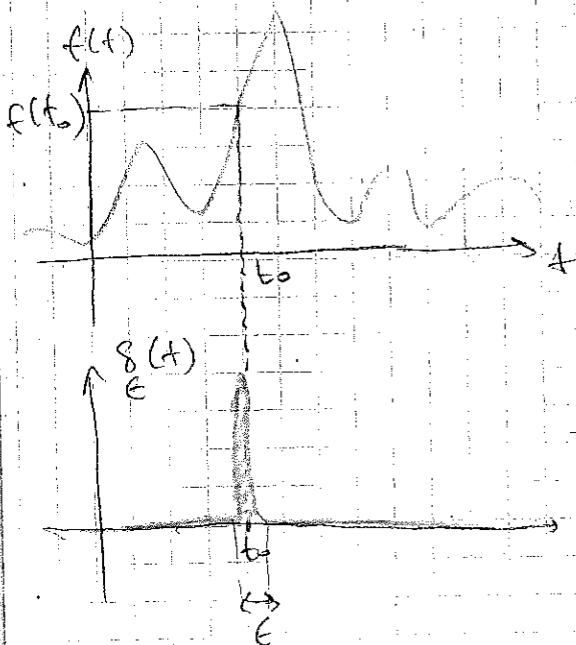interpretation: very narrow pulse at $t=t_0$



$$\int_{-\infty}^{\infty} f(t) \delta_{\epsilon}(t-t_0) dt \approx \int_{-\infty}^{\infty} f(t_0) \delta_{\epsilon}(t-t_0) dt = f(t_0) \cdot \int_{-\infty}^{\infty} \delta_{\epsilon}(t-t_0) dt$$

area under $\delta_{\epsilon}(t)$

$$\int f(t) \delta_{\epsilon}(t-t_0) dt = f(t_0)$$

$$\lim_{\epsilon \rightarrow 0} \int f(t) \delta_{\epsilon}(t-t_0) dt = f(t_0)$$

$$\int f(t) \lim_{\epsilon \rightarrow 0} \delta_{\epsilon}(t-t_0) dt = f(t_0) \stackrel{\Delta}{=} \int f(t) \delta(t-t_0) dt = f(t_0)$$

Note that impulse, $\delta(t)$ is not a regular calculus function.

$$\lim_{t_0 \rightarrow 0} \int_{-\infty}^{\infty} f(t) \delta(t-t_0) dt = \int_{-\infty}^{\infty} f(t) \delta(t) dt = f(0)$$

Properties:

$$\textcircled{1} \int_{0^-}^{0^+} \delta(t) dt = 1$$

Area under impulse (weight of impulse) is 1.

$0^- = 0 - \epsilon$
 $\epsilon > 0$, but ϵ is arbitrary small $\epsilon \approx 10^{-12}$

$$\int_{-\infty}^{\infty} f(t) \delta(t) dt = f(0)$$

$$\int_{-\infty}^{\infty} \delta(t) dt = 1$$

$$\int_{0^-}^{0^+} \delta(t) dt = 1$$

Impulse Function (cont'd)

$\delta(t-t_0)$ Its weight is 1.



Properties


$$\textcircled{1} \delta(t) = 0 \Rightarrow t \neq 0$$

$$[\delta(t) = ? \quad t = t_0!]$$

more on this later

$$\textcircled{2} \int_{-\infty}^{\infty} \delta(t) dt = \int_{0^-}^{0^+} \delta(t) dt = 1$$

③ Simplistic Explanation:

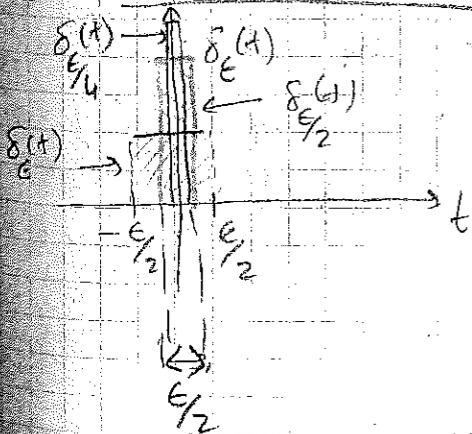


$$\delta_{\epsilon}(t) = \begin{cases} 1/\epsilon, & |t| < \epsilon/2 \\ 0, & \text{other} \end{cases}$$

$$\delta_{\epsilon}(t) \xrightarrow{\epsilon \rightarrow 0} \delta(t)$$

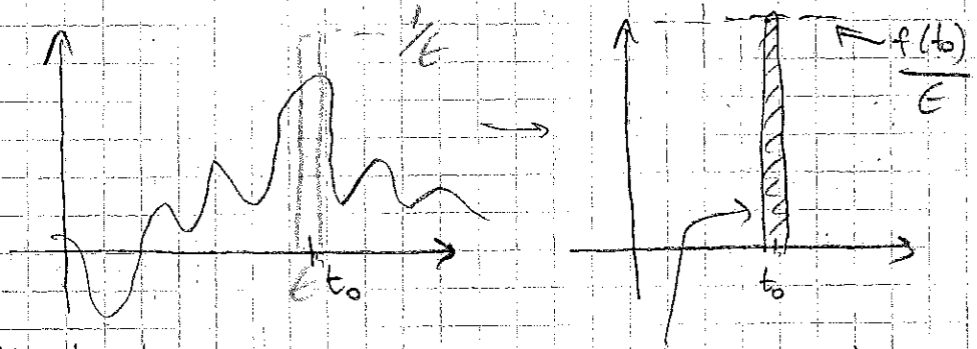4) More Accurate Explanation!

$$\lim_{\epsilon \rightarrow 0} \left(\int_{-\infty}^{\infty} f(t) \delta_{\epsilon}(t-t_0) dt \right) = f(t_0); \quad f(t) \text{ is continuous at } t=t_0$$



Additional note!

$$\lim_{\epsilon \rightarrow 0} \langle \delta_{\epsilon}(t-t_0), f(t) \rangle = f(t_0)$$

The area $\approx \frac{f(t_0)}{\epsilon} \cdot \epsilon$


Inner product $\rightarrow \delta_{\epsilon}(t) \rightarrow \delta(t)$
in the sense weak convergence

Finally, $f(t) \delta(t-t_0) = f(t_0) \delta(t-t_0)$

Don't forget this one

$$\int_{-\infty}^{\infty} f(t) \delta(t-t_0) dt = \int_{-\infty}^{\infty} f(t_0) \delta(t-t_0) dt = f(t_0)$$

4) Sinusoid Function

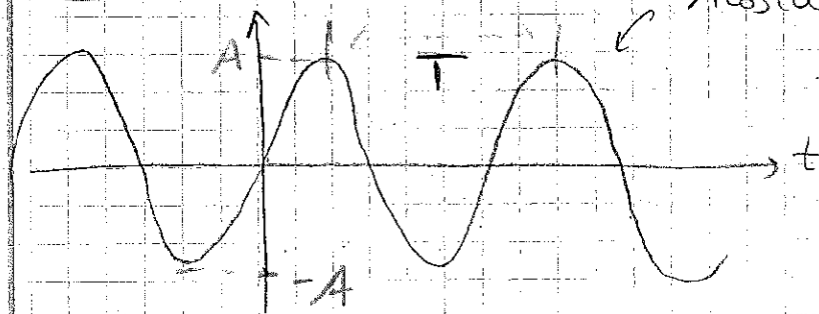

$$A \cos(\omega t + \theta)$$

A: amplitude
omega: radial frequency (rad)
omega (small case)
Capital Omega: Ω

Cosine function is a mapping from real numbers to real numbers, so argument of cosine is a real number.

$$\cos(\pi) = -1 \quad \cos(180^\circ) = -1$$

\uparrow
 ≈ 3.14159

don't forget degree sign !!

theta: phase of the sinusoid function

$$\omega = 2\pi f$$

rad/sec

freq: $1/2 \left(\frac{1}{\text{sec}} \right)$

$$T = \frac{1}{f}$$

Capacitor

LTI capacitor $Q = C \cdot V$ Inverses of each other

$$+ \begin{array}{c} i_c(t) \\ \downarrow \\ v_c(t) \\ \uparrow \\ - \end{array} \rightarrow \begin{cases} i_c(t) = C \frac{d v_c(t)}{dt} \\ v_c(t) = v_c(0^-) + \frac{1}{C} \int_{0^-}^t i_c(\tau) d\tau, t > 0^- \end{cases}$$

$$\frac{d}{dt} \int_a^t f(\tau) d\tau = \frac{d}{dt} \{ F(t) - F(a) \}$$

$$(f(t) = t^2, F(t) = \frac{t^3}{3})$$

Leibniz's rule for differentiation under integral sign

$$\frac{d v_c(t)}{dt} = \frac{1}{C} i_c(t)$$

General Capacitor Relation

$$Q_{cap}(t) = C(t) v_c(t)$$

total charge of capacitor



$$i_c(t) = \frac{d}{dt} (C(t) v_c(t))$$

$$= \left(\frac{d}{dt} C(t) \right) v_c(t) + C(t) \frac{d v_c(t)}{dt}$$

$$Q_{cap}(t) = C(t) \cdot v_{cap}(t)$$


$$\frac{d}{dt} \rightarrow i_c(t) = \frac{d}{dt} \{ C(t) \cdot v_{cap}(t) \}$$

Analog radio:

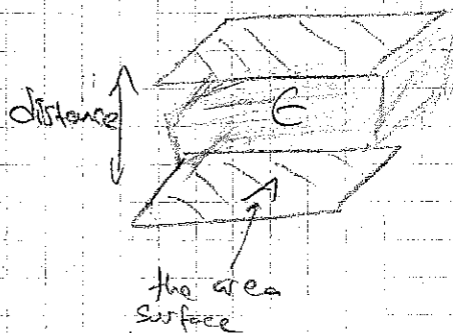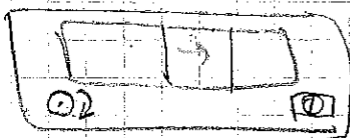


$$C = \epsilon \frac{A}{d}$$

Farads

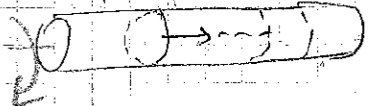


Power Calculation

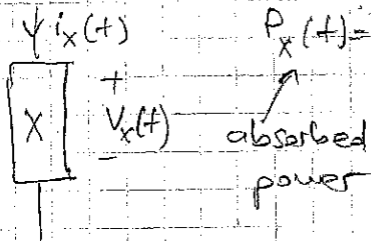

$$P_x(t) = v_x(t) \cdot i_x(t)$$

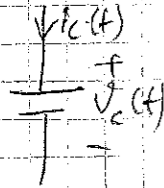Let's apply the power calculation on capacitor:



$$P_{cap}(t) = i_c(t) v_c(t)$$

$$= C \frac{dv_c(t)}{dt} v_c(t)$$

instantaneous power

$$\Delta E_{t_1 \rightarrow t_2} = \int_{t_1}^{t_2} P_x(t) dt$$

Energy change in between t_1 and t_2


$$\Delta E_{t_1 \rightarrow t_2} = \int_{t_1}^{t_2} P_{cap}(t) dt = \int_{t_1}^{t_2} C v_c(t) dv_c(t)$$

$$= C \int_{v_1=v_c(t_1)}^{v_2=v_c(t_2)} v dv = \frac{1}{2} C v^2 \Big|_{v_1=v_c(t_1)}^{v_2=v_c(t_2)} = \left[\frac{1}{2} C v_c^2(t_2) - \frac{1}{2} C v_c^2(t_1) \right]$$

Stored energy of the cap at $t=t_2$

Stored energy at $t=t_1$

Initial Condition Models for Capacitor

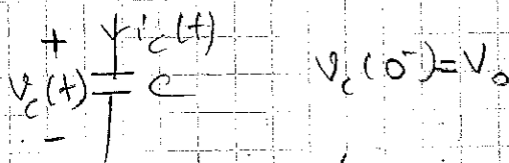


$$v_c(0^-) = V_0$$

$$v_c(t) = v_c(0^-) + \frac{1}{C} \int_{0^-}^t i_c(\tau) d\tau$$

$$v_c(t) = V_0 + \frac{1}{C} \int_{0^-}^t i_c(\tau) d\tau, t > 0 \quad (I)$$

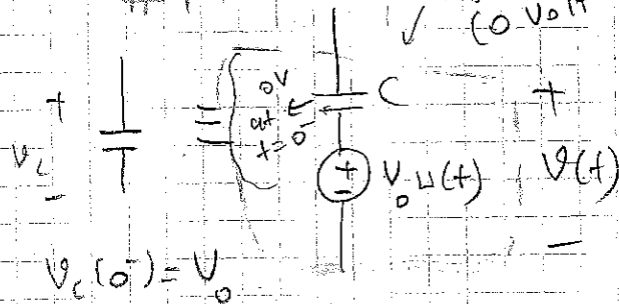Initial Condition Model #2: empty capacitor (0 Volt at $t=0^-$)



$$v_c(0^-) = V_0$$

$$v_c(t) = \left(0 + \frac{1}{C} \int_{0^-}^t i_c(\tau) d\tau \right) + V_0 u(t)$$



empty cap $v_c(t)$

$$v_c(t) = \frac{1}{C} \int_{0^-}^t i_c(\tau) d\tau + V_0, t > 0 \quad (II)$$

actually the same

Initial condition

Model #2

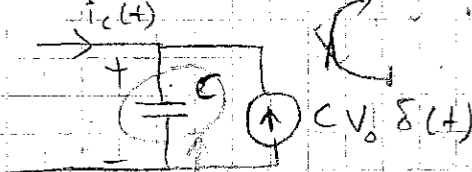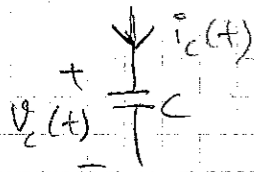

$$i_c^{empty}(t) = i_c(t) + C v_0 \delta(t)$$


$$v_c^{empty}(t) = 0 + \frac{1}{C} \int_0^t i_c(\tau) d\tau$$

empty cap.
0 Volt at $t=0^-$

$$v_c^{empty}(t) = \frac{1}{C} \cdot \int_0^t \delta(\tau) d\tau + \frac{1}{C} \int_0^t i_c(\tau) d\tau$$

(III)

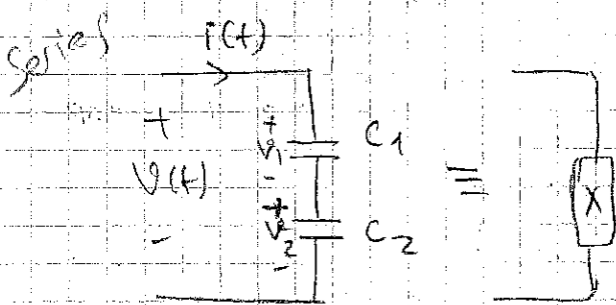Series and Parallel Combination of Capacitors



$$v(t) = v_1 + v_2$$


$$= \frac{1}{C_1} \int_0^t i(\tau) d\tau + \frac{1}{C_2} \int_0^t i(\tau) d\tau$$

$$v(t) = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \int_0^t i(\tau) d\tau$$

Assume C_1 and C_2 are uncharged (empty).


i-v relation of an empty capacitor with
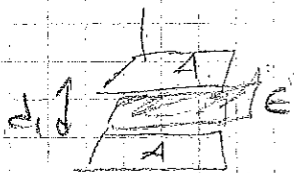
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$



$$C_1 = \epsilon \frac{A}{d_1}$$

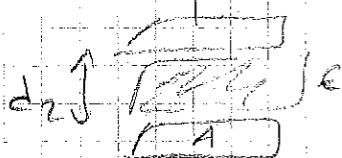
$$C_{eq} = \frac{\epsilon A}{d_1 + d_2} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$



$$C_2 = \epsilon \frac{A}{d_2}$$



$$\frac{\epsilon A}{\epsilon A \left(\frac{1}{C_1} + \frac{1}{C_2} \right)} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$

If C_1 and C_2 are charged:

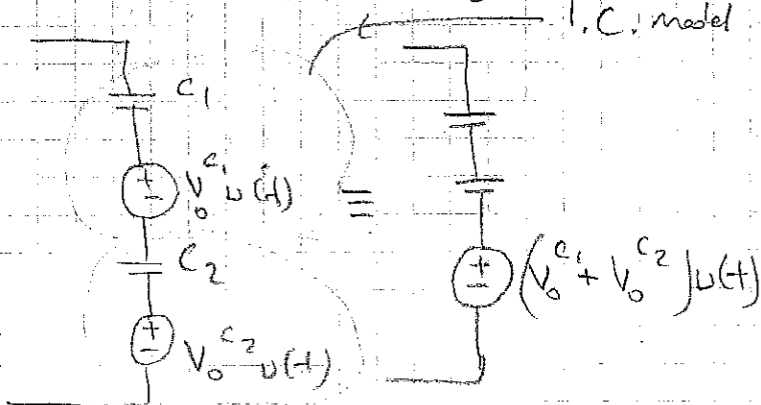

So, if caps are charged, the equivalent comp. is a charged cap with initial voltage $= v_{C_1}(0) + v_{C_2}(0)$ and $C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

Parallel

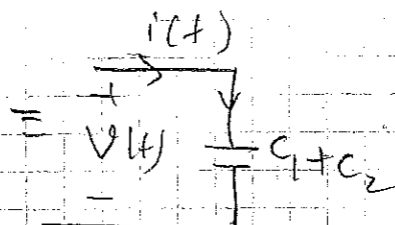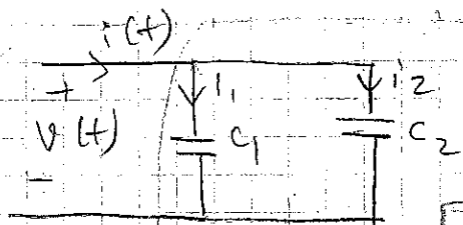

Assume C_1 and C_2 are empty

For [1]: $i(t) = i_1(t) + i_2(t)$
 $= C_1 \frac{d}{dt} V_{C_1}(t) + C_2 \frac{d}{dt} V_{C_2}(t)$





$$i(t) = (C_1 + C_2) \frac{dV_C(t)}{dt}$$

$$C_{eq} = C_1 + C_2$$

A terminal equation

for $C_1 + C_2 = C_{eq}$

Voltage Division for Capacitors

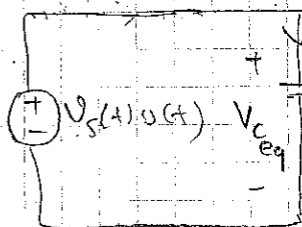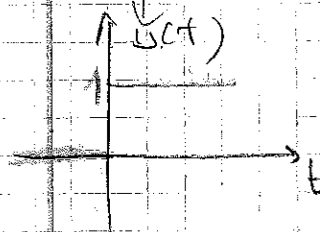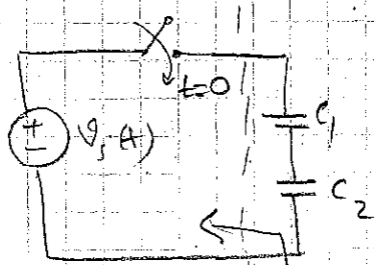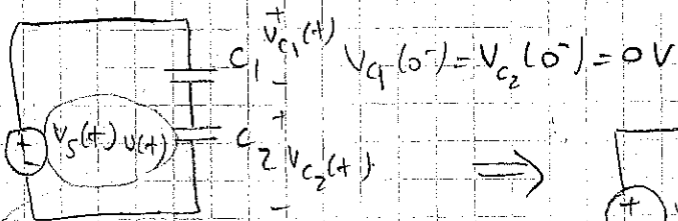

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} \text{ F}$$

$$i(t) = C_{eq} \frac{d}{dt} V_{C_{eq}}(t)$$

$$= C_{eq} \left(\frac{d}{dt} V_s(t) u(t) \right)$$

From original circuit


$$V_{C_1}(t) = V_{C_1}(0^-) + \frac{1}{C_2} \int_0^t i(\tau) d\tau$$

$$= \frac{1}{C_1} \cdot C_{eq} V_s(\tau) u(\tau) \Big|_{\tau=0^-}^{\tau=t}$$

$$= \frac{C_2}{C_1 + C_2} \left[V_s(t) u(t) - V_s(0^-) u(0^-) \right] = \frac{C_2}{C_1 + C_2} V_s(t) u(t)$$

$$V_{C_2}(t) = V_{C_2}(0^-) + \frac{1}{C_2} \int_0^t i(\tau) d\tau = \frac{C_1}{C_1 + C_2} V_s(t) u(t)$$

Note:

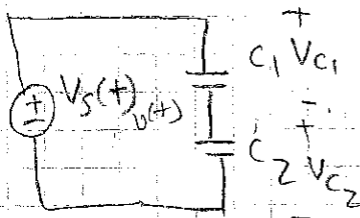


$$V_{C1} = \frac{1/C_1}{1/C_1 + 1/C_2} V_S(t)$$

$$V_{C2} = \frac{1/C_2}{1/C_1 + 1/C_2} V_S(t)$$


Vol. Div for capacitors has proportionality constant of $\frac{1}{C_1}$ or $\frac{1}{C_2}$

Voltage Division for charged capacitors

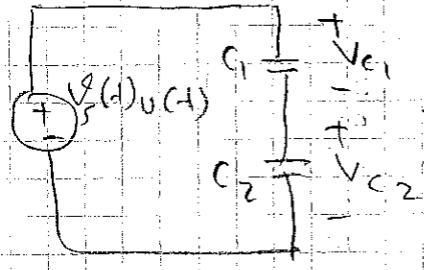


$$V_{C1}(0^-) = V_1$$

$$V_{C2}(0^-) = V_2$$

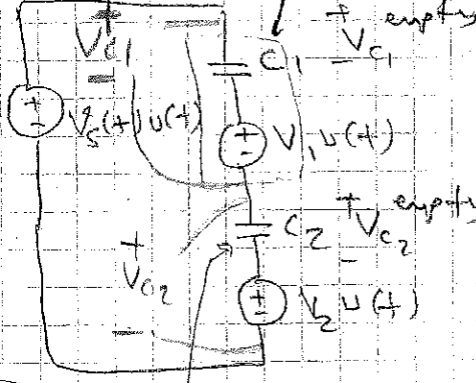

empty $V_{C1}(0^-) = 0$

empty $V_{C2}(0^-) = 0$

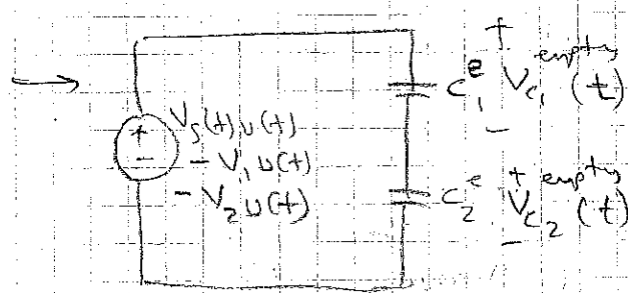

empty (not the same with initial capacitor)

$$V_{C1} = \frac{C_2}{C_1 + C_2} (V_S(t) - V_1 - V_2) u(t)$$


$$V_{C1}(t) = \left[V_1 + \frac{C_2}{C_1 + C_2} (V_S(t) - V_1 - V_2) \right] u(t)$$

$$= \left[\frac{C_2}{C_1 + C_2} (V_S - V_2) + \frac{C_1}{C_1 + C_2} V_1 \right] u(t)$$

Application of external input on capacitors and calculation of $t=0^-$ and $t=0^+$ changes in the cap circuit variables

$$V_C(t) = V_C(t_0) + \frac{1}{C} \int_{t_0}^t i_C(\tau) d\tau, \quad t > t_0$$

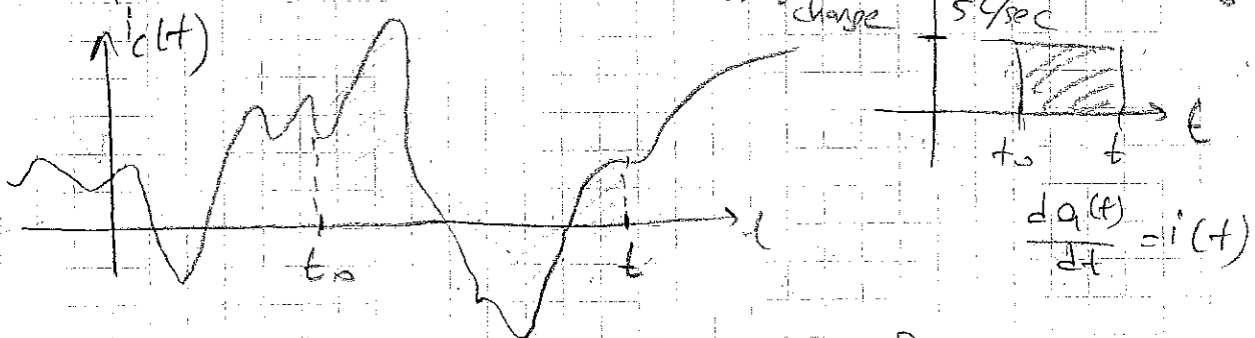total Δ of charge transferred to the capacitor between t_0 and t





Question: Is $V_C(t)$ a continuous function of t ?

$$A: V_c(t_0^+) = V_c(t_0^-) + \frac{1}{C} \int_{t_0^-}^{t_0^+} i_c(\tau) d\tau$$

($\exists M \in \mathbb{R}$)


$V_c(t_0^+) = V_c(t_0^-)$ provided that there is no impulse.

So, for bounded inputs (all inputs such that $|f(t)| < M \in \mathbb{R}$) that is for all practical inputs, we have the continuity of capacitor voltage.

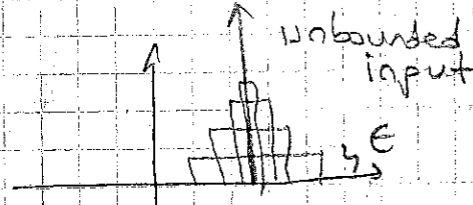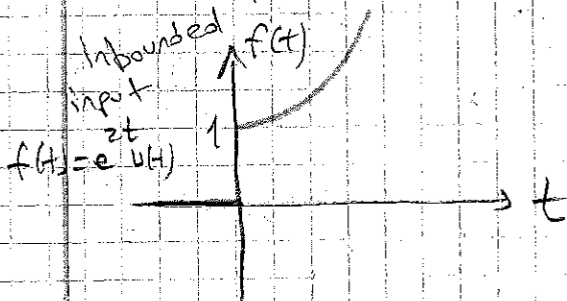



$$\delta_E(t) = \begin{cases} \frac{1}{E} & |t - t_0| < \frac{E}{2} \\ 0 & \text{otherwise} \end{cases}$$

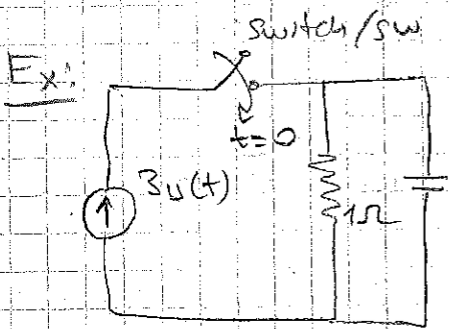and $\delta(t) \xrightarrow{E \rightarrow 0} \delta(t)$
 ↑ unbounded input




$V_c(t_0^-) = 2V$
 and sw is closed at $t=0$.
 Find $V_c(t_0^+)$ and $\dot{V}_c(t_0^+)$.
 ↑ or $V_c'(t_0^+) = \frac{dV_c(t)}{dt}$


at $t=0^-$

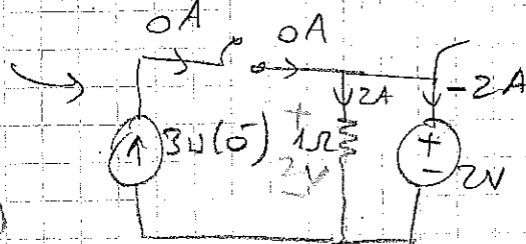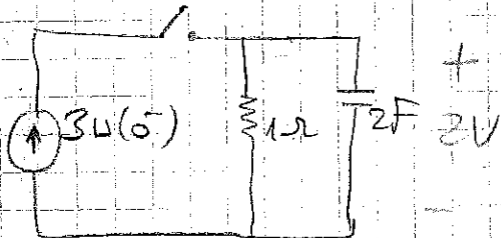


At $t=0^+$:

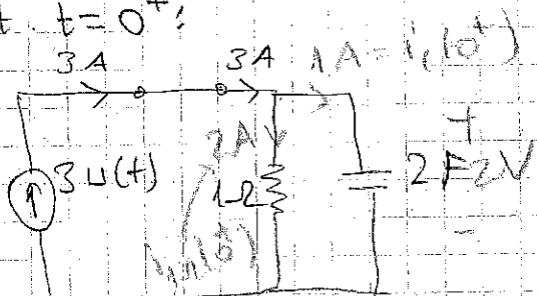

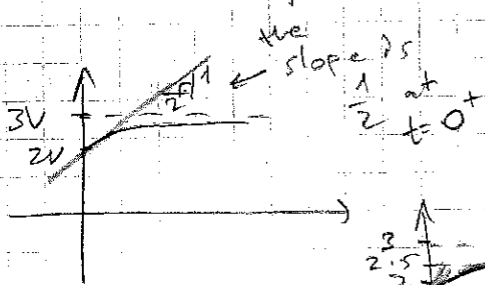Since input $3u(t)$ is bounded, $V_c(t_0^+) = V_c(t_0^-) = 2V$





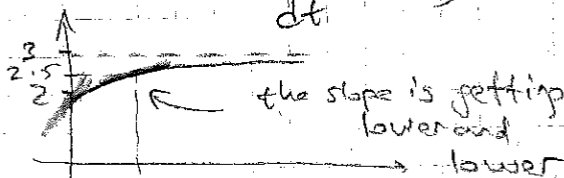$i_c(t_0^+) = 1A \rightarrow C \cdot \dot{V}_c(t_0^+) = 1A$
 $\dot{V}_c(t_0^+) = \frac{1}{2} \text{ Volts/Sec}$





2F

Ex:

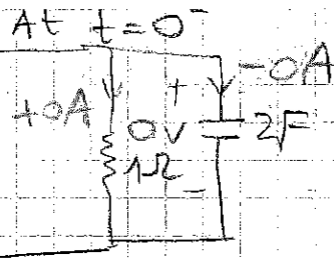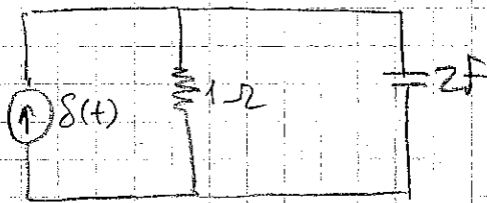


As in previous example

$V_c(0^-) = 0V$
 $0^- < t < 0^+$

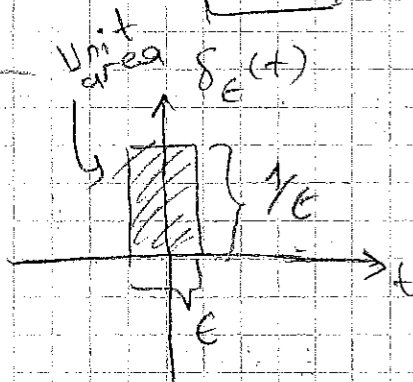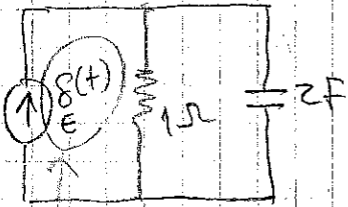

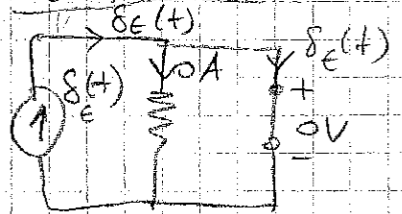During the application of $\delta_E(t)$, $V_c(t) = V(0^-) = 0V$




Bounded function approximating impulse $\delta(t)$


So, $V_c(0^+) = \frac{1}{2}$ Volts and independent of E

$i_c(t) = \delta_E(t)$, $0 < t < 0^+$
 $V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_c(\tau) d\tau$


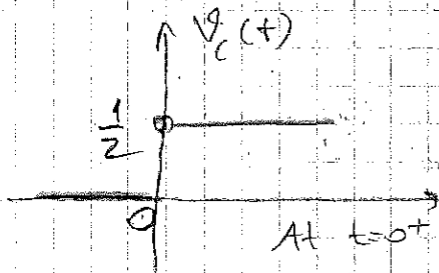
as $\delta_E(t) \rightarrow \delta(t)$, $\lim_{E \rightarrow 0} V_c(0^+) = \frac{1}{2} V$
 $= \frac{1}{2} \int_{0^-}^{0^+} \delta_E(\tau) d\tau = \frac{1}{2} \text{ Volts}$




$C V_c(0^+) = -\frac{1}{2}$

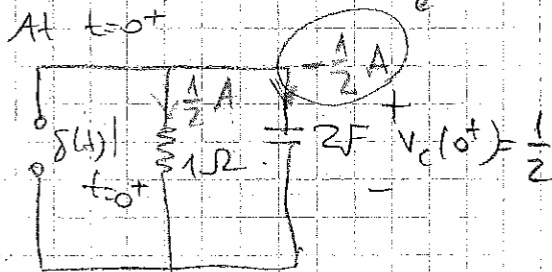

Ex:

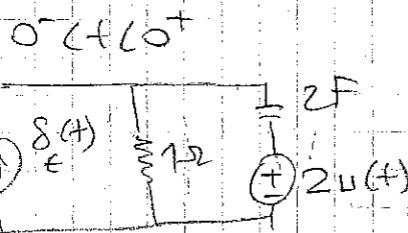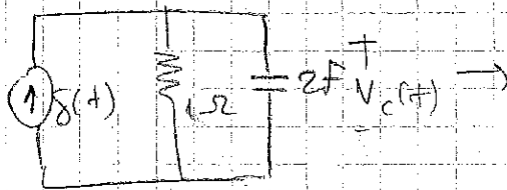

$V_c(0^-) = 2V$

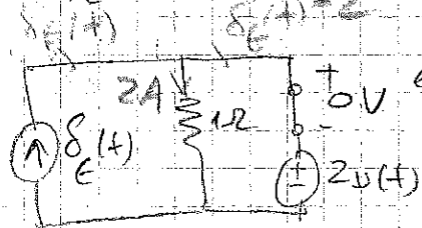

empty cap. remains at 0 Volts during $0 < t < 0^+$

$i_c(t) = \delta_E(t) - 2$, $0 < t < 0^+$

At $t=0^+$: $V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_0^-^{0^+} i_c(\tau) d\tau$

$$= 0 + \frac{1}{2} \left[\int_0^-^{0^+} \delta_c(\tau) d\tau \right] + \frac{1}{2} \int_0^-^{0^+} (-2) d\tau$$

$V_c^{empty}(0^+) = \frac{1}{2} \text{ Volts}$



$V_c(0^+) = V_c^{empty}(0^+) + 2V(t)$

$$= \frac{1}{2} + 2$$


$$= \frac{5}{2} \text{ Volts}$$

$\int_0^{0^+} f(t) dt \leq 1 \cdot \int_0^{0^+} \delta(t) dt$

$|f(t)| < 10$

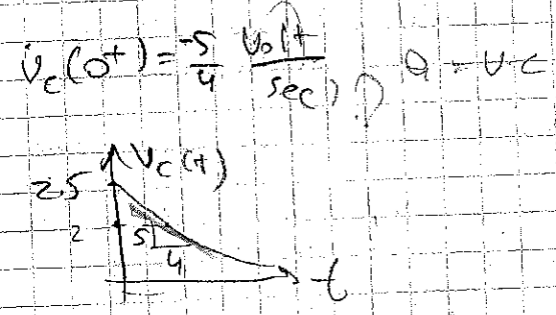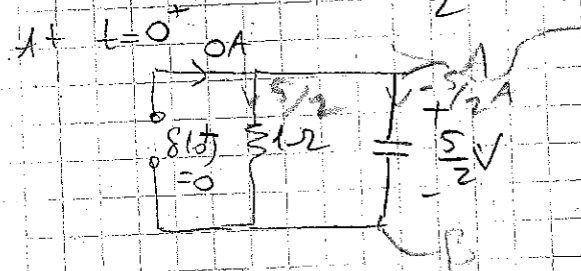


EX:



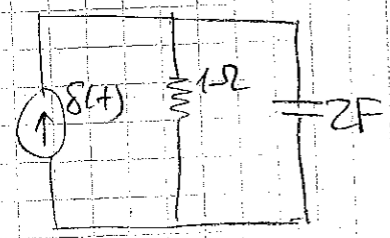


Let's use the following I.C. Model for Capa.:

$V_c(0^-) = 2V$

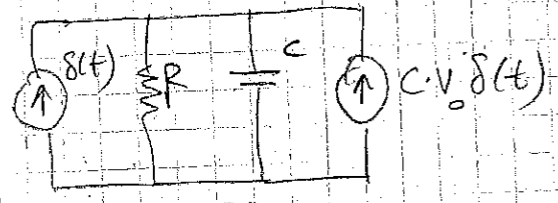


$0^- < t < 0^+$

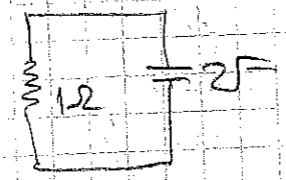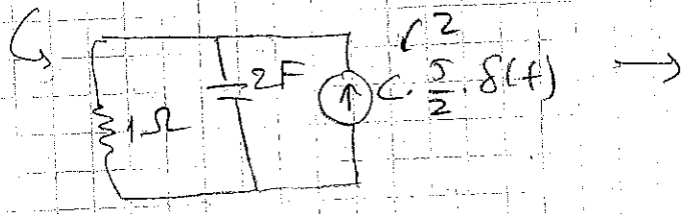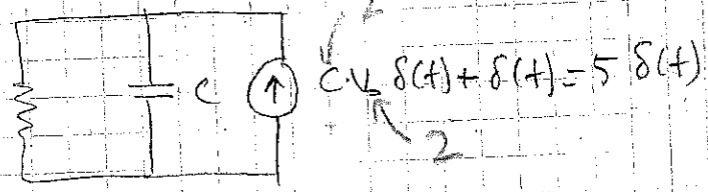

$V_c(0^+) = \frac{5}{2} \text{ Volts}$

Cuma 17:30 EE201


Ele ders var Ayri yerde

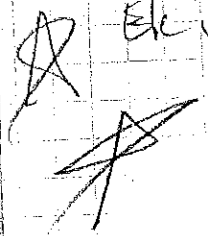

Reviews $\rightarrow t = t_{ini} + \epsilon$

$$v_L(t) = v_L(t_{ini}) + \frac{1}{L} \int_{t_{ini}}^t i_L(\tau) d\tau$$

Inductors

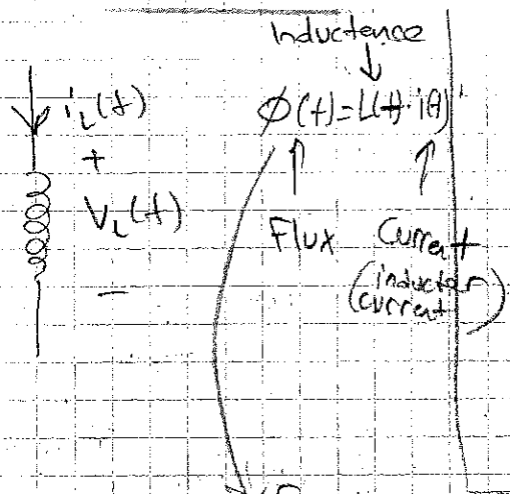

The area of this line is zero (unless there is impulse)
 For bounded currents, $v_L(t)$ is continuous.

Faraday's Law (for $i_L(t)$)

$$v_L(t) = \frac{d}{dt} \{ L(t) I_L(t) \}$$


LTI Inductor

$L(t) = L \leftarrow$ constant

$\phi(t) = L I_L(t)$

$$v_L(t) = L \frac{di_L(t)}{dt}$$

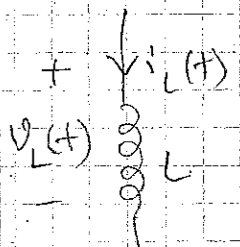$\phi = L \cdot i$
 $Q = C \cdot V$
 duals of each other.



$v_L(t) = L \frac{di_L(t)}{dt} \leftarrow$ differential form

$i_L(t) = i_L(0^-) + \frac{1}{L} \int_0^t v_L(\tau) d\tau \leftarrow$ integral form

By duality, we can immediately say that $i_L(t)$ is a continuous function provided that $v_L(t)$ does not contain impulse or $v_L(t)$ is bounded.


To remember the continuity of variables you may recall that


$E_{cap}(t) = \frac{1}{2} C v_C^2(t)$

$E_L(t) = \frac{1}{2} L I_L^2(t)$




Energy function of the dynamic component is continuous if there is no impulse!

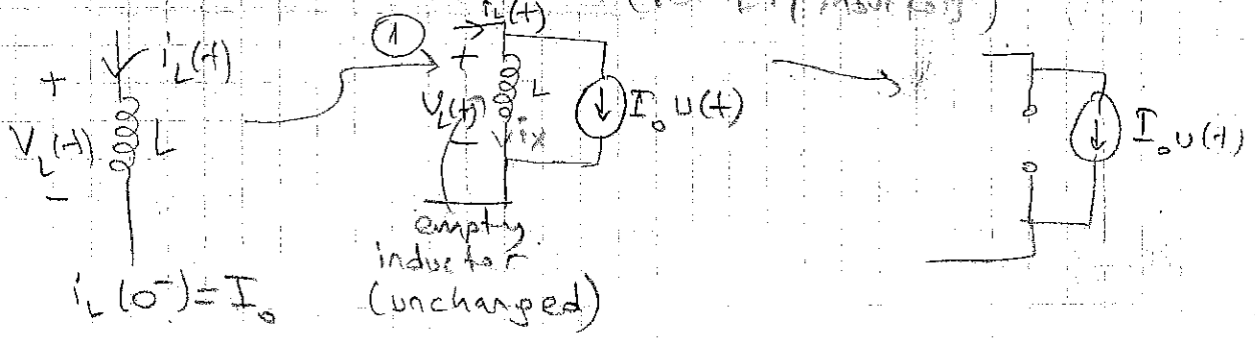Initial condition Models (For LTI inductors)




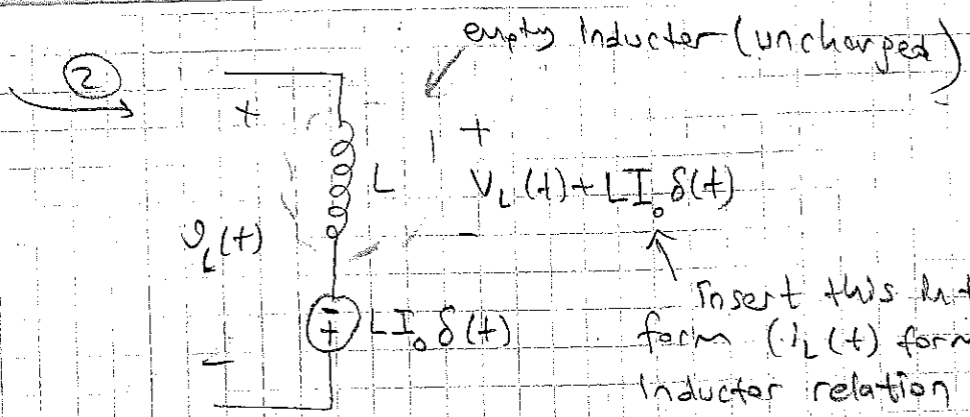

Series and Parallel Combination of Inductors

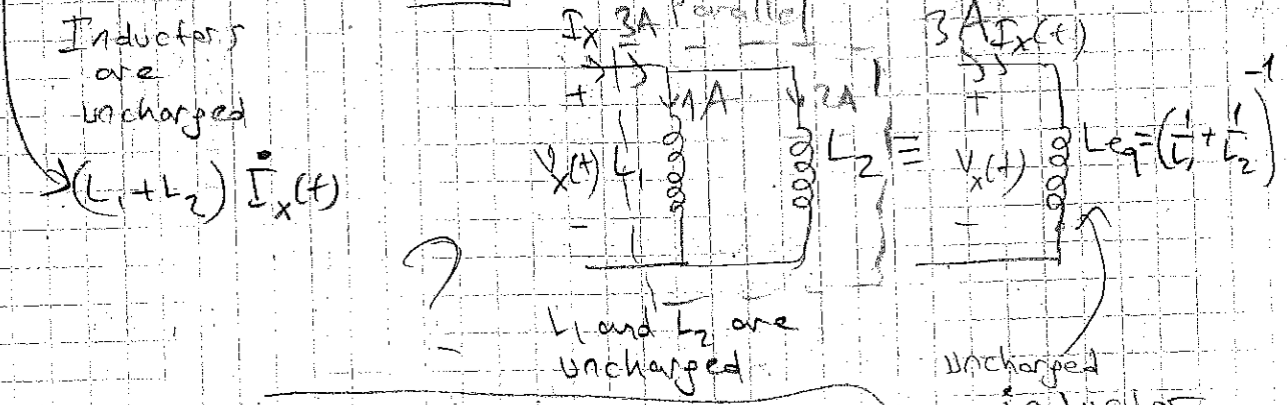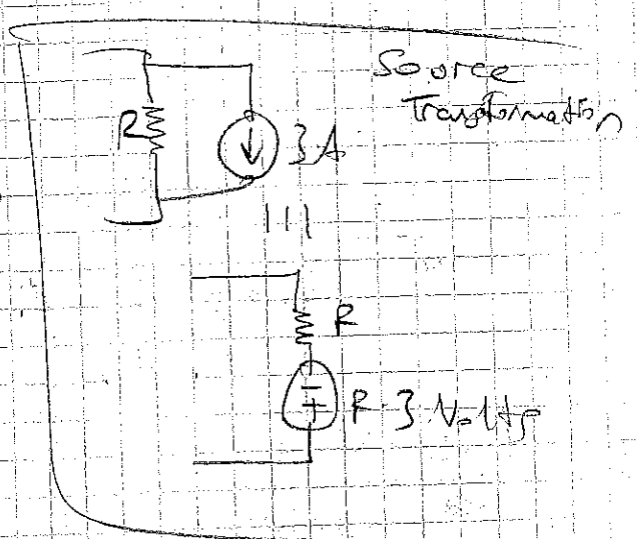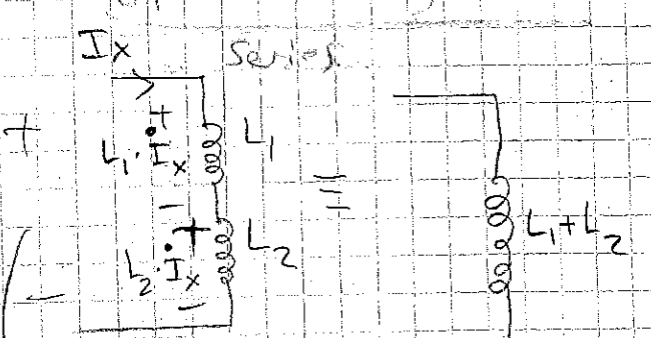



Ex1

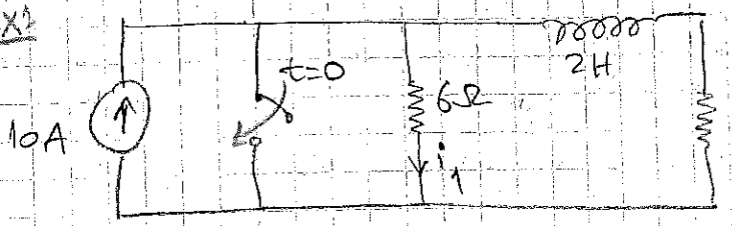

$i_L(0^-) = 2A$

Find $i_L(t^+), i_L(t^-)$

$\frac{d}{dt} i_L(t) \Big|_{t=0^+}$

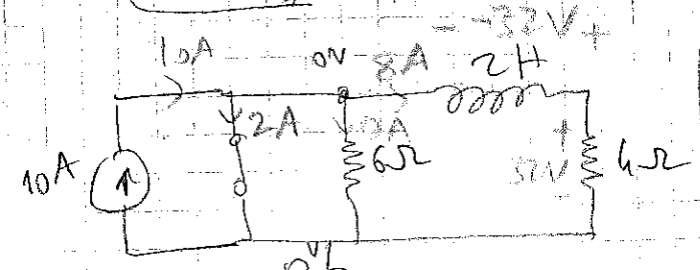
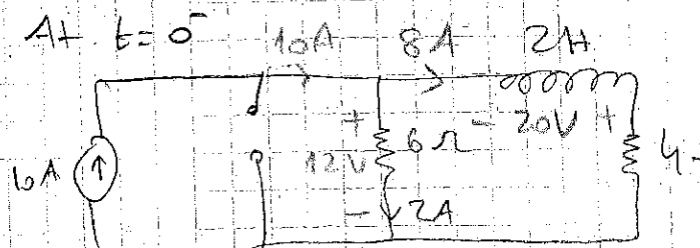


$i_L(t^+) = i_L(t^-) = 8A$
(there are no impulses)



$i_1(t^+) = 0A$

$$V_L(0^+) = L \frac{dI_L(0^+)}{dt} \rightarrow \frac{dI_L(t)}{dt} \Big|_{t=0^+} = -16 \text{ A/sec}$$


EX 4

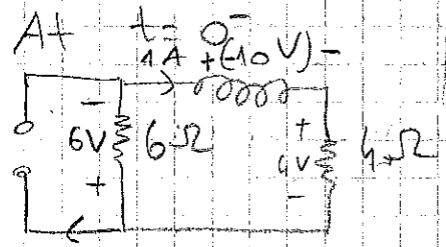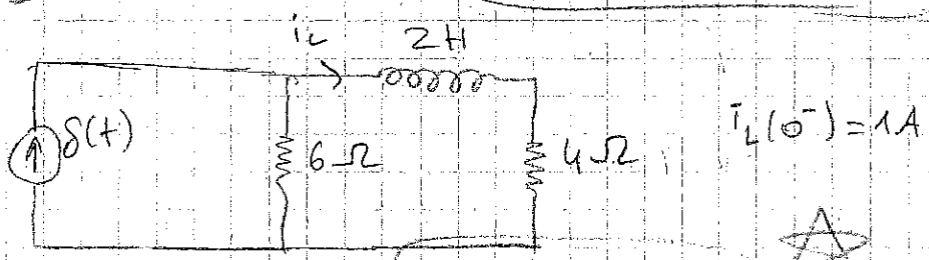

substitution theorem

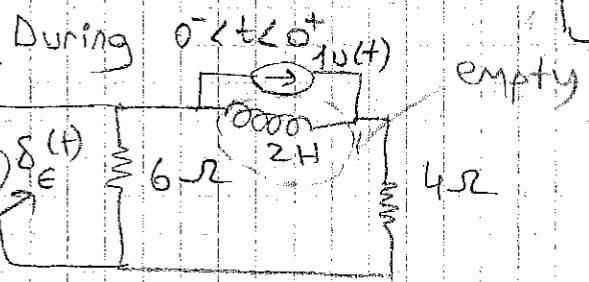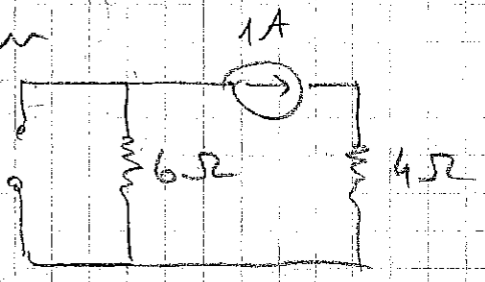


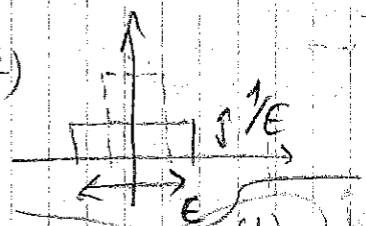Approximation to impulse (not impulse itself)



Since input $\delta_E(t)$ is bounded (not an impulse)
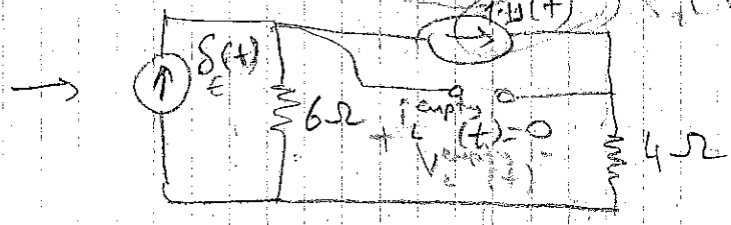
$$i_L^{empty}(t) = 0, \quad 0 < t < 0^+$$



$$V_L^{empty}(t) = 6\delta_E(t) + \dots 1u(t)$$

At $t = 0^+$

$$i_L^{empty}(0^+) = i_L^{empty}(0^-) + \frac{1}{L} \int_{0^-}^{0^+} V_L(\tau) d\tau$$


$$= 0 + \frac{1}{2} \int_{0^-}^{0^+} (6\delta_E(\tau) + \dots 1u(\tau)) d\tau$$

$$= 0 + \frac{1}{2} \cdot 6 \int_{0^-}^{0^+} \delta_E(\tau) d\tau + \frac{1}{2} \int_{0^-}^{0^+} 1 d\tau$$

$$i_L^{empty}(0^+) = 3A$$

Dirac!
 $\delta(t)$
 ↑
 Dirac-Pelta function

At $t=0^+$ $i_L^{exp}(0^+) = 3A$

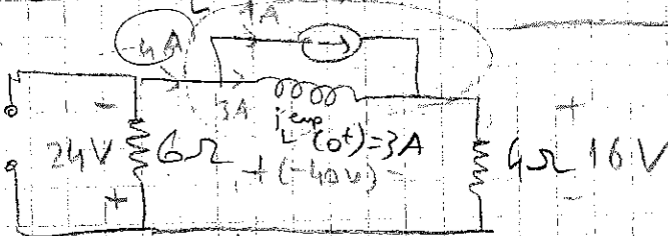


original
charged
inductor

changed inductor current:
 $i_L(0^+) = i_L(0^-) + 3A = 4A$
 1A


Inductors and capacitors are all passive elements. They are energy storage elements.

Ex 1

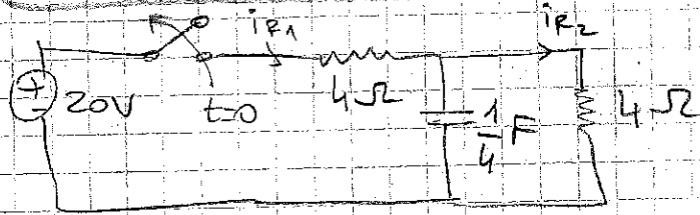


$i_{R_2}(0^-) = 2A$
 Find $q(0^-), q(0^+)$
 $i_{R_2}(0^-), i_{R_1}(0^+)$
 $i_C(0^-), i_C(0^+)$
 $V_C(0^-), V_C(0^+)$

At $t=0^-$

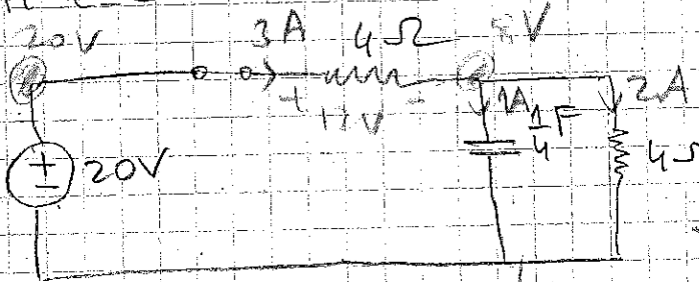


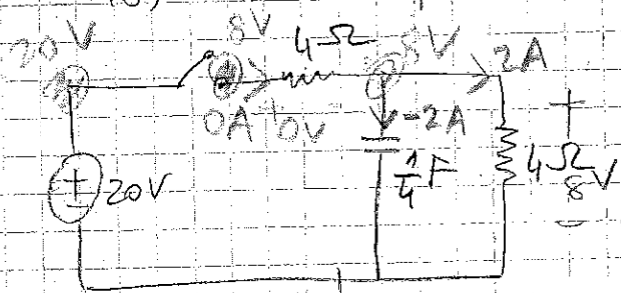$q(0^-) = C V_C(0^-) = \frac{1}{4} \cdot 8 = 2C$ $i_{R_1}(0^-) = 3A$ $i_{R_1}(0^+) = 0A$
 $q(0^+) = 2C$



$i_C(0^-) = 1A$ $i_C(0^+) = -2A$
 $V_C(0^-) = 8V$ $V_C(0^+) = 8V$
 $V_C(0^+) = V_C(0^-) = 8V$

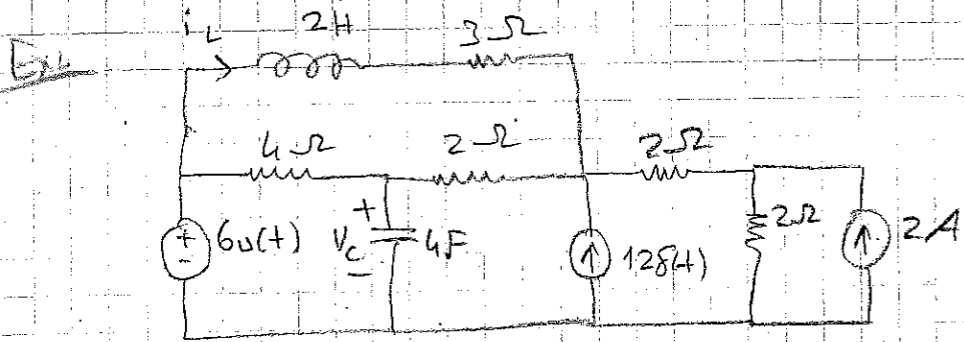$C \dot{V}_C(0^+) = i_C(0^+) = -2A \rightarrow \dot{V}_C(0^+) = \frac{-2}{\frac{1}{4}} = -8 \frac{V}{sec}$



$V_C(0^-) = 10V$
 $I_L(0^-) = 5A$
 Find $V_C(0^+), I_L(0^+)$

If we do not have any impulsive sources, then $V_C(t)$ and $I_L(t)$ should be continuous func. of time, (provided that there's no pathological switching).

$$V_C(0^+) = V_C(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_C(\tau) d\tau$$


$$I_L(0^+) = I_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} V_L(\tau) d\tau$$

Question is then finding the jump in $V_C(t)$ and $I_L(t)$ at $t=0$ due to the impulsive source.

During the application of impulse (Cap: short circuit, Ind: open circuit)

$$0^- < t < 0^+$$

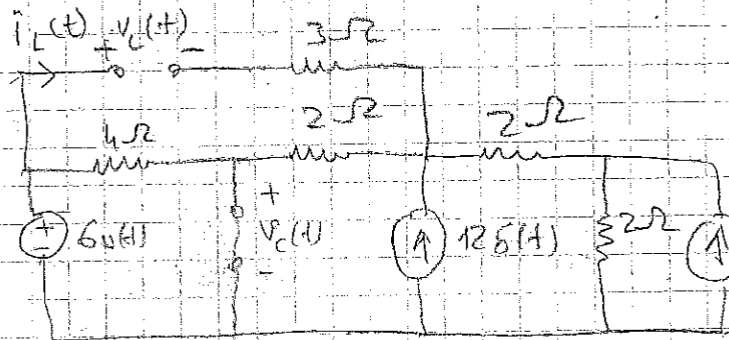
Note! This circuit has no D.C. associated, the goal is to find the voltage/current jump.



$i_C(t) = ?$
 $V_L(t) = ?$
 $0^- < t < 0^+$

$$i_C(t) = \frac{1}{6} ? \quad i_{s_1}(t) + \dots + i_{s_2}(t) + \dots + i_{s_3}(t)$$

by superposition

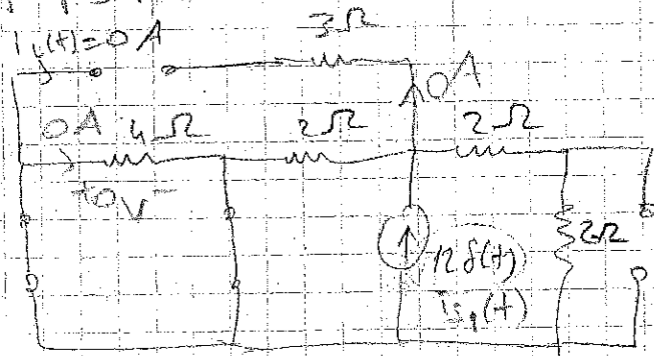

$$i_C(t) = 8\delta(t) + A \cdot 2 + B \cdot 6u(t)$$

$$\begin{aligned}
 V_C(0^+) &= V_C(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_C(\tau) d\tau \\
 &= 10 + \frac{1}{4} \int_{0^-}^{0^+} [8\delta(\tau) + A \cdot 2 + B \cdot 6u(\tau)] d\tau \\
 &= 10 + \frac{1}{4} \int_{0^-}^{0^+} 8\delta(\tau) d\tau \\
 &= 12 \text{ Volts}
 \end{aligned}$$

$$I_L(0^+) = ?$$

$$I_L(0^+) = I_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} V_L(\tau) d\tau$$

$$V_L(t) = \dots + i_{s_1}(t) + \dots + i_{s_2}(t) + \dots + i_{s_3}(t)$$

$$V_L(t) = -2i_L(t) = -16\delta(t) + \dots i_{s2}(t) + \dots i_{s3}(t)$$

important component


not important
(they will be integrated from 0 to 0+)

$$I_L(0^+) = 5 + \frac{1}{2} \int_{0^-}^{0^+} (-16\delta(\tau) + \dots) d\tau$$

$$= -3A$$

On Pathological Switching

Capacitor Case

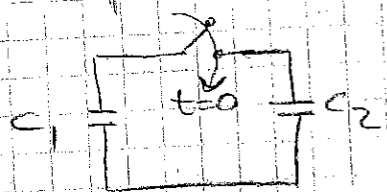

At $t=0^-$


$$V_{C1}(0^-) = V_1$$

$$V_{C2}(0^-) = V_2$$

Find $V_{C1}(0^+)$ and $V_{C2}(0^+)$



$$V_{C1}(0^-) =$$

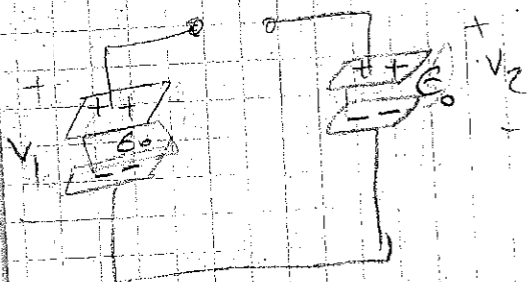

$$Q_{total}(0^-) = C_1 V_1(0^-) + C_2 V_2(0^-)$$

$$= C_1 V_1 + C_2 V_2 \quad (I)$$

total charge

(I) = (II) by claim

At $t=0^+$



$$V_1(0^+) = V_2(0^+) = V_{com}$$

= common voltage

claim: $Q_{before}^{total} = Q_{after}^{total}$

$$Q_{total}(0^+) = C_1 V_1(0^+) + C_2 V_2(0^+)$$



$$= (C_1 + C_2) V_{com} \quad (II)$$

$$C_1 V_1 + C_2 V_2 = (C_1 + C_2) V_{com}$$

$$V_{com} = \frac{C_1}{C_1 + C_2} V_1 + \frac{C_2}{C_1 + C_2} V_2$$

$$V_{C1}(0^+) = V_{C2}(0^+) = V_{com}$$

EX1

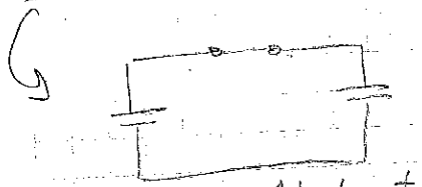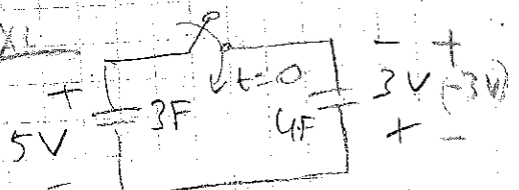

$$Q_{before} = 5 \cdot 3 + 4(-3)$$

$$= 3C$$


$$Q_{after} = 3C \quad V_{com} = \frac{Q_{after}}{C_1 + C_2}$$

2 sources of jumps in current/voltage


→ impulsive source
→ pathological switch

First order Circuits

RC circuit

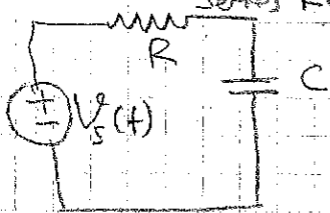


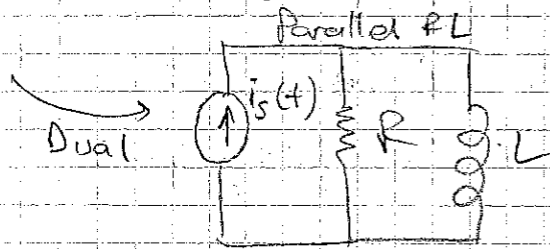$V_c(0^-) = V_0$ Find $V_c(t) \ t \geq 0$



$I_L(0^-) = I_0$
Find $I_L(t) \ t \geq 0$

Series RC

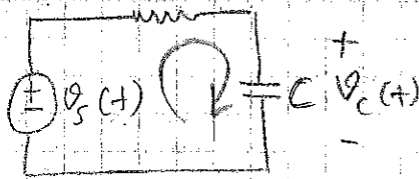

$V_c(0^-) = V_0$

KVL $-V_s(t) + V_R(t) + V_c(t) = 0, \ t \geq 0$

$V_R = i_c R$
 $i_c(t) = C \frac{dV_c(t)}{dt}$
 $= C \dot{V}_c(t)$

$-V_s(t) + R \cdot i_c(t) + V_c(t) = 0$
 $C \dot{V}_c(t)$

$RC \dot{V}_c(t) + V_c(t) = V_s(t)$

$(D + \frac{1}{RC}) V_c(t) = \frac{1}{RC} V_s(t), \ t \geq 0$

$V_c(0^-) = V_0$


1st Order Constant Coefficient Differential Equation (CCDE or ODE)

Ordinary (Not partial)

$D \triangleq \frac{d}{dt}$

Solutions

Differential Equation

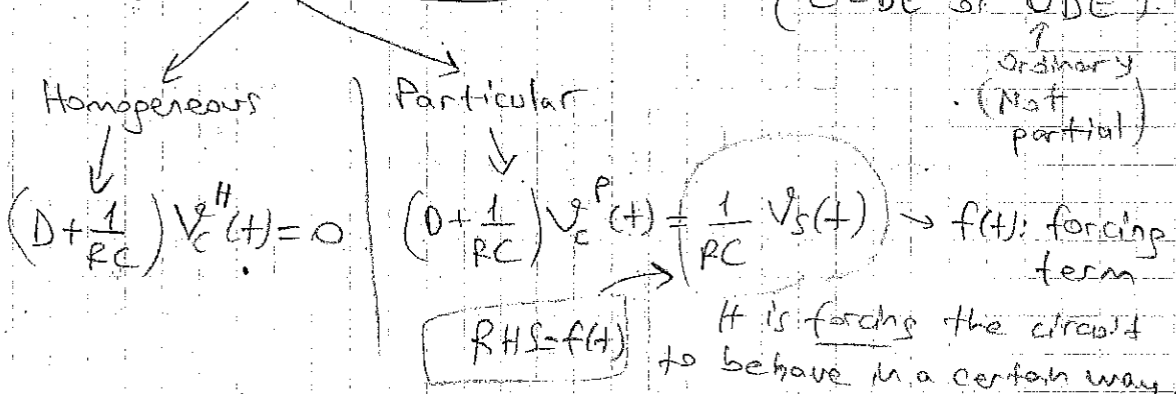

Case 1: $V_s(t) = u(t)$

$(D + \frac{1}{RC}) V_c(t) = \frac{1}{RC} u(t)$

(I) $(D + \frac{1}{RC}) V_c^H(t) = 0$ (II) $(D + \frac{1}{RC}) V_c^P(t) = \frac{1}{RC} u(t), \ t \geq 0$
 $= \frac{1}{RC}$

Guess:

$$V_c^H(t) = A e^{\lambda t}$$

Insert the "guess" into (I)

$$A \left(\lambda + \frac{1}{RC} \right) e^{\lambda t} = 0, t > 0$$

$$\rightarrow A \left(\lambda + \frac{1}{RC} \right) = 0$$

$A = 0 \rightarrow V_c^H(t) = A e^{\lambda t} = 0$
 ↳ trivial solution

$\lambda = -\frac{1}{RC} \rightarrow$ non-trivial solution

$$V_c^H(t) = A e^{-\frac{1}{RC} t}, t \geq 0$$

(for homogeneous solution)

$$\left(D + \frac{1}{RC} \right) V_c^P(t) = \frac{1}{RC}, t > 0$$

Guess:

$$V_c^P(t) = K$$

insert

$$\frac{K}{RC} = \frac{1}{RC}, t \geq 0$$

$$K = 1$$

$$V_c^P(t) = 1$$


$$V_c^{\text{complete}}(t) = V_c^H(t) + V_c^P(t) = (A e^{-\frac{1}{RC} t} + 1), t \geq 0$$

$$V_c(0^-) = V_0 \rightarrow V_c(0^+) = V_0$$


$$V_c^{\text{comp}}(t) \Big|_{t=0^+} = A + 1 = V_c(0^-) = V_c(0^+) = V_0 \rightarrow A = V_0 - 1$$

$$V_c^{\text{comp}}(t) = (V_0 - 1) e^{-\frac{t}{RC}} + 1, t \geq 0$$

$$V_0 = -2$$

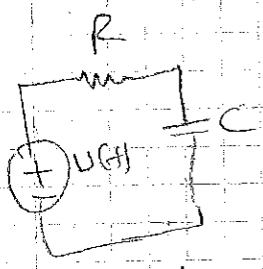


$$V_c(0^-) = V_0$$

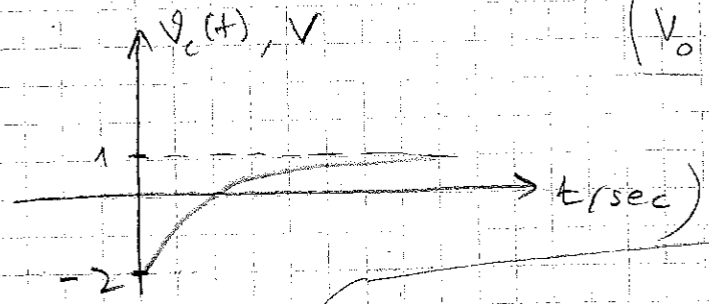

Case (2)

$$V_c(t) = r(t)$$

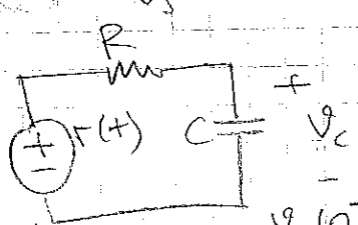


$$V_c(0^-) = V_0$$

$$\left(D + \frac{1}{RC} \right) V_c(t) = \frac{1}{RC} V_s(t) = \frac{1}{RC} t$$

$$V_c(0^-) = V_0$$

t=0(t)

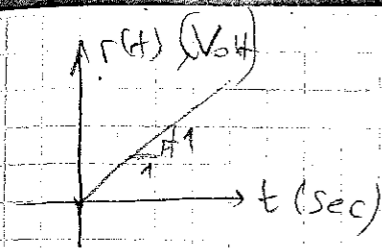

$$(D + \frac{1}{RC}) V_c(t) = \frac{1}{RC} t, t > 0$$

$$V_c(0^-) = V_0$$

homogeneous

$$V_c^H(t) = A \cdot e^{-\frac{1}{RC}t} \quad (I)$$

particular

$$(D + \frac{1}{RC}) V_c^P(t) = \frac{1}{RC} t \quad (II)$$

insert into (II)

$$\frac{k}{RC} + \frac{Lt}{RC} + L = \frac{t}{RC} + 0$$

Guess: $V_c^P(t) = k + Lt$

$$L = 1$$

$$\frac{k}{RC} + L = 0$$

$$\frac{k}{RC} = -L = -1$$

$$k = -RC$$


$$V_c^{comp}(t) = A e^{-\frac{1}{RC}t} - RC + t, t > 0$$

Select A to meet I.C. at $t = 0^+$

$$V_c(0^-) = V_c(0^+) = V_0 \rightarrow A = RC + V_0$$


$$V_c^P(t) = -RC + t$$
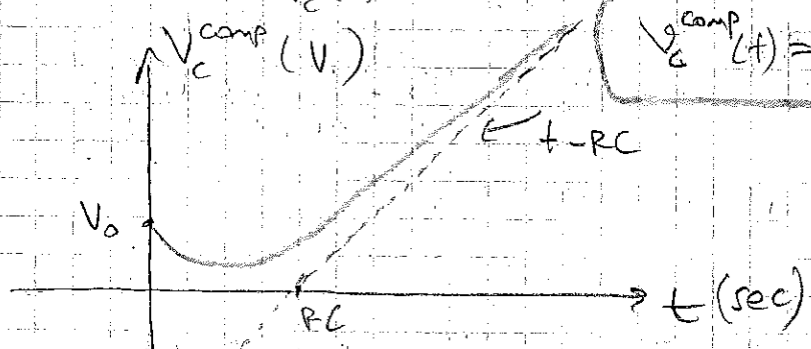
$$V_c^{comp}(t) = (RC + V_0) e^{-\frac{1}{RC}t} - RC + t, t > 0$$



Sol. of Dif. Eqn. for ramp input, meeting the I.C. at $t = 0^+$

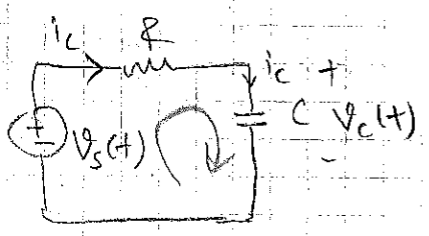1st Order Circuits with DC input (recall)



$$i_c = C \frac{dv_c(t)}{dt} \quad (= C \frac{dv_c(t)}{dt})$$

KVL: $-v_s(t) + R i_c + v_c = 0$

$$(D + \frac{1}{RC}) v_c(t) = \frac{v_s(t)}{RC}$$

$$D = \frac{d}{dt}$$

$$v_c(0^-) = V_0$$


Soln: $v_c(t) = v_c^H(t) + v_c^P(t)$

homogeneous particular

General form of the solution: $v_c(t) = A e^{-\frac{1}{RC}t} + v_c^P(t)$

Case of DC input

$$V_s(t) = V_s u(t)$$

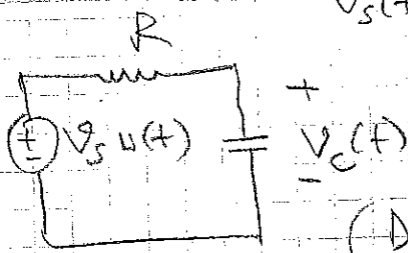

Homogeneous

$$\left(D + \frac{1}{RC}\right) V_c^h(t) = 0 \quad (1) \quad t > 0$$

Guess $V_c^h(t) = A \cdot e^{\lambda t}$ → insert into (1)

$$\rightarrow A \left(\lambda + \frac{1}{RC}\right) e^{\lambda t} = 0, \quad t > 0$$

$$A \left(\lambda + \frac{1}{RC}\right) = 0$$

$$A = 0$$

$$V_c^h(t) = 0$$

trivial soln.

$$A \neq 0, \quad \lambda = -\frac{1}{RC}$$

$$V_c^h(t) = A \cdot e^{-\frac{1}{RC} t}$$

non-trivial soln.

$$\begin{aligned} \text{complete } V_c(t) &= V_c^h + V_c^p \\ &= A \cdot e^{-\frac{1}{RC} t} + V_s, \quad t > 0 \end{aligned}$$


$$V_c^{\text{comp}}(0^+) = V_c^{\text{comp}}(0^-) = V_0 \rightarrow \left(\text{There is no impulsive current at } t=0 \right)$$

Continuity of Capacitor Voltage

$$V_c^{\text{comp}}(0^+) = A + V_s \rightarrow A = V_0 - V_s$$

$$V_c(0^-) = V_0$$

$$V_c^{\text{comp}}(t) \text{ (Volts)}$$

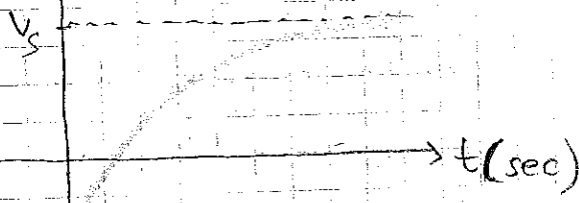

$$V_c^{\text{comp}}(t) = V_s + (V_0 - V_s) e^{-\frac{t}{RC}}, \quad t > 0$$

$t > 0$ is also true since the capacitor voltage is continuous.

The solution for DC input can also be expressed as:


$$V_c(t) = V_c^{\text{final}} + \left(V_c^{\text{initial}} - V_c^{\text{final}} \right) e^{-(t-t_{\text{initial}})/\tau}, \quad t > t_{\text{initial}}$$

↑
General formula for first order circuits with DC-input


In our example,

$$\left. \begin{aligned} t_{\text{initial}} &= 0 \\ V_c^{\text{initial}} &= V_c(0^-) = V_0 \\ V_c^{\text{final}} &= V_c(\infty) = V_s \\ \tau &= RC \end{aligned} \right\}$$

Ex:

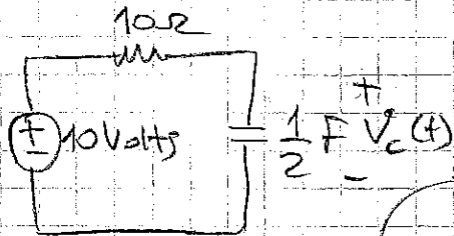

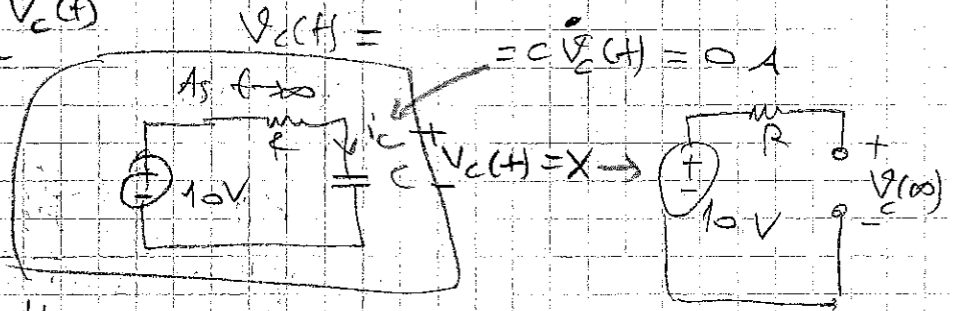$V_c(\pi^-) = 3 \text{ Volts}$. Find $V_c(t)$, $t \geq \pi$




$V_c(\pi^-) = 3 \text{ Volts}$

$$V_c(t) = 10 - 7e^{-(t-\pi)/5}, t \geq \pi$$

$V_c(\infty) = 10V$

Time constant of 1st order circuits describe how fast the circuit behaves or "reaches" the steady-state value.

$\tau = R \cdot C = 5 \text{ sec}$

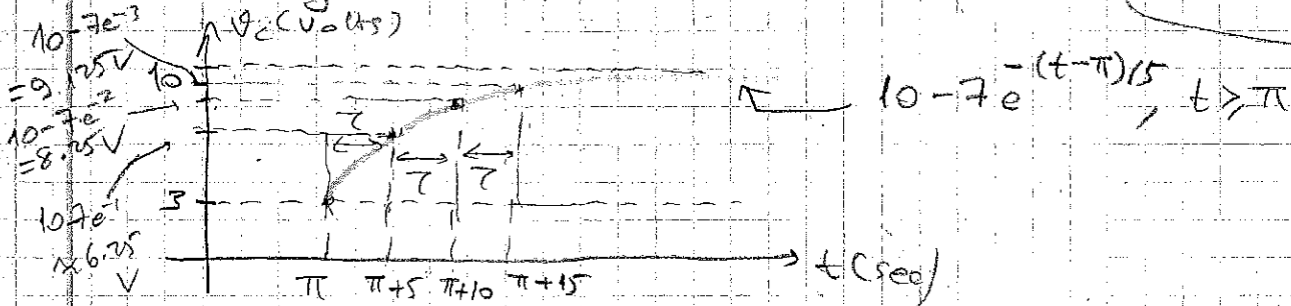

$\tau = 5 \text{ sec}$


Bad approximation $e \approx 2$

In practice, we take 3-5 time constants ($3\tau - 5\tau$) as the sufficient time to "reach" the final cap. state.

For this example, the time to reach steady state.

For $3\tau = 15 \text{ sec}$

$5\tau = 25 \text{ sec}$

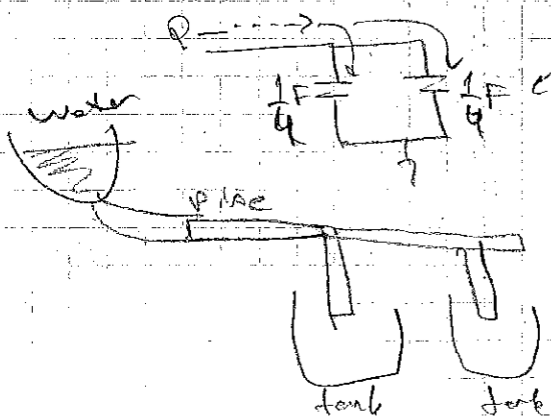

Takes longer than only 1 $\frac{1}{4} \text{ F}$ capacitor

Google

$\gg 1k\Omega \times 10\mu\text{F}$
10msec


$\gg 10\tau$ in US dollar
31 dollars...

$Q = C \cdot V$


$$Z = R(C) \rightarrow \frac{\text{Charge}}{\text{Voltage}} = \frac{Q}{V} = \frac{C \cdot V}{V} = C$$

$$\frac{V}{t} = \frac{Q}{t} = I$$

$\frac{V}{I} = R$
Current

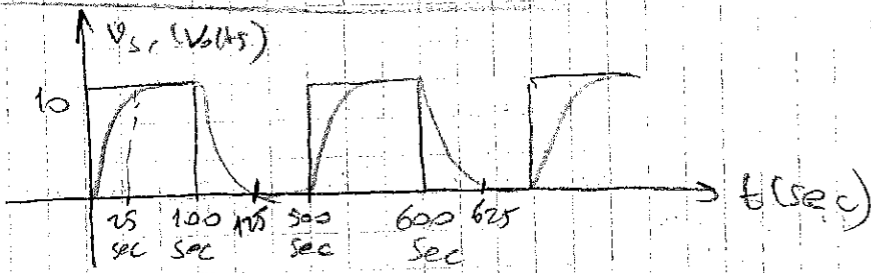


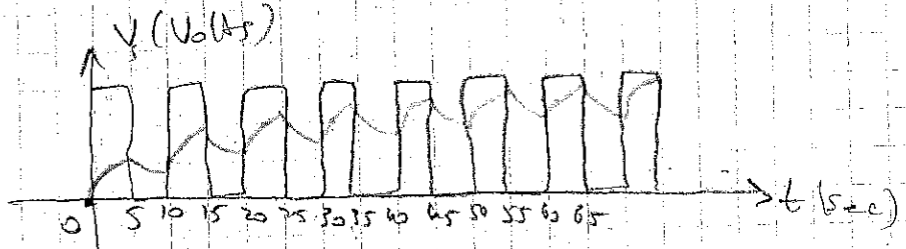$5\tau = 25 \text{ sec}$
 $V_c(0^-) = 0V$



Transient and Steady-State Part of the Solution

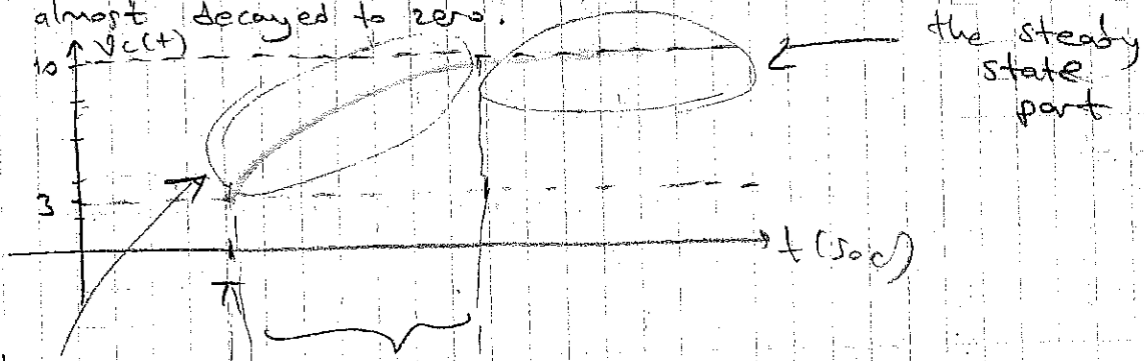Roughly the steady-state solution is the solution for which the components in the solution due to the initial conditions have almost decayed to zero.





the transient part $5\tau = 25 \text{ sec}$ ($\tau = 5 \text{ sec}$)

transient = in transient

(the part which is the segment of the solution that is dominated by the initial conditions)

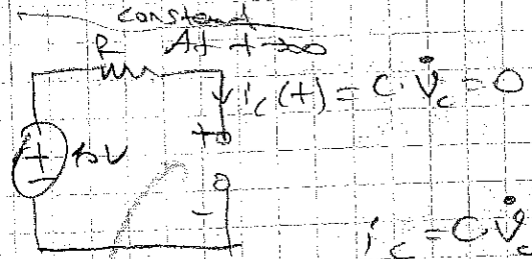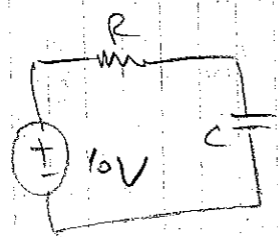Summary: Under DC input, the final value of the capacitor is found by setting $V_c(t) = \frac{K}{s}$ and this leads to:





$i_c = C \frac{dV_c}{dt} = C \frac{d}{dt} \{K\} = 0$

$V_c(\infty) = 10V$

i.e. Cap. is open circuited for DC input as $t \rightarrow \infty$

Similarly, for an inductor:

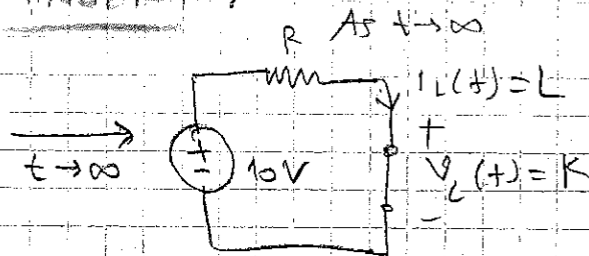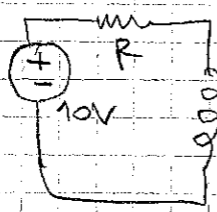

$$V_L(t) = L \frac{di_L(t)}{dt}$$


constant
= 0

$$i_L(\infty) = \frac{10}{R} \text{ A}$$

constant

i.e., inductor is short circuited (since $V_L(t) = L \frac{di_L(t)}{dt} = 0 \text{ V}$) for DC inputs as $t \rightarrow \infty$

EX:

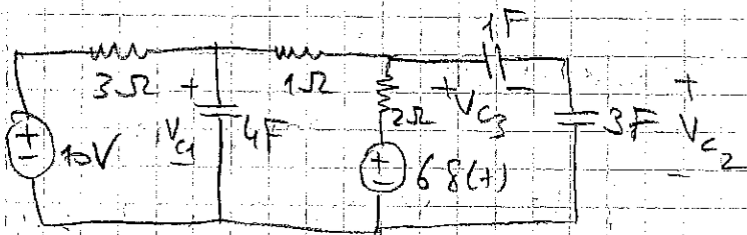

$$V_{c1}(0^-) = -2 \text{ V}$$


$$V_{c2}(0^-) = 4 \text{ V}$$

$$V_{c3}(0^-) = 3 \text{ V}$$

a) Find $V_{c1}(0^+)$, $V_{c2}(0^+)$, $V_{c3}(0^+)$.


$$0^- < t < 0^+$$

turn this off

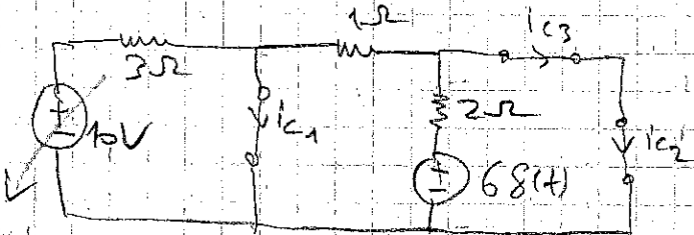

$$i_{c1}(t) = 0.8(t) + \dots$$

$$i_{c2}(t) = 3.8(t) + \dots$$

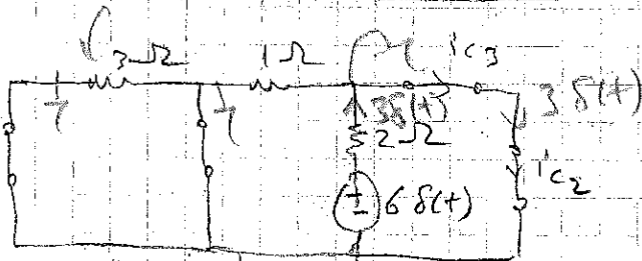

$$V_{c_k}(0^+) = V_{c_k}(0^-) + \frac{1}{C_k} \int_{0^-}^{0^+} i_{c_k}(\tau) d\tau, \quad k = \{1, 2, 3\}$$

$$V_{c1}(0^+) = V_{c1}(0^-) = -2 \text{ V}$$

$$V_{c2}(0^+) = 4 + 3 \cdot \frac{1}{3} = 5 \text{ V}$$

$$V_{c3}(0^+) = 3 + 3 \cdot 1 = 6 \text{ V}$$

b) Find $V_{c1}(\infty)$, $V_{c2}(\infty)$, $V_{c3}(\infty)$.

$$Q = C \cdot V$$

$$\frac{15}{6} = \frac{6}{6}$$

$$V_x = 2 \cdot 1 = \frac{10}{3} \text{ V}$$


$$V_{c1}(\infty) = 3 \cdot 1 = 3 \text{ V}$$

$$V_{c2}(\infty) + V_{c3}(\infty) = V_x$$

$$V_{c2}(\infty) = \frac{V_x}{2}$$


$$\frac{V_{c2} + 1}{3} = \frac{V_x}{6}$$
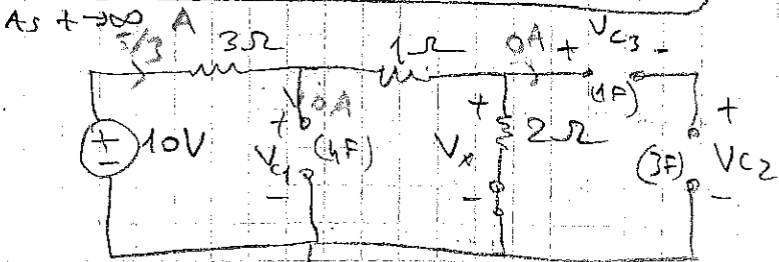
$$V_{c3}(\infty) = \frac{1}{2} V_x = \frac{15}{2} \text{ V}$$




Voltage Division for Capacitors

★ Number of dynamic components = The order of circuit.

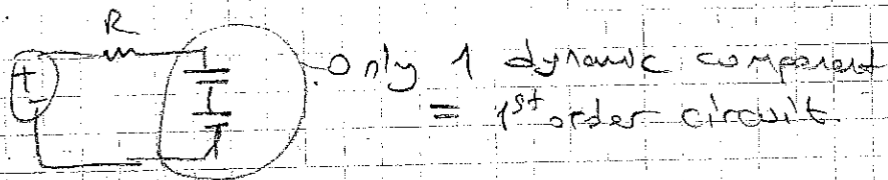

Ex 2

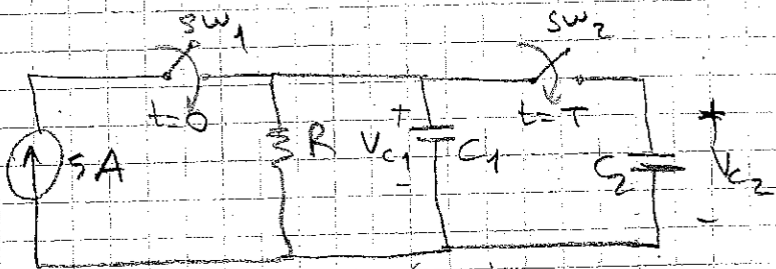

At $t=0$, SW_1 closes

At $t=T$, SW_2 closes

$$T = (RC) \ln 3$$

Find $V_{C1}(t)$ and $V_{C2}(t)$.


$$V_{C1}(0^-) = 2R$$

$$V_{C2}(0^-) = 6R$$

$$V_{Ck}(0^+) = V_{Ck}(0^-) \quad k = \{1, 2\}$$

Since no impulsive current or pathological switching.

$$0 \leq t < T$$

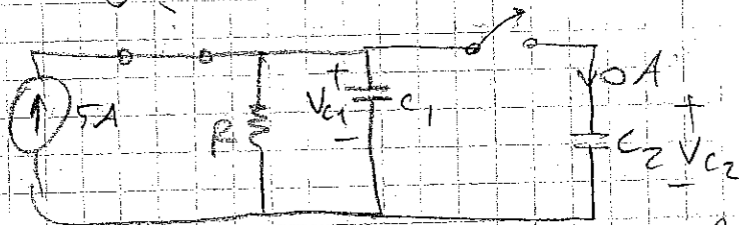

$$V_{C1}(0^+) = 2R$$

$$V_{C2}(0^+) = 6R$$

$$V_{C1}(t) = V_{C1}(\infty) + (V_{C1}(0^+) - V_{C1}(\infty)) e^{-(t-t_0)/\tau}$$

$$= 5R + (2R - 5R) e^{-t/\tau}$$

$$= 5R - 3R e^{-t/\tau}, \quad (\tau = RC_1)$$

$$V_{C2}(t) = V_{C2}(0^+) + \frac{1}{C_2} \int_0^t i_{C2}(t) dt = 6R \text{ Volts}$$

$$V_{C1}(T^-) = 5R - 3R e^{-T/\tau} = 5R - 3R e^{-\ln 3} = 4R$$

$$T^- < t < T^+$$

When SW_2 closes, two capacitors are put in parallel and they have different voltages.

$$V_{C1}(T^-) = 4R$$

$$V_{C2}(T^-) = 6R$$


$Q_{\text{before}} = Q_{\text{after}}$

$$C_1 V_{C1}(T^-) + C_2 V_{C2}(T^-) = (C_1 + C_2) V_{\text{com}}(T^+)$$

$$\frac{C_1 4R + C_2 6R}{C_1 + C_2} = V_{\text{com}}(T^+)$$


$$t > T$$
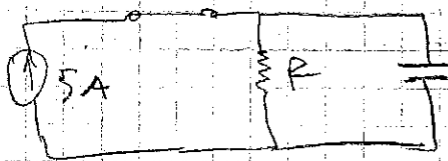
$$V_{C1}(T^+) = V_{C2}(T^+) = \frac{4RC_1 + 6RC_2}{C_1 + C_2}$$




$$V_{com}(t) = V_c^{final} + (V_c^{ini} - V_c^{final}) e^{-(t-t_{ini})/\tau_2}$$



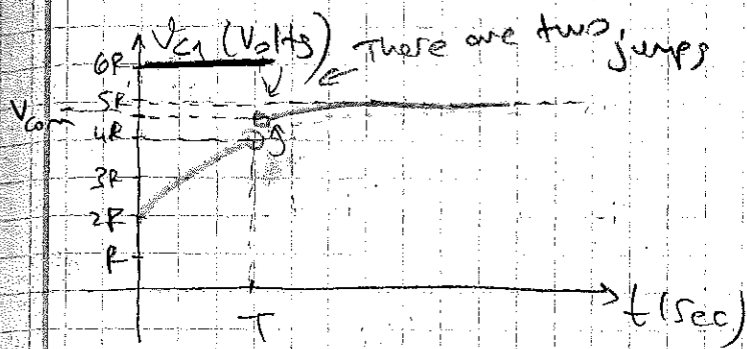
$$= 5R + \frac{(4RC_1 + 6RC_2 - 5R)}{C_1 + C_2} e^{-(t-\tau)/\tau_2}$$



1st order circuit (cont'd)

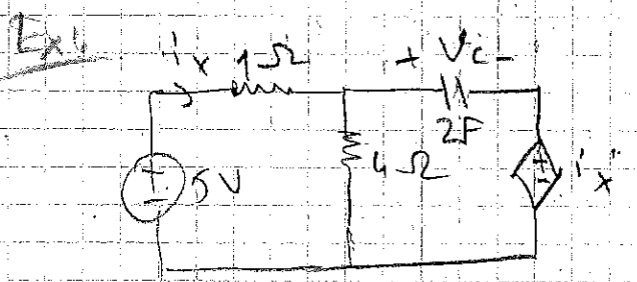

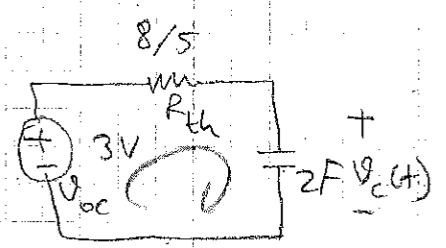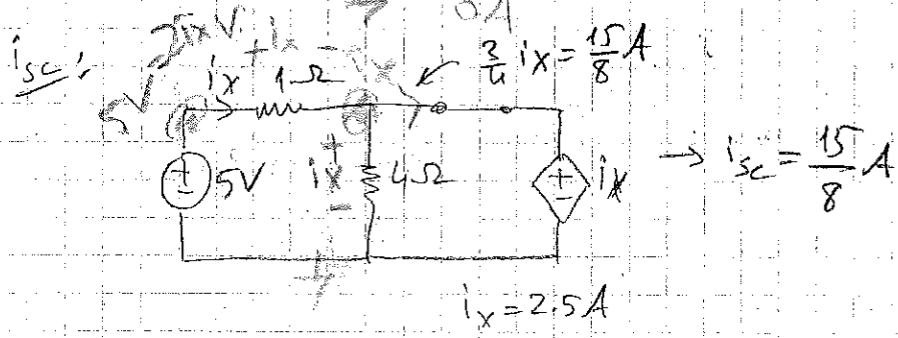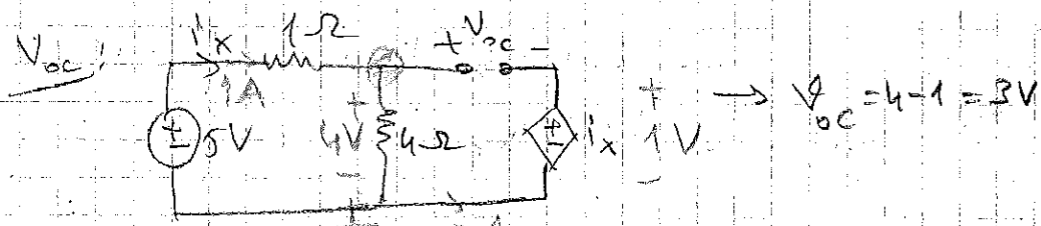Find $V_c(t)$, $i_x(t)$ for $t \geq 0$, ($V_c(0) = 5V$)
 Apply theorem equivalent $\rightarrow V_c(t)$
 $\rightarrow i_x(t)$



$$-V_{oc} + R \cdot i_c(t) + V_c(t) = 0$$

$$\uparrow e^{-t/\tau} V_c(t)$$

$$V_c(t) + \frac{1}{RC} V_c(t) = \frac{V_{oc}}{RC}$$


$$V_c(0) = 5V$$

$$V_c(t) = V_c^{final} + (V_c^{ini} - V_c^{final}) e^{-(t-t_{ini})/\tau}$$

$$= 3 + 2 e^{-t/3.2}, t \geq 0$$

$$\tau = RC_{eq} = \frac{16}{5} \text{ sec} = 3.2 \text{ sec}$$

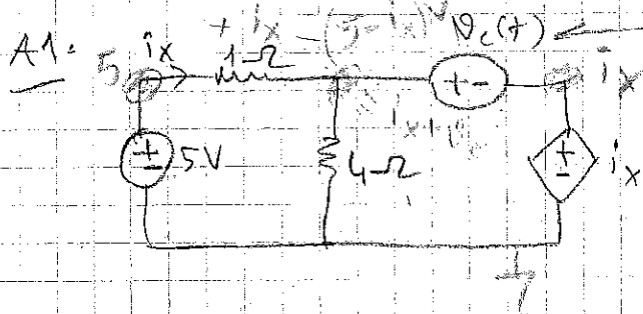Q1: Given your solution, can you immediately find $i_x(t)$?





We can consider the capacitor as a voltage source.

$$5 = 2i_x + V_c$$

$$i_x = \frac{5 - V_c}{2} = 1 - e^{-t/32}, t > 0$$

A2: I know that i_x also follows the function in the following form:

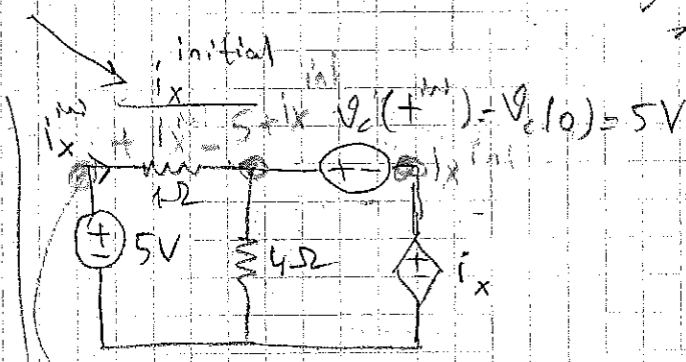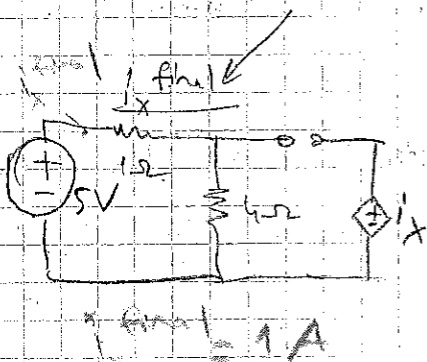
$$i_x(t) = i_x^{final} + (i_x^{initial} - i_x^{final}) e^{-(t-t_{initial})/\tau}, t > t_{initial}$$




$$5 = (5 + 1i_x^{initial}) + i_x^{initial} \rightarrow i_x^{initial} = 0 A$$

$$i_x(t) = 1 - e^{-t/32}, t \geq 0$$

In MT1 exam:

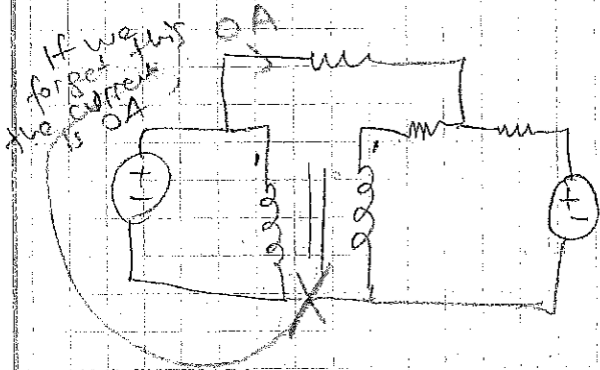

Zero Input and Zero State Responses

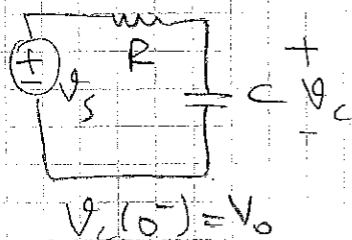

Zero input solution: This is the case for $V_s(t) = 0$ and $V_c(0^-) = V_0$. So, input is zero; circuit response is due to initial conditions.

Zero state solution: State is $V_c(t)$ [or $I_L(t)$] function and if this function is given to us (as in the previous example), all circuit branch voltages / currents can be found immediately.

Zero-state solution is the case for the initial conditions to be all zero; (initial conditions are in general state variables)

$$\begin{aligned} \rightarrow V_c(0^-) &= 0 \\ V_c(0^-) &= 0 \\ I_L(0^-) &= 0 \end{aligned}$$

and input $V_s(t) \neq 0$.

Complete Solution


$$V_c^{comp}(t) = V_c^{zi}(t) + V_c^{zs}(t)$$

zero-input zero-state solution

Zero-state Response


① Unit Step Response

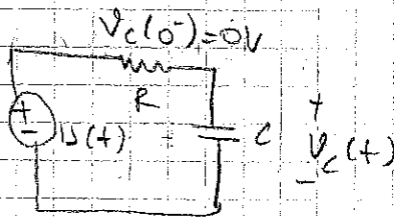Caution: All zero state responses are defined by definition at zero-state, i.e. zero initial conditions.




$$V_c^{step}(t) = ? \rightarrow V_c^{step}(t) = 1 - e^{-t/\tau}, t \geq 0$$

② Ramp Response

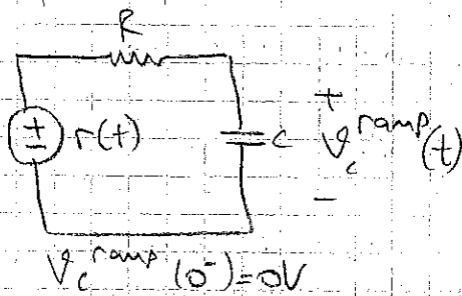
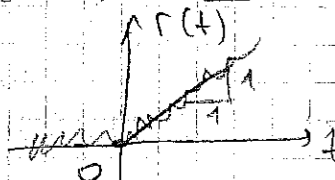
$$\begin{aligned} \left(D + \frac{1}{RC}\right) V_c^{ramp}(t) &= \frac{r(t)}{RC}, t \geq 0 \\ V_c^{ramp}(0^+) &= V_c^{ramp}(0^-) = 0V \end{aligned}$$



$$V_c^{ramp}(t) = \underbrace{A e^{-t/\tau}}_{\text{homogeneous}} + \underbrace{Kt + L}_{\text{particular}}$$

Insert particular solution into differential equation!

$$K + \frac{1}{RC}(Kt + L) = \frac{t}{RC}, t \geq 0$$

$$K + \frac{Kt}{RC} + \frac{L}{RC} = \frac{t}{RC} \quad K=1$$

$$\left(K + \frac{1}{RC}L\right) + \left(\frac{K}{RC}t\right) = \left(\frac{1}{RC}t\right), t \geq 0$$


$$\begin{aligned} -K &= \frac{L}{RC} \\ L &= -RC \end{aligned}$$

$f_1(t)$ $f_2(t)$ $t \geq 0$

$$V_c(t) = RC e^{-t/\tau} + t - RC, t \geq 0$$

$A = RC$ so that $V_c(0^+) = 0$

3 Impulse Response

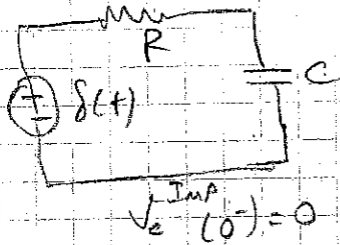


$$\left(D + \frac{1}{RC}\right) V_c^{imp}(t) = \frac{\delta(t)}{RC}, t > 0$$

$$V_c^{imp}(0^-) = 0$$

$$\left(D + \frac{1}{RC}\right) V_c^{imp}(t) = 0, t > 0$$

$$V_c^{imp}(0^+) = ?$$

Q: What is $V_c(0^+) = ?$

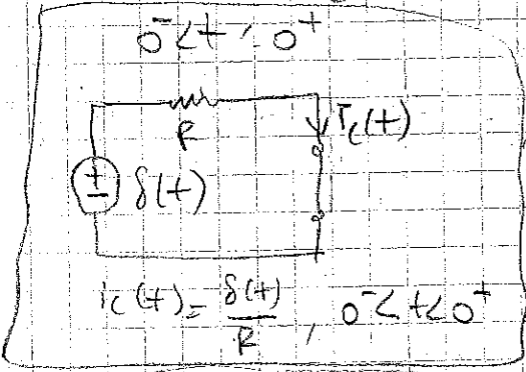

$$V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_c(t) dt$$

$$= \frac{1}{RC}$$

The integral term is shown as $\int_{0^-}^{0^+} \frac{\delta(t)}{R} dt$.

$$\left(D + \frac{1}{RC}\right) V_c^{imp}(t) = 0, t > 0$$


$$V_c^{imp}(0^+) = \frac{1}{RC}$$

$$V_c^{imp}(t) = \frac{1}{RC} e^{-t/RC} + 0, t > 0$$

The term $\frac{1}{RC} e^{-t/RC}$ is labeled as the homogeneous solution, and the term 0 is labeled as the particular solution.


Note: We denote impulse response by $h(t)$ in general.

Some general comments

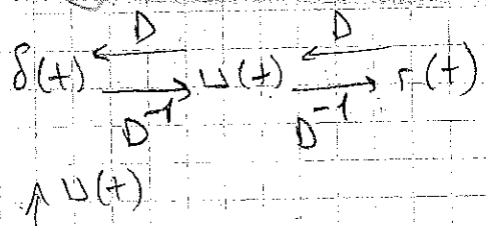



$$D = \frac{d}{dt}$$

$$D^{-1} = \int_{-\infty}^t (\cdot) dt$$

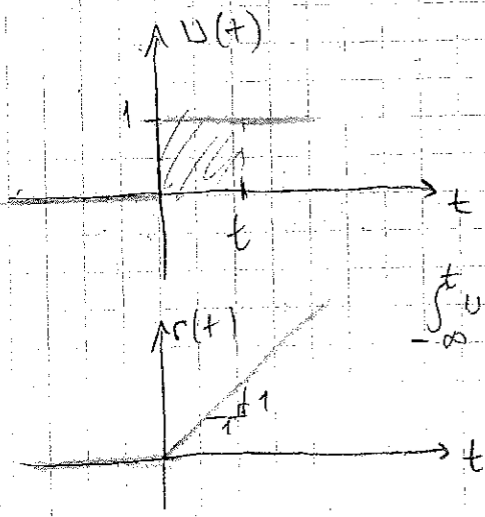


$$\int_{-\infty}^t u(\tau) d\tau = \delta^{-1} \left\{ \int_{-\infty}^t u(t) dt \right\} = r(t)$$


not multiplication

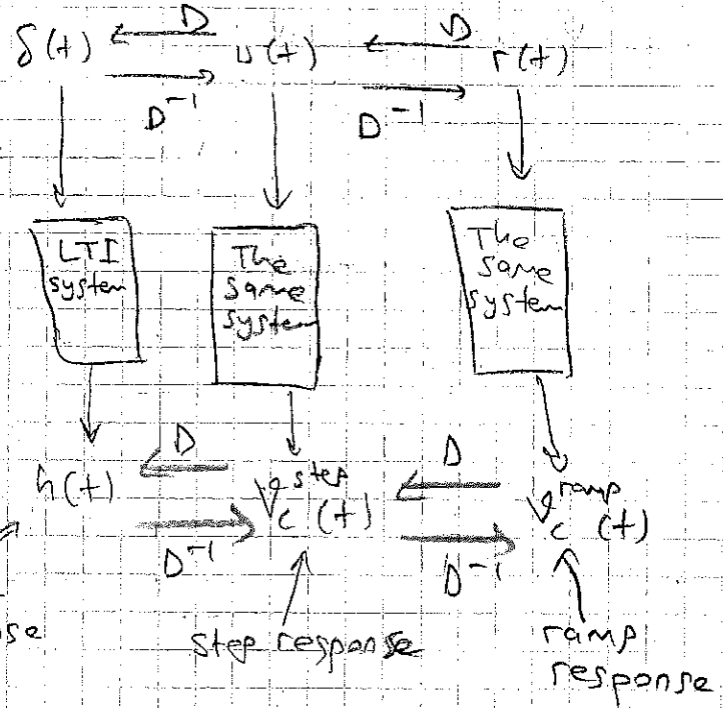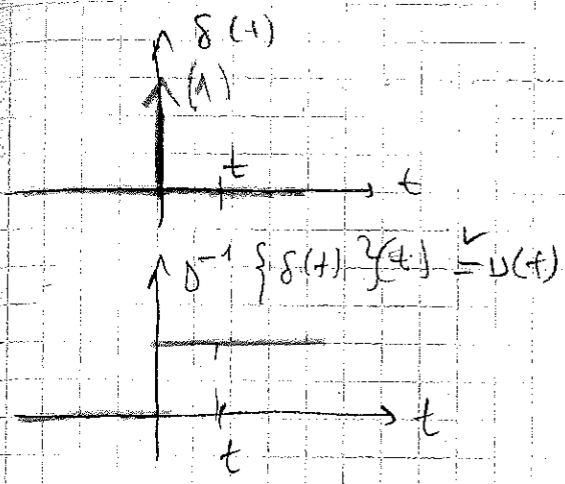

$$\begin{aligned}
 v_c^{ramp}(t) &= \int_{-\infty}^t v_c^{step}(\tau) d\tau \\
 &= \int_{-\infty}^t (1 - e^{-\tau/RC}) u(\tau) d\tau \\
 &= \int_0^t (1 - e^{-\tau/RC}) d\tau \\
 &= \tau - \frac{e^{-\tau/RC}}{-1/RC} \Big|_0^{\tau=t} \\
 &= (t + RC e^{-t/RC} - RC), t \geq 0
 \end{aligned}$$

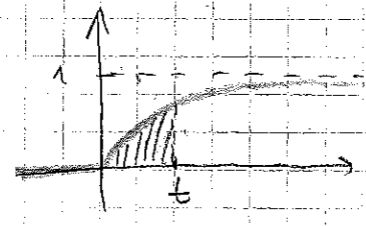

Ex:

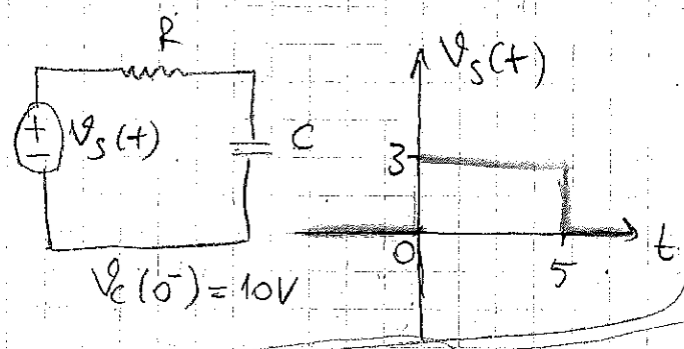


$$v_c(5^-) = 3 + 7e^{-5/\tau}, \quad \tau = RC$$

Method 1:


$$\begin{aligned}
 0 < t < 5^- \\
 v_c(0^+) &= 10V \\
 v_c(t) &= v_c^{th} + (v_c^{in} - v_c^{th}) e^{-t/\tau} \\
 &= 3 + 7e^{-t/\tau} V
 \end{aligned}$$

$t > 5$

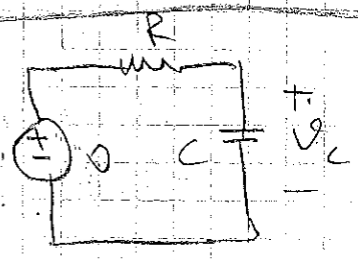


$$\begin{aligned}
 v_c(5^+) &= v_c(5^-) = v_5 \\
 v_c(t) &= 0 + v_5 e^{-(t-5)/\tau}, t > 5
 \end{aligned}$$

Method 2


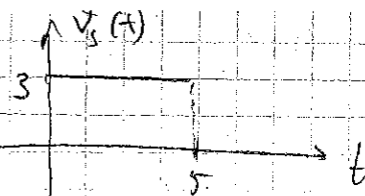


$$\rightarrow V_s(t) = 3u(t) - 3u(t-5)$$

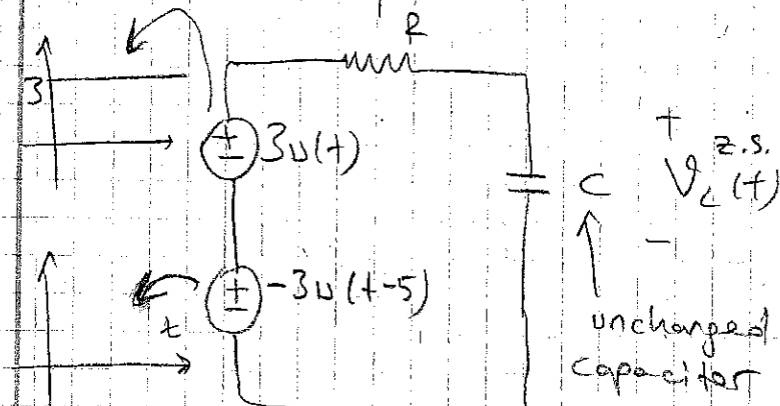


Assume cap. is uncharged then
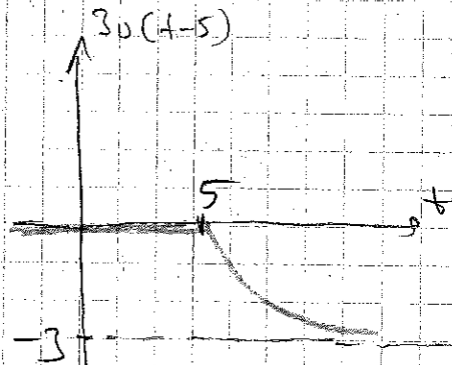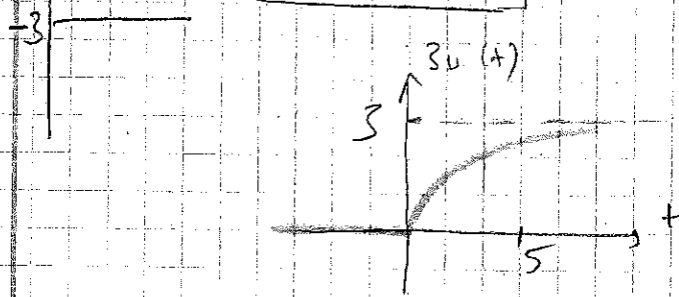
$$V_c^{z.s.}(t) = 3V_{step}(t) - 3V_{step}(t-5)$$



$$\begin{aligned} \text{Then } V_c^{z.s.}(t) &= 3V^{step}(t) - 3V^{step}(t-5) \\ &= 3(1 - e^{-t/\tau})u(t) - 3(1 - e^{-(t-5)/\tau})u(t-5) \end{aligned}$$
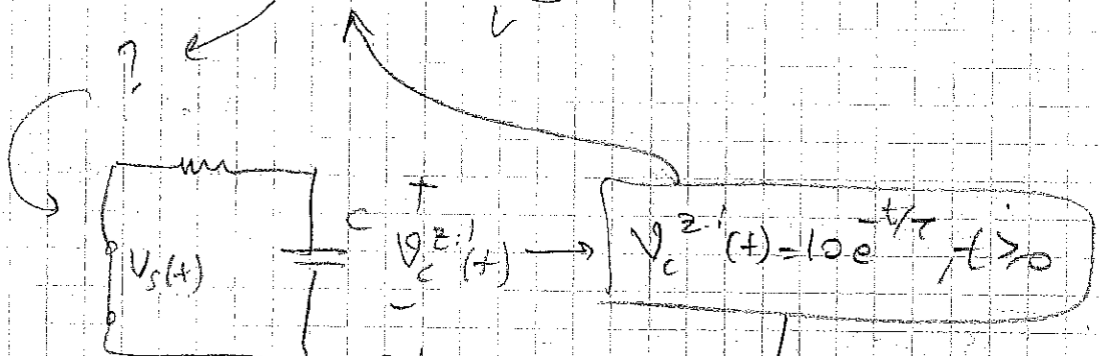
$$V_c^{comp}(t) = V_c^{z.s.}(t) + V_c^{z.i.}(t)$$



$$V_c^{z.i.}(0) = V_c^{z.i.}(0^+) = 10V$$



$$\begin{aligned} V_{comp}(t) &= 10e^{-t/\tau} u(t) + \\ & 3(1 - e^{-t/\tau})u(t) - \\ & 3(1 - e^{-(t-5)/\tau})u(t-5) \end{aligned}$$

Zero-state / Zero-input Decomposition and its applications in LTI circuit analysis


Claim: A dynamic circuit has a solution which can be decomposed as

$$V_c^{comp}(t) = \underbrace{V_c^{z.s.}(t)}_{\text{Zero state response}} + \underbrace{V_c^{z.i.}(t)}_{\text{Zero input response}}$$


Proof

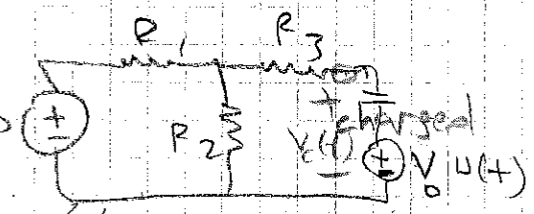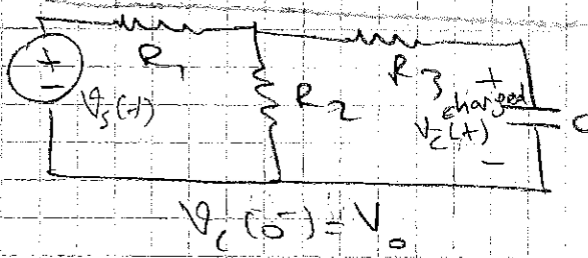

Superposition


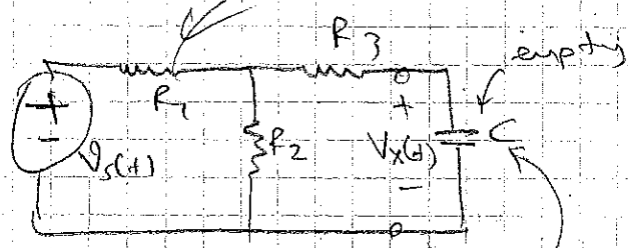


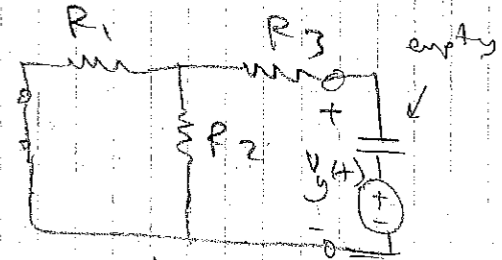$V_x(t)$, zero-state response shows this is the response to input when $I_C = 0$.



Charged cap. with I.C. V_0
 $V_y(t)$: zero-input is the response when $V_s(t) = 0$ (input = 0) and $I_C \neq 0$

Ex:

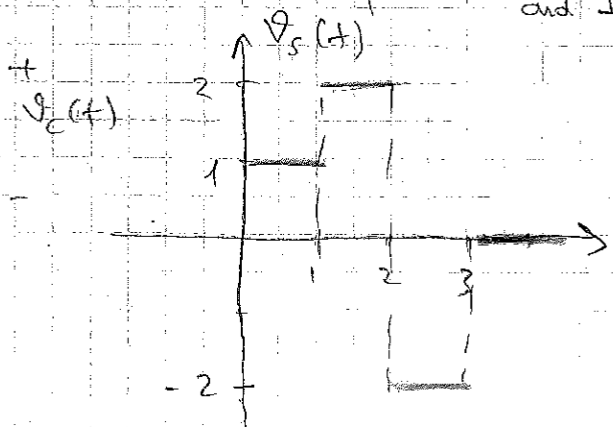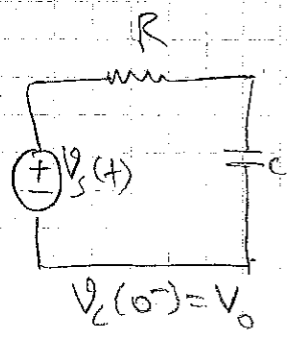



Find $V_c(t)$.

$$V_c(t) = V_c^{z.i.}(t) + V_c^{z.s.}(t)$$


$$V_c^{z.i.}(t) = V_0 e^{-t/\tau}, t \geq 0$$

$$= V_0 e^{-t/RC}$$

$$(\tau = RC)$$

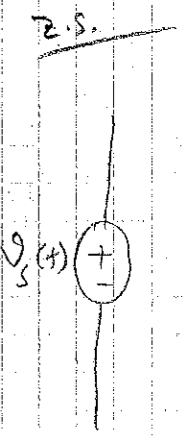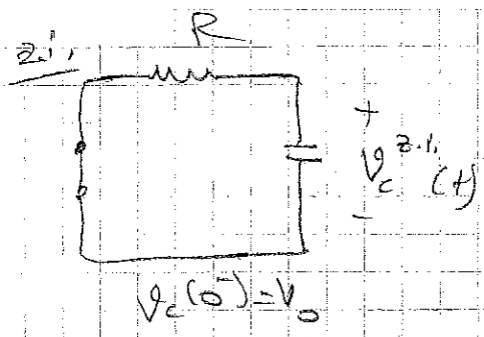
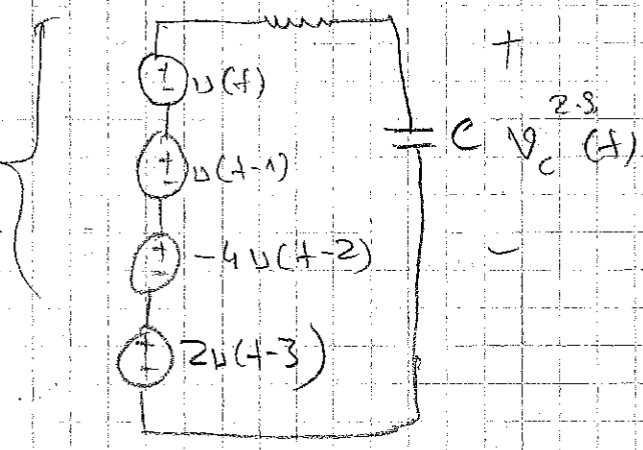
$$V_s(t) = u(t) + u(t-1) - 4u(t-2) + 2u(t-3)$$




$$V_c(0^-) = 0$$

$$V_c^{z.s.}(t) = V_c^{step}(t) + V_c^{step}(t-1) - 4V_c^{step}(t-2) + 2V_c^{step}(t-3)$$



Step response of the circuit

$$\tau = RC$$

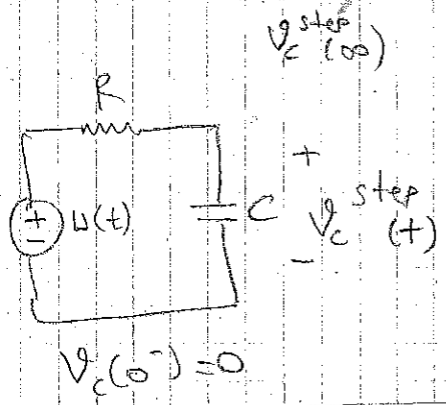
$$V_c^{step}(t) = (1 - e^{-t/\tau}) u(t) \rightarrow V_c^{step}(t) = (1 - e^{-t/RC}) u(t)$$



$$V_c(0^-) = 0$$

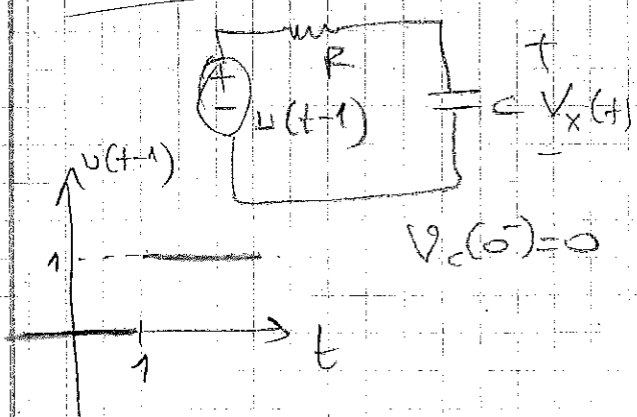
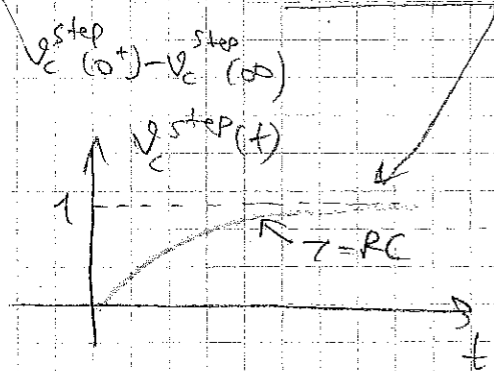


$$V_c(0^-) = 0$$

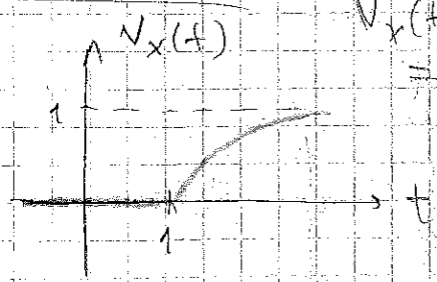



$$V_x(t) = V_c^{step}(t-1) = (1 - e^{-(t-1)/RC}) u(t-1)$$
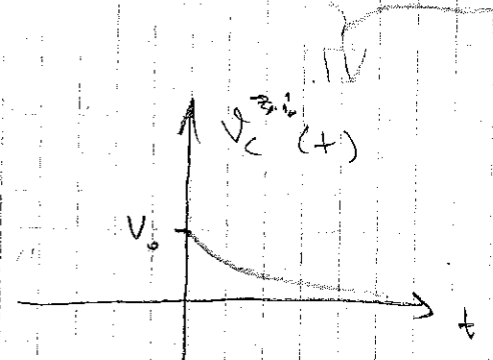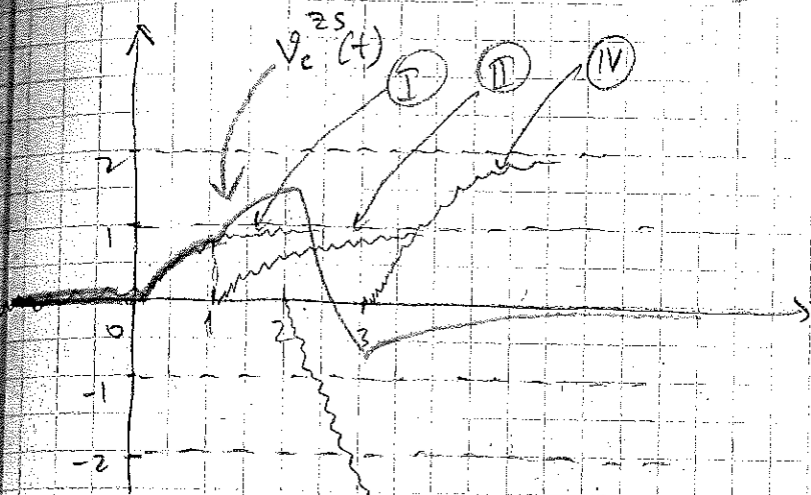
$$V_c^{zs}(t) = (1 - e^{-t/\tau})u(t) + (1 - e^{-(t-1)/\tau})u(t-1) - 4(1 - e^{-(t-2)/\tau})u(t-2) + 2(1 - e^{-(t-3)/\tau})u(t-3) \quad \text{III}$$



Note that: $u(t)$ functions given in I-IV is critical for the correctness of superposition sum for $V_c^{zs}(t)$.

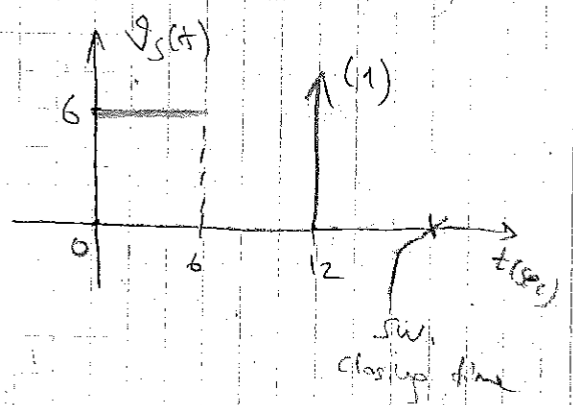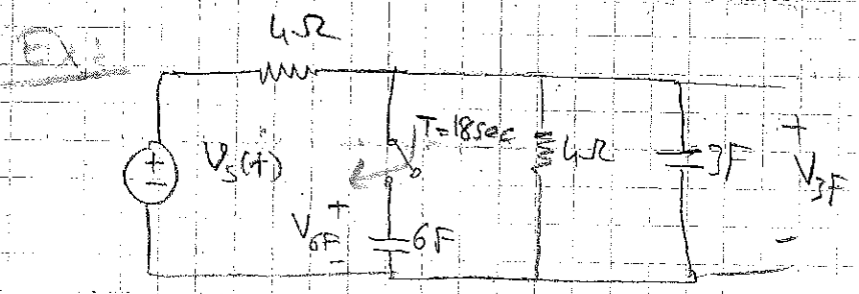
$$V_c^{comp}(t) = V_c^{zs}(t) + V_c^{zs}(t)$$



$$V_{6F}(0^-) = -2V$$

$$V_{3F}(0^-) = 7V$$

$0 < t < 18$

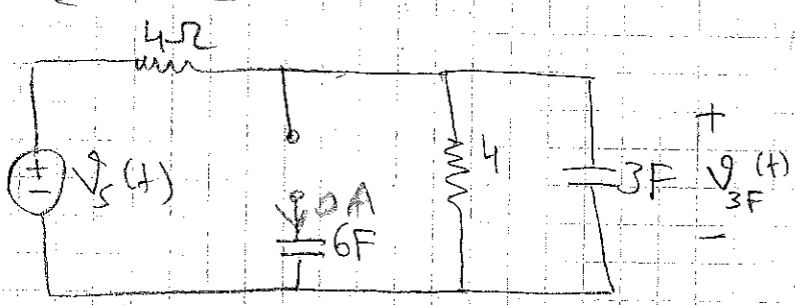

$$V_{3F}(t) = V_{3F}^{zs}(t) + V_{3F}^{zs}(t)$$

$$V_{3F}^{zs}(t) = 7e^{-t/\tau}, u(t), \tau = 3 \times (4 \parallel 4) = 6 \text{ sec}$$


$$V_{6F}(t) = V_{6F}(0^+) = V_{6F}(0^-) = -2, 0 < t < 18$$

$$V_c(0^+) + \frac{1}{C} \int_{0^+}^t i_c(\tau) d\tau$$

$$V_5(t) = [6u(t) - 6u(t-6) + 1\delta(t-12)]$$

$$V_{3F}^{zs}(t) = 6V_{3F}^{step}(t) - 6V_{3F}^{step}(t-6) + 1 \cdot V_c^{impulse}(t-12)$$

$V_C^{step}(t) = ?$

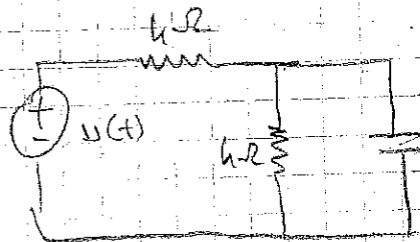

$V_{3F}(0^-) = 0V$

$V_{3F}^{step} = \left(\frac{1}{2} - \frac{1}{2} e^{-t/\tau} \right) u(t)$

$h(t) \rightarrow h(t) = \frac{d}{dt} V_{3F}^{step}(t) = \frac{1}{2} \frac{d}{dt} \left\{ (1 - e^{-t/\tau}) u(t) \right\}$
 $= \frac{1}{2} \left(\frac{1}{2} e^{-t/\tau} u(t) + (1 - e^{-t/\tau}) \delta(t) \right)$



$h(t) = \frac{1}{2} \left[\frac{1}{6} e^{-t/\tau} u(t) + (1 - e^{-t/6}) \delta(t) \right]$

$f(t) \cdot \delta(t) = f(0) \delta(t)$


or $f(t) \delta(t - t_x) = f(t_x) \delta(t - t_x)$

$h(t) = \frac{1}{12} e^{-t/\tau} u(t) + (1 - e^{0/6}) \delta(t)$

$= 0 \cdot \delta(t)$
 $= 0$

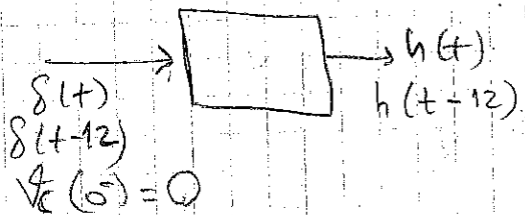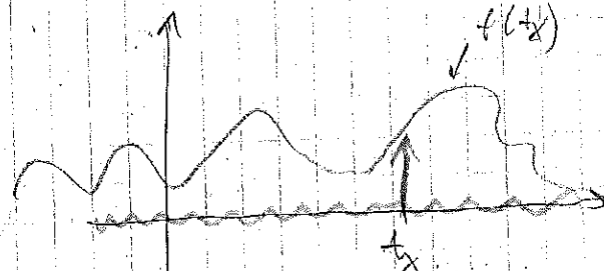

What is $h(t)$?

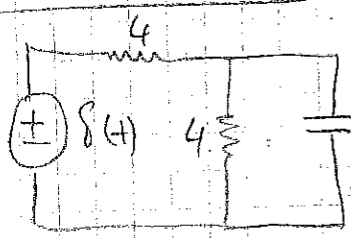

$h(t) = \frac{d}{dt} V_C^{step}(t)$



$0 < t < 18^-$
 $V_C^{comp}(t) = 7e^{-t/6} u(t) + 3(1 - e^{-t/\tau}) u(t) - 3(1 - e^{-(t-6)/\tau}) u(t-6)$
 $+ \frac{1}{12} e^{-(t-12)/\tau} u(t-12)$

$V_{3F}(18^-) = 2.14 \text{ Volts}$
 $18^- < t < 18^+ \quad \text{At } t = 18 \text{ sec.}$



Two caps. are forced by the switch operation to a common voltage level.

$q_{\text{before}} = q_{\text{after}}$

$3V_{3F}(18^-) + 6V_{6F}(18^-) = 9V_{\text{com}} \rightarrow V_{\text{com}} = -0.62V_{\text{at } t=18}$


$V_{3F}(18^+) = V_{6F}(18^+)$

$t > 18$

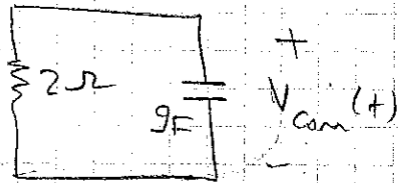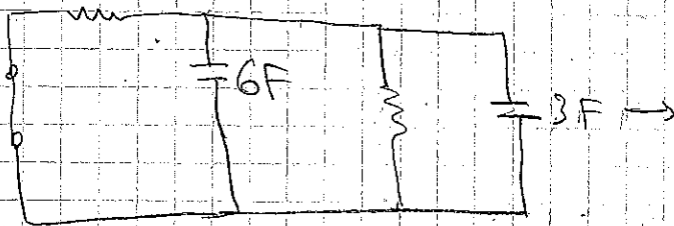

$V_{\text{com}}(18^+) = -0.62V$
 $V_{\text{com}}(t) = -0.62 \times e^{-(t-18)/\tau_2}$
 $t > 18$
 $\tau_2 = 9F \times 2\Omega = 18\text{sec}$

On RL Circuits

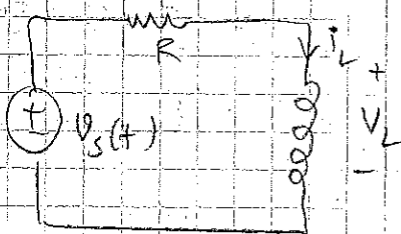

$-V_s(t) + R i_L(t) + V_L(t) = 0$
 $L \frac{d}{dt} i_L(t)$

$(D + \frac{R}{L}) i_L(t) = \frac{V_s(t)}{L}, t > 0$
 $i_L(0^-) = I_0$


$i_L(t) = A \cdot e^{-\frac{Rt}{L}} + \text{(Particular solution to } V_s(t)/L)$
 $t > 0$
 $\tau = L/R$

Let's remember $V_c(t) = A e^{-\frac{t}{RC}} + \text{(Particular solution)}, t > 0$
 $\tau = RC$

Comments


① If we have a complicated circuit with a single inductor, then apply Thevenin eq. to the part of the circuit seen by the inductor given us!

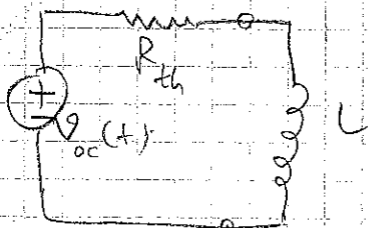Duality
 $R \leftrightarrow G$
 $C \leftrightarrow L$



The solution of this circuit is mathematically the same solution of RC circuits and only difference is the change in time constant.


Ex 1

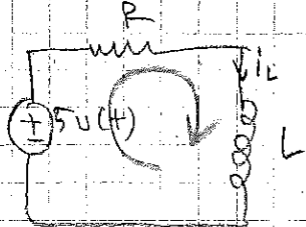

$i_L(0^-) = 10 \text{ A}$

$i_L(t) = i_L^{zi}(t) + i_L^{zs}(t)$

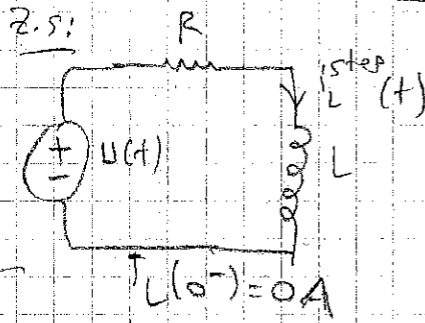
z.i.: $i_L^{zi}(t) = 10e^{-t/\tau} u(t)$ $\tau = \frac{L}{R}$



$i_L(0^-) = 0 \text{ A}$

z.s.: $i_L^{step}(t) = i_L(\infty) + (i_L(0) - i_L(\infty))e^{-t/\tau}, t \geq 0$
 $i_L(t) = 5 i_L^{step}(t) = \frac{5}{R} (1 - e^{-t/\tau}) u(t)$

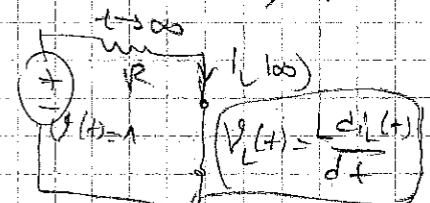$i_L(\infty) = \frac{1}{R}$ since $\lim_{t \rightarrow \infty} u(t) = 1$




Inductor acts as a short circuit as $t \rightarrow \infty$.

comp: $i_L(t) = i_L^{zi}(t) + i_L^{zs}(t)$

Time Invariant - Time Varying Non-linear Circuit

1st Order

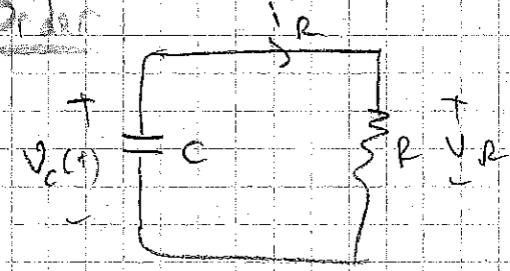

$V_C(0^-) = 1 \text{ V}$

- a) $R \Rightarrow \tau R \rightarrow$ Time Interval
- b) $R \Rightarrow R = \frac{1}{1+0.5 \cos t} R \rightarrow$ Time Varying
- c) $R \Rightarrow i_R^2 = V_R^2 \rightarrow$ Non-linear

a) $V_C(t) = \underbrace{V_C(0^+)}_{1 \text{ V}} e^{-t/\tau}, t \geq 0$ ($\tau = RC = (1 \Omega) \times (1 \text{ F}) = 1 \text{ sec}$)

b) $C \frac{dV_C(t)}{dt} + \frac{V_C}{R(t)} = 0 \rightarrow \frac{dV_C(t)}{dt} = -(1+0.5 \cos t) V_C(t)$

$\frac{dV_C(t)}{V_C(t)} = (-1+0.5 \cos t) dt$

$\ln(V_C(t)) = -(t+0.5 \sin t) + k$

$V_C(t) = e^{-(t+0.5 \sin t) + k}$

$V_C(t) = K' e^{-(t+0.5 \sin t)} e^k$

↑ Time-varying circuit case

c) $C \cdot \dot{V}_c(t) + i'_R = 0$

$\Rightarrow \dot{V}_R^2 = \dot{V}_c^2$

$\frac{dV_c(t)}{dt} = -\dot{V}_c^2(t)$

$\frac{dV_c(t)}{V_c^2(t)} = -dt$

$\int \leftarrow$ indefinite integral


$-\frac{1}{V_c(t)} = -t + K \rightarrow V_c(t) = \frac{1}{t-K}$

$V_c(t) = \frac{1}{t+1}$


$V_c(0^+) = V_c(0^-) = 1 \rightarrow K = -1$

non-linear resistor characteristic


EXL

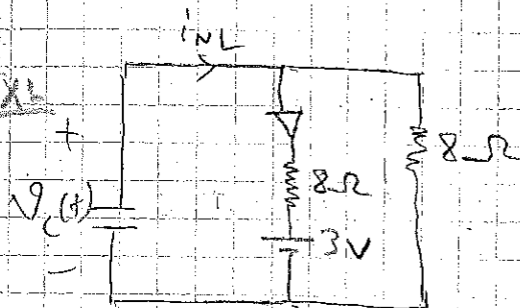

$V_c(0^-) = 10V$

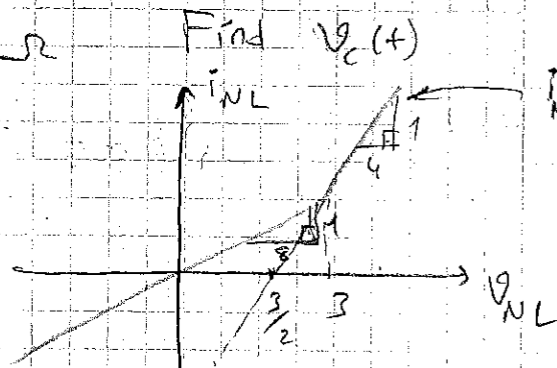


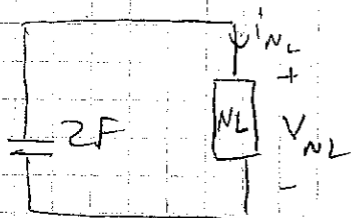$i'_{NL} = \frac{1}{4} V_{NL} - \frac{3}{8}$



$V_c(0^-) = 10V$

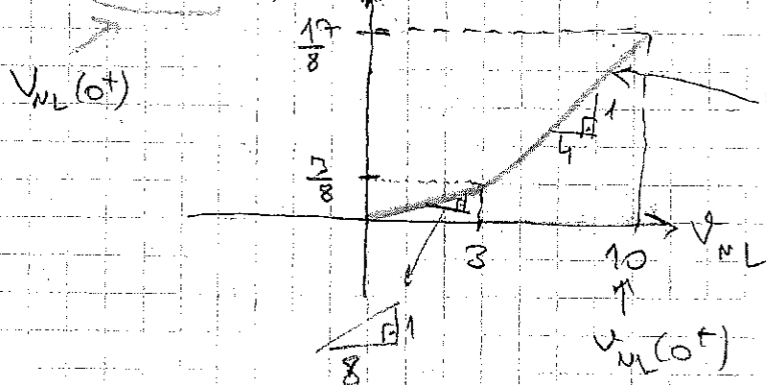$V_c(0^+) = 10V \rightarrow$ at $t=0^+$ D: ON



$i'_{NL} = \frac{1}{4} V_{NL} - \frac{3}{8}$

KCL:

$C \cdot \dot{V}_c(t) + i'_{NL}(t) = 0$

$\dot{V}_c(t) = \frac{-i'_{NL}(t)}{2}, t \geq 0$

$\dot{V}_c(0^+) = \frac{-i'_{NL}(0^+)}{2} = \frac{-17/8}{2} = \frac{-17}{16}$

$V_c(t)$ is decreasing at time $t=0$

The discharge of the capacitor continue until the diode turns off which is the case of $V_c(t)$ reaches 3 Volts or since Di: ON at $t=0^+$:


$$\dot{V}_c(t) = -\frac{I_m(t)}{2} \leftarrow \frac{1}{4} V_c - \frac{3}{8}$$

$$\left. \begin{aligned} \dot{V}_c(t) &= -\frac{1}{8} V_c + \frac{3}{16} \\ V_c(0^+) &= 10 \end{aligned} \right\} \begin{array}{l} \text{Valid for} \\ V_c > 3 \end{array}$$

$$V_c(t) = A \cdot e^{-\frac{1}{8}t} + \frac{3}{2} = \frac{17}{2} e^{-\frac{1}{8}t} + \frac{3}{2}$$


$$\frac{17}{2}$$

Another method: Di: ON

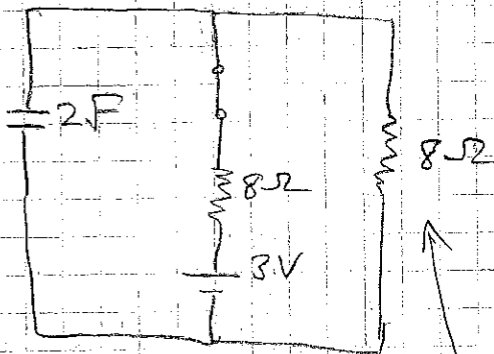

$$\rightarrow V_c(t) = \frac{3}{2} + \frac{17}{2} e^{-\frac{t}{\tau}}$$
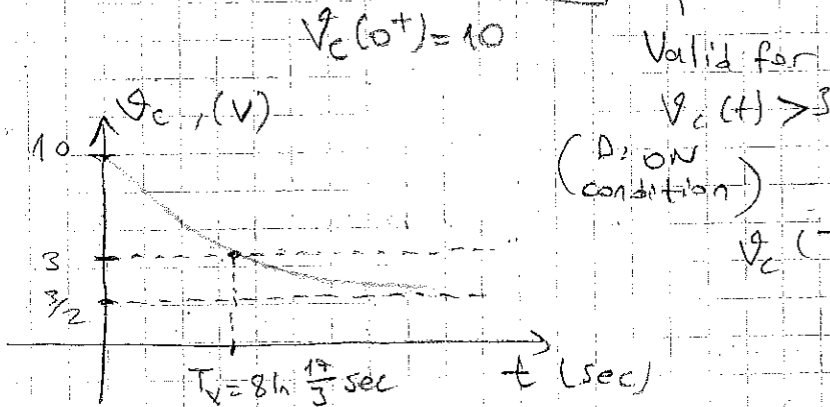
$$\begin{aligned} \tau &= C \cdot R_{\text{th}} \\ &= (2F) \times (8/8) \\ \tau &= 8 \text{ sec} \end{aligned}$$




$$V_c(T_x) = 3 \rightarrow T_x = ?$$

$$T_x = 8 \ln \frac{17}{3}$$

$t > T_x$ Di: OFF and the cap. discharged

(or $T = t_{\text{off}}$)

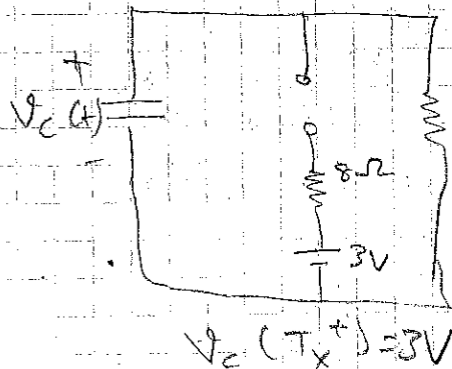


$$V_c(t) = 3 \cdot e^{-\frac{(t-T_x)}{\tau_2}}$$

$$\begin{aligned} \tau_2 &= 2 \times 8 \\ &= 16 \text{ sec} \end{aligned}$$

2nd Order Circuits

Parallel RLC:

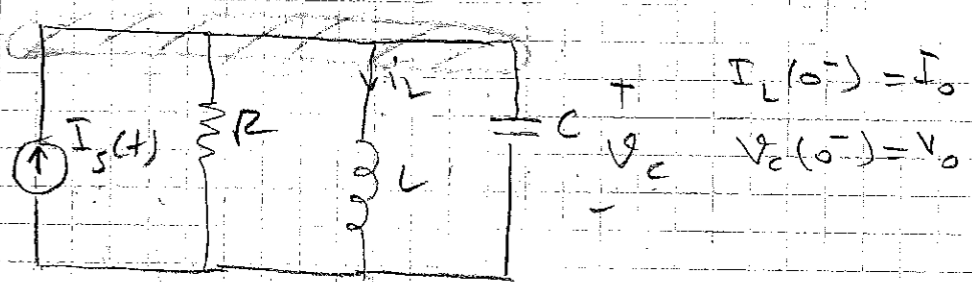

KCL: $-I_s(t) + i_R + i_L + i_C = 0, t > 0$

$\frac{v_c}{R}$ $i_L(t) = i_L(0^-) + \frac{1}{L} \int_0^t v_c(\tau) d\tau$ $C \frac{dv_c}{dt}$

$$-I_s(t) + \frac{1}{R} v_c + \left(I_0 + \frac{1}{L} \int_0^t v_c(\tau) d\tau \right) + C \frac{d}{dt} v_c(t) = 0$$

$$-I_s(t) + I_0 + \left(\frac{1}{R} + \frac{1}{L} D^{-1} + CD \right) v_c(t) = 0 (*)$$

integral-differential equations

Apply $\frac{1}{C} D = \frac{1}{C} \frac{d}{dt} \int$ to both sides of (*)

$$D = \frac{d}{dt}$$

$$D^{-1} = \int_0^t (-) d\tau$$


$$D \int t^2 = 2t$$

$$D \int_0^t t^2 = \int_0^t 2t d\tau = t^2$$

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) v_c(t) = \frac{d}{dt} I_s(t) \cdot \frac{1}{C} = \frac{\dot{I}_s(t)}{C}, t > 0$$


$v_c(0^+) = ?$
 $\dot{v}_c(0^+) = ?$

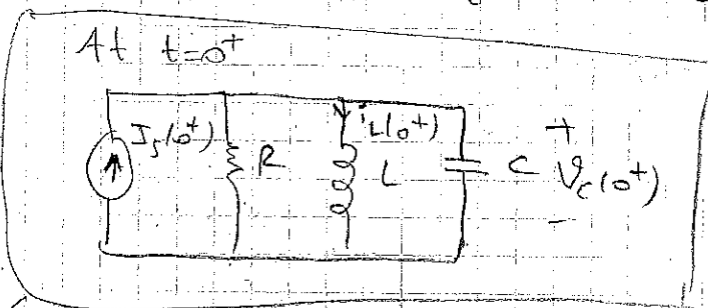
We need I.C. for $v_c(t)$ and its derivative at $t=0$ for the solution.



Assume $I_s(t)$ isn't $\delta(t)$

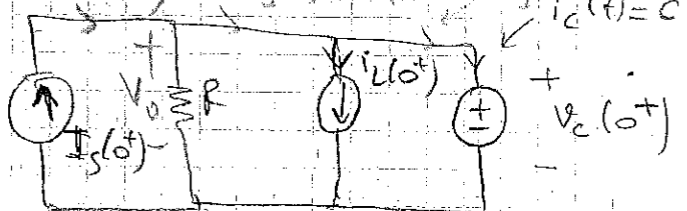$v_c(0^+) = v_c(0^-) = V_0$
 $i_L(0^+) = i_L(0^-) = I_0$
 $i_C(t) = C \dot{v}_c(t)$



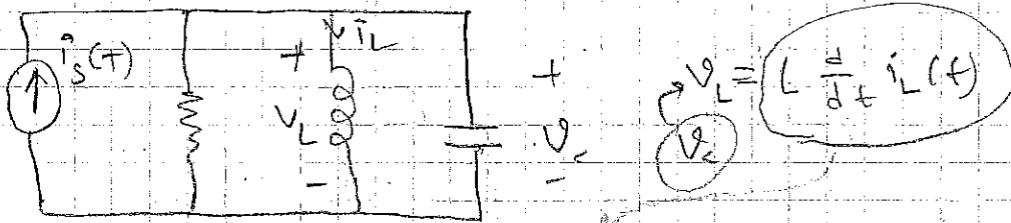

$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right) v_C(t) = \frac{1}{C} \int i_s(t) dt$$

$$\left\{ L \frac{d}{dt} \left\{ i_L(t) \right\} \right\}$$

Apply D^{-1} to both sides

$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right) D i_L(t) = \frac{1}{C} i_s(t)$$

$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right) i_L(t) = \frac{i_s(t)}{LC}$$

$$i_L(0^+) = i_L(0^-) = I_0$$

(no impulsive input)

Dis. eqn. for the variable $i_L(t)$.

$$v_L(0^+) = v_C(0^+) = v_C(0) = V_0$$

I.C.'s

$$L i_L(0^+)$$

$$i_L(0^+) = \frac{V_0}{L}$$

cons. coef. diff. eq.

Solution of 2nd order CCDE

1) Zero input solution

Parallel RLC $\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right) v_C(t) = \frac{1}{C} \int i_s(t) dt = 0$

$$v_C(0^-) = 0$$

$$i_C(0^-) = I_0$$

General form for 2nd order CCDE: $\left(D^2 + 2\alpha D + \omega_0^2\right) v_C(t) = 0$ (*)

Parallel RLC $\Rightarrow 2\alpha = \frac{1}{RC}$

α : Damping coefficient

ω_0 : resonance frequency

$$\omega_0^2 = \frac{1}{LC}$$

$v_C(t) = A e^{\lambda t}$ ← Guess for zero input solution

Insert into (*): $A(\lambda^2 + 2\alpha\lambda + \omega_0^2)e^{\lambda t} = 0$

$$A=0$$

$$V_c(t) = A e^{\lambda t} = 0!$$

trivial solution

$$\forall A, \lambda^2 + 2\alpha\lambda + \omega_0^2 = 0$$

$$\lambda_{1,2} = \frac{-2\alpha \pm \sqrt{4\alpha^2 - 4\omega_0^2}}{2}$$

$$\lambda_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

α : damping coefficient

$$V_c^{z.i.}(t) = A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}$$

A_1, A_2 : are the unknowns to be set to satisfy the I.C.

λ : Natural frequencies of the circuit \leftarrow Very important

Please pay attention to λ is the property of the circuit and isn't related with the input. (Actually, we've derived λ_1, λ_2 from zero-input response!)

$$\lambda^2 + 2\alpha\lambda + \omega_0^2 = 0 \leftarrow \text{characteristic equation}$$

characteristic polynomial

The roots of characteristic polynomial are called natural frequency.

There are 3 possible classes of solution for the char. equation.

① λ_1, λ_2 are real and distinct ($\Delta > 0$) $\alpha > \omega_0$ overdamped

② $\lambda_1 = \lambda_2$ roots are real valued but identical ($\Delta = 0$) $\alpha = \omega_0$ critically damped

③ λ_1, λ_2 are complex valued but distinct, ($\Delta < 0$) $\alpha < \omega_0$ underdamped

Parallel RLC

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$\alpha > \omega_0$$

$$\frac{1}{2RC} > \frac{1}{\sqrt{LC}} \rightarrow RC < \frac{1}{2} \sqrt{\frac{L}{C}}$$

condition for overdamped case (Parallel RLC)

$$V_c^{z.i.}(t) = A_1 e^{-2t} + A_2 e^{-3t}$$

Let $\lambda_1 = -2$

$\lambda_2 = -3$

$$V_c^{z.i.}(t) = A_1 e^{-2t} + A_2 t e^{-3t}$$

$$\lambda = \lambda_1 = \lambda_2 = -\alpha$$

$\alpha < \omega_0 \rightarrow v_c^{z.i.}(t) = A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}$
 $\lambda_2 = \lambda_1^*$ (complex conjugate)

$(\lambda^2 + 6\lambda + 16 = 0)$
 $\alpha = 3$ $\omega_0 = 4$

$j = i = \sqrt{-1}$

$\lambda_{1,2} = -3 \pm \sqrt{9-16} = -3 \pm j\sqrt{7}$

$v_c^{z.i.}(t) = A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}$
 $= A_1 e^{(-3+j\sqrt{7})t} + A_2 e^{(-3-j\sqrt{7})t}$
 $\lambda_1 = -3 + j\sqrt{7}$
 $\lambda_2 = -3 - j\sqrt{7}$

$= A_1 e^{-3t} \cdot e^{j\sqrt{7}t} + A_2 e^{-3t} \cdot e^{-j\sqrt{7}t}$
 $= e^{-3t} (A_1 e^{j\sqrt{7}t} + A_2 e^{-j\sqrt{7}t})$

$v_c^{z.i.}(0^+) = V_0$
 $\dot{v}_c^{z.i.}(0^+) = \dot{V}_0$

I.C. are utilized to find A_1, A_2

$A_1^* + A_2^* = V_0^*$
 $(-3+j\sqrt{7})A_1^* + (-3-j\sqrt{7})A_2^* = \dot{V}_0^*$
 $A_1 = A_2^*$

$v_c^{z.i.}(t) = e^{-3t} (A_1 e^{j\sqrt{7}t} + A_1^* e^{-j\sqrt{7}t})$
 $= e^{-3t} (\|A_1\| e^{j\sqrt{7}t} + \|A_1\| e^{-j\sqrt{7}t})$
 $= e^{-3t} \|A_1\| (e^{j(\sqrt{7}t + \phi A_1)} + e^{-j(\sqrt{7}t + \phi A_1)})$


$= e^{-3t} \|A_1\| \cdot 2 \cos(\sqrt{7}t + \phi A_1)$

$v_c^{z.i.}(t) = k e^{-3t} \cos(\sqrt{7}t + L)$

$k = 2 \|A_1\|$ $L = \phi A_1$

2nd order circuits (cont'd)

Parallel RLC:

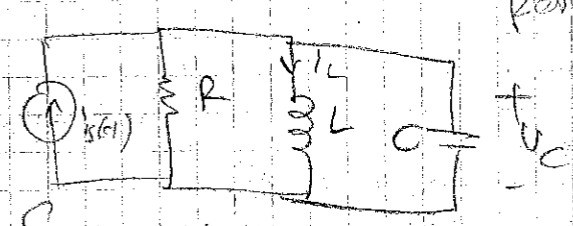

Parallel RLC

I.C. $\begin{cases} v_c(0^+) = V_0 \\ i_L(0^+) = I_0 \end{cases}$

Diff. Eqn: $(D^2 + \frac{1}{RC}D + \frac{1}{LC})v_c(t) = \frac{1}{C}D\{i_s(t)\}, t > 0$

$v_c(0^+) = \dots ?$
 $\dot{v}_c(0^+) = \dots ?$

→ Zero-input response ($i_f(t) = 0$)

Guess $v_c^{z.i.}(t) = Ae^{\lambda t}$

For the guess to be correct

$$A(\lambda^2 + \frac{1}{RC}\lambda + \frac{1}{LC}) = 0 \rightarrow A = 0$$

$$\rightarrow A \neq 0, \lambda^2 + \frac{1}{RC}\lambda + \frac{1}{LC} = 0$$

Char Poly: $\lambda^2 + \frac{1}{RC}\lambda + \frac{1}{LC}$

Char Eqn: $\lambda^2 + (\frac{1}{RC})\lambda + (\frac{1}{LC}) = 0$

ω_0 : resonant frequency
 α : damping constant

Roots of char. poly. →

$$\lambda_{1/2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


natural freq.

Cases:

① $\alpha > \omega_0$ (overdamped) → $v_c^{z.i.}(t) = A_1 e^{-2t} + A_2 e^{-3t}$


② $\alpha = \omega_0$ (critically damped) → $v_c^{z.i.}(t) = A_1 e^{-5t} + A_2 t e^{-5t}$

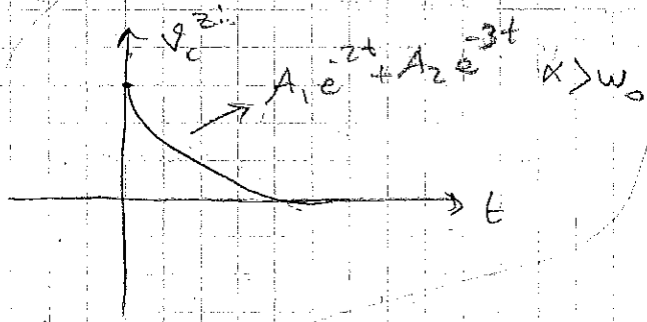③ $\alpha < \omega_0$ (underdamped) → $v_c^{z.i.}(t) = A e^{-3t} \cos(8t + \phi)$




Overdamped


(Too much friction)
mechanical analogy

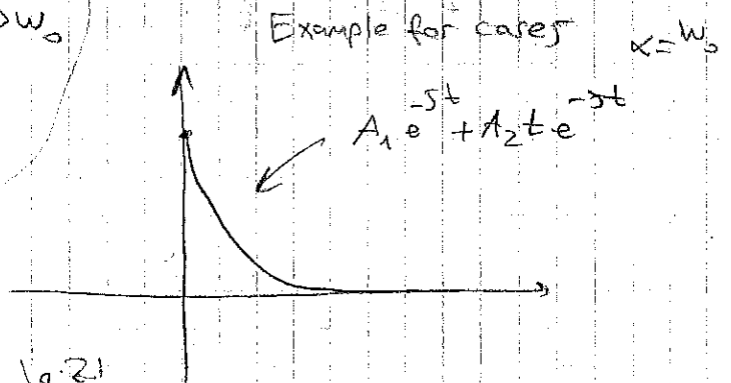

Example for cases $\alpha = \omega_0$

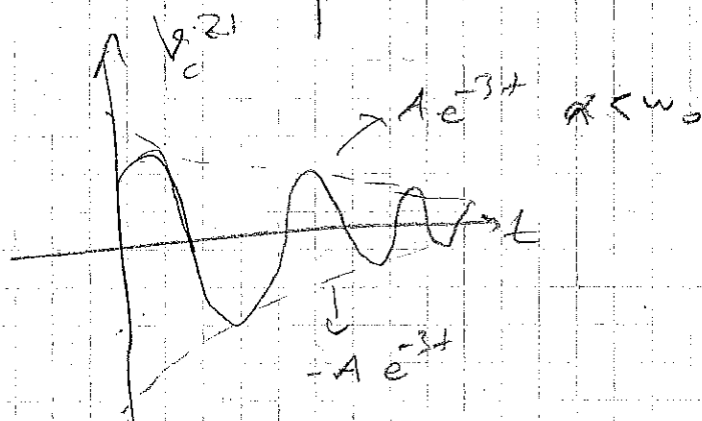


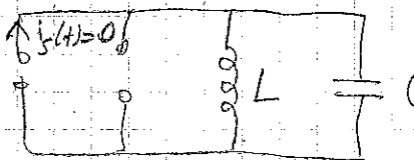Case ④ ($\alpha = 0$) i.e. for parallel RLC $R = \infty$




$$(D^2 + \frac{1}{LC}) v_c^{z.i.}(t) = 0$$
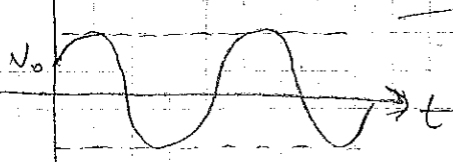
$$v_c^{z.i.}(t) = k \cos(\omega_0 t + \phi)$$



case of lossless circuit
(i.e. no friction)
→ no energy loss

Ex

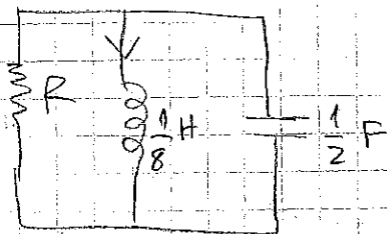

$$i_L(0^-) = -4A$$

$$v_C(0^-) = 5V$$

a) $R = \frac{1}{5}$, $v_C(t) = ?$ $t > 0$

$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right) v_C^{zi}(t) = 0$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = 4 \text{ rad/sec}$$

$$\alpha = \frac{1}{2RC} = 5 \left(\frac{1}{\text{sec}}\right)$$


$\alpha > \omega_0 \rightarrow$ overdamped

$$\lambda_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= \{-8, -2\}$$

$$\rightarrow v_C^{zi}(t) = A_1 e^{-8t} + A_2 e^{-2t}, t > 0$$

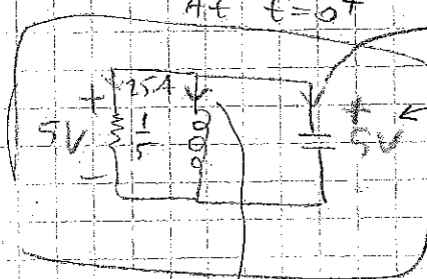Find A_1 and A_2 s.t. I.C. at $t=0^+$ is satisfied.



$$-4A = \dot{v}_C(0^+)$$

$$v_C(0^+) = v_C(0^-) = 5V$$

$$v_C(0^+) = 5V$$

$$\dot{v}_C(0^+) = -42 \text{ Volts/sec}$$

$$-4A = i_L(0^+) = i_L(0^-)$$

$$v_C(0^+) = A_1 e^{-8t} + A_2 e^{-2t} \Big|_{t=0^+} = 5$$

$$\dot{v}_C(0^+) = -8A_1 e^{-8t} - 2A_2 e^{-2t} \Big|_{t=0^+} = -42$$

$$\begin{bmatrix} 1 & 1 \\ -8 & -2 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 5 \\ -42 \end{bmatrix}$$

$$A_2 = -\frac{1}{3}$$

$$A_1 = \frac{16}{3}$$

$$\rightarrow v_C^{zi}(t) = -\frac{1}{3} e^{-2t} + \frac{16}{3} e^{-8t}, t > 0$$

b) $\rho = \frac{1}{4}$ $V_c(t) = ?$ $t > 0$

$\alpha = \frac{1}{2RC} = 4$
 $\omega_0 = 4$ } $\rightarrow \alpha = \omega_0$ critically damped

$\lambda_{1,2} = 4$

$V_c^{z.i.}(t) = A_1 e^{-4t} + A_2 t e^{-4t}$ $\rightarrow V_c^{z.i.}(0^+) = 5 = A_1$

$V_c^{z.i.}(0^+) = -32 = -4A_1 + A_2$
 $V_c^{z.i.}(t) = 5 e^{-4t} - 12 t e^{-4t}$ Volts

$V_c^{z.i.}(t) = A_1 e^{-4t} + A_2 t e^{-4t}$, $t > 0$
 $V_c^{z.i.}(0^+) = 5V$
 $V_c^{z.i.}(0^+) = -32$ Volts/sec

c) $\rho = \frac{1}{3}$, Find $V_c(t)$, $t > 0$

$\alpha = 3$
 $\omega_0 = 4$ } $\alpha < \omega_0 \rightarrow$ underdamped

$\lambda_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
 $= -3 \pm j\sqrt{7}$

From $t=0^+$
 Analysis

$V_c^{z.i.}(0^+) = 5$ Volts
 $V_c^{z.i.}(0^+) = -22$ Volts/sec

$\lambda_{1,2}$: natural frequencies

$V_c^{z.i.}(t) = A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}$, $t > 0$ I.C. at $t=0^+$ given

$V_c^{z.i.}(0^+) = A_1 + A_2 = 5$
 $V_c^{z.i.}(0^+) = \lambda_1 A_1 + \lambda_2 A_2 = -22$

$\begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} 1 & 1 \\ 3-j\sqrt{7} & 3+j\sqrt{7} \end{bmatrix} \begin{bmatrix} 5 \\ -22 \end{bmatrix}$

$\Delta = -j^2 7$

$A_1 = \frac{5}{2} + j \frac{\sqrt{7}}{2}$

$A_2 = \frac{5}{2} - j \frac{\sqrt{7}}{2}$

$V_c(t) = \underbrace{\left(\frac{5}{2} + j \frac{\sqrt{7}}{2} \right)}_{A_1} e^{\underbrace{(-3+j\sqrt{7})t}_{\lambda_1}} + \underbrace{\left(\frac{5}{2} - j \frac{\sqrt{7}}{2} \right)}_{A_2} e^{\underbrace{(-3-j\sqrt{7})t}_{\lambda_2}}$

Euler's formula:

$$e^{j\theta} = \cos\theta + j\sin\theta \quad \cos\theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

$$\sin\theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

Taylor series

$$V_c(t) = z + z^* \quad ; \quad z = \left(\frac{5}{2} + j\frac{\sqrt{7}}{2}\right) e^{(-3+j\sqrt{7})t}$$


$$= 2 \operatorname{Re}\{z\}$$

$$= 2 \operatorname{Re}\left\{\left(\frac{5}{2} + j\frac{\sqrt{7}}{2}\right) e^{(-3+j\sqrt{7})t}\right\}$$

$$= 2 \operatorname{Re}\left\{\frac{\sqrt{32}}{2} e^{-j4 \tan^{-1}(\sqrt{7}/5)} e^{-3t} e^{j\sqrt{7}t}\right\}$$


$$= \sqrt{32} e^{-3t} \operatorname{Re}\left\{e^{j(\sqrt{7}t + \tan^{-1}(\frac{\sqrt{7}}{5}))}\right\}$$
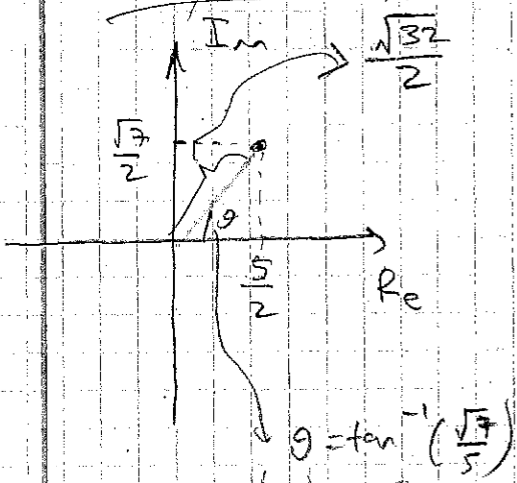
$$V_c(t) = \sqrt{32} e^{-3t} \cos\left(\sqrt{7}t + \tan^{-1}\left(\frac{\sqrt{7}}{5}\right)\right) \text{ Volts}$$



zero-state response

Ramp Response

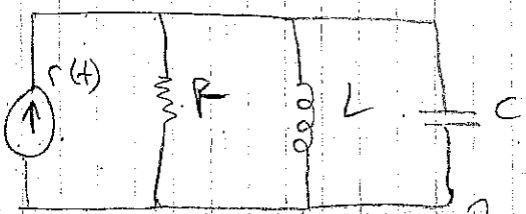

$V_c(0^-) = V_0 = 0$
 $I_L(0^-) = I_0 = 0$ } Zero-state response requires zero I.C. (zero initial energy)

$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right) V_c(t) = \frac{1}{C} \frac{d}{dt} \{i_s(t)\}, \quad t > 0$$

$$= \frac{1}{C} \cdot 1 \quad \text{where } i_s(t) = t u(t) = t, \quad t > 0$$

$$V_c^{\text{ramp}}(t) = \underbrace{A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}}_{\text{Homogeneous solution}} + \underbrace{P}_{\text{Particular Solution}}$$


Generic Solution for ramp input. Any A_1 and A_2 at this Soln.

$$= A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t} + P \quad t > 0$$

Insert into diff. equation to find

A_1 and A_2 are to be found from $t=0^+$ I.C.'s

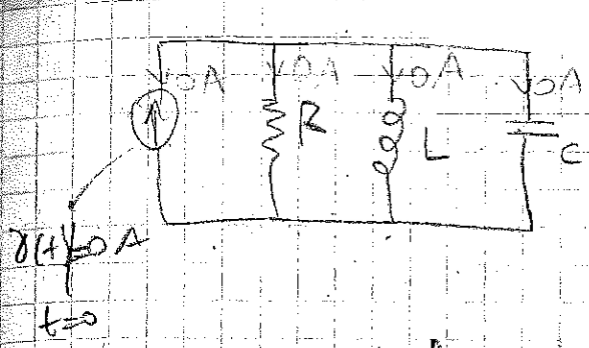
$$P \cdot \frac{1}{LC} = \frac{1}{C} \cdot 1 \rightarrow P = L$$



$(t \rightarrow \infty^+)$

$$\left. \begin{aligned} V_c^{\text{Ramp}}(0^+) &= 0 \\ \dot{V}_c^{\text{Ramp}}(0^+) &= 0 \end{aligned} \right\} \begin{aligned} &\text{Select } A_1 \text{ and } A_2 \\ &\text{in } A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t} \\ &\text{s.t.} \\ &t=0^+ \text{ cond. are} \\ &\text{satisfied} \end{aligned}$$

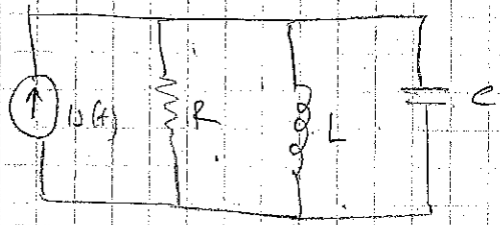
Zero-state response for step input (Step response):




$$\begin{aligned} V_c(0^+) &= 0 \\ I_L(0^+) &= 0 \end{aligned}$$

At $t=0^+$

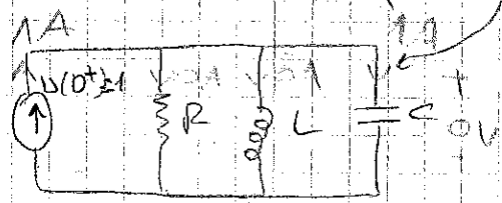At $t=0^+$, $V_c(0^+) = 0$
 $I_L(0^+) = 0$


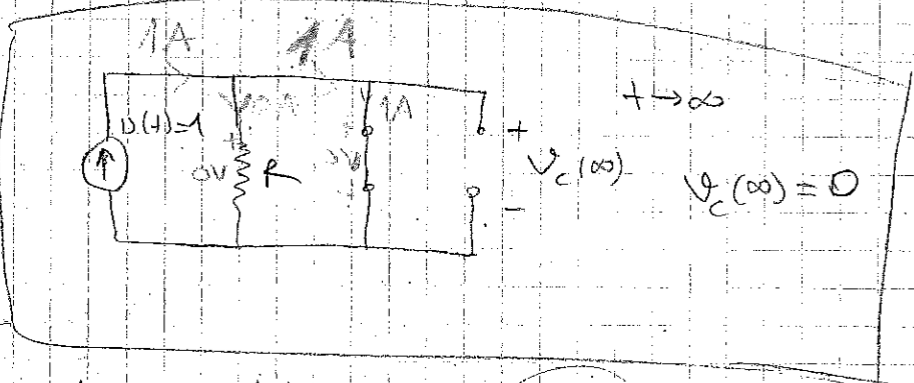
$$\begin{aligned} V_c(0^+) &= \frac{1}{C} \\ V_c(0^+) &= 0 \end{aligned}$$




$$V_c(\infty) = 0$$

$$\begin{aligned} V_c^{\text{step}}(t) &= A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t} + V_c(\infty) \\ V_c^{\text{step}}(t) &= A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}, \quad t > 0 \end{aligned}$$

A_1 and A_2 are selected to meet I.C. at $t=0^+$

For the same circuit

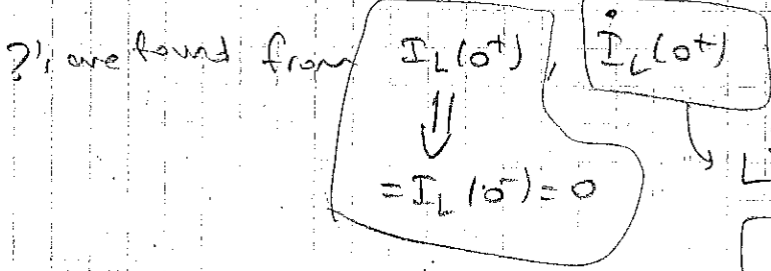
$$\begin{aligned} I_L(t) &= D_1 e^{\lambda_1 t} + D_2 e^{\lambda_2 t} + I_L(\infty) \\ &= D_1 e^{\lambda_1 t} + D_2 e^{\lambda_2 t} + 1 \end{aligned}$$



$$I_L(0^+) = 0$$

Zero-state solution (2.11.1)

Impulse response:

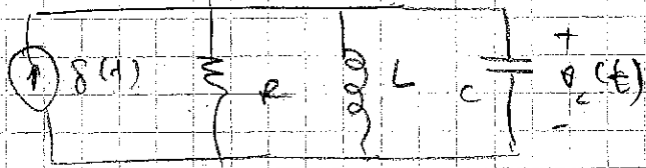

Let's find the response to $\delta(t)$ for the output $V_c(t)$, i.e. $V_c^{impulse}(t)$.

$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right) V_c(t) = \frac{1}{C} \frac{d}{dt} \left\{ i_L(t) \right\} = \frac{1}{C} \delta(t)$$


$V_c(0^-) = 0 \quad I_L(0^-) = 0$

$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right) V_c(t) = 0, \quad t > 0$$

$$V_c(0^+) = \frac{1}{C}$$

$$\dot{V}_c(0^+) = ?$$


$0^- < t < 0^+$

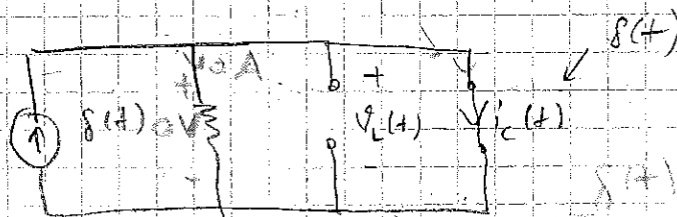

$$V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_C(z) dz = \frac{1}{C}$$

$$i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} V_L(z) dz = 0$$

At $t = 0^+$

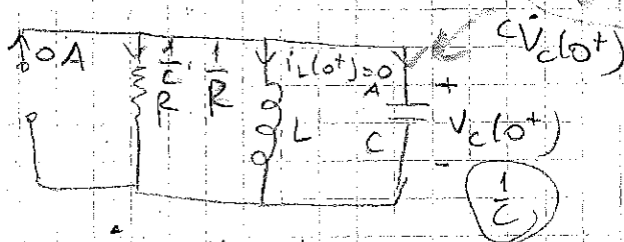

$$\dot{V}_c(0^+) = -\frac{1}{C^2 R}$$

then for $t > 0$

$$\left(D^2 + \frac{1}{RC}D + \frac{1}{LC}\right) V_c^{impulse}(t) = 0, \quad t > 0$$


$$V_c(0^+) = \frac{1}{C}$$

$$\dot{V}_c(0^+) = -\frac{1}{C^2 R}$$

$$V_c^{impulse}(t) = A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}, \quad t > 0$$

* Set A_1 and A_2 to match initial conditions

Ex 1 ZPS-VII
Problem 12

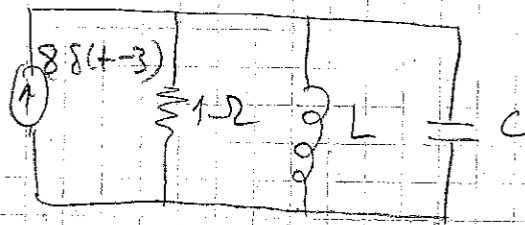

$V_C(0) = 0$
 $I_L(0) = 0$

Given $V_C(3^+) = 1V$ and the circuit is critically damped:



- a) Find L, C
- b) Find $V_C(t), t > 0$.

Critically damped

$\alpha = \omega_0$
 $V_C(t) = A_1 e^{-\lambda t} + A_2 t e^{-\lambda t}$

$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) V_C(t) = \frac{1}{C} \frac{d}{dt} \left[\int \delta(t) dt \right]$
 $\uparrow \quad \uparrow$
 $2\alpha \quad \omega_0^2$

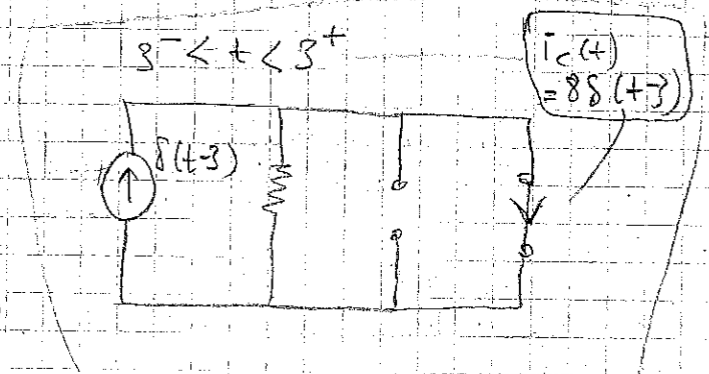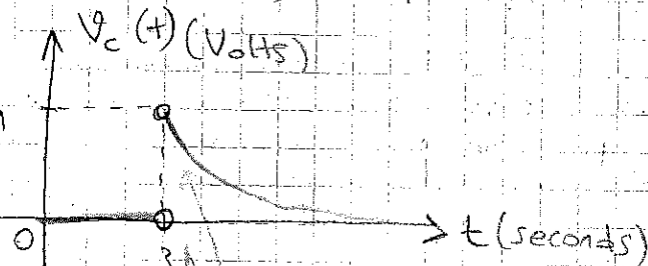For $\alpha = \omega_0 \Rightarrow \frac{1}{2RC} = \sqrt{\frac{1}{LC}}$
 $1\Omega \rightarrow \frac{1}{2RC}$
 $\rightarrow L = 4C$



Don't forget the circles.

$V_C(3^+) = V_C(3^-) + \frac{1}{C} \int_{3^-}^{3^+} i_C(\tau) d\tau = \frac{8}{C}$
 $\rightarrow V_C(3^+) = 1$
 $\rightarrow C = 8F$
 $L = 32H$

$\omega_0^2 = \frac{1}{256} \rightarrow \omega_0 = \frac{1}{16} \rightarrow \left(D^2 + \frac{1}{8} D + \frac{1}{256} \right) V_C(t) = 0, t > 3$

$V_C(t) = A_1 e^{-\frac{t}{16}} + A_2 t e^{-\frac{t}{16}}, t > 3$

$\lambda^2 + \frac{1}{8}\lambda + \frac{1}{256} = 0$


$V_C(3^+) = 1$

$V_C'(3^+) = -\frac{1}{8} \text{ Volts/sec}$

$\lambda = \left\{ -\frac{1}{16} \right\}$

$C \cdot V_C(3^+)$

At $t = 3^+$

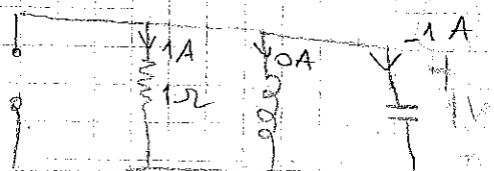


$$V_c(t) = \beta_1 e^{-\frac{(t-3)}{16}} + \beta_2 (t-3) e^{-\frac{(t-3)}{16}}, t > 3$$

$$V_c(3^+) = 1 \rightarrow \beta_1 = 1$$

$$\dot{V}_c(3^+) = -\frac{1}{8} \rightarrow -\frac{1}{16} \beta_1 + \beta_2 = -\frac{1}{8} \rightarrow \beta_2 = -\frac{1}{16}$$

$$V_c(t) = 1 e^{-(t-3)/16} - \frac{1}{16} (t-3) e^{-(t-3)/16}, t > 3$$

Ex:

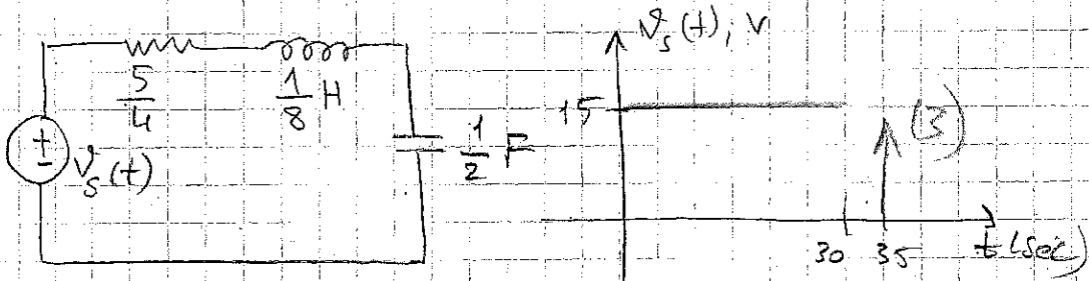

$$V_c(0^-) = -3V$$

$$i_L(0^-) = 0A$$


Find $V_c(t)$

Solution method: ① Decompose $V_s(t)$ into elementary functions and find zero-state response to each elementary function and find the sum of the zero-state response.


② Find zero-input solution

$$V_c^{complete}(t) = V_c^{z.i.}(t) + V_c^{z.s.}(t)$$
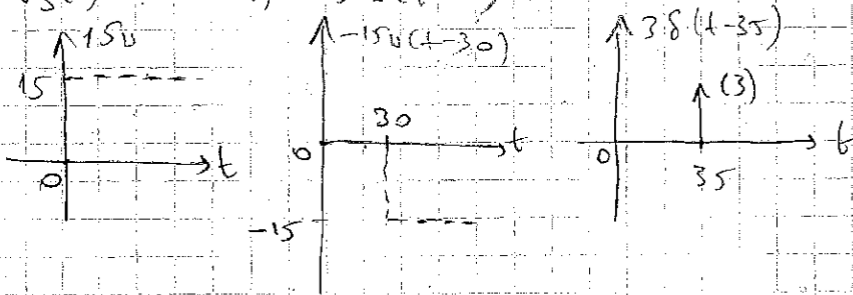
$$V_s(t) = 15u(t) - 15u(t-30) + 3\delta(t-35)$$



Step Response:

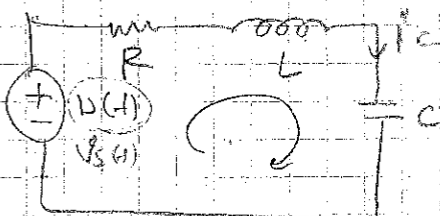

$$-V_s(t) + R \cdot i_c + V_L(t) + V_C(t) = 0$$

$$V_L(t) = L \frac{di_c(t)}{dt} = LC \ddot{V}_c(t)$$

$$[(LC)D^2 + (RC)D + 1] V_c(t) = V_s(t)$$

$$\left(D^2 + \frac{R}{L}D + \frac{1}{LC} \right) V_c(t) = \frac{V_s(t)}{LC}, t > 0$$

$$2\alpha = \frac{R}{L} \Rightarrow \alpha = 5$$

$$\omega_0^2 = \frac{1}{LC} = 16 \rightarrow \omega_0 = 4$$

$\alpha > \omega_0 \rightarrow$ Overdamped response

$$\lambda_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= \{-2, -8\}$$


$$\lambda^2 + 10\lambda + 16 = 0$$

$$(\lambda + 8)(\lambda + 2) = 0$$

$$V_c(t) = (A_1 e^{-2t} + A_2 e^{-8t}) + (\text{particular soln.})$$

Then for step-response $V_s(t) = u(t)$ and $V_c(0^+) = 0$
 $I_L(0^+) = 0$ } $\rightarrow V_c(\infty) = 1$



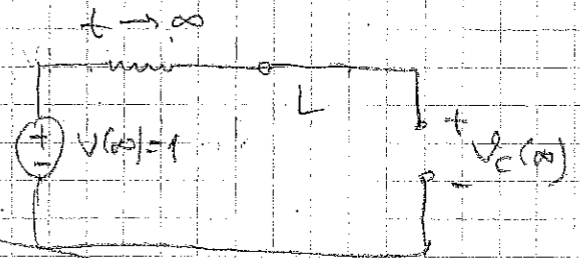
$$V_c(t) = 1 - \frac{4}{3} e^{-2t} + \frac{1}{3} e^{-8t}$$



Impulse response


$$h(t) = \frac{d}{dt} V_c^{\text{step}}(t)$$
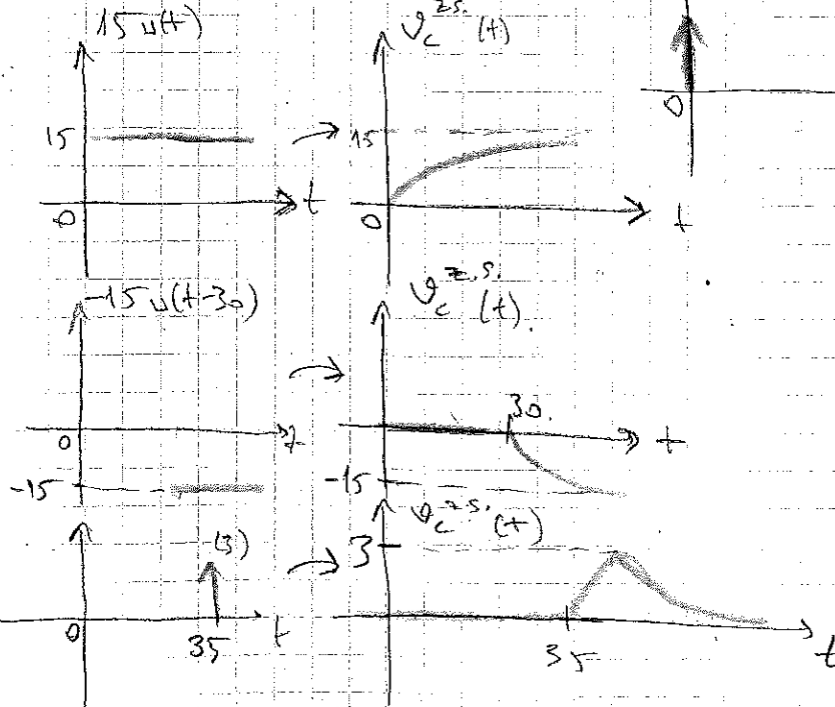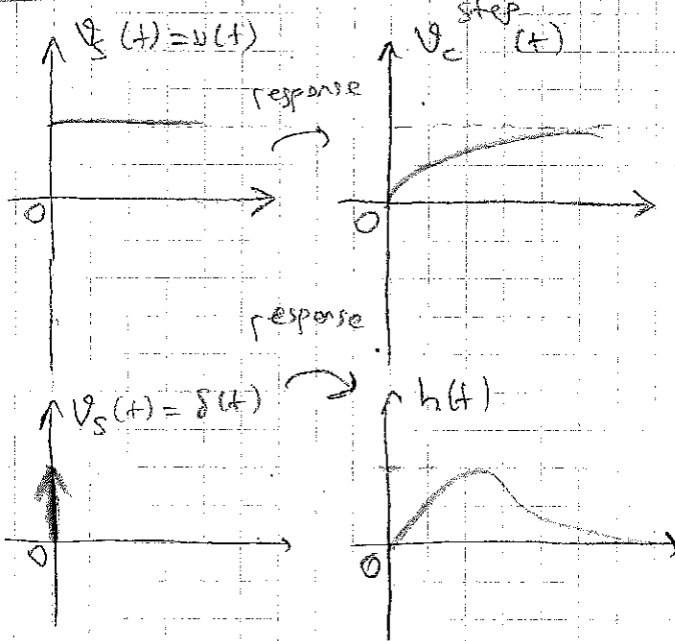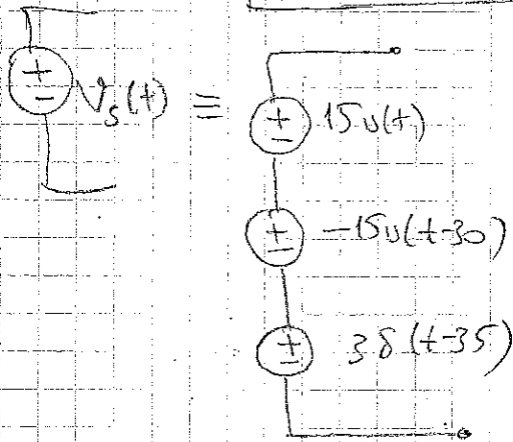
$$= \frac{8}{3} (e^{-2t} - e^{-8t}) u(t)$$



$$\begin{aligned} \textcircled{1} \quad v_c^{zs}(t) &= 15 v_c^{\text{step}}(t) - 15 v_c^{\text{step}}(t-30) + 3h(t-35) \\ &= 15 \left(1 - \frac{4}{3} e^{-2t} + \frac{1}{3} e^{-8t} \right) u(t) - 15 \left(1 - \frac{4}{3} e^{-2(t-30)} + \frac{1}{3} e^{-8(t-30)} \right) u(t-30) \\ &\quad + 3 \left(\frac{8}{3} \left(e^{-2(t-35)} - e^{-8(t-35)} \right) \right) u(t-35) \end{aligned}$$

② Zero input

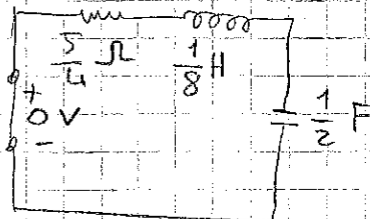

$$\begin{aligned} \alpha &= 5 \\ \omega_0 &= 4 \\ \lambda_{1,2} &= \left\{ -2 \pm j8 \right\} \end{aligned}$$

$$\begin{aligned} v_c(0^-) &= -3V \\ i_L(0^-) &= 0A \end{aligned}$$

$$v_c^{zi}(t) = B_1 e^{-2t} + B_2 e^{-8t}, \quad t > 0$$


At $t=0^+$ $\dot{v}_c(0^+) = 0$

$$v_c(0^+) = -3V$$

$$\dot{v}_c(0^+) = 0$$

Find B_1 and B_2
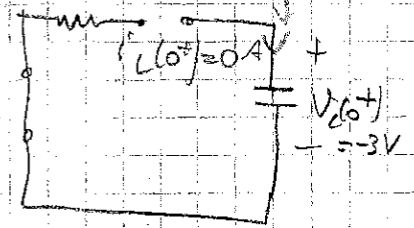
$$\begin{aligned} \rightarrow B_1 + B_2 &= -3 \\ -2B_1 - 8B_2 &= 0 \\ B_1 &= -4, \quad B_2 = 1 \end{aligned}$$



$$\textcircled{2} \quad v_c^{zi}(t) = (-4 e^{-2t} + e^{-8t}) u(t)$$

$$v_c^{\text{comp.}}(t) = v_c^{zs}(t) + v_c^{zi}(t)$$